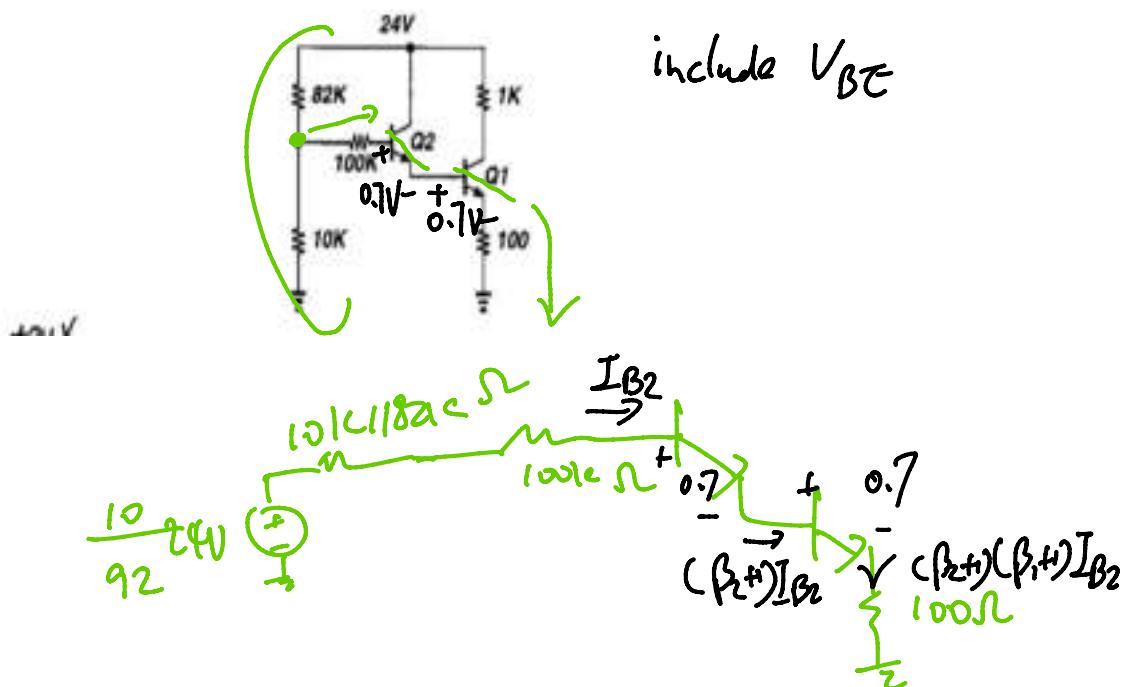


$$\Rightarrow \text{find } I_B, I_C.$$

$$I_B = I_1 - I_2$$

Problem 7 (Bonus - 10 marks)

For the circuit shown, transistors Q₁ and Q₂ operate in the active mode region with V_{BE1} = V_{BE2} = 0.7 V, β₁ = 100 and β₂ = 50. Find I_{B1}, V_{C1} and V_{E2}.



Problem 2 (20 marks)


For the circuit shown, utilizing ideal diodes, sketch the output waveform for the input shown.
Label the most positive and most negative output levels.

- (a) CR >> T
- (b) CR = 0.5 T

$$+V -$$

$$= (n1) V_{out} = 10 - 11$$

(b) CR = 0.5 T

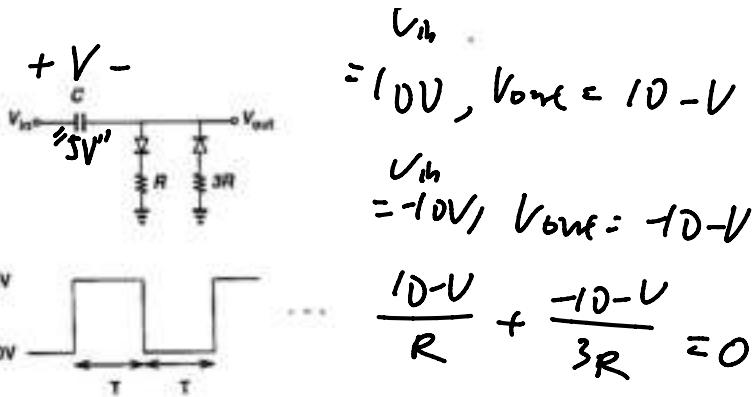


(a) current discharging C
 \downarrow \leftarrow current charging capacitor

$$\frac{V_1}{R} = \frac{V_2}{3R} \quad \left. \begin{array}{l} \rightarrow \\ \text{and } V_1 + V_2 = 20V \end{array} \right\} \rightarrow V_1 = 5V \text{ and } V_2 = 15V$$

\uparrow input swing = output swing

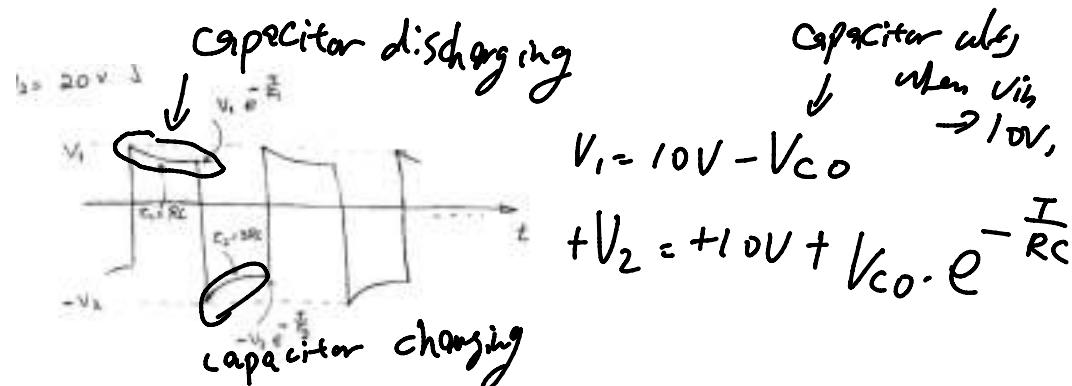(b) vs. (a): in (b), cap voltage changes
 after $+10V, -10V$

but, after a whole
 period, cap voltage
 resumes,



$$C_1 = RC = \frac{T}{2}, \quad C_2 = 3RC = \frac{3T}{2}$$

$$V_1 + V_2 e^{-\frac{t}{RC}} = 20 \rightarrow V_1 + e^{-\frac{t}{RC}} V_2 = 20 \rightarrow V_1 = 0.3333 V_2 + 20 \quad (1)$$

$$\text{or } V_1(1 - e^{-\frac{T}{RC}}) = V_2(1 - e^{-\frac{T}{RC}})$$

$$\therefore V_1(1 - e^{-2}) = V_2(1 - e^{-\frac{2}{3}}) \rightarrow 0.86466 V_1 = 0.48633 V_2 \quad (2)$$

From (1) to (2) $\rightarrow V_1 = 10.458 V$

Capacitor abs,
 \downarrow when V_{ih}
 $\rightarrow 10V$,

$$V_1 = 10V - V_{c0} \quad + V_2 = +10V + V_{c0} \cdot e^{-\frac{I}{RC}}$$

$$C_1 = RC \times \frac{1}{2}, \quad C_2 = 3RC = \frac{3}{2}T$$

$$V_1 + V_2 e^{\frac{-t}{T}} = 20 \rightarrow V_1 + e^{-\frac{t}{T}} V_2 = 20 \rightarrow V_1 = 0.515 V_2 - 20 \quad (1)$$

$$\therefore V_1 (1 - e^{-\frac{t}{T}}) = V_2 (1 - e^{-\frac{T}{T}})$$

$$\therefore V_1 (1 - e^{-\frac{t}{T}}) = V_2 (1 - e^{-\frac{t}{T}}) \rightarrow 0.515 V_2 = 0.48638 V_2 \quad (2)$$

From (1) & (2) \rightarrow


$V_1 = 10.456 \text{ V}$
$V_2 = 18.59 \text{ V}$

Problem 3 (20marks)

For the common-emitter amplifier circuit shown below:

- Find the dc collector current of the transistor and the output dc voltage.
- Find g_m and r_π .
- Find the voltage gain (v_{out}/v_{in}) and the input resistance.

Assume $\beta=100$

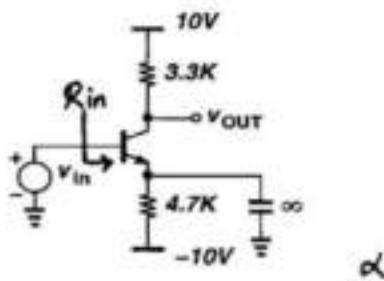


$0V$ $0V$
 $-0.7V$ $-0.7V - (-10V) = I_E \cdot 4.7k\Omega$
 β βI_E
 $4.7k\Omega$
 $-10V$

$$g_m = \frac{I_e}{\beta}$$

$$r_\pi = \beta g_m$$

(c) :

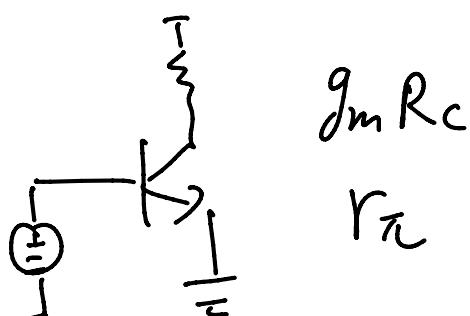


±

$\frac{1}{\infty}$


'n'

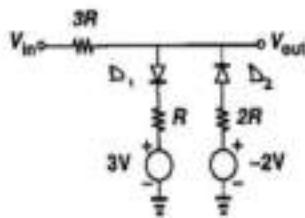Problem 1 (20 marks)

For the shown circuit, sketch V_{out} vs. V_{in} . Let V_{in} changes from -5 V to 5 V. Label the important break points. Assume ideal diodes.



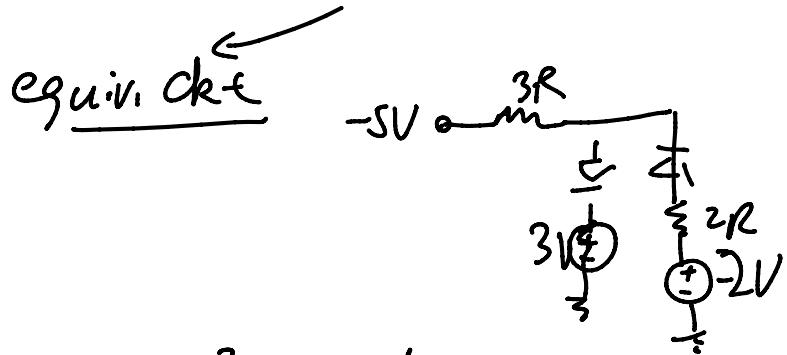① $V_{\text{in}} = -5 \text{ V}$, assume D_1 off D_2 on



$$V_{\text{out}} = \frac{2}{5}V_{\text{in}} - \frac{6}{5}\text{V}$$

verify } D_1 off
} D_2 current

$$I_{D2} = -2 - \frac{\frac{2}{5}V_{\text{in}} + \frac{6}{5}}{2R}$$


$$I_{D2} = \frac{-\frac{2}{5}V_{\text{in}} - \frac{4}{5}}{2R} \rightarrow \overbrace{\begin{array}{l} I_{D2} \\ V_{\text{in}} = -2 \end{array}}^*$$

Th. \leftarrow

$$V_{in} = -2$$

$$I_{D2} = 0$$

$V_{in} > -2$, D_1 OFF, D_2 OFF

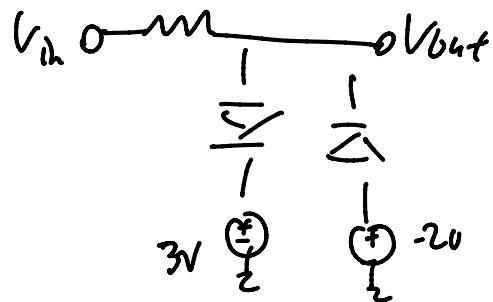

$V_{in} = 3V$

D_1 will be ON

Th.

$V_{in} > 3V$, D_1 ON, D_2 OFF