

**EE 115A  
Winter 2007  
Midterm Exam  
Feb 12<sup>th</sup> 2007  
Instructor: Prof. M.F. Chang**

**Name:**

*Solution*

**UID:**

**Left student's name:**

**Right student's name:**

**Problem1:**

**Problem2:**

**Problem3:**

**Problem4:**


**Problem5:**

**Bonus:**


**Total:**
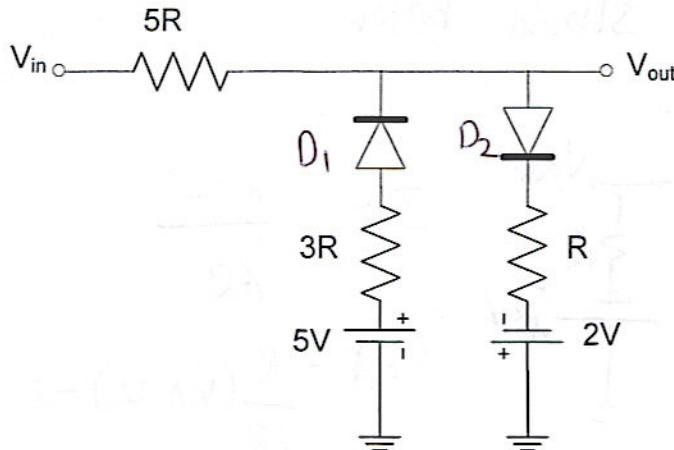
### Problem 1 (10%)

For the circuit shown, plot the input-output characteristics ( $V_{out}$  VS.  $V_{in}$ ) for  $-\infty < V_{in} < +\infty$ . Assume the diodes are ideal. Please label all the important breakpoints for full credit.



At  $V_{in} = -\infty$

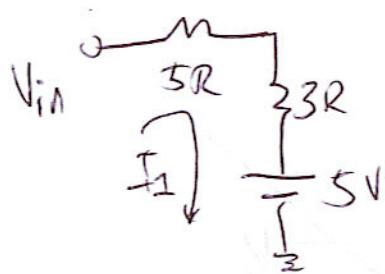


$$\frac{V_{in} - 5V}{8R} = I_1$$

$$\begin{aligned} V_{out} &= 3R \left( \frac{V_{in} - 5V}{8R} \right) + 5V \\ &= \frac{3}{8} V_{in} + 3.125 \\ &= \frac{3}{8} V_{in} + \frac{25}{8} \end{aligned}$$

At  $-2V = \frac{3}{8} V_{in} + 3.125$ ,  $V_{in} = -3.607 \left( -\frac{41}{3} \right)$

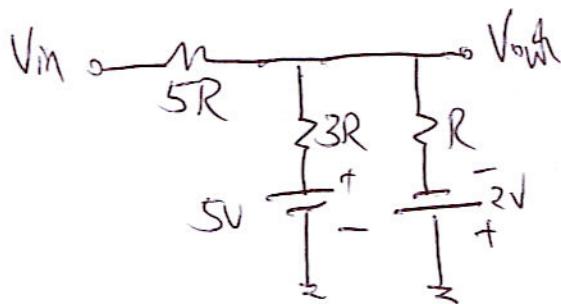$D_2$  turns on and we have the circuit shown below




KCL at  $V_{out}$  gives us

$$V_{out} = \frac{3}{23} V_{in} - \frac{5}{23}$$

$$\text{When } V_{\text{out}} = 5 = \frac{3}{23} V_{\text{in}} - \frac{5}{23} \Rightarrow V_{\text{in}} = 40$$

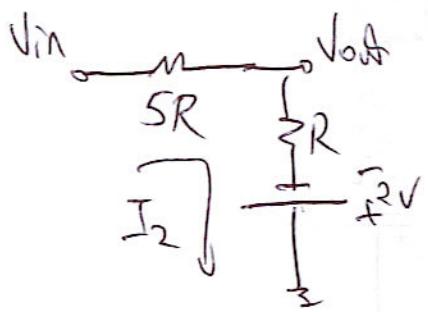
D<sub>1</sub> turns off and we have the circuit shown below.



$$I_2 = \frac{V_{\text{in}} + 2}{6R}$$

$$V_{\text{out}} = \frac{R}{6R} (V_{\text{in}} + 2) \sim 2V$$
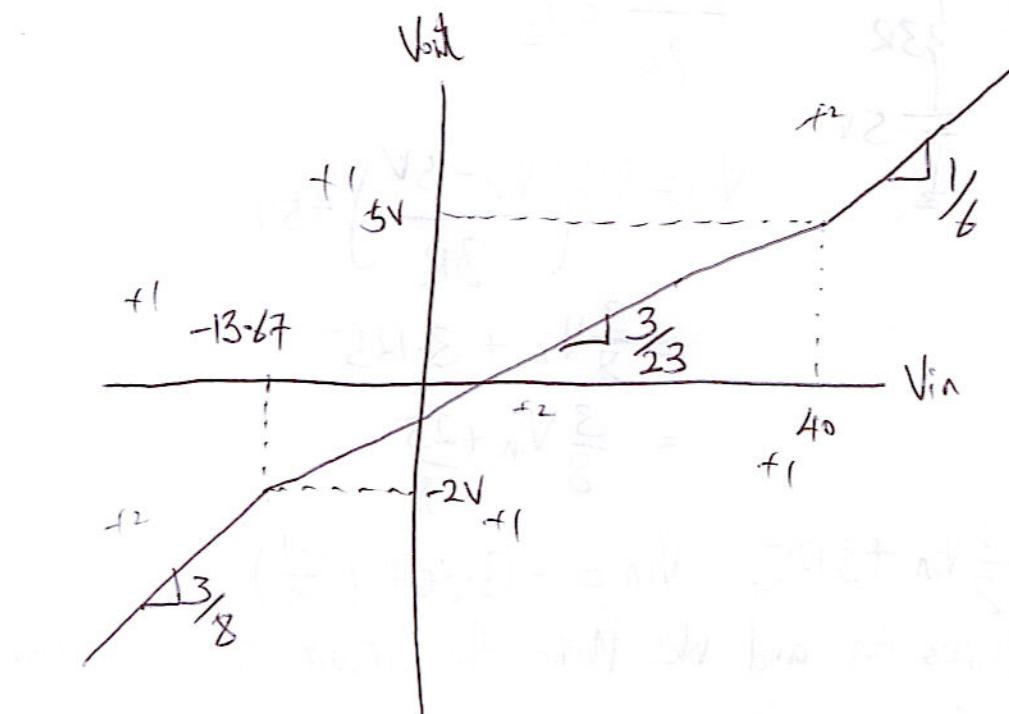
$$V_{\text{out}} = \frac{V_{\text{in}}}{6} - \frac{5}{3}$$




## Problem 2 (20%)



For the circuit shown and the input waveform given, plot the output waveform for the duration of the input waveform for the two cases below. Assume the diodes are ideal and the capacitors are initially not charged. Label the most positive and negative output levels. Please note that this problem asks for the transient behavior of the circuit, not its steady state.

+5  
-5

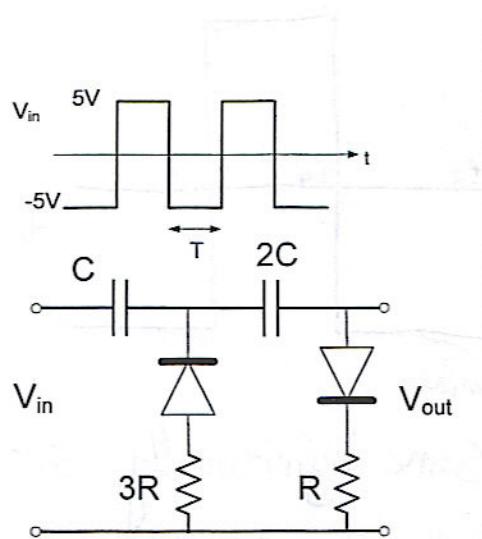
- (a) Assume  $RC > T$
- (b) Assume  $RC = T$



a)

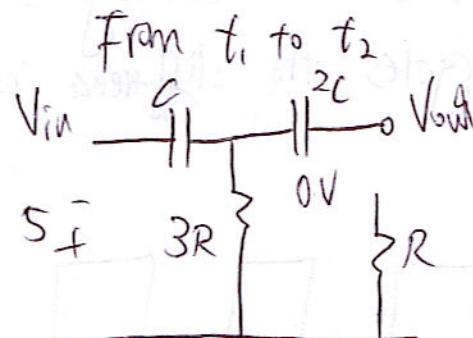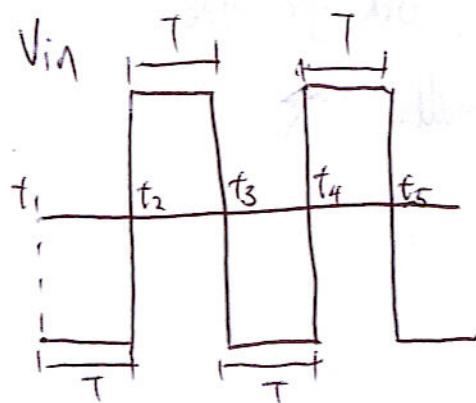

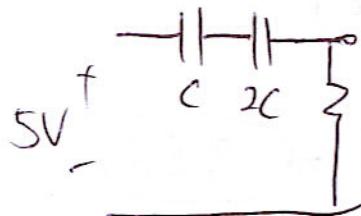
Since  $RC \gg T$ ,  $C$  will not get charged up!!! Therefore, the cap will remain a short for most of  $T$  and  $V_{out} \approx -5$ .  
From  $t_2$  to  $t_3$



Again, since  $RC \gg T$ , neither  $C$  nor  $2C$  will get charged up to any significant voltage and hence  $V_{out} \approx 5$


This process will continue till the end of the input duration.

So

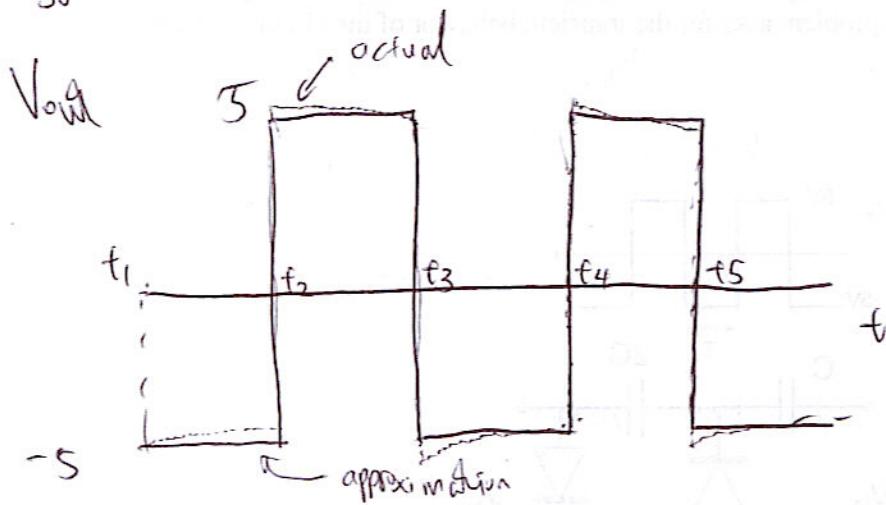


However, in reality some infinitesimally small voltage will get charged onto the capacitors and eventually this process will enter steady-state. But for the first few cycles, the difference is small.

b)  $V_{in}$

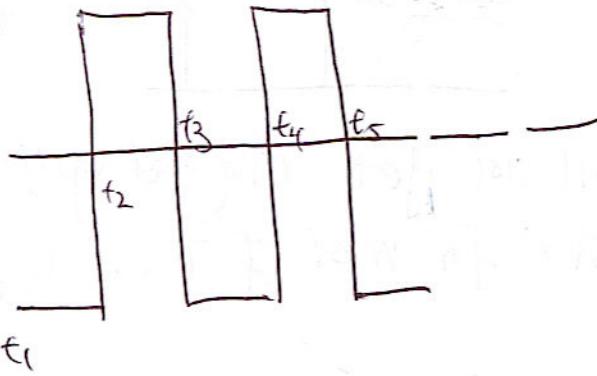

From  $t_1$  to  $t_2$

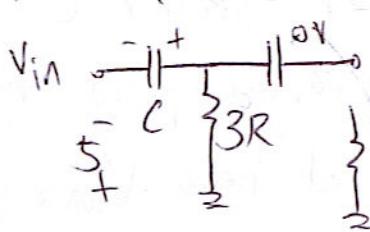


$$V_{out} = -5 + 5(1 - e^{-\frac{t}{3RC}})$$

$$\alpha = t = T = RC$$

$$V_{out} = -5 + 5(1 - e^{-\frac{1}{3}}) = \boxed{-3.58}$$

At  $t_2$ ,  $V_{in}$  jumps by  $10V$  and hence  $V_{out}$  jump by  $10V$ , so  $V_{out} = -3.58 + 10V = 6.42V$

From  $t_2$  to  $t_3$ :

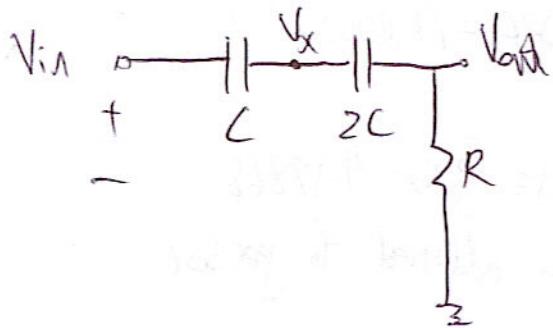

Use charge conservation at node x  
We get  $(V_x - V_{in})C + (V_x - V_{out})2C = (-3.58 + 5)C = \text{Total charge stored on node}$

$$\text{Since } V_{in}=5 \Rightarrow V_{out} = \frac{3}{2}V_x - 3.2V$$

If this condition is allowed to persist indefinitely,  $V_{out} = 0$  and  $V_x = 2.14V$

$$\text{So } V_x = 6.42e^{-\frac{t}{\frac{2}{3}RC}} + 2.14(1 - e^{-\frac{t}{\frac{2}{3}RC}})$$

[Note:  $\frac{2}{3}RC$  because  $C$  and  $2C$  are in series]


$$@ t=RC$$

$$V_x = 3.095 \text{ and } \boxed{V_{out} = 1.4325}$$

At  $t_3$ ,  $V_{in}$  jumps by  $-10V$ , so  $V_{out}$  will jump by  $-10V$  as well

$$\boxed{V_{out} = -8.568V}$$

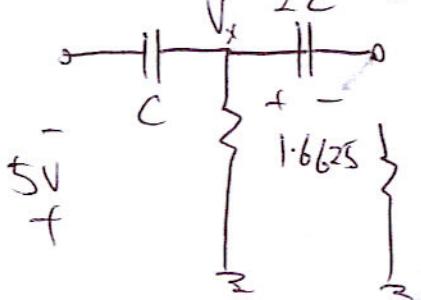From  $t_3$  to  $t_4$   $(3.095 - 1.4325) = 1.6625$




$$V_{out} = (3.095 - 10)e^{-\frac{t}{\frac{2}{3}RC}} - 1.6625$$

$$@ t=RC \quad \boxed{V_{out} = -6.6V}$$

@  $t_4$   $V_{in}$  jumps by  $10V$ , the output will also jump by  $10V$ , so  $V_{out} = -6.610 + 10 = 3.39V$

From  $t_4 - t_5$

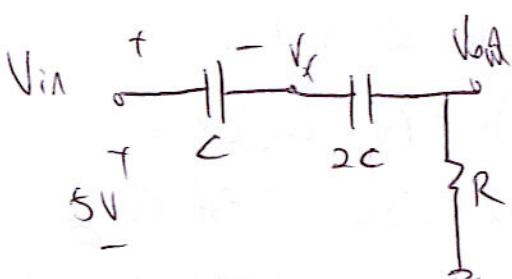

charge conservation @ node x

$$(V_x - V_{in})C + (V_x - V_{out})2C = (1.6625)2C + (-4.94765 + 5)C$$

$$\text{Since } V_{in} = 5V \Rightarrow V_{out} = \frac{3}{2}V_x - 4.18868$$

If this condition is allowed to persist indefinitely  $V_{out} = 0$  and  $V_x = 2.79248$


@  $t_4$   $V_x$  also jumps to  $-4.94765 + 10 = 5.052$

$$\text{So } V_x = 5.052 e^{-\frac{t}{3RC}} + 2.79245 (1 - e^{-\frac{t}{3RC}})$$


@  $t=RC$ ,  $V_x = 3.2967$  and  $V_{out} = 0.75637$

@ time  $t_5$   $V_{out}$  jump down by  $-10$  so  $-10.75637$ .

From  $t_5$  and on

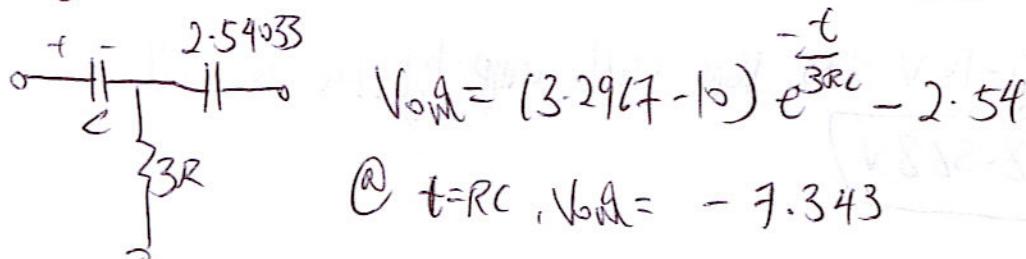


@  $t=RC$ ,  $V_{out} = -7.343$

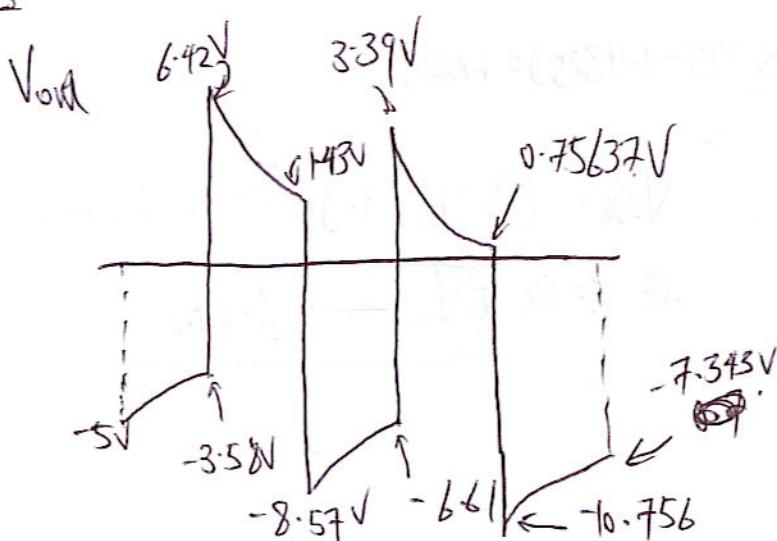

### Problem 3 (30%)

For the circuit shown below assume that all  $V_{BE}$ 's = 0.7V,  $\beta = 100$ ,  $V_{CC}$  equals 2.5V,  $|V_{CE,Sat}| = 0.2V$  and the Early voltage is  $\infty$ .

- 10 (a) For the circuit shown in part a), if  $R_{C1} = R_{C2} = 1K$ , what are  $I_{C1}$ ,  $I_{C2}$ , the output voltage and the voltage across  $R_{C1}$ ?  
 15 (b) For the circuit shown in part b), if  $R_1 = R_2$ ,  $R_{C1} = 1K$  and  $R_{C2} = 0.5R_{C1}$ , calculate  $I_{C1}$  and  $I_{C2}$ , the output voltage and the voltage drop across  $R_{C1}$ .  
 5 (c) Which bias technique would you choose and why?

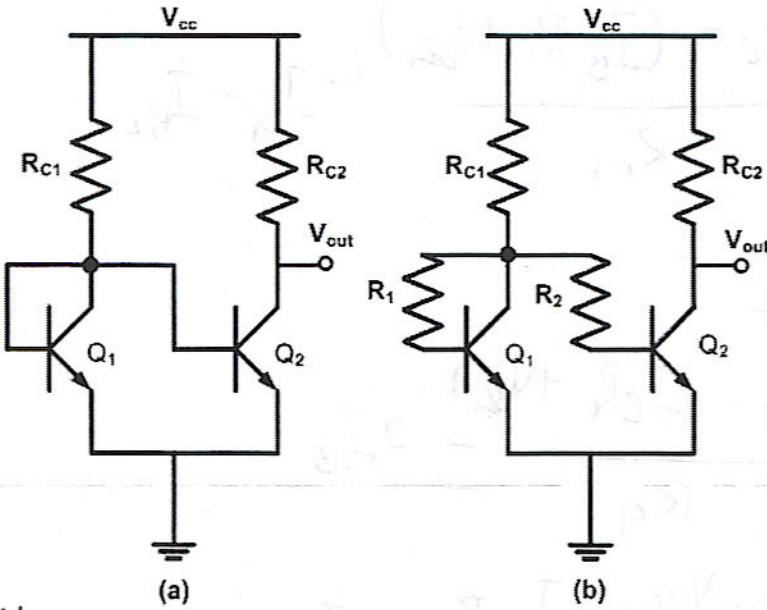

Assume all  $I_{SS}$ 's are equal and  $R_1 = R_2 \ll R_{C1}$

$$I_{C1} = \frac{V_{CC} - V_{BE}}{R_{C1}} - I_{B1} - I_{B2} \quad \text{Since } V_{BE_1} = V_{BE},$$

$$I_{C1} = \frac{V_{CC} - V_{BE}}{R_{C1}} - \frac{2I_c}{\beta} \quad I_{S1} = I_{S2} \Rightarrow I_{B1} = I_{B2}$$

$$I_c + \frac{2I_c}{\beta} = \frac{V_{CC} - V_{BE}}{R_{C1}}$$

$$I_c \left(1 + \frac{2}{\beta}\right) = \frac{V_{CC} - V_{BE}}{R_{C1}} \Rightarrow I_c = \frac{V_{CC} - V_{BE}}{R_{C1} \left(1 + \frac{2}{\beta}\right)} = \frac{2.5 - 0.7}{1K \left(1 + \frac{2}{100}\right)} = 1.765 \text{ mA}$$

$$a) I_{C1} = I_{C2} = \boxed{1.765 \text{ mA}}$$

$$V_{oA} = 2.5 - 1.765 = \boxed{0.735 \text{ V}}$$

$$V_{R_{C1}} = V_{CC} - 0.7 = \boxed{1.8 \text{ V}}$$

$$b) I_{C1} = \frac{V_{CC} - (I_{B1} R_1 + V_{BE1})}{R_{C1}} - I_{B1} - I_{B2}$$

$$I_{B1} = I_{B2}$$

$$I_C = \frac{V_{CC} - (I_B R_1 + V_{BE1})}{R_{C1}} - 2 I_B$$

$$I_C = \frac{V_{CC} - V_{BE}}{R_{C1}} - \frac{I_C R_1}{\beta R_{C1}} - 2 \frac{I_C}{\beta}$$

$$I_C = \frac{V_{CC} - V_{BE}}{R_{C1} \left( 1 + \frac{R_1}{\beta R_{C1}} + \frac{2}{\beta} \right)}$$

since  $R_1 \ll R_{C1}$   $\frac{1}{\beta} \left( \frac{R_1}{R_{C1}} \right) \approx 0$

$$I_C \approx \frac{V_{CC} - V_{BE}}{R_{C1} \left( 1 + \frac{2}{\beta} \right)} = 1.765 \text{ mA}$$

$$I_{C1} = I_{C2} = \boxed{1.765 \text{ mA}}$$

$$V_{oA} = 2.5 - \frac{1}{2} 1.765 = \boxed{1.6175 \text{ V}}$$

$$V_{R_{C1}} = \boxed{1.8 \text{ V}}$$

of course this is an approximation since we didn't account for the drop of  $R_1$ .


c) I would choose part b) since the collector current is less dependent on variation in  $V_{BE}$  (which results in an exponential change in  $I_C$ )

### Problem 4 (30%)

For the circuit shown  $I_S = 5 \times 10^{-16} A$ ,  $\beta = 100$ , Early voltage is  $\infty$  and  $|V_{CE,Sat}| = 0.2 V$ .

Assume the capacitors are large

- 15 (a) Calculate the small-signal parameters for both transistors.  
 15 (b) Draw the small-signal model for the circuit shown.  
 16 (c) Calculate the input and output impedances ( $R_{in}$  and  $R_{out}$ ), voltage gain and current gain ( $A_v$  and  $A_i$ ). (Note: The current gain is defined as the ratio of the currents flowing in the output 50 Ohm resistor to that of the input 50 Ohm resistor).

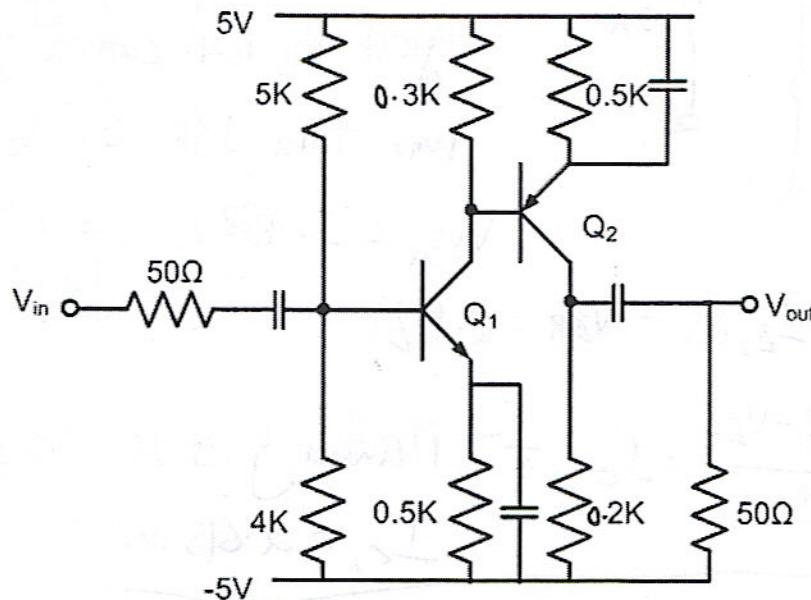

a) DC Analysis:

$$\begin{array}{c} 5k \\ \text{---} \\ 4k \\ \text{---} \\ -5 \end{array} \xrightarrow{\text{Thevenin equivalent}} \frac{R_{th}}{V_{th}} \quad V_{th} = \left( \frac{4}{5+4} \right) 10 - 5 = -0.5556 V$$


$$R_{th} = \frac{(4)(5)}{4+5} = 2.22 k$$

$$\begin{array}{c} 5V \\ \text{---} \\ 3k \\ \text{---} \\ -5V \end{array} \quad -0.5556 - I_B R_{th} - V_{BE} - I_E 0.5k = -5$$

$$\Rightarrow I_C = \frac{4.444 - V_{BE}}{0.5273}$$

Iteration gives me  $V_{EB} = 0.787 \text{ V}$

$$I_c = 6.94 \mu\text{A}$$

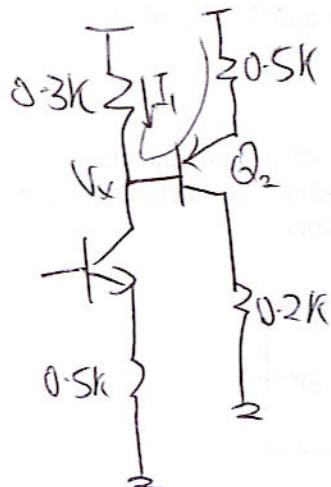

$I_c$  consists of the collector current of  $Q_1$  and the base current of  $Q_2$ .

However, since  $\beta$  is large we can neglect the base current of  $Q_2$  that runs thru  $0.3\text{K}$ . So  $V_{0.3\text{K}} = (6.94)(0.3)$

$$V_{0.3\text{K}} = 2.082 \text{ V}, V_x = 2.918 \text{ V. } (5 - 2.082)$$

$$\Rightarrow 5 - I_{E2} 0.5 - V_{EB} = 2.918 \text{ V}$$

$$\frac{2.082 - V_{EB}}{0.5051} = I_c \Rightarrow \text{iteration gives us } V_{EB} = 0.7614$$


$$I_{c2} = 2.615 \mu\text{A}$$

$$g_m = \frac{I_{c1}}{V_T} = 0.267 \frac{1}{\mu\text{A}}$$

$$g_m = 0.101 \frac{1}{\mu\text{A}}$$

$$V_{A1} = 374.64 \mu\text{V}$$

$$V_{A2} = 994.3 \mu\text{V}$$

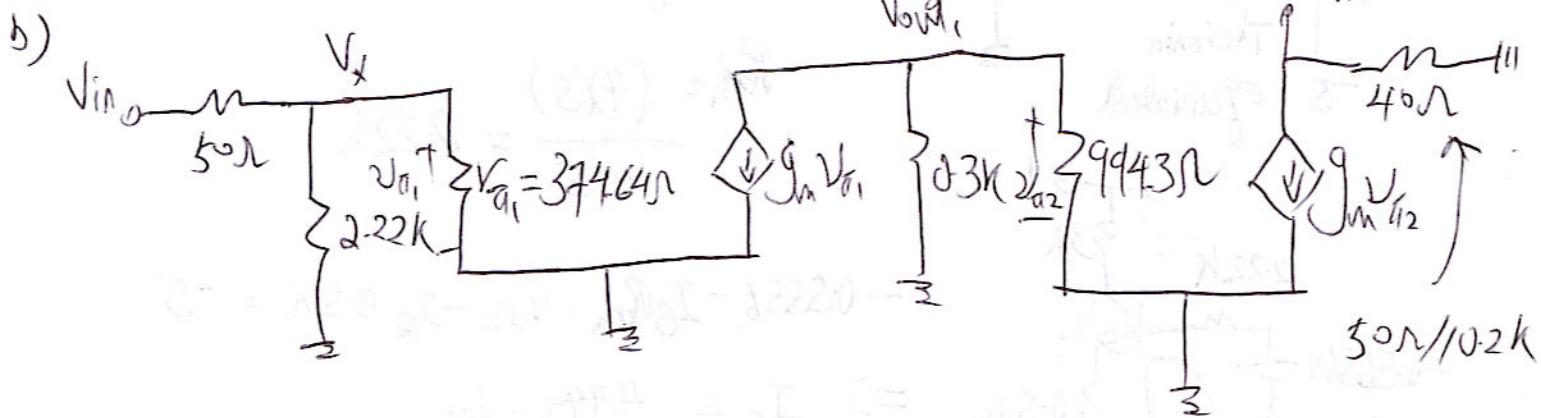

$$() R_{in} = 50\Omega + (2.22k/1374.64) \boxed{370.5\Omega}$$

$$\boxed{R_{out} = 40\Omega}$$

$$A_V = \left( \frac{V_x}{V_{in}} \right) \left( \frac{V_{out_1}}{V_x} \right) \left( \frac{V_{out_2}}{V_{out_1}} \right)$$

$$\frac{V_x}{V_{in}} = \frac{320.5}{370.5} = 0.865, \quad \frac{V_{out_1}}{V_x} = -g_m (0.3k/0.9943) \\ = -61.534$$

$$\frac{V_{out_2}}{V_{out_1}} = (-g_m)(40\Omega) = -4.04$$

$$A_V = (0.865)(-61.534)(-4.04) = \boxed{215}$$

$$A_I = \frac{\frac{V_{out}}{50\Omega}}{\frac{V_{in}}{R_{in}}} = \left( \frac{V_{out}}{V_{in}} \right) \left( \frac{R_{in}}{50} \right) = (215) \left( \frac{370.5}{50} \right) = \boxed{1593.15}$$

### Problem 5 (10%)

For the 5 devices shown in table below list their regions of operation. Assume  $V_{BE,ON}=0.7V$  and  $V_{BC,ON}=0.5V$ .

	Device	$V_B(V)$	$V_E(V)$	$V_C(V)$
1	PNP	1	2	1
2	NPN	1	2	1
3	PNP	0.3	2	0.8
4	NPN	0	0.7	0.5
5	PNP	2	2	2.5

1)  $V_{EB} = 1$ ,  $V_{CB} = 0$ ,  $\Rightarrow$  Forward Active

2)  $V_{BE} = -1$ ,  $V_{BC} = 0 \Rightarrow$  off


3)  $V_{EB} = 1.7$ ,  $V_{CB} = 0.5 \Rightarrow$  Sat

4)  $V_{BE} = -0.7$ ,  $V_{BC} = -0.5 \Rightarrow$  off

5)  $V_{EB} = 0$ ,  $V_{CB} = 0.5 \Rightarrow$  off / Reverse Active (edge)
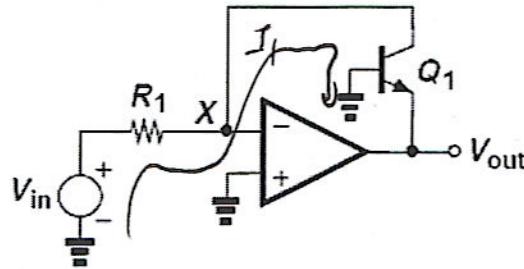
## Bonus (20%)

- For the circuit shown below assume the Op-amp is ideal
- (a) What is  $V_{out}$  in terms of  $V_{in}$ ,  $I_s$ , and  $R_1$ .
  - (b) If  $I_s = 5 \times 10^{-16} A$ ,  $R_1 = 1K$  and  $V_{BE,ON} = 0.7V$ , for what value of  $V_{in}$  will this circuit cease to operate at room temperature.



$$a) I_1 = \frac{V_{in}}{R_1} = I_s \exp\left(\frac{V_{BE}}{V_T}\right)$$

$$V_{out} = -V_{BE} = -V_T \ln\left(\frac{V_{in}}{R_1 I_s}\right)$$

$$b) 0.7 = V_T \ln\left(\frac{V_{in}}{R_1 I_s}\right) = 26 \ln\left(\frac{V_{in}}{(1K)(5 \times 10^{-16})}\right)$$

$$V_{in} = 0.2463 V$$

So for anything less than 0.2463 V,  
 $Q_1$  is off and this circuit will fail.

$$V_{in} > 0.2463 V \text{ (for correct operation)}$$