

EE 115A Analog Electronic Circuits
Winter 2013

Test 1
Closed Book

Name: Solution

Student ID No.: Solution

1) _____ / 10

2) _____ / 12

3) _____ / 10

4) _____ / 8

TOTAL _____ / 40

10 pts

- 1) Provide a short answer to each of the following.

2 pts

- a) Why/How is the depletion region formed in a PN junction when there is nothing connected to the terminals?

Electrons tend to diffuse from N-type to P-type while holes tend to diffuse from P-type to N-type. Diffusion leaves immobile atoms which forms depletion region. (1pt)

Depletion region creates electrical field which opposes diffusion so that net current is zero at equilibrium. (1pt)

2 pts

- b) Name 4 Operations that are possible with analog electronics but are not possible if you were constrained to the tools and circuit elements used in EE10 and EE110?

(1) AC-DC converter (Voltage doubler, tripler....)

(2) Rectifier (Full wave, half wave...)


(3) Switch (Frequency translation, create digital logic...)

(4) Data Converters (Analog to digital, digital to analog)


2 pts

- c) Name the three different diode models/equations. Why do we have three different diode models?


(1) Ideal diode

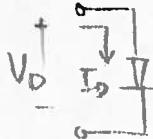

(2) Constant Voltage model

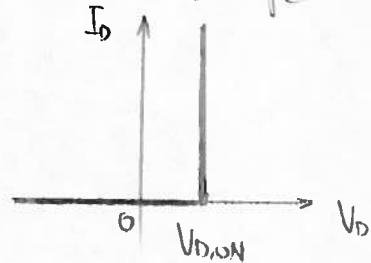

(3) Exponential model

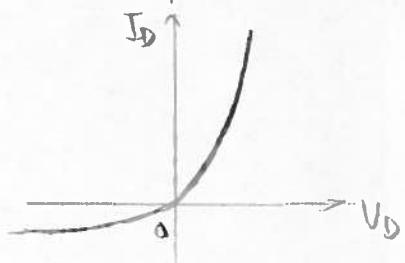

$$\begin{cases} I_D = I_s (e^{\frac{V_D}{V_T}} - 1) \\ V_T = \frac{kT}{q} \end{cases}$$

(c) & (d) graded together, 4 pts in total

2 pts

- d) When should we use each of the three different diode models?

Ideal diode model provides a quick understanding of circuit behavior.

Constant voltage model is a much better approximation to real model.

Exponential model is the most accurate, but takes much more effort to solve. It is only use when great accuracy is demanded.

2 pts

- e) Name 4 of the factors that determine the amount of current flowing in a PN-junction

(1) Doping density

(2) cross section area of PN-junction

(3) Voltage applied to PN-junction

(4) temperature, determines V_T

2) Find the value of the current flowing in the 1K resistance.


(a) Use the constant voltage drop model for the diodes, with $V_{D\text{-on}} = 0.8V$

(b) Use the real-diode equation with $I_s = 1.7 \times 10^{-17} A$. Feel free to make "engineering" assumptions to solve the problem. Be sure to state all your assumptions.

12 pts

(a) Assume D_1 OFF, D_2 ON

Equivalent circuit is shown below

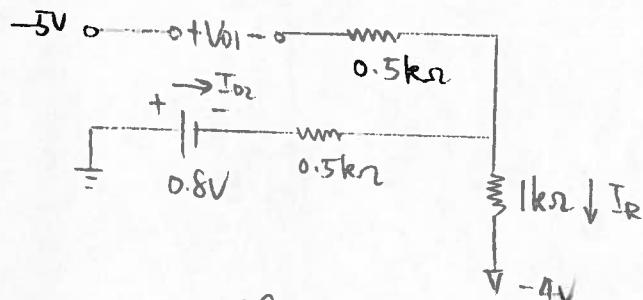

$$I_{D2} = \frac{0.8V - (-4V)}{0.5k\Omega + 1k\Omega} = 2.13mA > 0$$

$$V_{D1} = -5V - (-4V + 2.13mA \times 1k\Omega) = -3.13V < 0.8V \Rightarrow \text{Assumption is correct}$$

D_1 OFF, D_2 ON


Thus, $I_R = I_{D2} = 2.13mA$

(b) From (a), we know that V_{D1} is very negative, so

$$I_{D1} = I_s (e^{\frac{V_{D1}}{V_T}} - 1) \approx -I_s \approx 0 \text{ with } V_{D1} \ll 0 \text{ and } I_{s1} = 1.7 \times 10^{-17} A$$

With $I_{D1} \approx 0$, D_1 can be regarded as open circuit. This assumption only creates ignorable error with $I_{D2} \gg I_s$.

Equivalent circuit is shown below

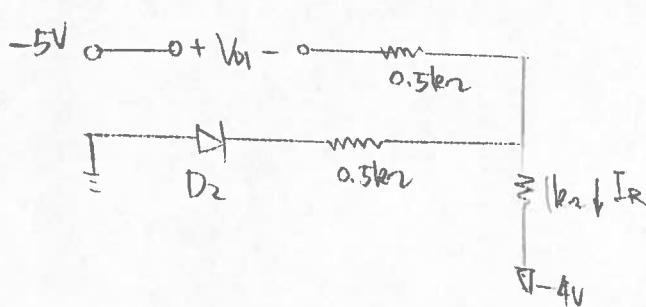

$$I_s (e^{\frac{V_{D2}}{V_T}} - 1) = \frac{0 - V_D - (-4V)}{1.5k\Omega}$$


$$V_T = 26mV @ 300K, \text{ room temperature}$$

$$\Rightarrow I_R = I_s (e^{\frac{V_{D2}}{V_T}} - 1) = 2.105mA$$


$$\Rightarrow V_{D1} = -5V - (-4V + 2.105mA \times 1k\Omega) = -3.1V$$

If further verifies that our assumption that $I_{D1} \approx -I_{s1} = -1.7 \times 10^{-17} A \ll I_{D2}$


So $I_R = I_{D2} = 2.105mA$

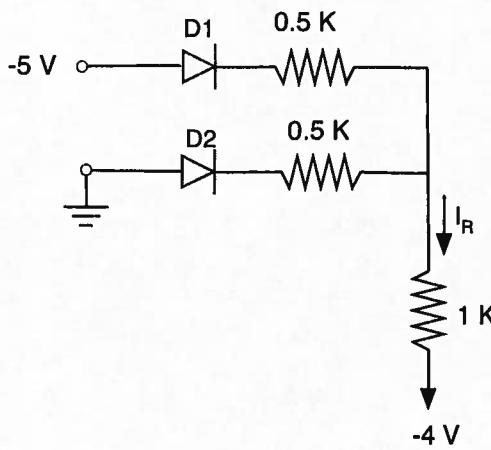

(3) Excluding R_C ,

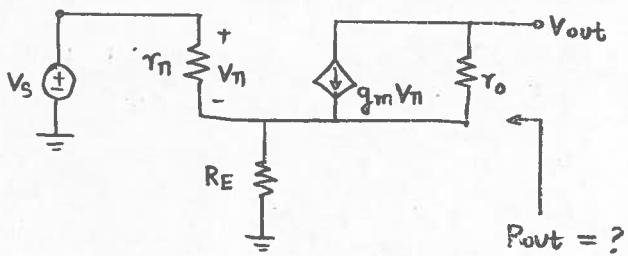

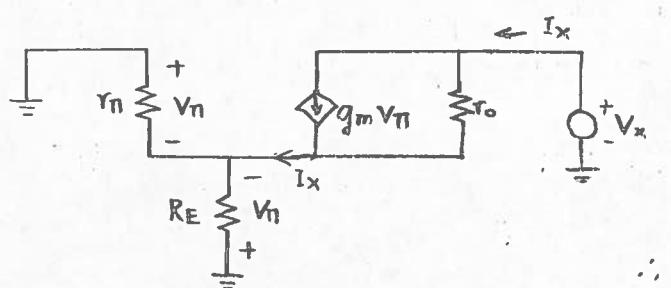To calculate R_{out} , we suppress all independent sources



$$R_{out} = V_x / I_x$$

$$I_x = -V_n / (R_E \parallel R_n)$$


$$V_x = V_{r_o} - V_n$$

$$\therefore V_x = (I_x - g_m V_n) r_o - V_n$$

$$\therefore V_x = I_x \{ 1 + g_m (R_E \parallel R_n) \} r_o + (R_E \parallel R_n) I_x$$

$$\therefore R_{out} = \frac{V_x}{I_x} = (R_E \parallel R_n) + r_o + g_m r_o (R_E \parallel R_n)$$

(4)

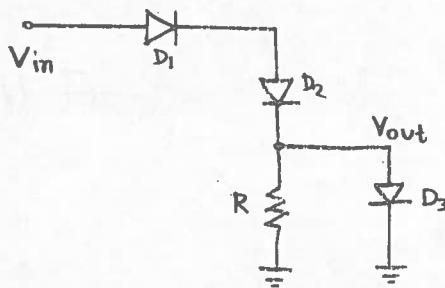


Plot. V_{out} vs V_{in} .

For $V_{in} < 2V_{D_{on}}$, D_1 & D_2 off $\Rightarrow V_{out} = 0 \Rightarrow D_3$ off

For $2V_{D_{on}} \leq V_{in} < 3V_{D_{on}}$, D_1 & D_2 on
 $\Rightarrow V_{out} = V_{in} - 2V_{D_{on}}$

But when $V_{out} \geq V_{D_{on}}$, D_3 turns on
& now we have following situation

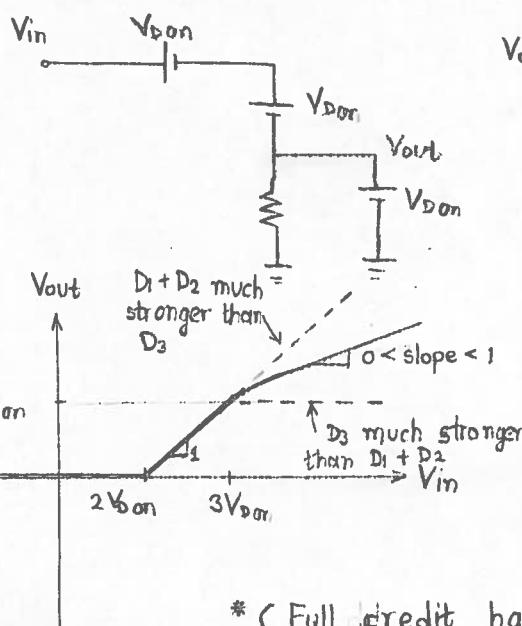At $V_{out} \geq V_{D_{on}}$ i.e. $V_{in} \geq 3V_{D_{on}}$



$V_{out} = V_{in} - 2V_{D_{on}}$ which is not possible. Hence constant voltage model fails. So, at this point we can make following argument. If D_3 was absent, $V_{out} = V_{in} - 2V_{D_{on}}$. If $D_1 + D_2$ were absent, $V_{out} = V_{D_{on}}$. But since all 3 are present V_{out} will be some intermediate voltage as shown (a first order approximation) & slope of V_{out} will depend on relative strength of D_3 & $D_1 + D_2$.

* (Full credit has been given if you got either of the dotted lines)