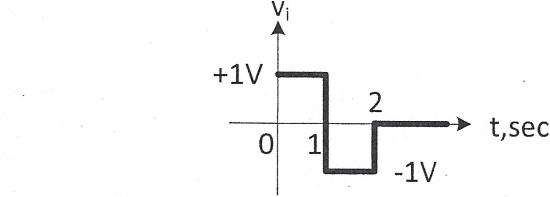


1. The circuit shown below is in zero state at  $t = 0$ . Calculate and plot the capacitor voltage ( $v_c(t)$ ) for  $t \geq 0$  given the input signal shown. The diode is ideal.



$$i(+)=\frac{cdv_c}{dt}$$

$$-1 = i(+) \cdot 1 + v_c(+)$$

$$-1 = \frac{dv_c(t)}{dt} + v_c(t)$$

$$e^t v_c(0) = \int 1 e^t$$

$$e^t v_c(0) = -e^t + c$$

$$v_c(t) = -1 + ce^{-t}$$

$$v_c(0) = -1 + ce^{-(t-0)}$$

$$1 = -1 + c$$

$$2 = c$$

$$v_c(t) = 2e^{-(t-1)} - 1$$

$$i(t) = \frac{cdv_c}{dt}$$

$$v_i = 1 i(+) + v_c(+)$$

$$v_i = \frac{cdv_c}{dt} + v_c(+)$$

$$\frac{dv_c}{dt} + v_c(+) = v_i$$

$$= e^{\int dt}$$

$$= e^t v_c(+) = \int v_i e^t \quad v_i = -1$$

$$e^t v_c(t) = v_i e^t + c$$

$$v_c(+) = v_i + ce^{-(t-1)}$$


$$1 = v_i + c \quad c = 2$$

$$c = 1 - v_i = 2 \quad (v_i = -1)$$

$$v_c(t) = -1 + 2e^{-(t-1)}$$

$$v_c(t) = 2e^{-(t-1)} - 1$$


$$v_c(2) = -0.264$$

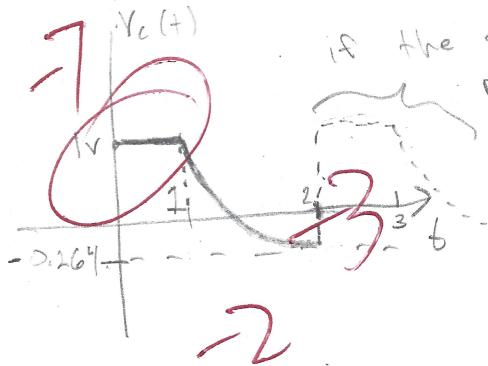

2. For the circuit below, let  $I_{ES} = 1\text{pA}$ ,  $V_A = \infty$ ,  $\beta = 100$ ,  $V_{CE,SAT} = 0.2\text{V}$ ,  $R_B = 89\text{k}\Omega$ .

a. For  $R_C = 1\text{k}\Omega$ , find the exact transistors operating point and the region of operation.

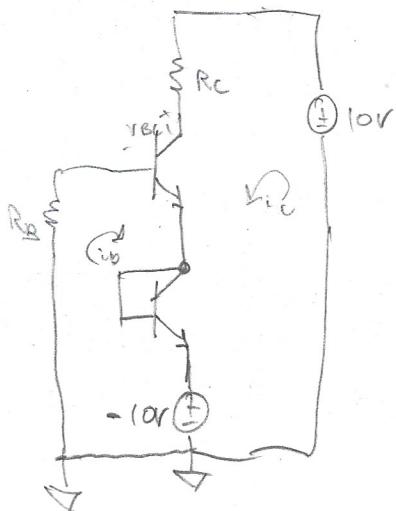b. Using  $V_{BE,ON} = 0.6\text{V}$  approximation, find the maximum value of  $R_C$  that puts  $Q_2$  on the edge of saturation.



left loop

$$i_b R_B + V_{BE2} + V_{BE1} + (-10\text{V}) = 0$$



$$V_{BE1} =$$

$$10\text{V} = i_b R_B + V_{BE2} + V_{BE1} \quad (1)$$

right loop

$$10\text{V} = i_c R_C + V_{CE1} + V_{CE2} + (-10\text{V})$$

$$20\text{V} = i_c R_C + V_{CE1} + V_{CE2} \quad | \quad 20\text{V} = i_c R_C + V_{CE1} + V_{BE2} \quad (2)$$

Outer loop

$$10\text{V} = R_C i_C + V_{BE1} - V_{CE1} - R_B i_b \quad (3)$$

$$10\text{V} = i_b R_B + 2V_{BE1}$$

$$20\text{V} = i_C R_C + V_{CE1} + V_{BE2}$$

$$i_b = \frac{i_c}{\beta}$$

$$V_{CE1} = 20 - (9.75\text{mA})(1\text{k}) = 0.589\text{mA}$$

$$10\text{V} = \frac{1}{\beta} (1 \times 10^{-12}) \exp\left(\frac{V_{BE1}}{V_T}\right) R_B + 2V_{BE1}$$

(Solved using calculator)

$$V_{BE1} = 9.652\text{V}$$

$$V_{CE1} = V_{BE1} = 0.598\text{V}$$

$$V_{BE1} = V_{BE2} = 0.598\text{V}$$

$$I_{C1} = (1 \times 10^{-12}) \exp\left(\frac{0.598}{0.026}\right)$$

$$I_{C1} = 9.75\text{mA}$$

$$I_E = 9.75\text{mA}$$


$$I_B = 97.45\text{nA}$$

$$V_{BC1} =$$

$$V_{CE1} = V_{BE1} - V_{BC1}$$

$$V_{BC2} = V_{BE2} - V_{CE2}$$

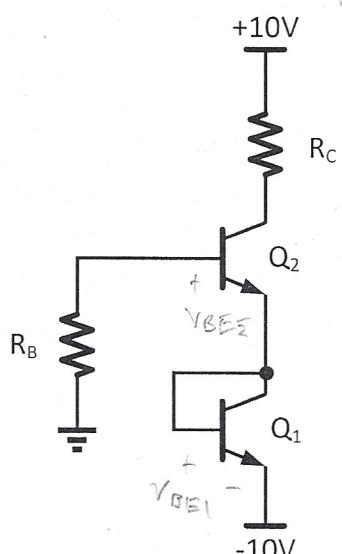(if they are same transistor then they will have same  $V_{BE}$ )



$$V_{BE1} = V_{BE2}$$

$$V_{CE1} = V_{BE1}$$

$$i_{e2} = i_{B1} + i_{E1}$$

$$V_{BE,ON} = 0.6V$$

b)

$$10V = i_b R_b + V_{BE1} + V_{BE2}$$

$$10V = i_b R_b + 2V_{BE1}$$

$$\frac{10V - 2(0.6)}{R_b} = i_b \quad i_b = 98.88\mu A$$

$$i_b = \frac{8.8}{89000}$$


$$i_c = 9.89mA$$

$$i_o = 9.89mA$$

$$20V = i_{C1} R_C + V_{CE2} + \underbrace{V_{CE1}}_{V_{BE2} = 0.6V}$$

$$\frac{20 - 0.6 - 0.2}{i_{C1} = 9.89mA} = R_C$$


$$R_C = 1.941k\Omega$$

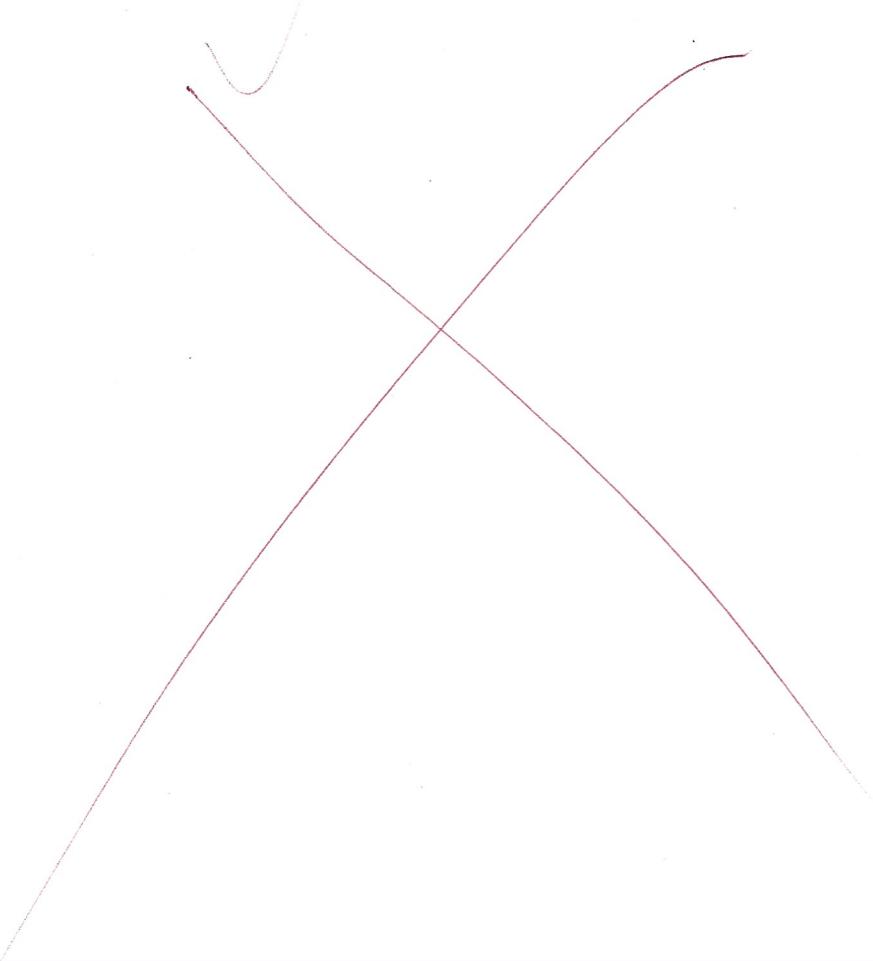

3. In the common-emitter amplifier below,  $V_{BE,ON} = 0.6V$ ,  $V_A = \infty$ ,  $\beta = 100$ ,  $V_{CE,SAT} = 0.2V$ .

a. Find the DC operating point and the transistor region of operation.

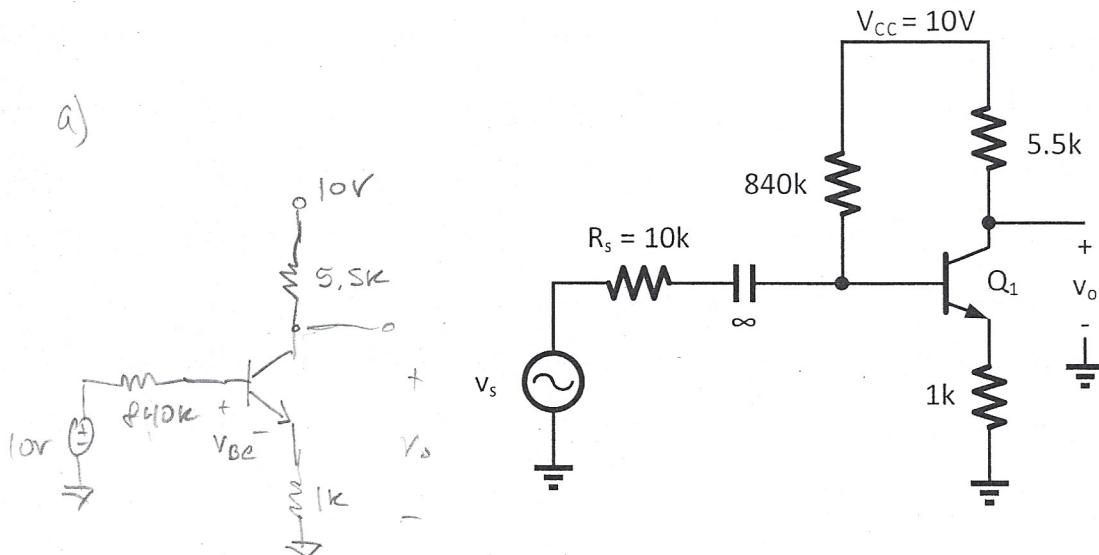b. Calculate the amplifier small signal voltage gain ( $\frac{v_o}{v_s}$ ).



$$g_m = \frac{I_c}{V_T}$$

$$r_{\pi} = \frac{\beta}{g_m}$$

$$r_{\pi} = 5.5$$

$$i_e = i_b + i_c$$

$$= i_b + \beta i_b$$

$$i_e = (1 + \beta) i_b$$

$$i_{OB} = 840k i_b + V_{BE} + i_e(1k)$$

$$i_b = \frac{10V - 0.6V}{840k + ((10)(1k))} = 9.99 \mu A$$

$$i_c = 0.999mA \approx 1mA$$

$$i_e = 1mA$$


$$- V_{ce} + V_o + i_c R_C$$

$$V_o = V_{CC} - i_c R_C$$

$$V_o = 10V - (1mA)(5.5k)$$

$$V_o = 4.5V$$

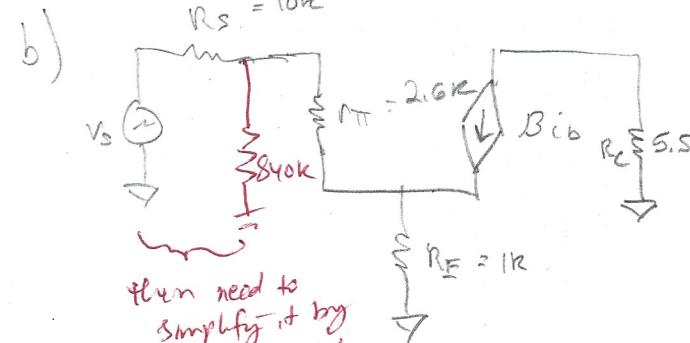Region of operation?  
 $V_{CE} > V_{CE,SAT}$   
 forward active  
 forward region



$$V_S = (R_S + r_{\pi}) i_O + R_E i_O$$

$$V_S = (R_S + r_{\pi}) i_O + (10) R_E i_O$$

$$15/20 i_O = - R_E \beta i_b$$

$$\frac{V_o}{V_S} = - \frac{R_E \beta}{(R_S + r_{\pi}) + (10) R_E} = \frac{550k}{113.6k}$$

$$\left| \frac{V_o}{V_S} \right| = 4.84$$