



Name: _____

UID: _____


Total of 3 questions, 120 minutes.

P1 (30)	30
P2 (30)	30
P3 (40)	40
Total (100)	100

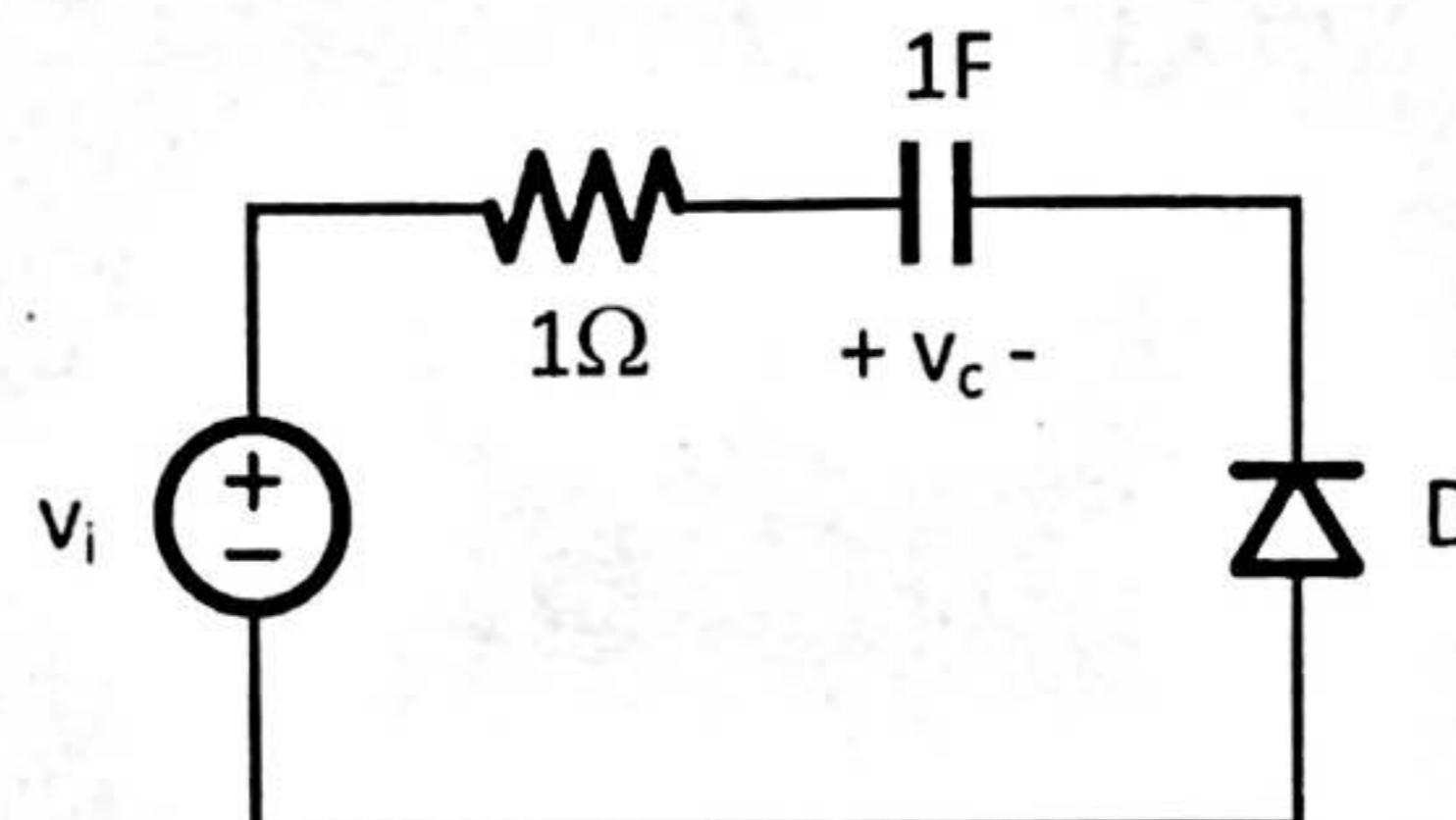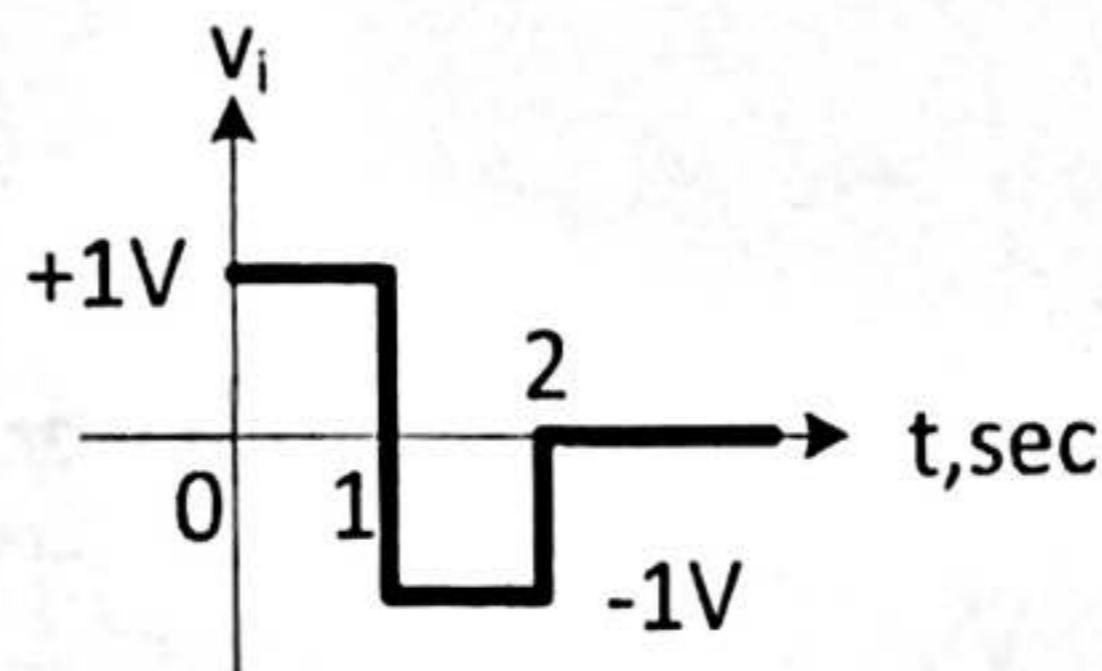1. The circuit shown below is in zero state at $t = 0$. Calculate and plot the capacitor voltage ($v_c(t)$) for $t \geq 0$ given the input signal shown. The diode is ideal.




for $0 < t < 1$, diode is off

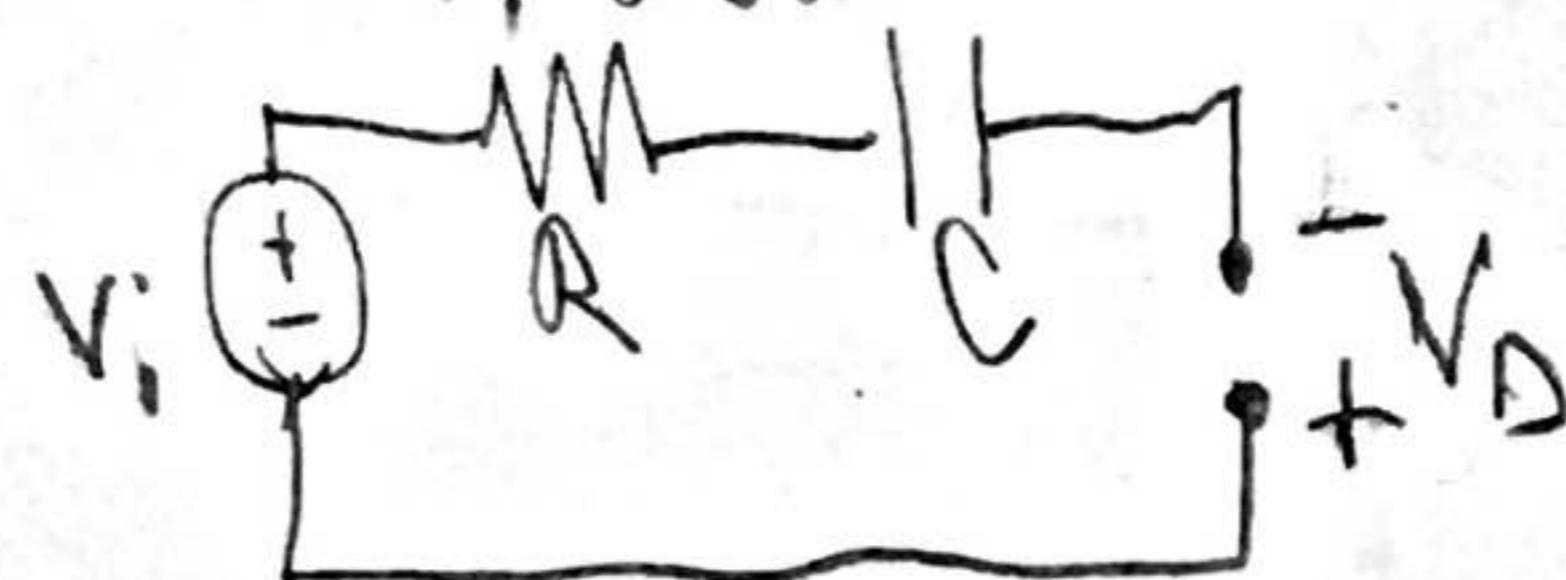

$v_c \geq 0$
 $v_i = -V_D \Rightarrow V_D = -1$ so diode must be off
 diode turns on when $v_i < 0$

for $1 < t < 2$, diode is on

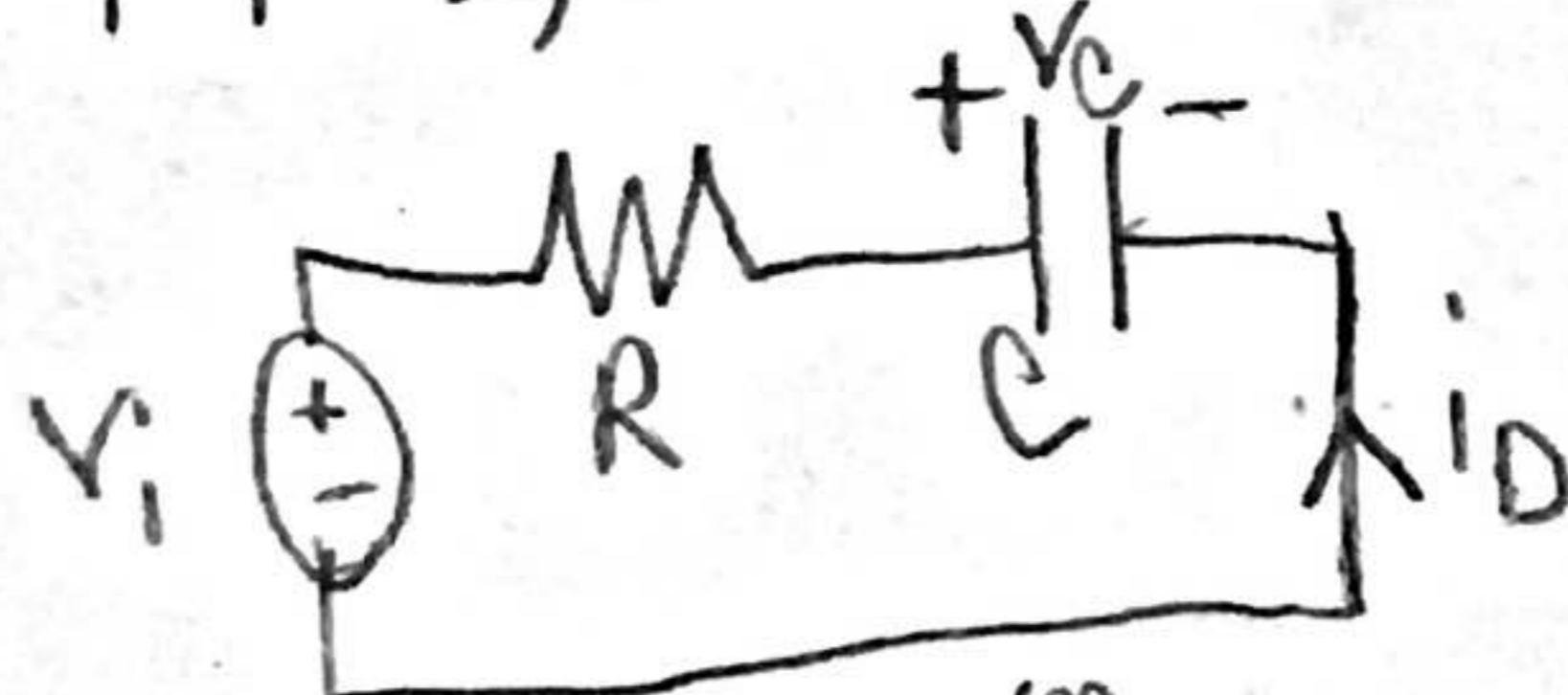


$$v_c(t) = (v_i - V_f) e^{-t/RC} + V_f \quad \text{zero-state}$$

$$= e^{-t} - 1 = -(1 - e^{-t})$$


needs to be time shifted: $- (1 - e^{-(t-1)}) = v_c(t)$

for $t > 2$, $v_i = 0$

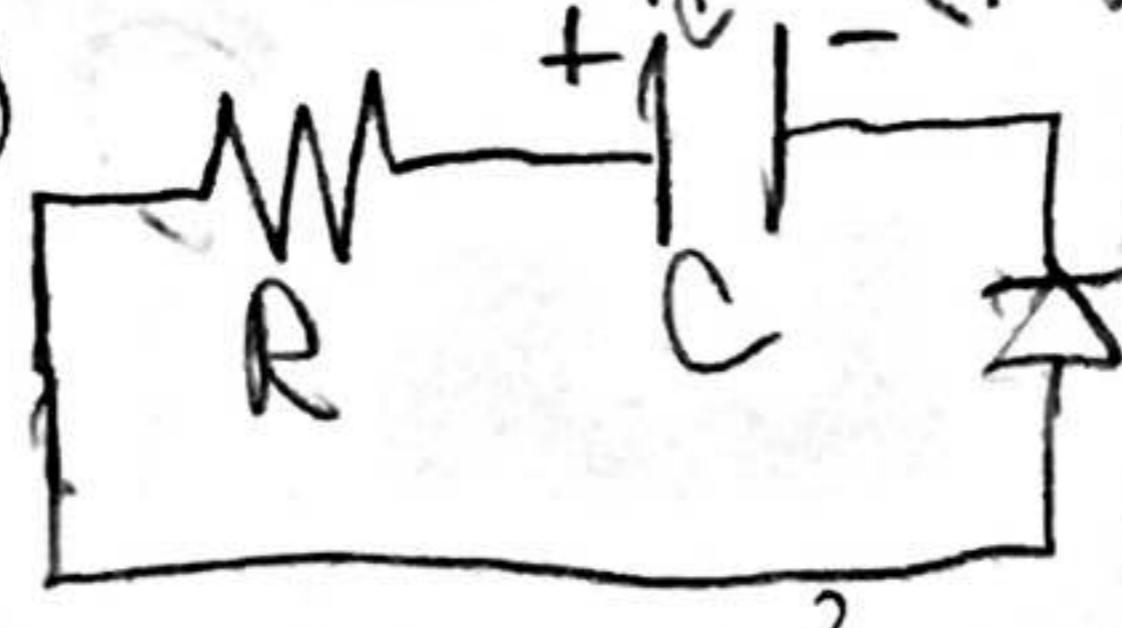

$v_c < 0$, so current flows clockwise, so diode is off


equivalently,

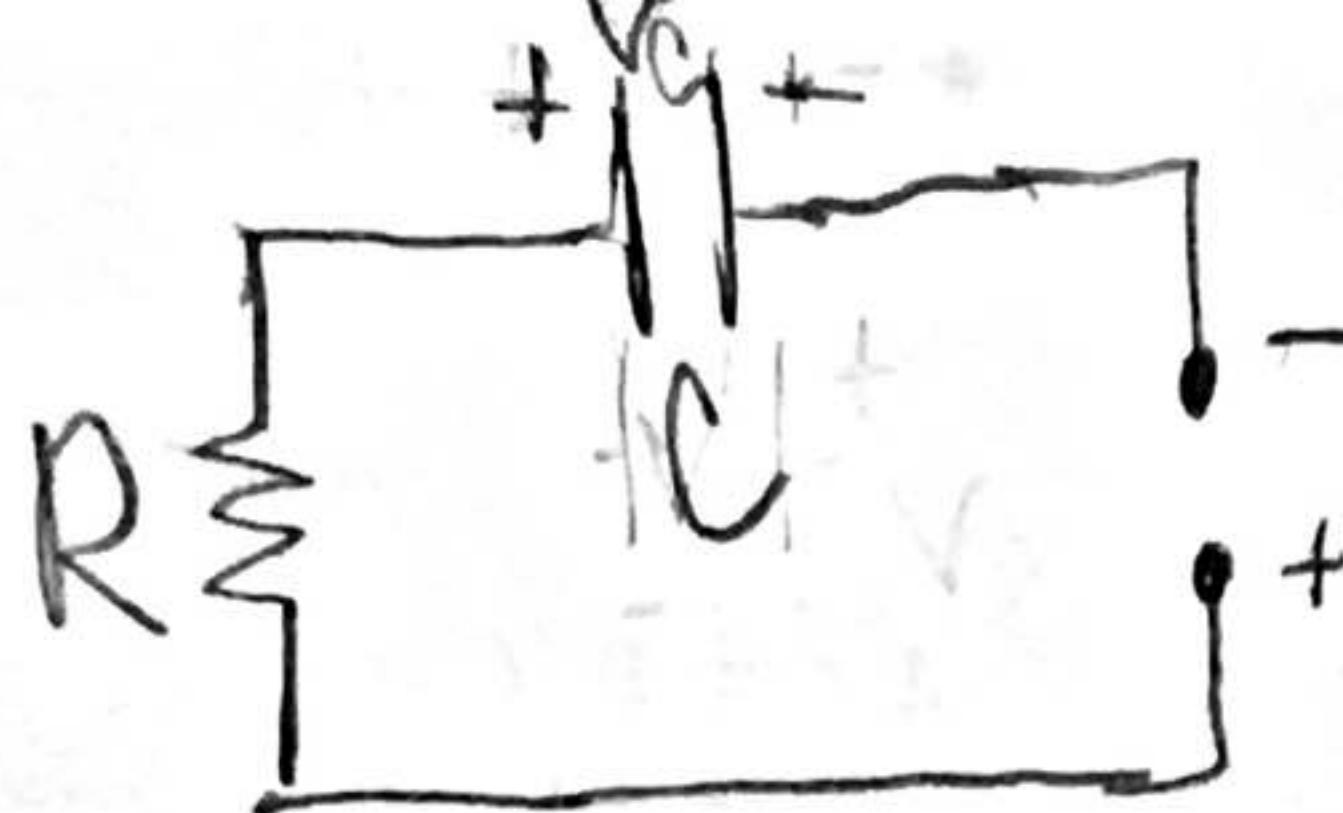

$$V_C = V_D = -(1 - e^{-t})$$


$V_D < 0 \Rightarrow$ diode must be off
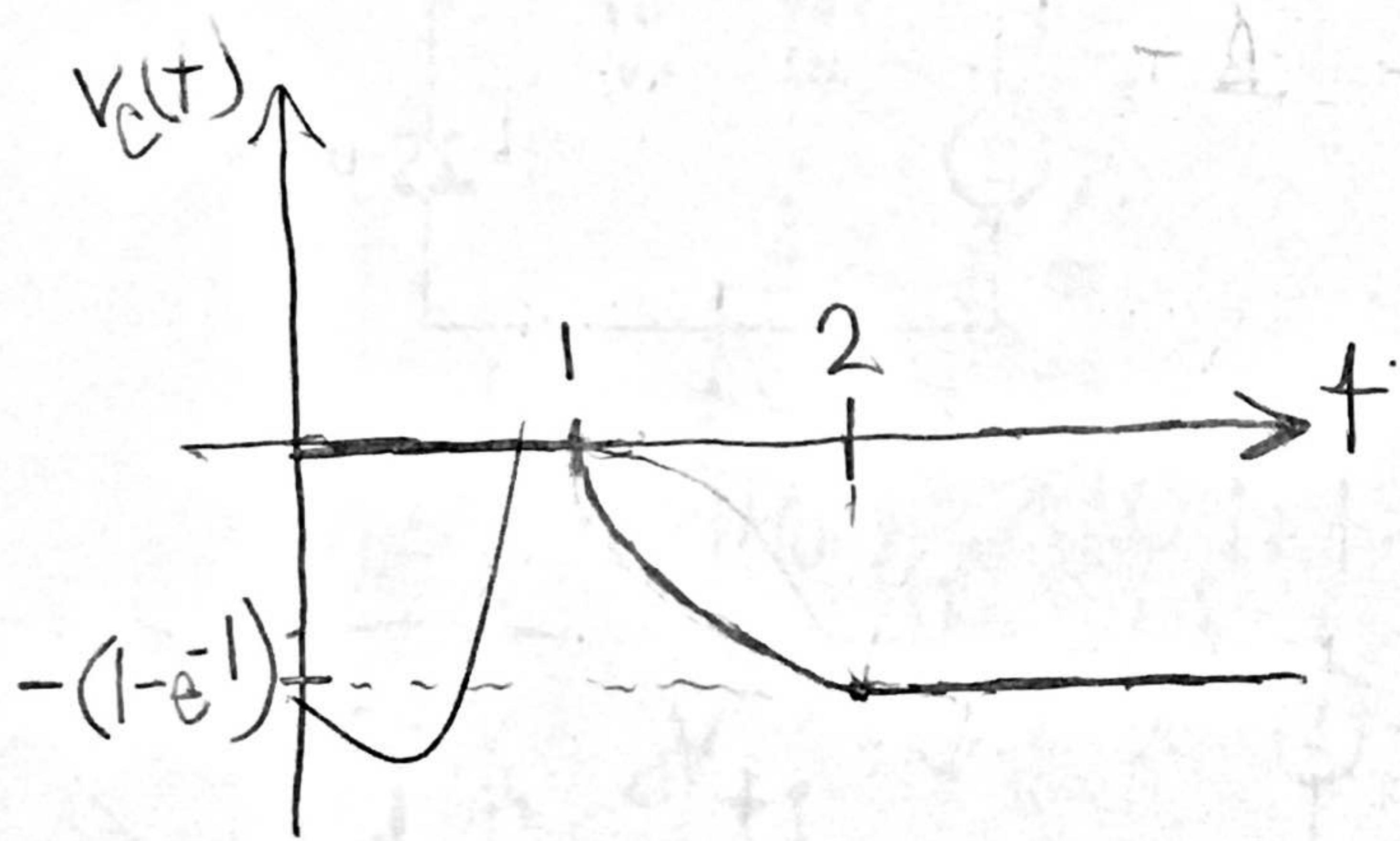
$$V_C(t) = \begin{cases} 0 & 0 < t \leq 1 \\ -(1 - e^{-(t-1)}) & 1 < t \leq 2 \\ -(1 - e^{-1}) & t > 2 \end{cases}$$



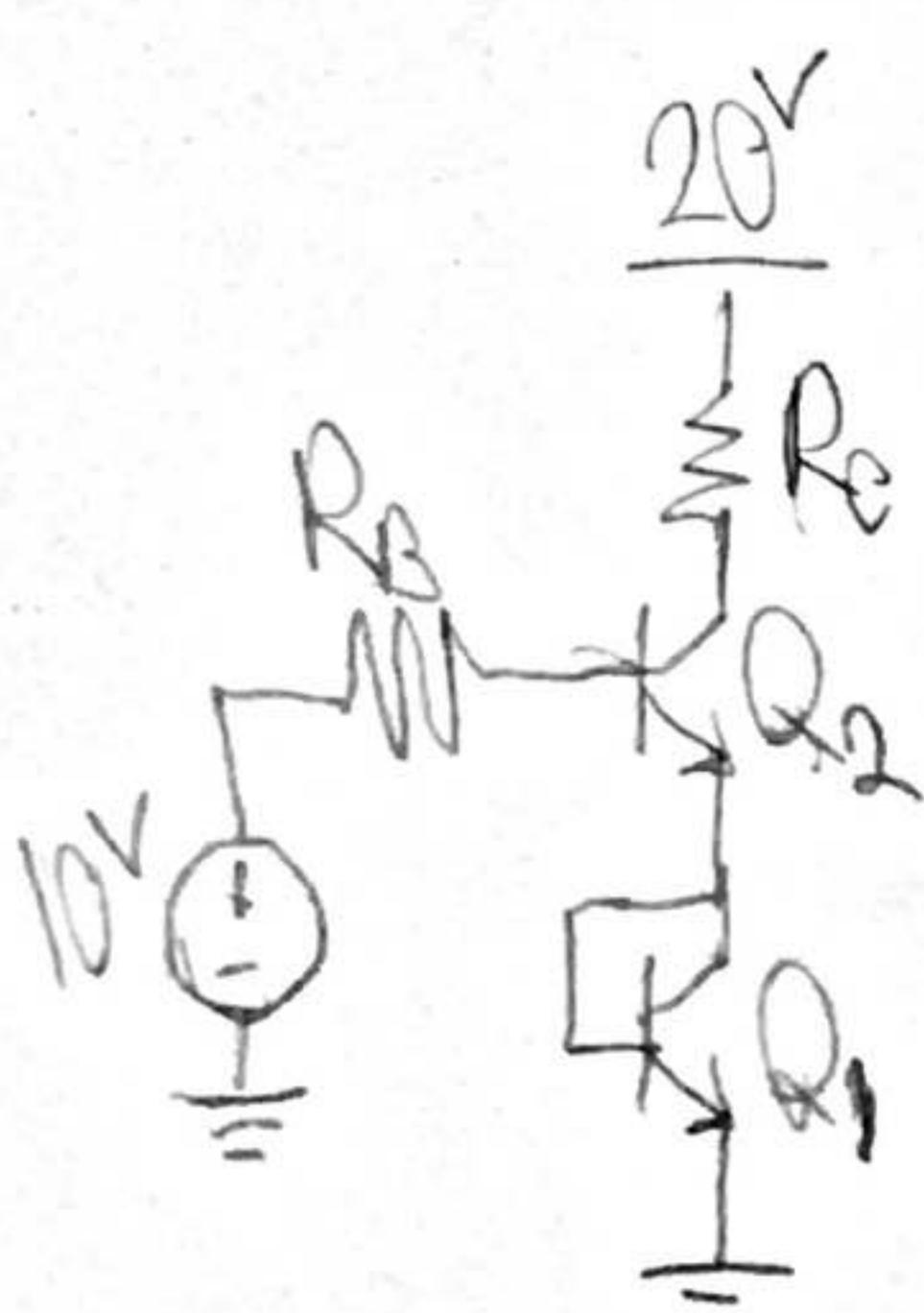
2. For the circuit below, let $I_{ES} = 1\text{pA}$, $V_A = \infty$, $\beta = 100$, $V_{CE,SAT} = 0.2\text{V}$, $R_B = 89\text{k}\Omega$.

- For $R_C = 1\text{k}\Omega$, find the exact transistors operating point and the region of operation.
- Using $V_{BE,ON} = 0.6\text{V}$ approximation, find the maximum value of R_C that puts Q_2 on the edge of saturation.



$$I_B = \frac{I_C}{\beta} = \frac{I_E}{\beta + 1}$$

$$I_C = \frac{\beta + 1}{\beta} I_E$$

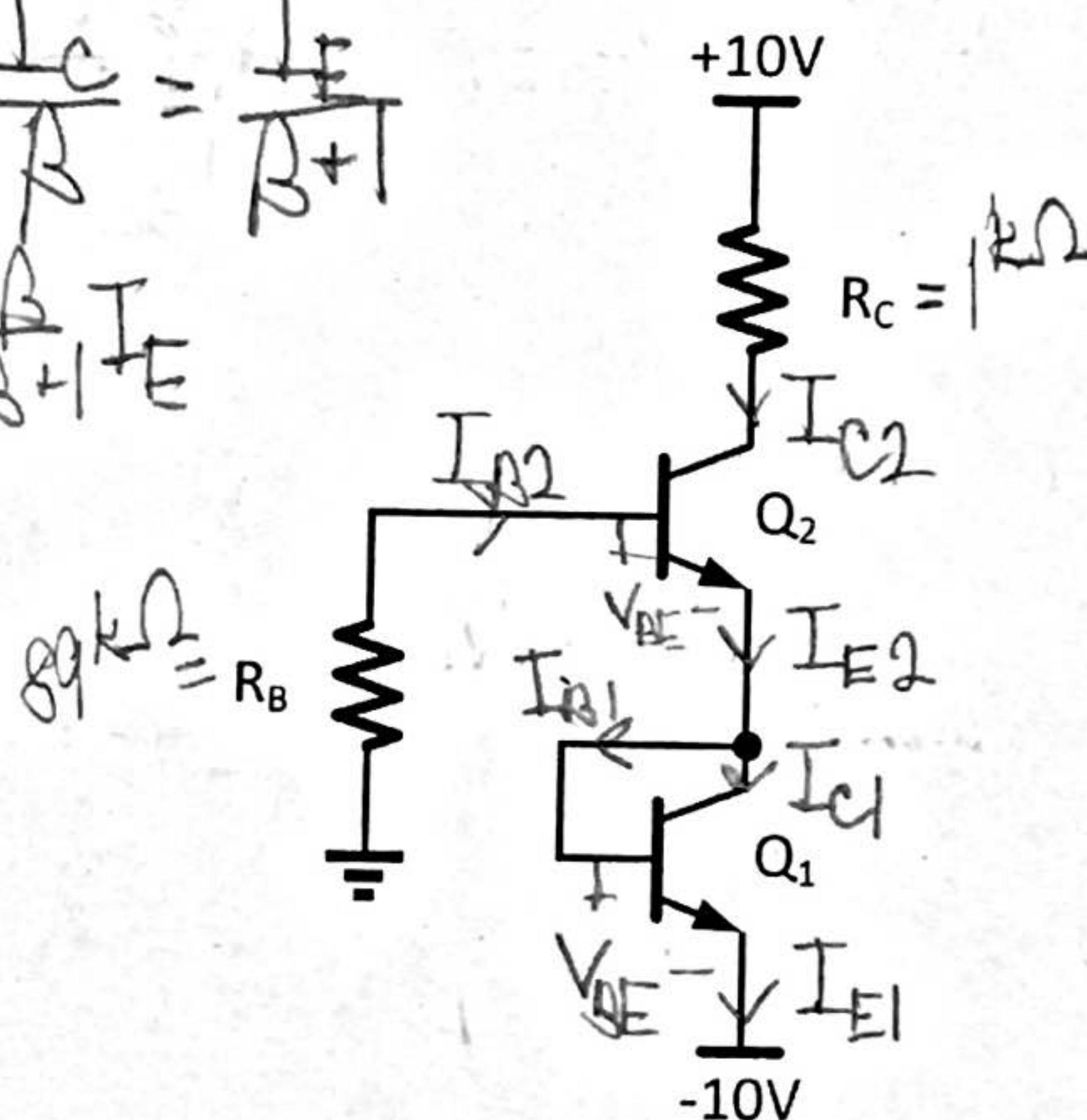

$$I_C = I_{ES} (e^{V_{BE} N_T} - 1)$$

$$= \frac{\beta}{\beta + 1} I_{ES} (e^{V_{BE} N_T} - 1)$$

$$\text{a) } 10V - I_B R_C - V_{CE2} - V_{BE,ON} = -10V$$
~~$$10V - I_B R_C - V_{CE2} - V_{BE,ON} = -10V$$~~

$$\text{KVLs} \rightarrow 0 - I_{B2} R_B - V_{BE} - V_{BE,ON} = -10V$$

$$I_{B2} = \frac{I_{C2}}{\beta} \quad \frac{10 - I_{B2} R_B}{2} = V_{BE,ON} = 5 - \frac{I_{ES} (e^{V_{BE,ON} N_T} - 1) R_B}{(\beta + 1) \cdot 2}$$

$$5 - \frac{I_{ES} (e^{V_{BE,ON} N_T} - 1) R_B}{2(\beta + 1)} - V_{BE,ON} = 0$$

graph and
find zero

$$V_{BE,ON} = 0.596356 \approx 0.596\text{V}$$

$$I_{C2} = \frac{\beta}{\beta + 1} I_{ES} (e^{V_{BE,ON} N_T} - 1) \Rightarrow I_{C2} = 9.90\text{ mA}$$

$$I_{C1} = I_{E2} \text{ b/c same } V_{BE,ON} \text{ so } I_{C1} = 9.90\text{ mA}$$

$$I_B = \frac{I_C}{\beta}$$

$$I_E = \frac{\beta + 1}{\beta} I_C$$

$$I_{Q1} = I_{Q2} = 99.0\text{ }\mu\text{A}$$

$$I_{E1} = I_{E2} = 9.99\text{ mA}$$

$$KVL: 10V - I_{C2}R_C - V_{CE,2} - V_{BE,on} = -10V$$

$$\underline{V_{CE,2} = 20V - I_{C1}R_C - V_{BE,on} = 9.5V > V_{CE,sat}}$$

Q_2 is in forward active

$$KVL: -I_{B2}R_B - V_{BE,2} - V_{CE,1} = -10V$$


$$10V - I_{B2}R_B - V_{BE,2} = V_{CE,1} = 0.596V > V_{CE,sat}$$

Q_1 is in forward active

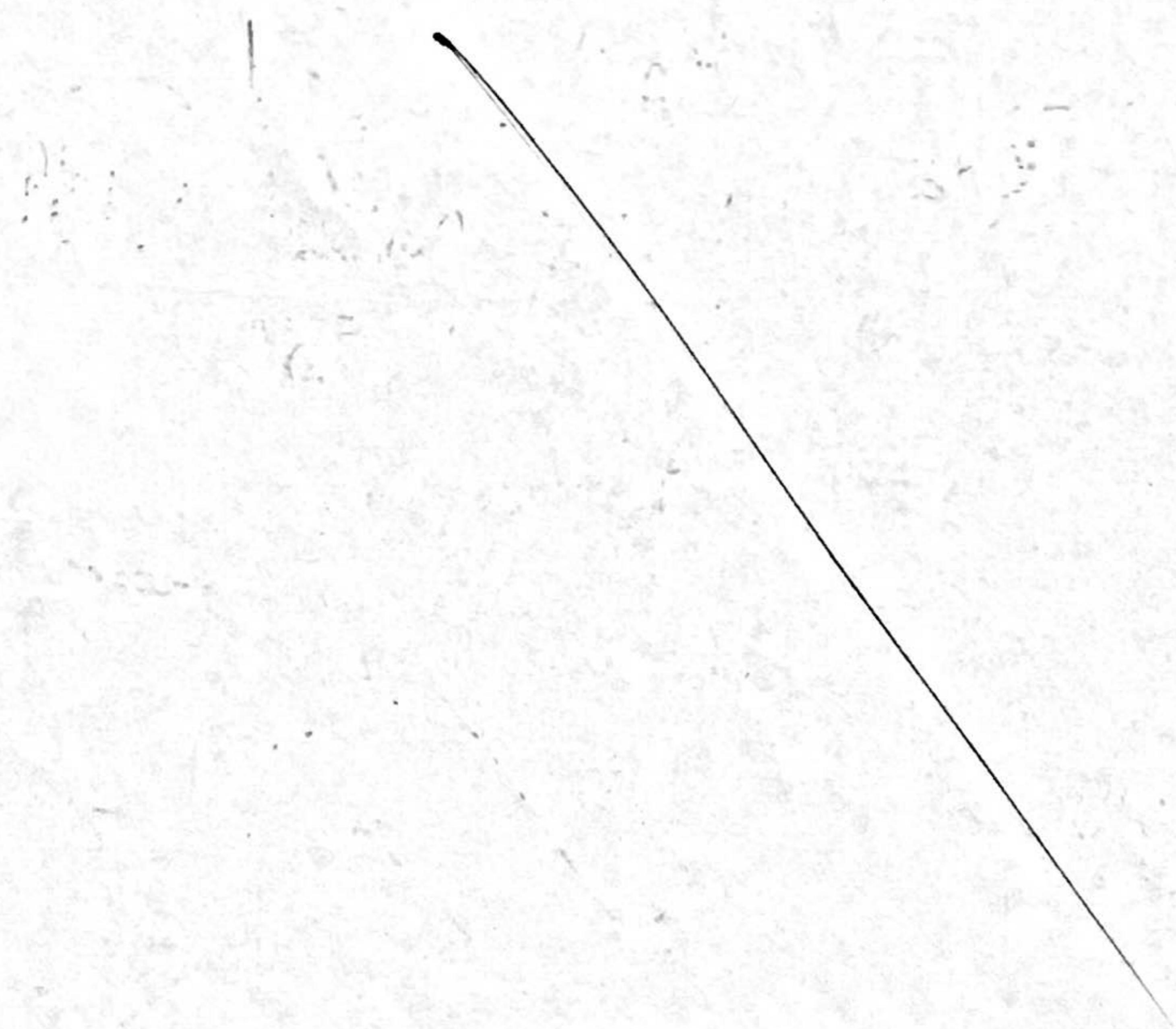b) for edge of saturation, $V_{CE,2} = V_{CE,sat}$

$$10V - I_{C2}R_{C,max} - V_{CE,sat} - V_{BE,on} = -10V$$


$$\frac{20V - V_{CE,sat} - V_{BE,on}}{I_{C2}} = \boxed{R_{C,max} = 1940\Omega}$$



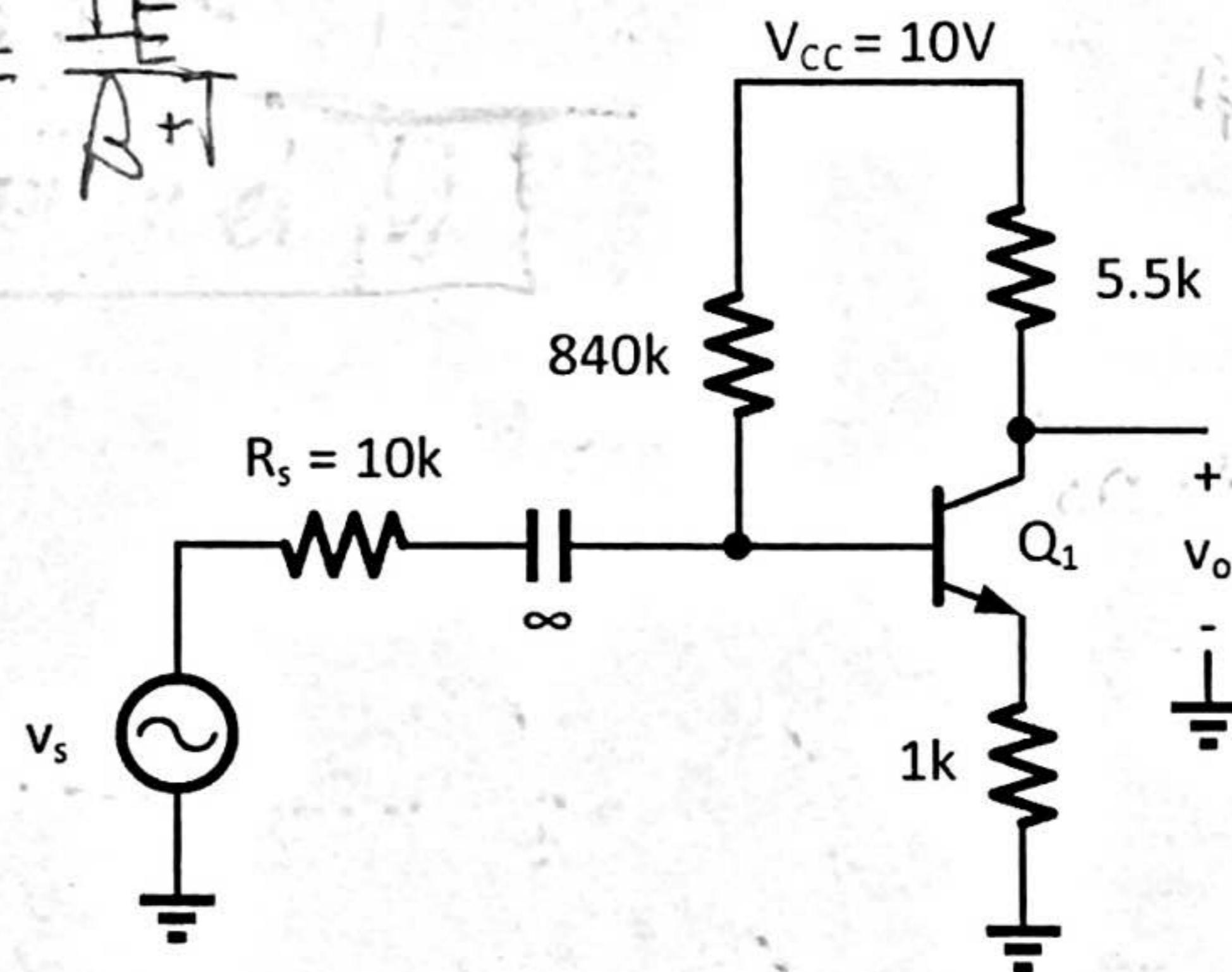
3. In the common-emitter amplifier below, $V_{BE,ON} = 0.6V$, $V_A = \infty$, $\beta = 100$, $V_{CE,SAT} = 0.2V$.

- Find the DC operating point and the transistor region of operation.
- Calculate the amplifier small signal voltage gain ($\frac{v_o}{v_s}$).

$$I_B = \frac{I_C}{\beta} = \frac{I_E}{\beta + 1}$$



$$I_B(\beta+1) = I_E$$

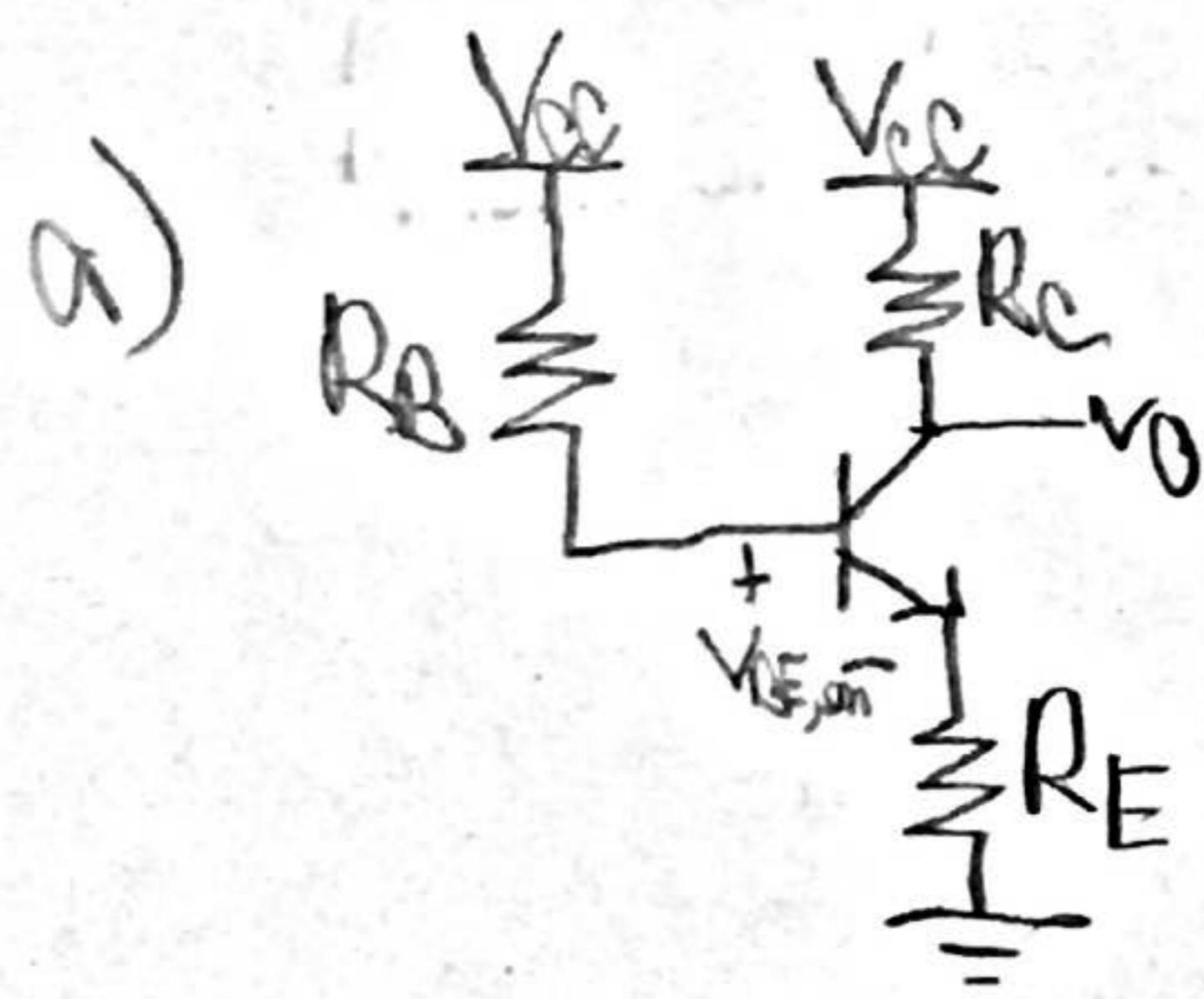

$$V_{CC} - I_B R_B - V_{BE,ON} - I_E R_E = 0$$

$$V_{CC} - V_{BE,ON} = I_B (R_B + (\beta+1)R_E)$$

$$I_B = \frac{V_{CC} - V_{BE,ON}}{R_B + R_E(\beta+1)} = 9,99 \mu A$$


$$I_C = \beta I_B = 0,999 mA$$

$$I_E = (\beta+1) I_B = 1,01 mA$$

$$10V - I_C R_C - V_{CE} - I_E R_E = 0$$

$$V_{CE} = 10V - I_C R_C - I_E R_E = 3,50V > V_{CE,SAT}$$

Q_1 is in forward active

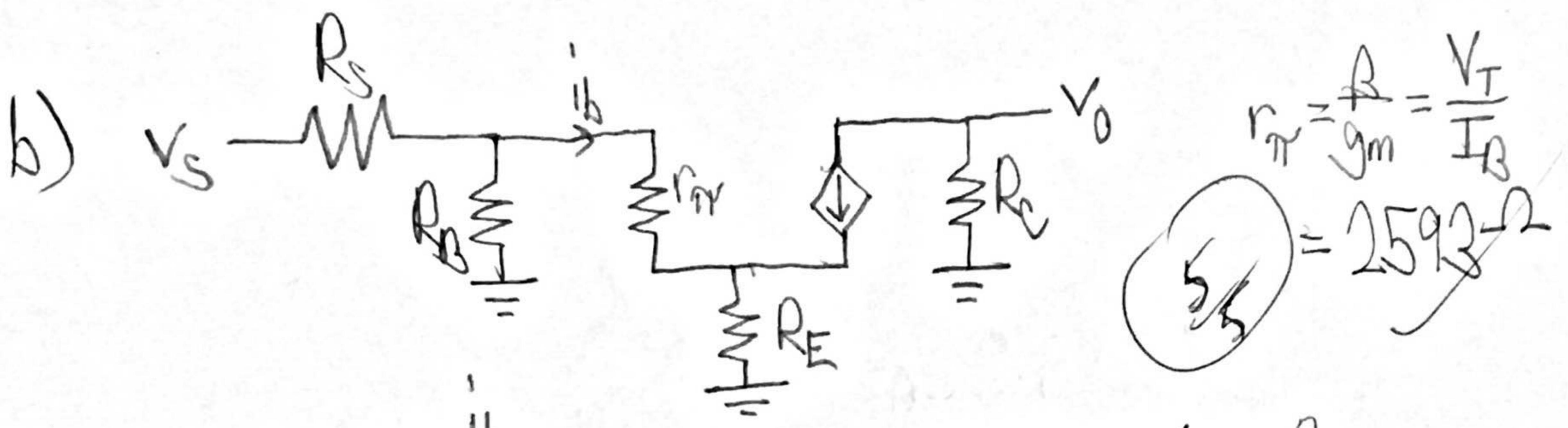


$$\frac{V_s}{R_s} \cdot \frac{R_s R_B}{R + R_B} = \frac{R_B}{R + R_B} V_s$$

$$\frac{V_s}{R_s} \frac{R_B}{R + R_B} \parallel$$

$$V_s' \approx 0.988 V_s$$
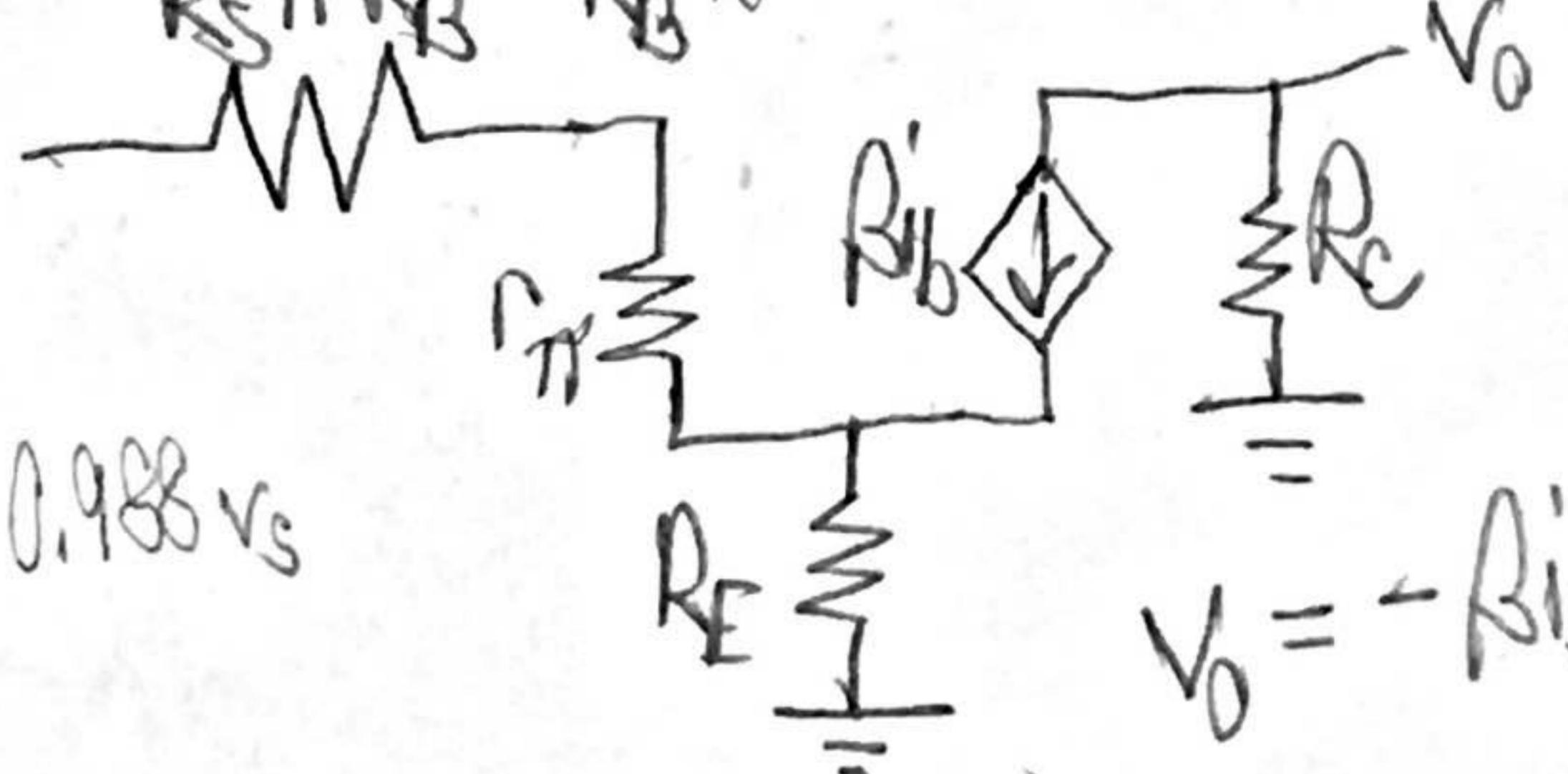
$$R_s \parallel R_B = R'_B \approx 988 \Omega$$



$$V_s' - i_b R'_B - i_b r_{\pi} - (\beta + 1) i_b R_E = 0$$

$$\frac{V_s'}{R'_B + r_{\pi} + (\beta + 1) R_E} = i_b = V_s \frac{\frac{R_B}{R_s + R_B}}{(\beta + 1) R_E + r_{\pi} + (\beta + 1) R_E} \approx \frac{V_s}{(\beta + 1) R_E}$$

$$\boxed{\frac{V_o}{V_s} = - \frac{\beta \frac{R_o R_E}{R_s + R_B}}{(\beta + 1) R_E + r_{\pi} + (\beta + 1) R_E} = -4.79}$$

$$R_B = 840 \text{ k}\Omega, R_E = 5.5 \text{ k}\Omega, r_{\pi} = 2593 \Omega, R_C = 1 \text{ k}\Omega, R_s = 10 \text{ k}\Omega$$

$$\frac{V_o}{V_s} = \frac{-\beta R_C}{(\beta + 1) R_E} = -\alpha \frac{R_C}{R_E} = -5.55$$

sanity check: using i_b approximation,

Good.

gain approximation
for CE w/ degeneration