



Name: _____

UID: _____

Total of 3 questions, 120 minutes.

P1 (30)	27
P2 (30)	30
P3 (40)	40
Total (100)	97

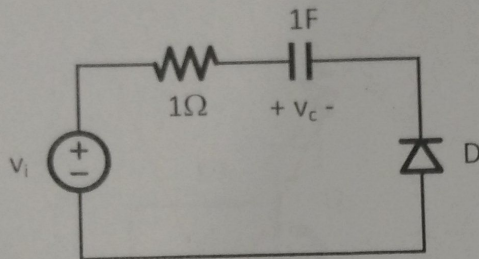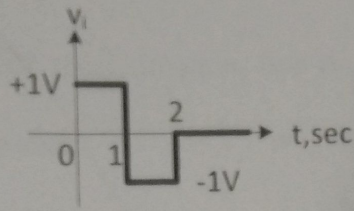1. The circuit shown below is in zero state at $t = 0$. Calculate and plot the capacitor voltage ($v_c(t)$) for $t \geq 0$ given the input signal shown. The diode is ideal.




$$\tau = RC = 1 \text{ sec}$$

From $t=0 \rightarrow t=1$, no current flows
 $t=1 \rightarrow t=2$, capacitor charges according to $-(1 - e^{-(t-1)})$
 $t=2 \rightarrow t \rightarrow \infty$, no current flows.

$$v_c(2) = -(1 - e^{-(2-1)}) = -(1 - e^{-1}) = e^{-1} - 1$$
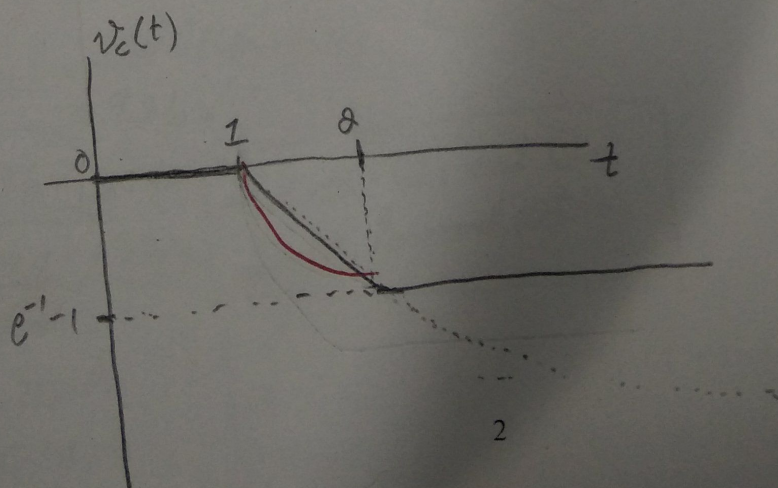
$$v_c(t) = \begin{cases} 0 & 0 \leq t < 1 \\ e^{-(t-1)} - 1 & 1 \leq t < 2 \\ e^{-1} - 1 & 2 \leq t \end{cases}$$



2. For the circuit below, let $I_{ES} = 1 \mu A$, $V_A = \infty$, $\beta = 100$, $V_{CE,SAT} = 0.2V$, $R_B = 89k\Omega$.

a. For $R_C = 1k\Omega$, find the exact transistors operating point and the region of operation.

b. Using $V_{BE,ON} = 0.6V$ approximation, find the maximum value of R_C that puts Q_2 on the edge of saturation.

(a) Assume Forward Active

$$V_{BE} = V_T \ln \frac{I_E}{I_{ES}}$$

$$V_{BE1} = V_{C1} + 10$$

$$0 - V_{B2} = I_{E2} \frac{R_B}{\beta + 1}$$

$$V_{B2} = -\frac{R_B}{\beta + 1} I_{E2}$$

$$V_{E2} = V_{C1} = V_{BE1} - 10$$

$$\Rightarrow V_{E2} = V_{BE2} - 10$$

$$V_{BE2} = V_{B2} - V_{E2} = -\frac{R_B}{\beta + 1} I_{E2} - V_{BE2} + 10$$

$$2V_{BE2} = -\frac{R_B}{\beta + 1} I_{E2} + 10$$

$$V_{BE2} = -440.6 I_{E2} + 5$$

$$= 4.406 \times 10^{-10} \exp \frac{V_{BE2}}{V_T} + 5$$

Solving for V_{BE2} , we find $V_{BE2} \approx 0.597V$

$$I_{E2} = 10.25mA$$

$$I_{C2} = \alpha I_{E2} = 10.14mA$$

$$I_{B2} = \frac{I_{E2}}{\beta + 1} = 0.101mA$$

$$V_{C2} = 10 - I_{C2}R_C = -1.4V$$

$$V_{CE2} = V_{C2} - V_{E1} = -1.4V - (-10 + 0.6)$$

$$= 9.26V$$


$V_{CE2} = 9.26V > 0.2$
 $V_{BE2} = 0.597V > 0.2$
 Both Q_1 and Q_2 are forward active

$$I_{B1} = I_{B2} = 0.101mA$$

$$I_{E1} = I_{E2} = 10.25mA$$

$$\Rightarrow I_{C1} = I_{C2} = 10.14mA$$



$$V_{CE1} = V_{BE1} \approx 0.597V$$

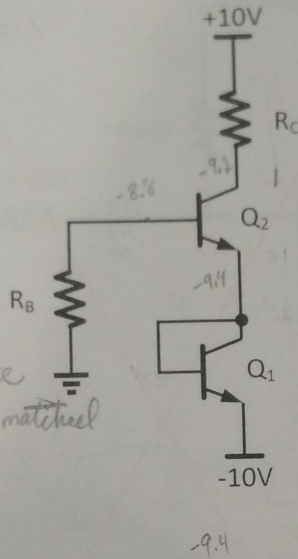

(b) $V_{C2} = -10 + 0.6 = -9.4V$
 $V_{B1} = V_{E1} + 0.6 = -9.4 + 0.6 = -8.8V$
 $I_{B1} = \frac{0 - (-8.8)}{R_B} = 98.9 \mu A$
 $I_{C1} = \beta I_{B1} = 9.89mA$
 $V_{C1} = 10 - I_{C1}R_C$
 $V_{CE} = 0.2 = V_{C1} - V_{E1}$
 $0.2 = 10 - I_{C1}R_C - (-9.4)$
 $I_{C1}R_C = 19.2V$
 $R_C = 1.94k\Omega$

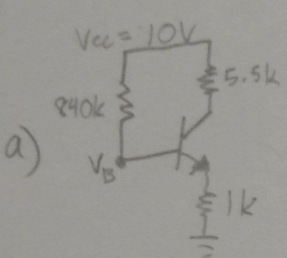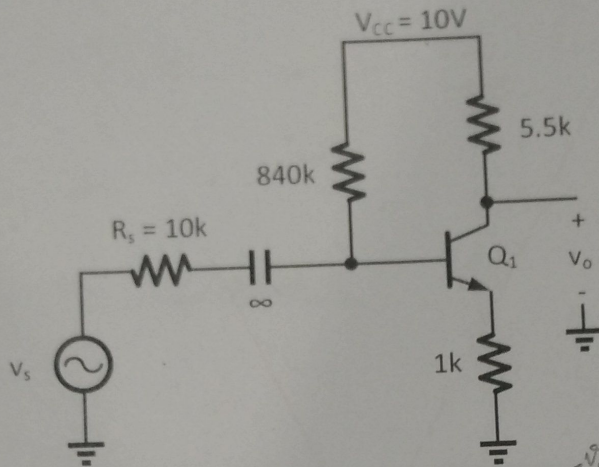3. In the common-emitter amplifier below, $V_{BE,ON} = 0.6V$, $V_A = \infty$, $\beta = 100$, $V_{CE,SAT} = 0.2V$.

- Find the DC operating point and the transistor region of operation.
- Calculate the amplifier small signal voltage gain ($\frac{v_o}{v_s}$).



$$\frac{V_B - V_{CC}}{840k} + \left(\frac{V_B - V_{BE,ON}}{1k} \right) \frac{1}{\beta + 1} = 0$$

$$\left(\frac{1}{840k} + \frac{1}{(\beta + 1)1k} \right) V_B = \frac{10}{840k} + \frac{0.6}{101k}$$

$$1.109 \times 10^{-5} V_B = 1.785 \times 10^{-5}$$

$$V_B = 1.61V$$

$$\Rightarrow V_E = 1.01V$$

15/15

$$I_E = \frac{V_E}{1k} = 1.01mA$$

$$I_C = \alpha I_E = 1mA$$

$$I_B = \frac{I_C}{\beta} = 10\mu A$$

$$V_{CE} = V_{CC} - I_C(5.5k) - V_E$$

$$V_{CE} = 3.49V > 0.2V$$


$$V_{BE} = 0.6V$$

$$V_T = 26mV$$

$$g_m = \frac{I_C}{V_T} = 38.6mS$$

$$r_{\pi} = \frac{\beta}{g_m} = 2.59k\Omega$$

Region of Operation: Forward Active

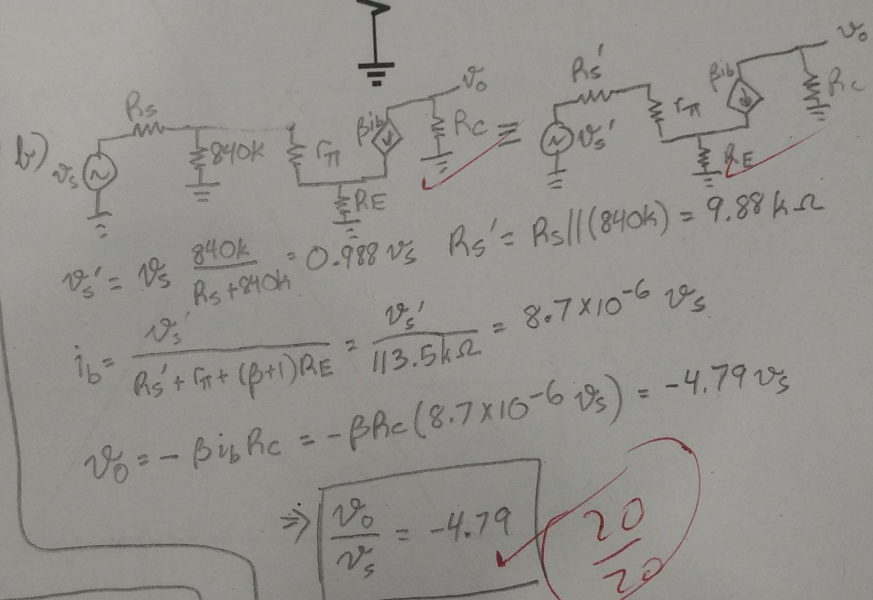

$$v_s' = v_s \frac{840k}{R_s + 840k} = 0.988 v_s$$

$$R_s' = R_s || (840k) = 9.88k\Omega$$

$$i_b = \frac{v_s'}{R_s' + r_{\pi} + (\beta + 1)R_E} = \frac{v_s'}{113.5k\Omega} = 8.7 \times 10^{-6} v_s$$

$$v_o = -\beta i_b R_C = -\beta R_C (8.7 \times 10^{-6} v_s) = -4.79 v_s$$

$$\Rightarrow \frac{v_o}{v_s} = -4.79$$

20/20

5/5