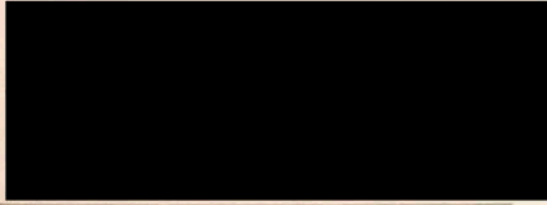


ECE115A


Midterm Exam

Fall 2019

Name:





UID:

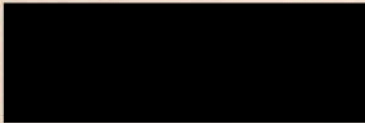


Total of 3 questions, 120 minutes.

P1 (30)	30
P2 (30)	30
P3 (40)	40
Total (100)	100

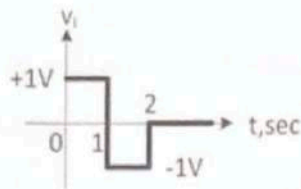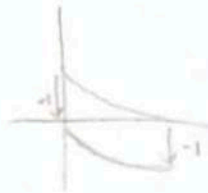1. The circuit shown below is in zero state at  $t = 0$ . Calculate and plot the capacitor voltage ( $v_c(t)$ ) for  $t \geq 0$  given the input signal shown. The diode is ideal.




$$e^{-\frac{t}{\tau}}$$

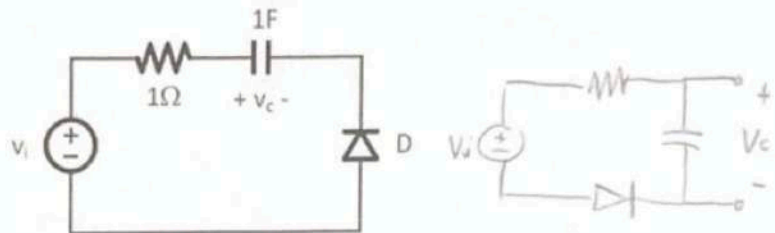

At  $t=0$ :

D is off due to reverse-active.

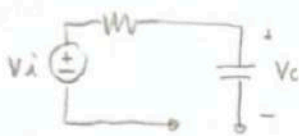

→ no current flows, thus  $V_c(t) = 0$

At  $t=1$ :

D is on due to forward active.



→ a simple charging capacitor

$$V_c(t) = -1(1 - e^{-\frac{t-1}{\tau}}) \quad \tau = RC = 1$$

$$= -(1 - e^{-t})$$

$$= (e^{-t} - 1)$$

$$\rightarrow V_c(t) = e^{-(t-1)} - 1$$


(account for the time when it actually starts charging)

$$t=1: e^0 = 1$$

$$t=2: e^{-1} = 1/e$$

At  $t=2$ :

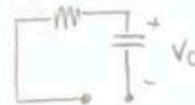
D is off due to no bias (not forward active).



→ again, no current flows, meaning capacitor is unable to discharge:

→ maintains voltage from before:
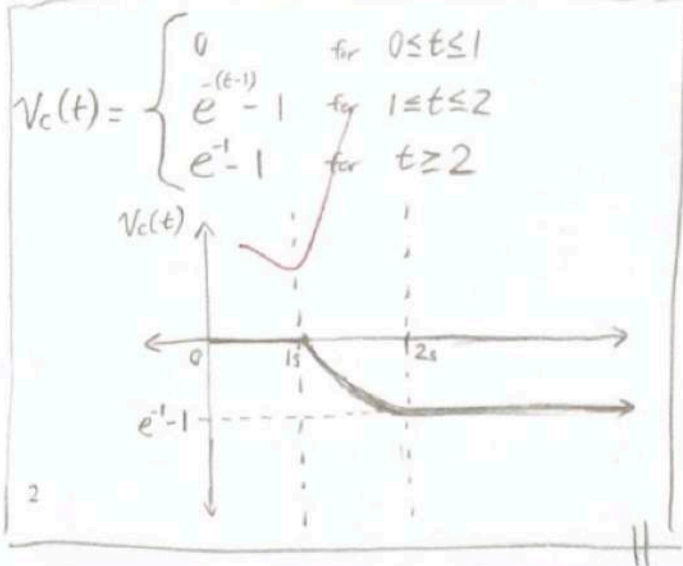
$$V_c(t) = (e^{-1} - 1) \leftarrow \text{hence, } t=1 \text{ since it only charged for } t=1 \text{ seconds}$$



no early effect  
 2. For the circuit below, let  $I_{ES} = 1 \mu A$ ,  $V_A = \infty$ ,  $\beta = 100$ ,  $V_{CE,SAT} = 0.2V$ ,  $R_B = 89k\Omega$ .

a. For  $R_C = 1k\Omega$ , find the exact transistors operating point and the region of operation.

$$V_T = 0.026V$$

b. Using  $V_{BE,ON} = 0.6V$  approximation, find the maximum value of  $R_C$  that puts  $Q_2$  on the edge of saturation.

a)

$$I_{ES} = 1 \mu A = 1 \times 10^{-6} A$$

$$I_E = I_{ES} \left( \exp\left(\frac{V_{BE,ON}}{V_T}\right) - 1 \right)$$

KVL:

$$-10 + 2V_{BE,ON} + (89k)I_{B2} = 0 \dots (1)$$

Assume forward active:

$$\left. \begin{aligned} I_C &= \alpha I_E \\ I_C &= \beta I_B \end{aligned} \right\} \left( \frac{\beta}{\beta+1} \right) I_E = \beta I_B$$

$$I_B = \frac{I_E}{\beta+1}$$

$$I_{B2} = \frac{I_{ES} \left( \exp\left(\frac{V_{BE,ON}}{V_T}\right) - 1 \right)}{\beta+1} \dots (2)$$

Using (1) & (2):

$$-10 + 2V_{BE,ON} + 89000 \left( \frac{10^{-12} \left( \exp\left(\frac{V_{BE,ON}}{0.026}\right) \right)}{101} \right) = 0$$

→ solve non-linear equation:

$V_{BE,ON}$  Result: ← trying to get 0

0.6	+0.4736
0.65	+54.7499
0.595	-1.1588
0.598	-0.21699
0.599	+0.1217


$$V_{BE,ON} = 0.599V$$

Check:  $V_{CE1} = (-9.4010V) - (-10V) = 0.599V > V_{CE,SAT} (0.2V)$   
 →  $Q_1$  also confirmed forward active

$$I_{E1} = I_{E2} = 9.9888 \times 10^{-3} A$$

$$I_{C1} = \alpha I_{E1} = \frac{100}{101} I_{E1}$$

$$I_{C1} = 9.8899 \times 10^{-3} A$$

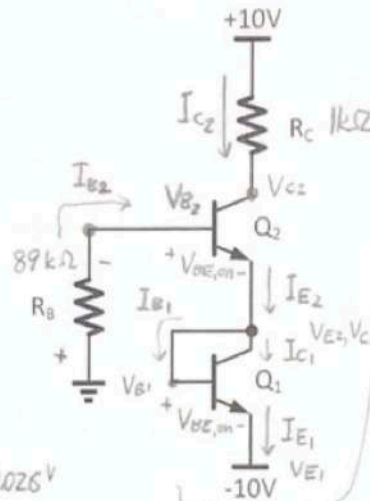

a) continued:

$$-10 + 2(0.599V) + (89k)I_{B2} = 0$$

$$89000 I_{B2} = 8.802$$

$$I_{B2} = 9.8899 \times 10^{-5} A$$

$$I_{C2} = \beta I_{B2}$$

$$I_{C2} = 9.8899 \times 10^{-3} A$$

$$I_{E2} = (\beta+1) I_{B2}$$

$$I_{E2} = 9.9888 \times 10^{-3} A$$

$$V_{C2} = 10 - (1k\Omega)I_{C2}$$

$$V_{C2} = 0.1101V$$

$$V_{E2} = -10 + V_{BE,ON}$$

$$V_{E2} = -9.4010V$$

Check:  $V_{CE2} = (0.1101V) - (-9.4010V) = 9.5111V > V_{CE,SAT} (0.2V)$   
 →  $Q_2$  confirmed forward active

$$V_{C1} = V_{B1} = V_{E2} = -9.4010V$$

$$V_{E1} = -10V$$

$$V_{B2} = -89k(I_{B2})$$

$$V_{B2} = -8.8020V$$

$$g_m = \frac{I_C}{V_T}$$

$$g_m = 0.3804 \frac{1}{\Omega}$$


$$I_{B1} = I_{E1} - I_{C1}$$

$$I_{B1} = 9.89 \times 10^{-5} A$$

$$r_\pi = \frac{\beta}{g_m}$$

$$r_\pi = 262.8745 \Omega$$

b) on the back

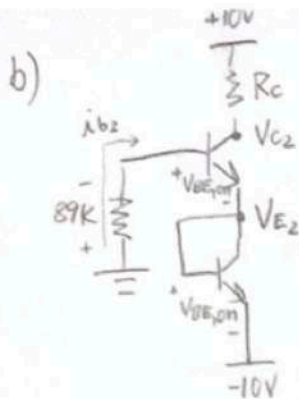

$$-10 + 2(0.6) + 89k(I_{B2}) = 0$$

$$89000(I_{B2}) = 8.8V$$

$$I_{B2} = 9.8876 \times 10^{-5} A$$

Edge of saturation:

$$I_{C2} = \beta I_{B2} \leftarrow \text{still holds}$$

$$I_{C2} = (100) I_{B2}$$

$$= 9.8876 \times 10^{-3} A$$

$$V_{C2} = 10 - I_{C2} R_C \dots \textcircled{1}$$

$$V_{E2} = -10 + V_{BE,on} = -9.4V \dots \textcircled{2}$$

Using  $\textcircled{1}$  &  $\textcircled{2}$

$$V_{CE} = V_{C2} - V_{E2}$$

$$V_{CE} = (10 - I_{C2} R_C) - (-9.4) \geq 0.2V$$

↑  
in order to be on edge of saturation

$$-I_{C2} R_C \geq -19.2V$$

$$R_C \leq \frac{19.2}{9.8876 \times 10^{-3}}$$

$$R_C = 1941.8261 \Omega$$

← max  $R_C$  value that puts  $Q_2$  in edge of saturation

3. In the common-emitter amplifier below,  $V_{BE,ON} = 0.6V$ ,  $V_A = \infty$ ,  $\beta = 100$ ,


$V_{CE,SAT} = 0.2V$ .

$V_T = 0.026V$

- Find the DC operating point and the transistor region of operation.
- Calculate the amplifier small signal voltage gain ( $\frac{v_o}{v_s}$ ).

$I_c = \alpha I_E$   
 $I_c = \beta I_B$   
 $\alpha I_E = \beta I_B$   
 $\frac{\alpha}{\beta+1} I_E = \beta I_B$   
 $I_E = (\beta+1) I_B$

→ Assume forward active: (check later!)

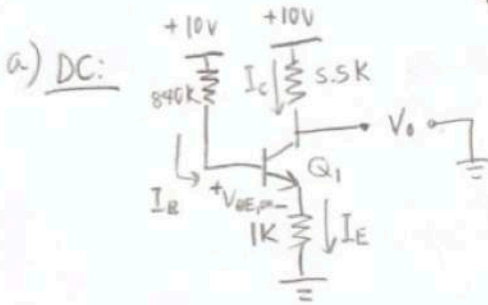

KVL:

$10 - 840000(I_B) - V_{BE,ON} - 1000(I_E) = 0$

$10 - 840000(I_B) - 0.6 - 1000(101 \cdot I_B) = 0$

$9.4 = I_B(840000 + 101000)$

$9.4 = I_B(941000)$

$I_B = 9.9894 \times 10^{-6} A$

$I_C = \beta I_B = 9.9894 \times 10^{-4} A$

$I_E = (\beta+1) I_B = 1.0089 \times 10^{-3} A$

a) continued:

$V_E = I_E(1k)$

$V_E = 1.0089V$

$V_C = 10 - I_C(5.5k)$

$V_C = 4.5058V$

check:


$V_{CE} = V_C - V_E = (4.5058) - (1.0089)$   
 $= 3.4969 > V_{CE,SAT}$

→ Q1 confirmed to be forward-active

$V_B = 10 - I_B(840k)$

$V_B = 10 - 8.3911$

$V_B = 1.6089V$

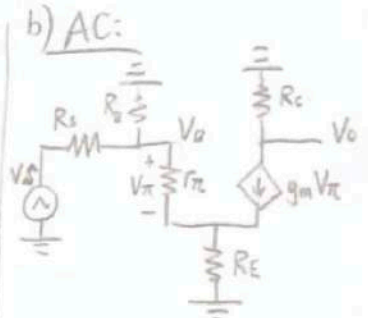

$V_B = \frac{R_B \parallel (r_{\pi} + (\beta+1)R_E)}{R_{in} \parallel (r_{\pi} + (\beta+1)R_E) + R_s} V_s$

$r_{\pi} + (\beta+1)R_E = 103602.7589\Omega$

$R_B \parallel R_{tot} = 92227.7056\Omega$

$V_B = 0.9021791603 V_s$

$\frac{V_o}{V_s} = 0.9021791603$

see backside

$g_m = \frac{I_C}{V_T}, r_{\pi} = \frac{\beta}{g_m}$   
 $V_T = 0.026V$


$g_m = 0.03842076923$

$g_m = 0.0384 \mu S$

$r_{\pi} = 2602.7589\Omega$

5/5

b) continued:

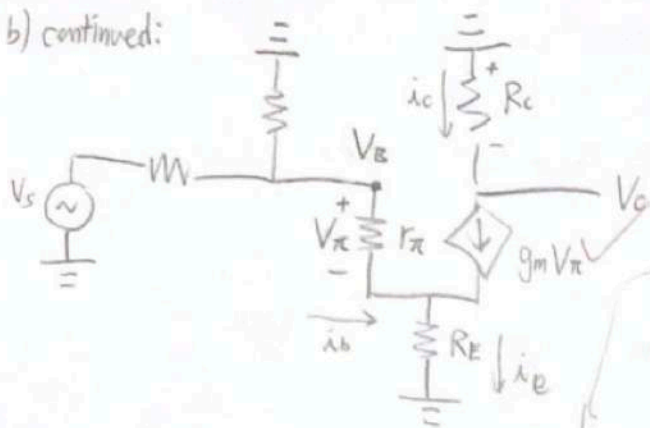

$$\frac{V_o}{V_s} = \frac{V_B}{V_s} \cdot \frac{V_\pi}{V_B} \cdot \frac{V_o}{V_\pi}$$

KVL:

$$V_B = R_E i_e + V_\pi \dots (1)$$

KCL:

$$\frac{V_\pi}{r_\pi} + g_m V_\pi = i_e$$

$$V_\pi \left( \frac{1}{r_\pi} + g_m \right) = i_e \dots (2)$$

Using (1) & (2):

$$V_B = R_E \left( V_\pi \left( \frac{1}{r_\pi} + g_m \right) \right) + V_\pi$$

$$V_B = V_\pi \left( R_E \left( \frac{1}{r_\pi} + g_m \right) + 1 \right)$$

$$V_B = V_\pi \left( \frac{R_E}{r_\pi} + g_m R_E + 1 \right)$$

$$\frac{V_B}{V_\pi} = \left( \frac{1000 \Omega}{2602 \Omega} + (0.0384)(1000 \Omega) + 1 \right)$$

$$\frac{V_B}{V_\pi} = 39.7842$$

$$\frac{V_\pi}{V_B} = 0.02513560174$$

$$V_o = -i_c R_C$$

$$= -g_m V_\pi R_C$$

$$\frac{V_o}{V_\pi} = -g_m R_C$$

$$\frac{V_o}{V_\pi} = -211.2$$

$$\rightarrow \frac{V_o}{V_s} = \frac{V_B}{V_s} \cdot \frac{V_\pi}{V_B} \cdot \frac{V_o}{V_\pi} \checkmark$$

$$= (0.9022)(0.0251)(-211.2)$$

$$= -4.7827$$

20/20

check:

$$\frac{V_o}{V_s} = -\alpha \frac{R_C}{R_E + \frac{r_\pi + R_C}{\beta + 1}}$$

$$= -\left( \frac{100}{101} \right) \frac{(5500)}{(1000) + \frac{(2602) + (10000)}{101}}$$

$$= -4.8414 \checkmark$$

$$\approx -4.7827 \checkmark$$