
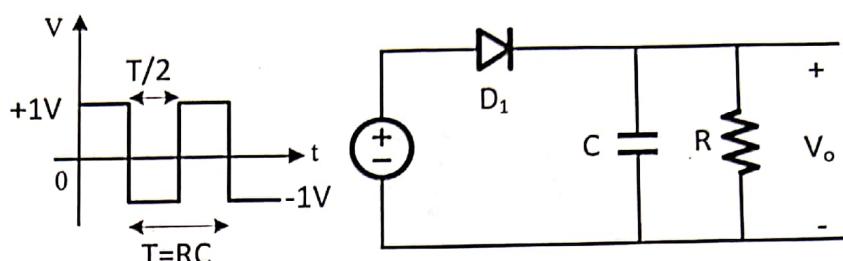


1. Plot the output voltage ( $V_o$ ) waveform for the peak detector shown below. The diode is ideal.

20

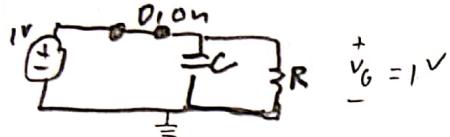

At  $t=0$ :




At  $t = \frac{RC}{2}$ :

$$V_o = 1V e^{-\frac{t-RC}{RC}}$$

(discharging)  $\Rightarrow$  decays to  $V_o = 1V e^{-\frac{RC/2}{RC}} = 0.606V$

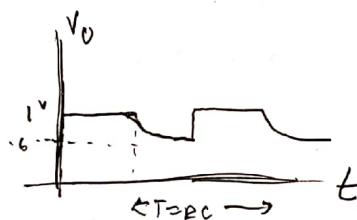At  $t = RC$ :  $V_o = 1V$  again and the cycles repeat.





30

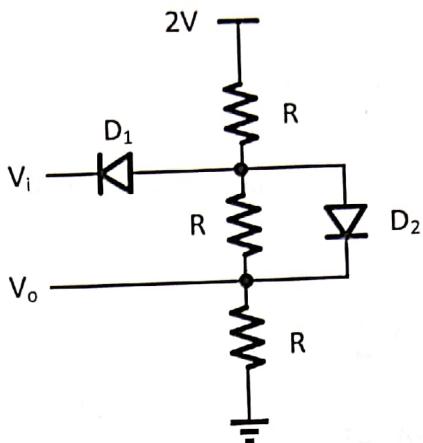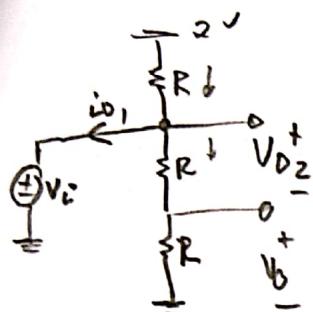2. For the following circuit, plot the output-input characteristics. The diodes are ideal.

sweep from  $V_i = -2V$  to  $1V$


at  $V_i = -2V$ ,  $D_1$  on,  $D_2$  off




$$\text{KCL: } i_{D_1} = \frac{2-V_i}{R} - \frac{V_i}{2R} > 0 \quad \text{turns off at } V_i = \frac{4}{3}V$$

$$\text{Voltage divider} \rightarrow V_{D_2} = \frac{V_i}{2} < 0 \quad \text{turns on at } V_i \geq 0 \quad \text{and} \quad V_o = \frac{V_i}{2}$$

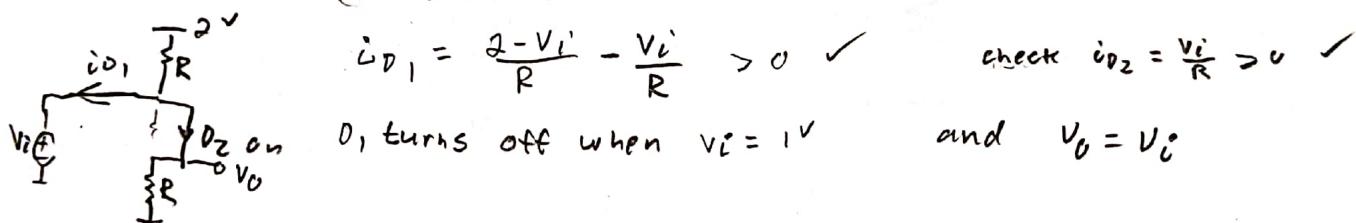$D_2$  turns on first: ( $\text{at } V_i \geq 0V$ )




at  $V_i > 1V$ :

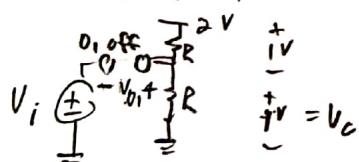

$$\text{Voltage divider: } V_o = 2V \left( \frac{R}{2R} \right) = 1V$$

$$i_{D_2} = 1V/R > 0 \quad \text{remains on}$$

$$V_{D_1} = -V_i < 0 \quad \text{off}$$

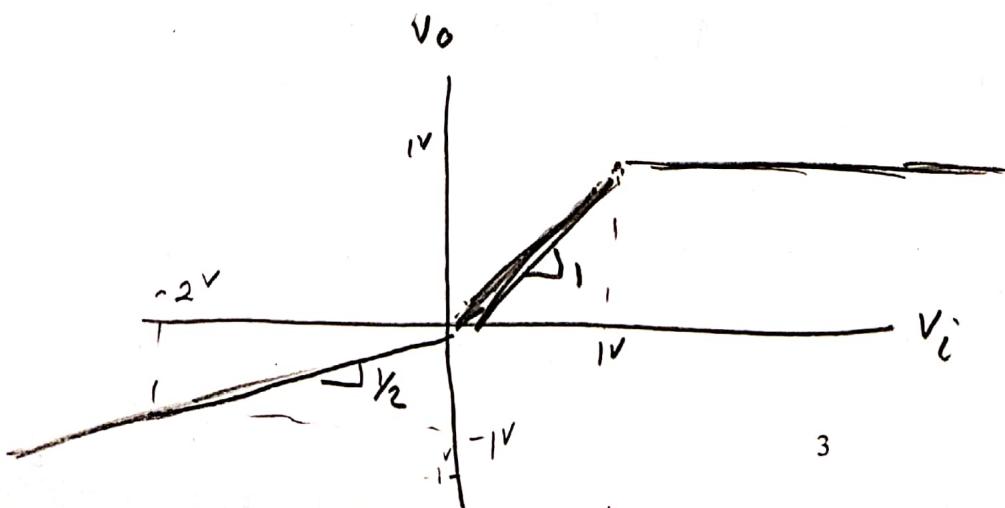

3


$$U_B = \frac{10}{6} = 2.5 \text{ mV}$$

3. A self-biased CE amplifier is shown below.

- Find the transistor DC operating points. Check what region of operation the transistor is biased at.
- Calculate the small signal voltage gain  $\frac{v_o}{v_s}$ , and the input impedance of the amplifier,  $R_{in}$ . The resistor  $R_B$  may be ignored.
- Calculate the small signal voltage gain  $\frac{v_o}{v_s}$  without ignoring  $R_B$ .

$$V_{BE,ON} = 0.6V, \beta = 100, \text{ and } V_A = \infty.$$

Assume fA.  
a) DC analysis:

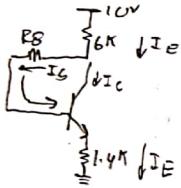

$$\text{KVL: } 10V = 6kI_E + 202kI_B + V_{BE,ON} + 1.4kI_E$$

$$10V - 0.6V = 7.4k(\beta+1)I_B + 202k \cdot I_B$$


$$\frac{9.4V}{(7.4)(101) + 202k} = I_B$$


$$I_E = (\beta+1)I_B \rightarrow \left( \begin{array}{l} I_E \approx 1mA \\ I_C = \beta I_B \approx 0.99mA \end{array} \right)$$

$$V_{CE} = 10V - 6k \cdot I_E \Rightarrow V_{CE} = 4V$$

$$V_{CE} = 4V > V_{CE, \text{sat}} \checkmark \text{ forward Active Mode.}$$

Problem 3 b, c on attached paper.

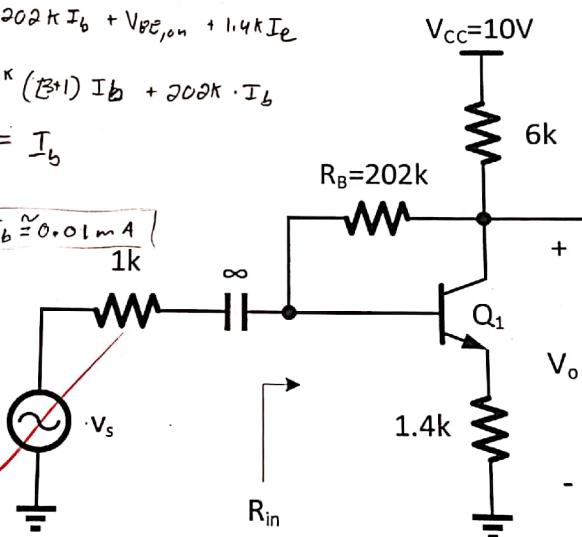

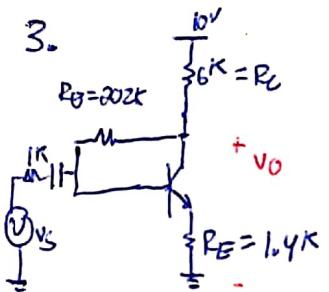


a) OC:

$$(I_B + I_C)R + I_B R_B + V_{BE(on)} + I_E R_E = 10V$$

$$I_C \approx 1mA \quad I_B = \frac{I_C}{\beta}$$

F-A region ✓

b)

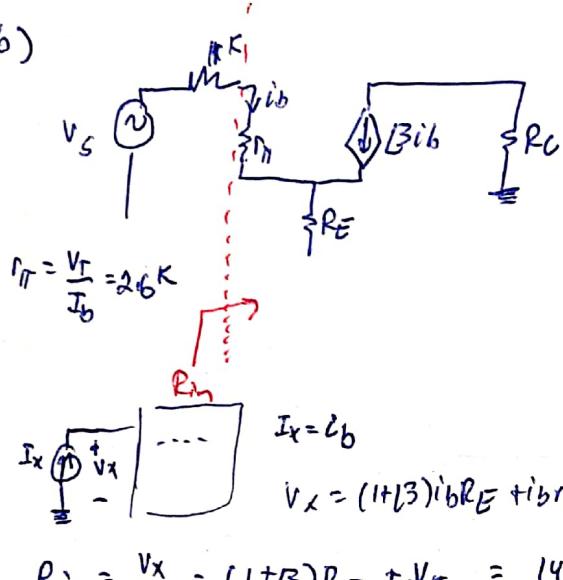

$$r_\pi = \frac{V_T}{I_B} = 2.6k\Omega$$

$$I_x = i_B$$


$$V_x = (1+\beta)i_B R_E + i_B r_\pi$$

$$R_{in} = \frac{V_x}{I_x} = (1+\beta)R_E + r_\pi = 144k\Omega$$

$$V_O = -\beta i_B R_C$$

$$\frac{V_O}{V_S} = \frac{\beta R_C}{R_{in} + R_S} = \boxed{-4.1}$$

c)

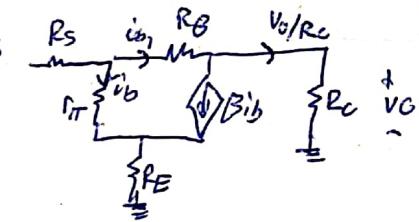

$$i_{b_1} = (\beta i_B + V_o / R_C)$$

outer loop:

$$V_S = R_S(i_B + i_{b_1}) + R_B i_{b_1} + V_O$$

left loop:

$$V_S = R_S(i_B + i_{b_1}) + i_B r_\pi + (1+\beta) i_B R_E$$

$$\boxed{\frac{V_O}{V_S} = -3.9}$$