

Name:

Student ID:

Page:2/8

1- True or False?

✓ T	In an NPN BJT the emitter is N+ to ensure the BE current is dominated by free electrons.
✓ F	In a PNP BJT the base layer is thin to ensure the rate of thermal ionization is sufficiently high.
✓ F	N-type semiconductors are made by adding a dopant element from group V of the periodic table to a crystalline material of atoms from group III.
✓ F	In a PN junction the width of the depletion region is larger on the P side.
✓ T	A semiconductor becomes more conductive as the temperatures rises above the room temperature.


(10 points)

Name:

Student ID:


Page: 3/8

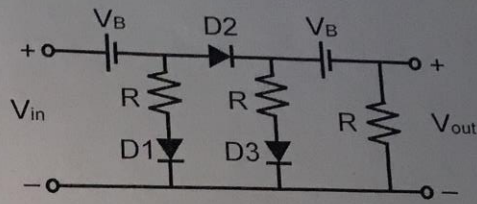2- Find V_{out} versus V_{in} , as V_{in} varies from $-\infty$ to $+\infty$, if the diodes have a turn on voltage of $V_{Don}=0$ and are otherwise ideal (Use a piece-wise linear model). V_B is larger than 0.



(40 points)

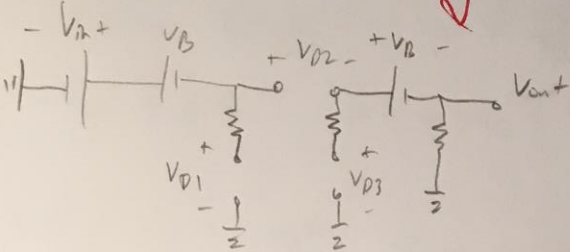As $V \rightarrow -\infty$, Assume D_1, D_2, D_3 off




$$V_{in} = V_B + V_{D1}, \quad V_{D1} = V_{in} - V_B \quad \checkmark$$

$$V_{in} = V_B + V_{D2} + V_{D3}$$

$$\underline{V_B = V_{D3} > 0} \quad \text{Wrong assumption}$$

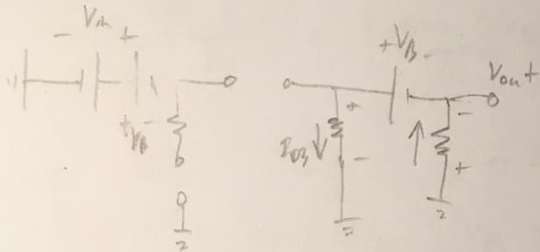As $V \rightarrow -\infty$, Assume D_1, D_2 off, D_3 on



$$V_{in} = V_B + V_{D1}, \quad V_{D1} < 0 \quad \text{verified}$$

$$\underline{V_{in} = V_B + V_{D2} + I_{D3} R} \quad \checkmark$$

As $V_{in} \rightarrow -\infty$, $V_{D2} < 0$ verified

$$V_B = I_{D3} R + I_{D3} R$$

$$V_B = 2 I_{D3} R, \quad I_{D3} > 0 \quad \text{verified}$$


$$I_{D3} R = \frac{V_B}{2}$$

$$V_{in} - V_B - \frac{V_B}{2} = V_{D2} \quad V_{in} - V_B = V_{D1}$$

$$V_{in} - \frac{3V_B}{2} = V_{D2}$$

D_2 turns on at $V_{in} = \frac{3V_B}{2}$, D_1 turns on at V_B So

D_1 turns on first

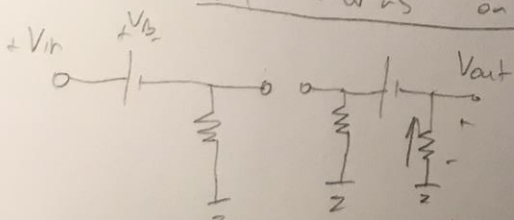


$$V_{in} = V_B + I_{D1} R$$

$$\frac{V_{in} - V_B}{R} = I_{D1} \quad \text{when } V_{in} > V_B, \quad I_{D1} > 0 \quad \text{verified}$$

$$V_{in} = V_B + V_{D2} + I_{D3} R, \quad I_{D3} R \neq \frac{V_B}{2}$$

$$V_{in} - V_B - \frac{V_B}{2} = V_{D2} \quad \text{when } V_{in} = V_B, \quad V_{D2} = -\frac{V_B}{2} < 0 \quad \text{verified}$$
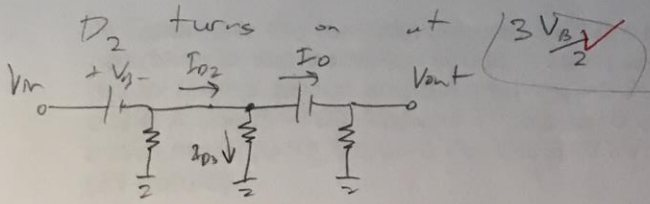
$$\underline{V_{out} = -I_{D3} R = -\frac{V_B}{2}} \quad \checkmark$$



$$V_{in} = V_B + I_{01}R$$

$$I_{01} = \frac{V_{in} - V_B}{R}, \quad V_{in} > \frac{3V_B}{2}, \quad I_{01} > 0 \text{ verified}$$

$$V_{out} = I_0 R \quad V_{in} = 2V_B + I_0 R, \quad \left\{ I_0 = \frac{V_{in} - 2V_B}{R} \right.$$

$$\left. V_{out} = V_{in} - 2V_B \right\}$$


$$V_{in} = V_B + I_{03}R, \quad I_{03} = \frac{V_{in} - V_B}{R} > 0 \text{ verified}$$

$$I_{D2} = I_{03} + I_0$$

$$= \frac{V_{in} - V_B}{R} + \frac{V_{in} - 2V_B}{R} = \frac{2V_{in} - 3V_B}{R} > 0 \text{ when } V_{in} > \frac{3V_B}{2}$$


Verified ✓
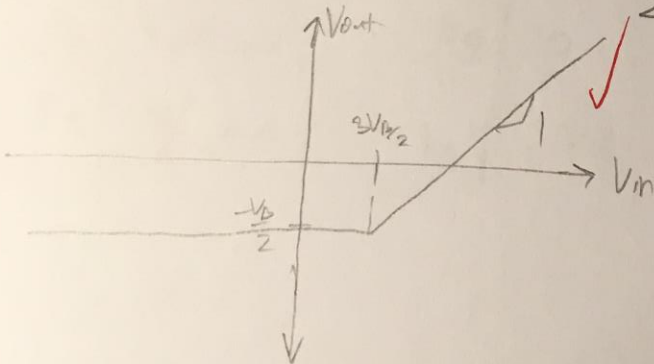
$$V_{out} = \begin{cases} -\frac{V_B}{2} & V_{in} < \frac{3V_B}{2} \\ V_{in} - 2V_B & V_{in} > \frac{3V_B}{2} \end{cases}$$



$$\frac{3V_B}{2} - 2V_B = -\frac{1}{2}V_B$$

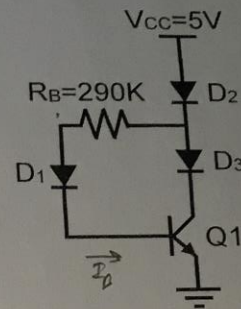3- Determine the terminal currents and the region of operation in this transistor circuit. Use a piecewise linear model for the diodes and assume $V_{D_{on}}=0.7V$. In forward active mode $\beta_F=100$, $V_{BE_{on}}=0.7V$, $V_{CE_{sat}}=0.2V$, and in reverse active mode $\beta_R=3$, $V_{BC_{on}}=0.7V$, $V_{EC_{sat}}=0.2V$. (25 points)



Assume Active

$$5 = 0.7 + 290k(I_B) + 0.7 + 0.7$$

$$\frac{2.9}{290k} = I_B = \cancel{1\mu A} > 0 \text{ verified } \checkmark$$

$$5 = 0.7 + 0.7 + V_{CE}$$

$$V_{CE} = 3.6 > V_{CE_{sat}} \checkmark \text{ verified } \checkmark \text{ Assumption verified}$$

$$I_C = \beta_F I_B = 1\mu A$$

$$I_E = (\beta + 1) I_B = 1.01\mu A$$


$$5 - 0.7 - 290k(1\mu A) - 0.7 = V_B$$

$$V_B = 0.7V$$

I_C	$1\mu A$	V_C	$3.6V$
I_E	$1.01\mu A$	V_E	0
I_B	$\cancel{1\mu A}$	V_B	$0.7V$

-3

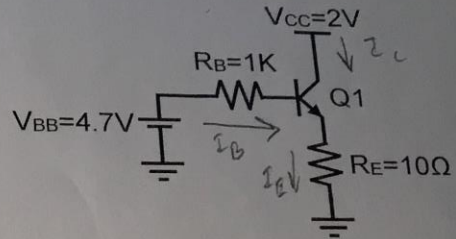4- Determine the terminal currents and the region of operation in this transistor circuit. In forward active mode $\beta_F=99$, $V_{BEon}=0.7V$, $V_{CEsat}=0.2V$, and in reverse active mode $\beta_R=3$, $V_{BCon}=0.7V$, $V_{ECsat}=0.2V$.



(25 points) Assume Active

$$2 = V_{CE} + I_E R_E$$

$$2 - I_E R_E = V_{CE}$$

$$2 - \frac{1}{5}(10) = V_{CE} = 0$$

$$V_{CE} < V_{CEsat}$$

Wrong Assumption

$$4.7 = I_B(1k) + V_{BEon} + I_E R_E$$

$$4 = I_E \left(R_E + 1k \left(\frac{1}{\beta+1} \right) \right)$$

$$I_E = \frac{4}{R_E + \frac{1000}{100}} = \frac{4}{10 + 10} = \frac{4}{20} = \boxed{\frac{1}{5} A}$$

$$I_B = \frac{1}{\beta+1} I_E = \frac{1}{100} \left(\frac{1}{5} \right) = \boxed{\frac{1}{500} A}$$

$I_B > 0$ verified ✓

Assume Saturation

$$2 = V_{CEsat} + I_E R_E$$

$$I_E = \frac{1.8}{10} = \boxed{0.18 A}$$

$$I_E = I_B + I_C$$


$$I_C = I_E - I_B = \boxed{0.177 A}$$

$$\beta I_B = 0.22 + I_C$$

$$I_C = \beta I_B$$

1.50 verified ✓

I_C	0.1778 A	V_C	2V
I_B	0.00224	V_B	2.5 V
I_E	0.18 A	V_E	1.8 V

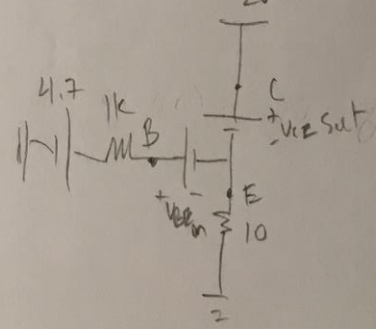

$$V_B = 4.7 - 1k(I_B) = 4.7 - 2.2 = 2.5$$

$$V_E = V_B - 0.7 = 1.8V$$