

**EE115A – Analog Electronic Circuits
Fall 2017 – Prof. Shervin Moloudi
Mid-term Exam – Monday November 6, 2017**

READ THE INSTRUCTIONS BEFORE YOU START

- 1- You have 1 hour and 50 minutes.
 - 2- Write your name on top of all pages and do not remove the staple.
 - 3- If you need extra pages, ask the proctor.
 - 4- A 5.5in x 8.5in 2-sided formula sheet is allowed.
- No electronic devices including calculators, laptops, cell phones, etc. are allowed. You can use a regular wrist watch if you so choose.

Question	Points
1	/ 10
2	/ 40
3	/ 25
4	/ 25
Grade	/ 100


1- True or False?

<input checked="" type="checkbox"/>	In an NPN BJT the emitter is N+ to ensure the BE current is dominated by free electrons.
<input checked="" type="checkbox"/>	In a PNP BJT the base layer is thin to ensure the rate of thermal ionization is sufficiently high.
<input checked="" type="checkbox"/>	N-type semiconductors are made by adding a dopant element from group V of the periodic table to a crystalline material of atoms from group III. \times
<input checked="" type="checkbox"/>	In a PN junction the width of the depletion region is larger on the P side.
<input checked="" type="checkbox"/>	A semiconductor becomes more conductive as the temperatures rises above the room temperature.

(10 points)


forward bias No
reverse bias Yes

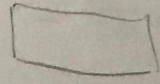$T \uparrow$ $\frac{kT}{q} \uparrow$ $V_T \uparrow$ $\frac{V_D}{V_T} \downarrow$



V-

Si 14
P 15

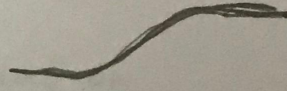

$I_D = I_S \left(\exp \frac{V_D}{V_T} - 1 \right)$

$I_D = I_S e^{\frac{V_D}{V_T}}$

$V_T = \frac{kT}{q}$

kT $kT \uparrow$


$I_S =$

26 4

H.

V_D

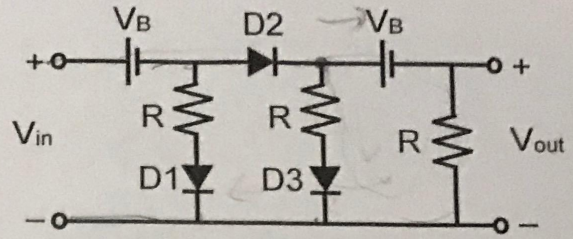2- Find V_{out} versus V_{in} , as V_{in} varies from $-\infty$ to $+\infty$, if the diodes have a turn on voltage of $V_{Don}=0$ and are otherwise ideal (Use a piece-wise linear model). V_B is larger than 0.



(40 points)

for D_1 to turn on: $V_{in} - V_B > 0$.


∴ D_2 ... : $V_{in} - V_B - V_B > 0$ (marked with a circled -1)

∴ D_3 ... ; because of V_B , D_3 always on. $V_{in} @ -\infty$, V_B enables D_3 on as $V_{in} \uparrow$, V_{in} enables D_3 on.

start from $-\infty = V_{in}$

D_1, D_2 off, D_3 on


ckt \Rightarrow

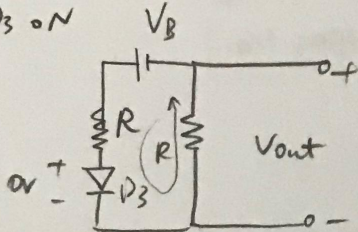

$$V_{out} = -\frac{V_B}{2R} \cdot R = -\frac{V_B}{2}$$


state change @ $V_{in} \geq V_B \rightarrow D_1$ on, D_3 remains on.

ckt \rightarrow

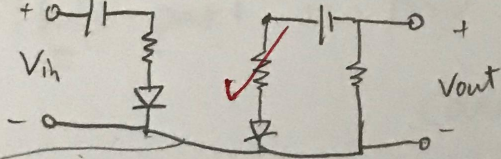


\rightarrow this is like common grounded 2 parts of ckt $V_{out} = -\frac{V_B}{2}$

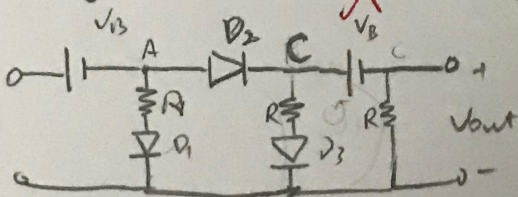state change 2 @ $V_{in} \geq 2V_B$ (marked with a circled -2) D_1, D_2, D_3 all on.



\equiv

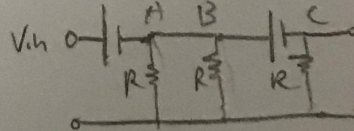


$$V_A = V_{in} - V_B$$

$$V_C = V_{in} - V_B$$

$$V_{out} = V_C - V_B$$

$$\Rightarrow V_{out} = V_{in} - 2V_B$$

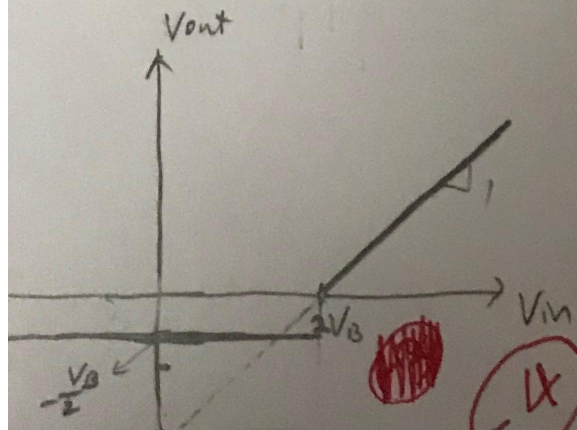

in sum:

• for $V_{in} < 2V_B$

$$V_{out} = -\frac{V_B}{2}$$

• for $V_{in} \geq 2V_B$



$$V_{out} = V_{in}$$

$D_3 > 0?$
(-5)

3- Determine the terminal currents and the region of operation in this transistor circuit. Use a piecewise linear model for the diodes and assume $V_{D_{on}}=0.7V$. In forward active mode $\beta_F=100$, $V_{BE_{on}}=0.7V$, $V_{CE_{sat}}=0.2V$, and in reverse active mode $\beta_R=3$, $V_{BC_{on}}=0.7V$, $V_{EC_{sat}}=0.2V$.

(25 points)

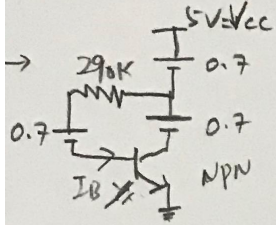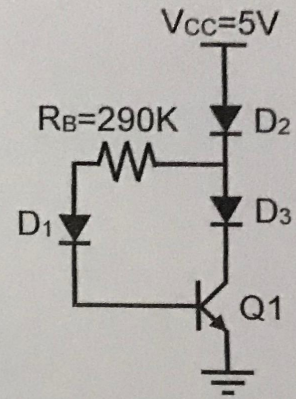Assume Q_1 active mode (forward)
(D_1, D_2, D_3 all on)



KVL @ Base:

$$5 = 0.7 + I_B \times 290k + 0.7 - 0.7 = 0$$

$$I_B = \frac{2.9}{290k} = 10^{-5} \text{ A}$$

$$I_B > 0 \quad \checkmark$$

$$\beta_F = 100 \rightarrow I_E = \beta I_B = 10^{-3} \text{ A}$$

$$I_E = (\beta + 1) I_B = 1.01 \text{ mA} \quad (1.01 \times 10^{-3})$$

$$V_E \text{ is grounded} \Rightarrow V_E = 0$$

$$V_C = 5 - 0.7 - 0.7 = 3.6 \text{ V}$$

$$V_{CE} = 3.6 \text{ V} > V_{CE_{sat}} (0.2 \text{ V}) \quad \checkmark$$

$\Rightarrow Q_1$ active

Now we need to verify D_1, D_2, D_3 diodes.

$$I_{D2} = I_B + I_E = I_E = 1.01 \times 10^{-3} \text{ A} > 0 \Rightarrow D_2 \text{ ON} \quad \checkmark$$

$$I_{D1} = I_B = 10^{-5} \text{ A} > 0 \Rightarrow D_1 \text{ ON} \quad \checkmark$$


$$I_{D3} = I_C = 10^{-3} \text{ A} > 0 \Rightarrow D_3 \text{ ON} \quad \checkmark$$

all assumption right

$$\Rightarrow \begin{cases} I_B = 10^{-5} \text{ A} \\ I_C = 10^{-3} \text{ A} \\ I_E = 1.01 \times 10^{-3} \text{ A} \end{cases}$$

Q is in forward active region

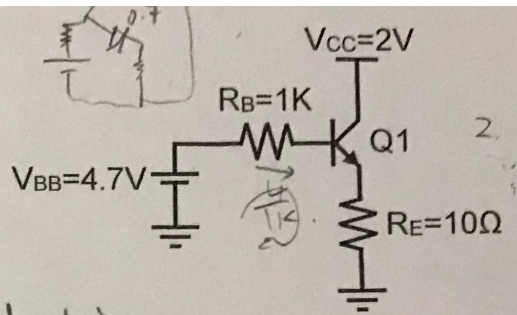
4- Determine the terminal currents and the region of operation in this transistor circuit. In forward active mode $\beta_F=99$, $V_{BEon}=0.7V$, $V_{CEsat}=0.2V$, and in reverse active mode $\beta_R=3$, $V_{BCon}=0.7V$, $V_{ECsat}=0.2V$.



(25 points)

guess.

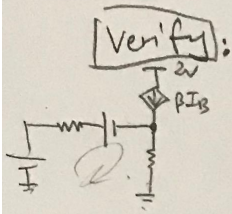By observation: $V_{BB} > V_{CC}$. \Rightarrow 2. forward bias \Rightarrow 2 independent diodes.




Verify: assume forward active

$I_B < V_L$ @ base: $I_B = \frac{4.7 - 0.7}{1010} > 0$. $\beta_F = 99$


$I_E = 100 \times \frac{4.7 - 4}{1010} \approx 0.4A$

$V_E = 0.4 \times 10 = 4V > V_{CC} \Rightarrow V_{CE} < 0$
 $V_{CE} < V_{CEsat}$

$I_B > 0 \Rightarrow$ Saturation

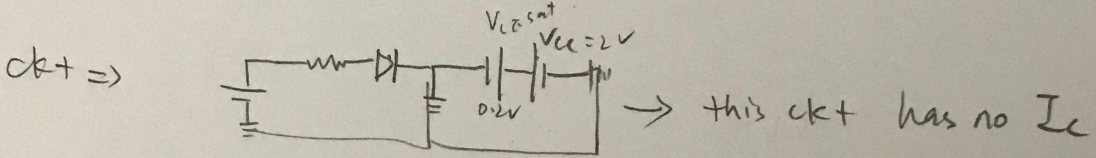

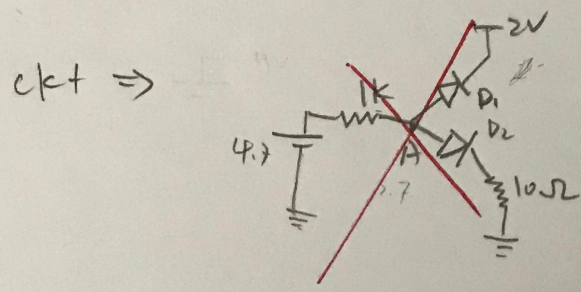\Rightarrow 2 independent diodes \Rightarrow assumption is correct



if D_1, D_2 ON:

$V_A = 2.7$
 $I_B = \frac{4.7 - 2.7}{1k}$ $I_C = \frac{2.7 - 0.7}{10}$

$I_B < I_C \Rightarrow$ impossible at +

if D_1, D_2 off $V_A = 4.7 > 0.7 \Rightarrow$ also wrong assumption

if D_1 ON, D_2 off $\Rightarrow V_A = 2.7V > 0.7V \Rightarrow$ wrong again

-15

$\Rightarrow D_1$ off, D_2 ON $\Rightarrow I = \frac{4.7 - 0.7}{1010} = \frac{4}{1010} A, I > 0$

$V_A = \frac{4}{1010} \times 10 + 0.7 = \frac{4}{101} + 0.7 \approx 0.74V < (2 + 0.7)V$ D_1 off

\Rightarrow 2 independent diodes. " $I_B = I_C = I = \frac{2}{505} A$ "
 { BC diode off
 { 2 independent