

EE 115A

Final Exam

Fall 2004

Your Name:

Solutions

Name of Person to Your Left:

Name of Person to Your Right:

Time Limit: 3 Hours

Use all approximations specified in each problem.

1.

2.

3.


4.

5.

6.

Total:

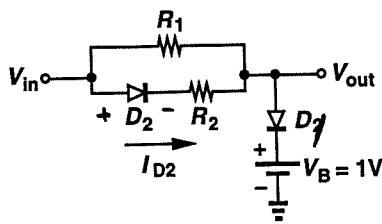1. Plot V_{out} and I_{D2} as a function of V_{in} as V_{in} goes from $-\infty$ to $+\infty$. Determine the coordinates of each break point in the plot. Assume a constant-voltage diode model and $R_1 = R_2 = 1 \text{ k}\Omega$.



(10)

① when V_{in} is negative infinity,

D_1, D_2 both turn off. $V_{out} = V_{in}$ $I_{D2} = 0$

② When V_{in} increase at the point that D_1 begins turning on.



$V_{out} = V_D + 1$, since D_2 still keeps off, $I_{D2} = 0$

③ As V_{in} keeps increasing, the breakpoint that D_2 turns on and off is the $I_{D2} = 0$, $V_{in} - V_{out} = V_D$.


So. $V_{in} = V_D + V_{out} = 2V_D + 1$. Beyond that, I_{D2} increases.

$$I_{D2} = \frac{V_{in} - V_{out} - V_D}{R_2} = \frac{V_{in} - 2V_D - 1}{R_2}$$

$$V_{out} = V_D + 1$$

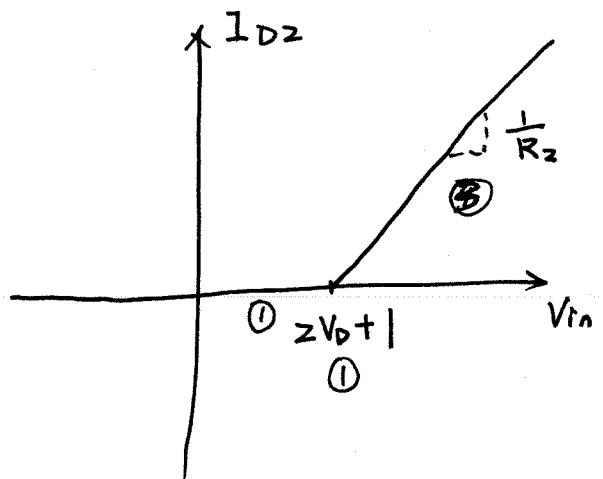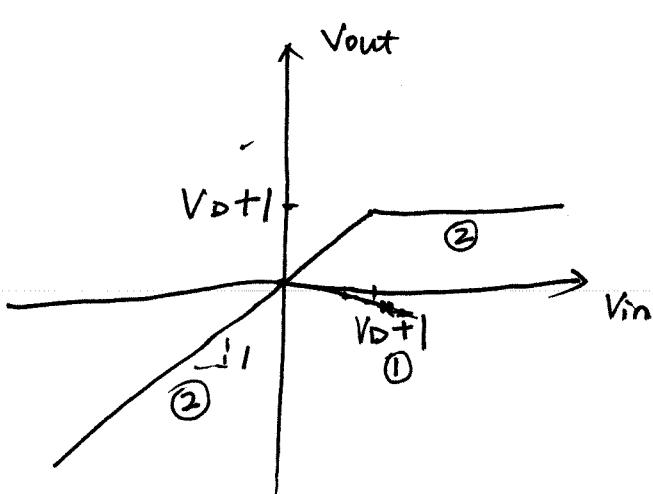

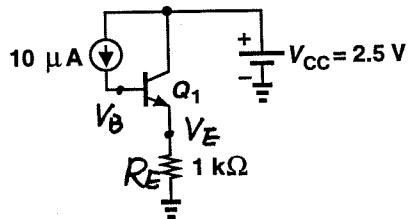2. Determine the maximum allowable value of β if Q_1 must not enter saturation. Assume the current source is ideal, $V_A = \infty$, and $I_S = 8 \times 10^{-16} \text{ A}$.



(10)

For Q_1 not in saturation mode, "BC" should. reverse biased.

$$\text{So. } V_B \leq V_{CC} = 2.5 \text{ V.}$$

Based on equation $I_C = I_S \exp \frac{V_{BE}}{V_T}$, we get

$$\beta I_B = I_S \exp \frac{V_B - (\beta + 1) I_B \cdot R_E}{V_T} \quad \text{Assume } V_T = 26 \text{ mV.}$$

$$V_B = 2.5 \text{ V.}$$


$$\beta \times 10 \times 10^{-6} = 8 \times 10^{-16} \exp \frac{2.5 - (\beta + 1) 10 \times 10^{-6} \times 1 \times 10^3}{26 \times 10^{-3}} \quad (2)$$

Solve above equation, we can get maximum $\beta = 175.12$


(3)

3. Compute the input impedance of each circuit assuming $V_A = \infty$.


(10)

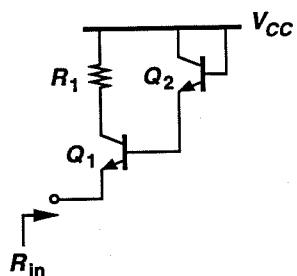


(a)

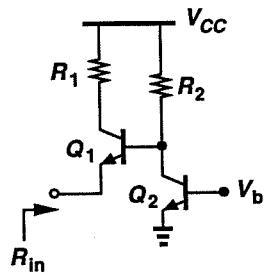

(b)

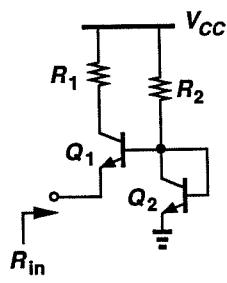

(c)

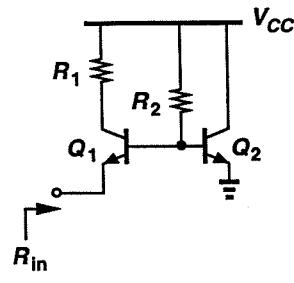

(d)

$$(2.5) (a) R_{in} = \frac{r_{\pi 1} + \frac{r_{\pi 2}}{1 + \beta_2}}{1 + \beta_1} \quad \text{if. consider } \beta_1, \beta_2 \text{ is big enough. } R_{in} \approx \frac{1}{g_m},$$


$$(2.5) (b) R_{in} = \frac{r_{\pi 1} + R_2}{1 + \beta_1}$$

$$(2.5) (c) R_{in} = \frac{r_{\pi 1} + R_2 / / \frac{1}{g_m 2} / / r_{\pi 2}}{1 + \beta_1} = \frac{r_{\pi 1} + R_2 / / \frac{r_{\pi 2}}{1 + \beta_2}}{1 + \beta_1}$$


$$(2.5) (d) R_{in} = \frac{r_{\pi 1} + R_2 / / r_{\pi 2}}{1 + \beta_1}$$

4. Determine the region of operation of each transistor. Assume a threshold voltage of 0.5 V for NMOS devices and -0.5 V for PMOS devices.


(10)

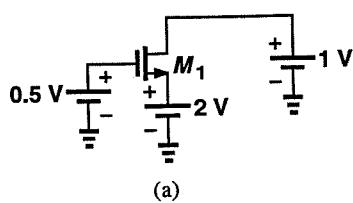


(a)

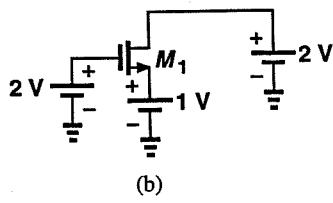


(b)

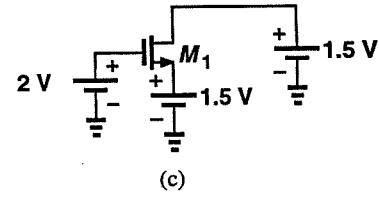

(c)

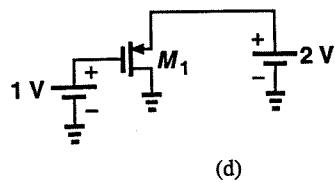

(d)

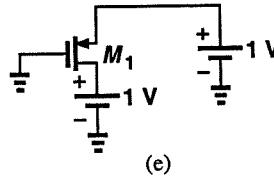

(e)

(a) $V_{GS} < 0 \quad V_{GD} < 0$. off


(b) $V_{GS} = 1V > 0.5V \quad V_{GD} = 0 < V_{th}$ SAT

(c) $V_{GS} = 0.5 = V_{th} \quad V_{GD} = 0.5 = V_{th}$
Current is zero. But since $V_{GS} = V_{th}$, the device is SAT.


(d) $V_{SG} = 1V > |V_{thp}| \quad V_{DG} = -1V < V_{thp}$. SAT.

(e) $V_{SG} = 1V > |V_{thp}| \quad V_{DG} = 1V > |V_{thp}|$ ~~not~~ Triode

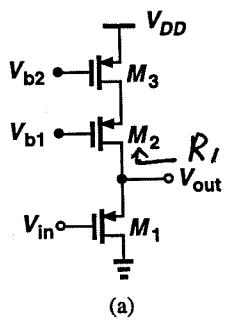5. Calculate the voltage gain of each circuit. Assume $\lambda \neq 0$ for (a) but $\lambda = 0$ for (b).



(a)

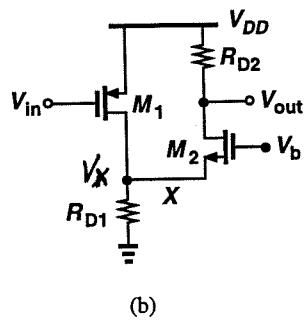

(b)

$$(a) \text{ The impedance of } R_1 = r_{o2} + (1 + g_{m2} r_{o2}) r_{o3}$$

This circuit is basically a source follower.

$$\begin{aligned} A_v &= \frac{g_{m1} (R_1 // r_{o1})}{1 + g_{m1} (R_1 // r_{o1})} \\ &= \frac{g_{m1} [(r_{o2} + (1 + g_{m2} r_{o2}) r_{o3}) // r_{o1}]}{1 + g_{m1} [(r_{o2} + (1 + g_{m2} r_{o2}) r_{o3}) // r_{o1}]} \end{aligned}$$

$$(b) \frac{V_{out}}{V_{in}} = \frac{V_{out}}{V_x} \cdot \frac{V_x}{V_{in}}$$


$$\frac{V_x}{V_{in}} = -g_{m1} \cdot (R_{D1} // \frac{1}{g_{m2}})$$

$$\frac{V_{out}}{V_x} = g_{m2} \cdot R_{D2}$$

$$\text{so. } \frac{V_{out}}{V_{in}} = -g_{m1} g_{m2} R_{D2} (R_{D1} // \frac{1}{g_{m2}})$$

6. Plot V_{out} and V_Y as a function of V_{in} as V_{in} goes from $-\infty$ to $+\infty$. Assume $R_P = 3 \text{ k}\Omega$ and $R_1 = 1 \text{ k}\Omega$, and use a constant-voltage model for the diode. Also, assume an ideal op amp.

(10)

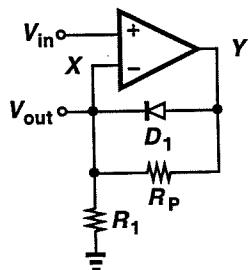

Since the opamp is ideal, $V_{out} = V_{in}$.

① When V_{in} is $-\infty$, V_{out} is also $-\infty$. D_1 off.

$$\cancel{\text{V}_Y = \frac{R_1 + R_P}{R_1} V_{out}} = \frac{R_1 + R_P}{R_1} V_{in}$$

② when $V_{in} = 0$, $V_{out} = 0$, V_Y is also 0. D_1 still turns off.

$$\text{when } V_Y = \frac{R_1 + R_P}{R_1} V_{in} = 4V_{in}$$

when $V_Y - V_{out} = V_D$, D_1 begins turning on. So the point to turn on D_1 is:

$$V_Y - V_{out} = \frac{R_1 + R_P}{R_1} V_{in} - V_{in} = V_D \Rightarrow V_{in} = \frac{R_1}{R_P} V_D = \frac{1}{3} V_D$$

After D_1 turns on, $V_Y = V_{out} + V_D = V_{in} + V_D$

