

**EE 115A**

**Midterm Exam**

**Fall 2015  
Group I**

**Your Name:**

\_\_\_\_\_

**Name of Person to Your Left:**

\_\_\_\_\_

**Name of Person to Your Right:**

\_\_\_\_\_

**Time Limit: 1 Hour and 50 Minutes**


1. 10

2. 15

3. 10

4. 15

**Total: 50**

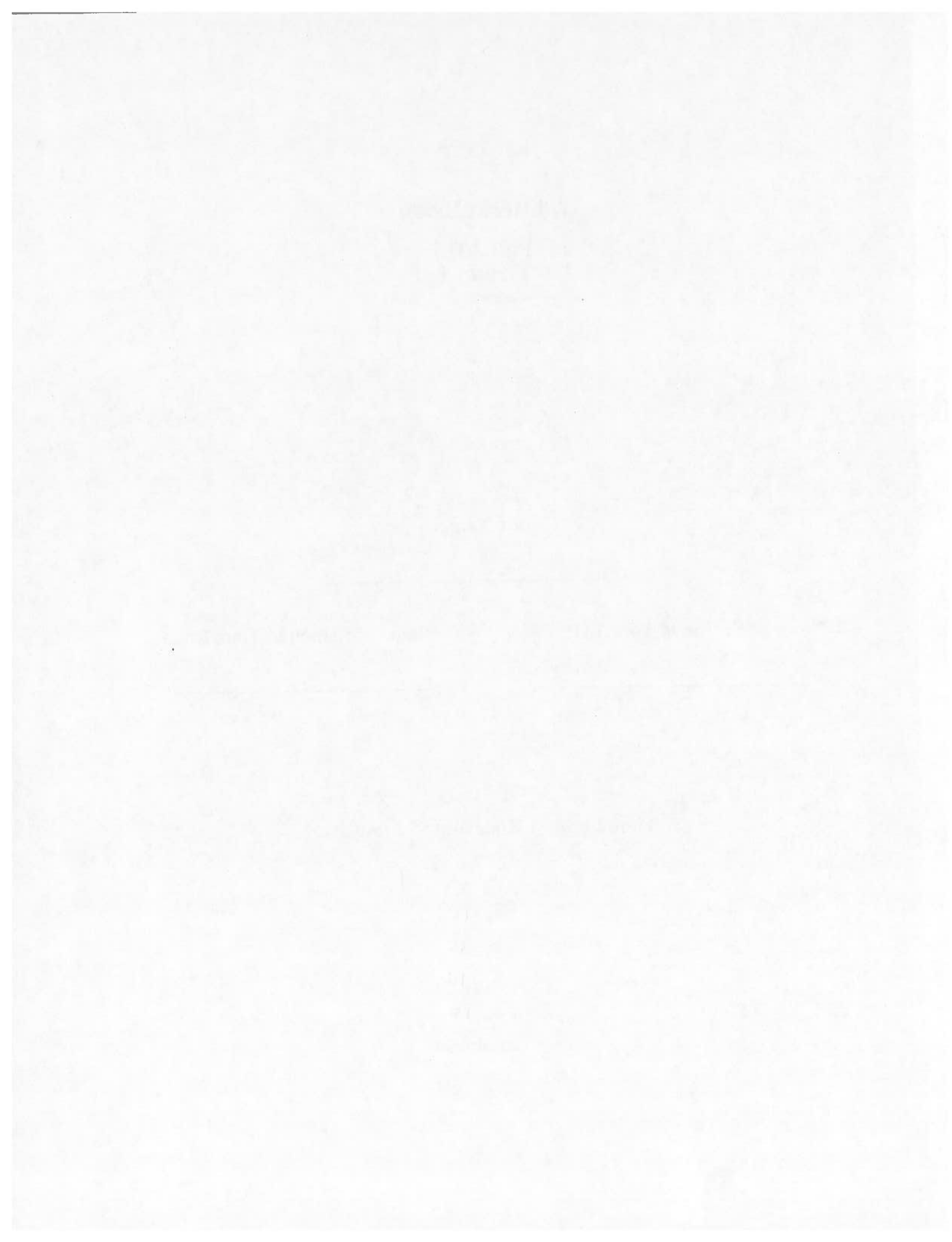


Total marks  $\rightarrow 10$

1. Assuming a constant-voltage diode model with  $V_{D,on} = 0.8\text{ V}$ ,

(a) plot  $V_{out}$  and  $I_{D1}$  as a function of  $V_{in}$  if  $I_1 = 0$ . Show the details of your calculations.

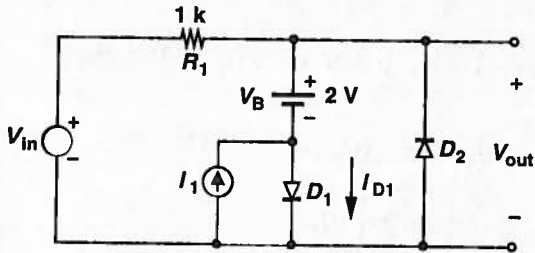
(b) plot  $V_{out}$  and  $I_{D1}$  as a function of  $V_{in}$  if  $I_1$  is constant and equal to 1 mA. Show the details of your calculations.



(a)

Solution: Step 1: Find Breakpoint

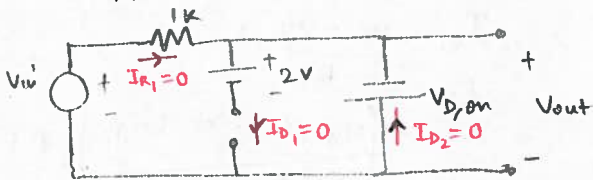
Assume, D2 just turns off while D1 is off.



$$\therefore V_{in} = -V_{D,on} = -0.8\text{ V}$$

Breakpoint 1 1/2

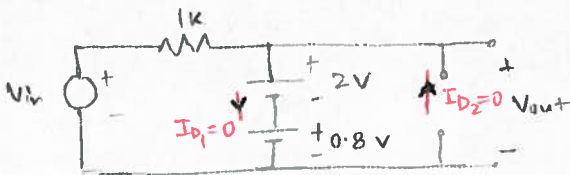Now, we have to find another Breakpoint when D1 turns on.



$$\therefore V_{in} = 2 + V_{D,on} = 2.8\text{ V}$$

Breakpoint 2 1/2

Hence

$$V_{in} \leq -0.8\text{ V} \quad D_2 \text{ ON, } D_1 \text{ OFF}$$

$$-0.8 < V_{in} < 2.8\text{ V} \quad D_2 \text{ OFF, } D_1 \text{ OFF}$$

$$V_{in} \geq 2.8\text{ V} \quad D_2 \text{ OFF, } D_1 \text{ ON}$$

Case 1:  $V_{in} \leq -0.8\text{ V}$

$$V_{out} = -0.8\text{ V} \quad \textcircled{1}$$

$$I_{D1} = 0$$

Case 2:  $-0.8\text{ V} < V_{in} < 2.8\text{ V}$



$$V_{out} = V_{in} \quad \textcircled{1}$$

$$I_{D1} = 0$$

Case 3:  $V_{in} \geq 2.8\text{ V}$

$$V_{out} = 2.8\text{ V} \quad \textcircled{1}$$
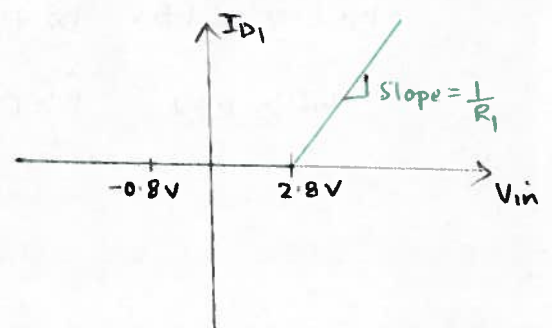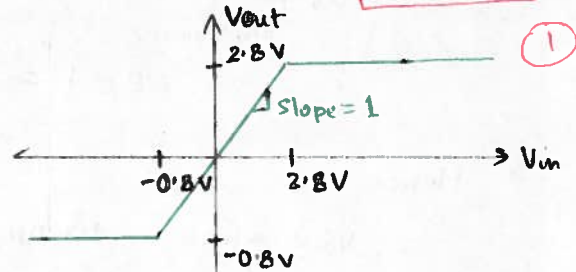
$$I_{D1} = \frac{V_{in} - 2.8}{R_1} = \frac{V_{in} - 2.8}{1\text{ k}}$$




(b)

Solution :


Step 1 : Find Breakpoint

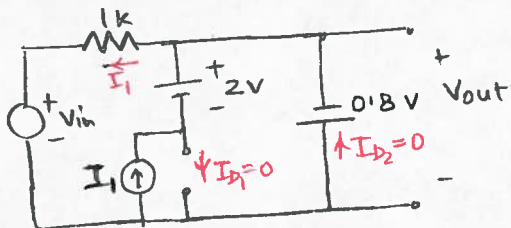Assume, D2 just turns off while D1 is off.



$$\begin{aligned} \therefore V_{in} &= -0.8 - I_1 \times 1k \\ \text{Breakpoint 1} \\ &= -0.8 - 1 = -1.8V \quad \left(\frac{1}{2}\right) \end{aligned}$$

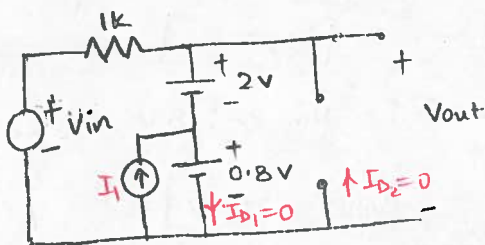Now, we have to find another Breakpoint when D1 turns on.



$$\begin{aligned} \therefore V_{in} &= 2.8 - I_1 \times 1k \\ \text{Breakpoint 2} \\ &= 2.8 - 1 = 1.8V \quad \left(\frac{1}{2}\right) \end{aligned}$$

Hence,

$$V_{in} \leq -1.8V \quad D2 \text{ ON, } D1 \text{ OFF}$$

$$-1.8 < V_{in} < 1.8V \quad D2 \text{ OFF, } D1 \text{ OFF}$$

$$V_{in} \geq 1.8V \quad D2 \text{ OFF, } D1 \text{ ON}$$

$$\text{Case 1 : } V_{in} \leq -1.8V$$

$$V_{out} = -0.8V \quad (1)$$

$$I_{D1} = 0$$

$$\text{Case 2 : } -1.8V < V_{in} < 1.8V$$

$$V_{out} = V_{in} + I_1 \times 1k$$

$$= V_{in} + 1 \quad (1)$$



$$I_{D1} = 0$$

$$\text{Case 3 : } V_{in} \geq 1.8V$$

$$V_{out} = 2.8V \quad (1)$$



$$I_{D1} = \frac{V_{in} - 2.8}{R_1} + I_1$$
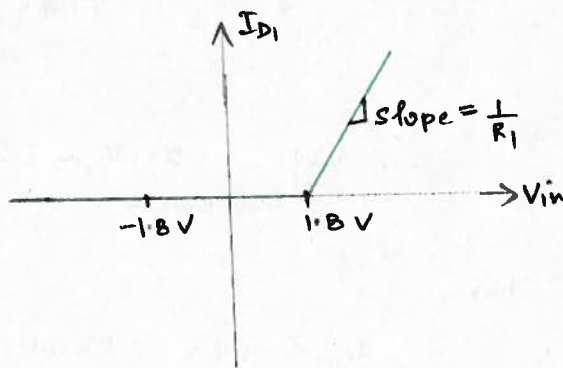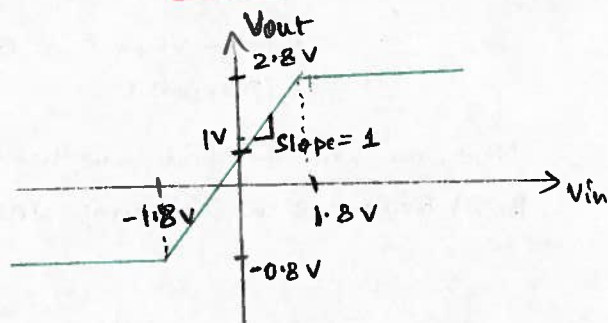
$$= \frac{V_{in} - 2.8 + 1mA}{1k} \quad (1)$$



Total marks  $\rightarrow 15$

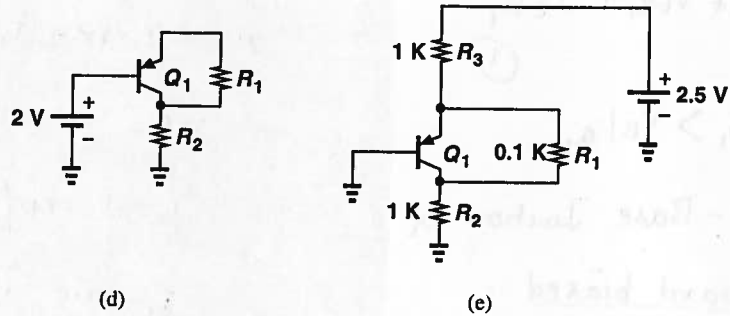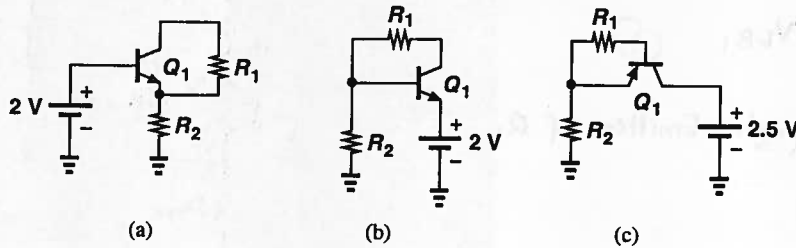2. Determine the region of operation of  $Q_1$  in each of the circuits shown below. Assume  $I_S = 2 \times 10^{-16}$  A,  $\beta = 100$ ,  $V_A = \infty$ . You need only show whether the transistor is in the forward active region, saturated, at the edge of saturation, or off ( $I_C = 0$ ). Indicate which region and explain why.




(a) For  $Q_1$  to be ON, it needs a positive  $V_{BE1}$   
 $\therefore V_{E|Q_1} = 2 - V_{BE1}$  ①  
 Now if +ve current  $I_C$  goes through collector of  $Q_1$ .  
 $V_{C|Q_1} = V_{E|Q_1} - I_C R_1$   
 $= 2 - V_{BE1} - I_C R_1$   
 As  $V_{C|Q_1} < V_{B|Q_1}$  ①  
 $\Rightarrow$  Collector-Base Junction of  $Q_1$  is forward biased  
 $\therefore Q_1$  lies in saturation region. ①

(b) For  $Q_1$  to be ON, it needs positive  $V_{BE1}$   
 $\Rightarrow V_B = 2 + V_{BE1}$  ①  
 Thus, positive current  $I_1 = \frac{2 + V_{BE1}}{R_2}$  flows from Base of  $Q_1$  to ground.  
  
 If  $I_B$  is neglected then  $I_C = -I_1$   
 Collector current can't be negative while  $Q_1$  is ON.  
 Hence,  $Q_1$  is OFF ②

(c)  
  
 For  $Q_1$  to be ON, it needs to follow current direction Convention labelled in the diagram above.  
 Now, current flow from ground to 2.5V. Also,  $V_{BE}$  cannot be positive for pnp transistors  
 $\therefore Q$  is OFF ②

(d) For  $Q_1$  to be ON,

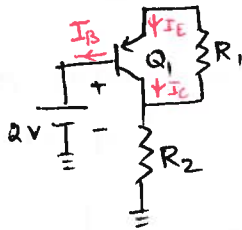


the Above mentioned convention of currents needs to be followed.

This implies  $I_B$  needs to  $\textcircled{1}$  charge 2V Battery which is not possible. In this circuit 2V is the highest possible voltage source. Thus, voltage at Emitter will be lower than voltage at Base.

$\therefore$   $Q_1$  is OFF  $\textcircled{2}$

(e)

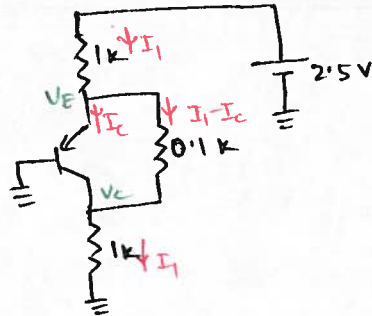

$$2.5 = I_1 \times 1k + (I_1 - I_C) \times 0.1k + I_1 \times 1k$$

$$2.5 = 2.1k I_1 - I_C \times 0.1k$$

$$I_C = I_S \exp\left(\frac{V_E}{V_T}\right)$$

$$I_1 = \frac{2.5 - V_E}{1k}$$

$$2.5 = 2.1k \left(\frac{2.5 - V_E}{1k}\right) - I_S \exp\left(\frac{V_E}{V_T}\right) \times 0.1k$$

$$2.5 = 2.1 \times 2.5 - 2.1 V_E - I_S \exp\left(\frac{V_E}{V_T}\right) \times 0.1k$$

$$I_S \exp\left(\frac{V_E}{V_T}\right) \times 0.1k = 1.1 \times 2.5 - 2.1 V_E$$

$$V_E = V_T \ln\left(\frac{1.1 \times 2.5 - 2.1 V_E}{I_S \times 0.1k}\right)$$

Putting  $V_E = 0.8V$  and performing  $\textcircled{1}$  iterations.

$$V_E = 0.8218V$$

Now putting  $V_E = 0.8218V$  in  $\textcircled{1}$ , we get  $V_E = 0.8207V$   $\textcircled{1}$

This is the final converged value.

$$I_1 = \frac{2.5 - 0.8207}{1k} = 1.679 \text{ mA}$$

$$V_C|_{Q_1} = I_1 \times 1k = 1.679V$$


Now  $V_C|_{Q_1} > V_B|_{Q_1} \Rightarrow Q_1$  lies in saturation region  $\textcircled{1}$

Total marks  $\rightarrow 10$

3. Consider the circuit shown below, where  $I_{S1} = 3I_{S2} = 2 \times 10^{-16}$  A,  $\beta_{npn} = 2\beta_{pnp} = 100$ , and  $V_A = \infty$ . You can assume the collector and emitter currents are equal.

(a) We wish to forward-bias the collector-base junction of  $Q_2$  by no more than 150 mV. Determine the maximum allowable value of  $V_{in}$ .

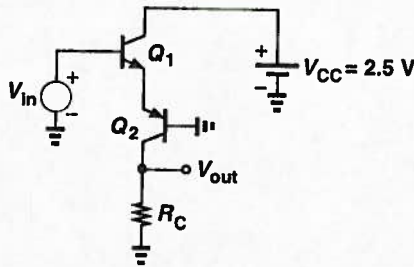(b) Suppose  $V_{in} = 1.5$  V. What is the maximum value of  $R_C$  that forward-biases the collector-base junction of  $Q_2$  by no more than 150 mV?



(a)  
Solution : Given :

$$V_{CB2} < 150 \text{ mV}$$

$$I_{C2} R_C < 150 \text{ mV}$$

$$I_{C2} < \frac{150 \text{ mV}}{R_C}$$

$$V_{EB2} = V_{E2} = V_T \ln \left( \frac{I_{C2}}{I_{S2}} \right)$$

$$< V_T \ln \left( \frac{150 \text{ mV}}{R_C I_{S2}} \right) \quad (1)$$

$$\frac{\beta_2}{1+\beta_2} I_{E2} R_C < 150 \text{ mV}$$

$$\frac{1+\beta_1}{\beta_1} \frac{\beta_2}{1+\beta_2} I_{C1} R_C < 150 \text{ mV} \quad (1)$$

$$I_{C1} < \frac{150 \text{ mV}}{\left( \frac{1+\beta_1}{\beta_1} \right) \left( \frac{\beta_2}{1+\beta_2} \right) R_C}$$

$$V_{BE1} = V_T \ln \left( \frac{I_{C1}}{I_{S1}} \right) \quad (1)$$

$$< V_T \ln \left( \frac{150 \text{ mV}}{\frac{1+\beta_1}{\beta_1} \frac{\beta_2}{1+\beta_2} R_C I_{S1}} \right)$$

$$V_{in} = V_{BE1} + V_{EB2} \quad (1)$$

$$V_{in} < V_T \ln \left( \frac{150 \text{ mV}}{I_{S2} R_C} \frac{150 \text{ mV}}{\frac{1+\beta_1}{\beta_1} \frac{\beta_2}{1+\beta_2} R_C I_{S1}} \right)$$

$$= V_T \ln \left[ \left( \frac{V_{out}}{I_{S1} R_C} \right)^2 \times \frac{1+\beta_1}{\beta_1} \times \frac{\beta_2}{1+\beta_2} \right] \frac{1}{\beta_1} \frac{1+\beta_2}{1+\beta_2} V$$

$$V_{in} < 1.81 \text{ V} + 0.026 \ln \left( \frac{1}{R_C^2} \right) \text{ V}$$

$$V_{in} < 1.81 \text{ V} - 0.052 \ln(R_C) \text{ V} \quad (1)$$

(b)

Given  $I_{C2} R_C < 150 \text{ mV}$

$$V_{in} = V_{BE1} + V_{EB2}$$

$$= V_T \ln \left( \frac{I_{C2}}{I_{S2}} \right) + V_T \ln \left( \frac{I_{C2}}{I_{S1}} \frac{1+\beta_2}{\beta_2} \frac{\beta_1}{1+\beta_1} \right) \quad (1)$$

$$V_{in} = V_T \ln \left( \frac{I_{C2}^2}{I_{S2} I_{S1}} \frac{1+\beta_2}{\beta_2} \frac{\beta_1}{1+\beta_1} \right)$$

$$I_{C2}^2 = I_{S1} I_{S2} \exp \left( \frac{V_{in}}{V_T} \right) \frac{\beta_2}{1+\beta_2} \frac{1+\beta_1}{\beta_1}$$

$$I_{C2} = \sqrt{I_{S1} I_{S2}} \left( \exp \left( \frac{V_{in}}{V_T} \right) \right)^{\frac{1}{2}} \left( \frac{\beta_2}{1+\beta_2} \frac{1+\beta_1}{\beta_1} \right)^{\frac{1}{2}}$$


$$R_c < \frac{150 \text{ mV}}{\sqrt{I_{S1} I_{S2}} \left( \exp\left(\frac{v_{in}}{V_T}\right) \right)^{\frac{1}{2}} \left( \frac{\beta_2}{1+\beta_2} \frac{1+\beta_1}{\beta_1} \right)^{\frac{1}{2}}}$$

$$R_c < 387.28 \, \Omega \quad (1)$$




Total marks  $\rightarrow 15$

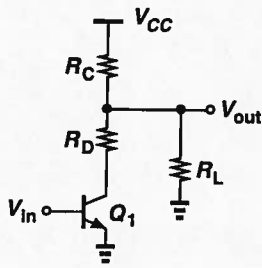
4. Compute the voltage gain of the circuits shown below, assuming that all transistors are biased in the forward active region and  $V_A < \infty$  and  $\beta \gg 1$ .



(a)

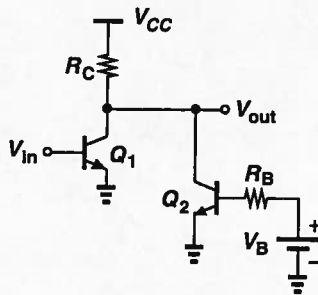


(b)

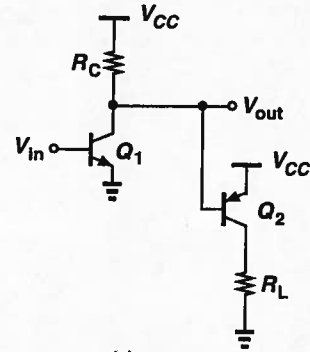

(c)

Solution (a)

From small-signal model

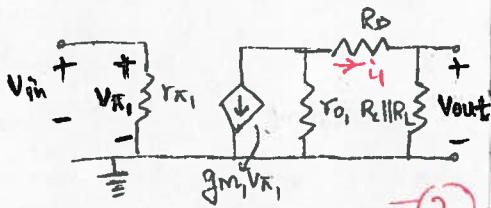

Using current division

$$i_1 = \frac{-g_{m1} v_{k1} r_{o1}}{r_{o1} + R_D + R_C \parallel R_L} \quad (1)$$


$$V_{out} = i_1 R_C \parallel R_L$$

$$= \frac{-g_{m1} v_{k1} r_{o1} R_C \parallel R_L}{r_{o1} + R_D + R_C \parallel R_L}$$

$$= \frac{-g_{m1} v_{in} r_{o1} R_C \parallel R_L}{r_{o1} + R_D + R_C \parallel R_L}$$

$$\frac{V_{out}}{V_{in}} = \frac{-g_{m1} r_{o1} R_C \parallel R_L}{r_{o1} + R_D + R_C \parallel R_L} \quad (2)$$

(b) From small-signal model

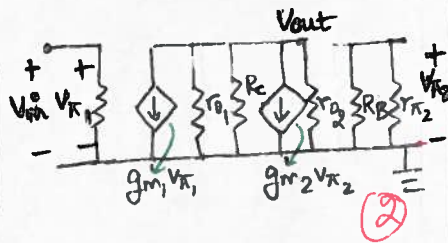

$$\text{Now } v_{k2} = 0 \quad (1)$$


$$\therefore g_{m2} v_{k2} = 0$$

$$V_{out} = -g_{m1} v_{k1} R_C \parallel r_{o1} \parallel r_{o2}$$

$$= -g_{m1} v_{in} R_C \parallel r_{o1} \parallel r_{o2}$$

$$\frac{V_{out}}{V_{in}} = -g_{m1} R_C \parallel r_{o1} \parallel r_{o2} \quad (2)$$

(c) Small-signal model.

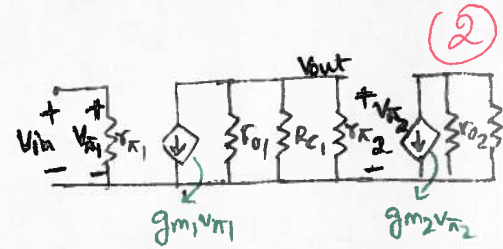

$$V_{out} = -g_{m1} v_{k1} r_{o1} \parallel R_C \parallel r_{k2}$$

$$= -g_{m1} v_{in} r_{o1} \parallel R_C \parallel r_{k2}$$

$$\frac{V_{out}}{V_{in}} = -g_{m1} r_{o1} \parallel R_C \parallel r_{k2} \quad (3)$$

