

**EE 115A**

**Midterm Exam**

**Fall 2015**  
**Group I**

Name of Person to Your Right:

No body

**Time Limit: 1 Hour and 50 Minutes**

1. ~~25/50~~ 10/10
2. ~~10.5/15~~
3. 0/10
4. 2/15

Total:



22.5  
—  
50

1. Assuming a constant-voltage diode model with  $V_{D,on} = 0.8$  V,


(a) plot  $V_{out}$  and  $I_{D1}$  as a function of  $V_{in}$  if  $I_1 = 0$ . Show the details of your calculations. 5/5

(b) plot  $V_{out}$  and  $I_{D1}$  as a function of  $V_{in}$  if  $I_1$  is constant and equal to 1 mA. Show the details of your calculations.

4.5  
5

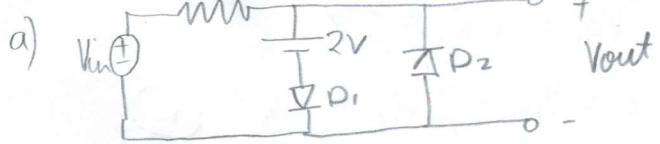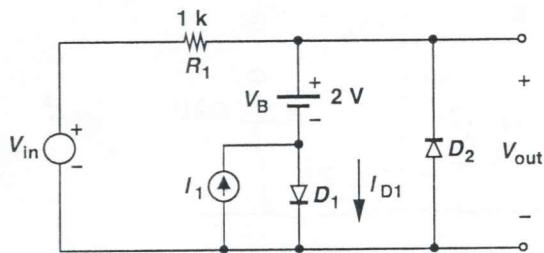

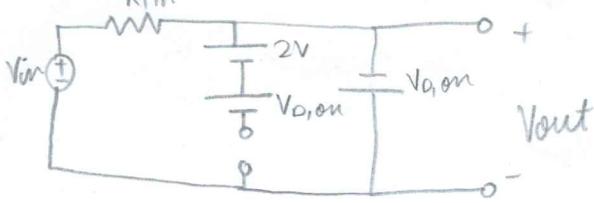
①  $V_{in} \rightarrow -\infty$   $D_1$  off  $D_2$  on



$$V_{out} = -V_{D,ON}$$

$$V_{in} < -V_{D,ON} \quad I_{D1} = 0 \quad \text{①}$$

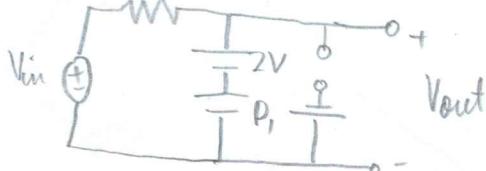③  $V_{in} \uparrow D_1$  on,  $D_2$  off




$$V_{out} = V_{D,ON} + 2V$$

$$I_{D1} = \frac{V_{in} - 2V - V_{D,ON}}{R_1} \quad \text{①}$$

$$I_{D1} = \frac{V_{in}}{R_1} - \frac{2.8}{1000}$$


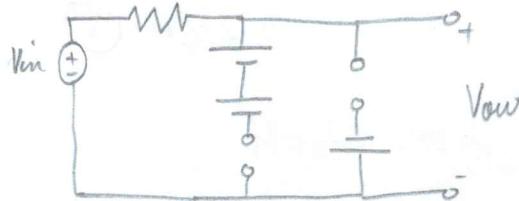
②  $V_{in} \uparrow D_2$  off  $D_1$  off



$$V_{out} = V_{in} \quad \text{①}$$


$$-V_{D,ON} < V_{in} < 2V + V_{D,ON} \quad I_{D1} = 0$$

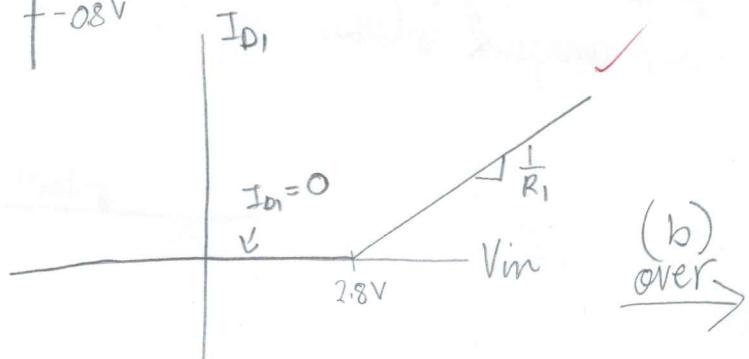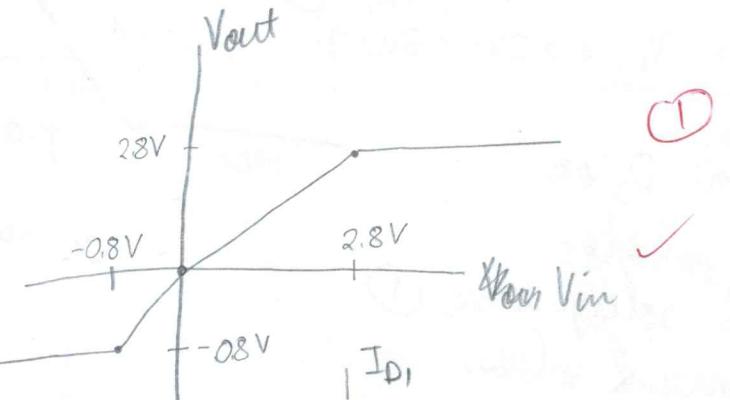④  $D_1$  on  $D_2$  on  
not possible  $\rightarrow \frac{2V}{V_{D,ON}} = \frac{1}{R_1}$




2. Determine the region of operation of  $Q_1$  in each of the circuits shown below. Assume  $I_S = 2 \times 10^{-16} \text{ A}$ ,  $\beta = 100$ ,  $V_A = \infty$ . You need only show whether the transistor is in the forward active region, saturated, at the edge of saturation, or off ( $I_C = 0$ ). Indicate which region and explain why.


10.5  
15

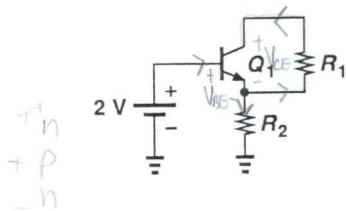


(a)

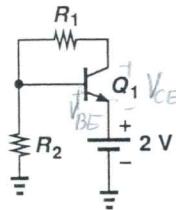


(b)

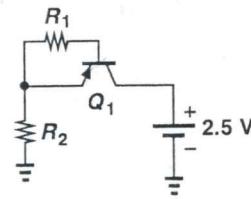

(c)

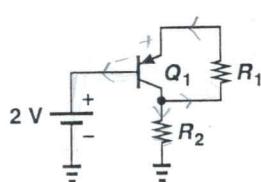

(d)

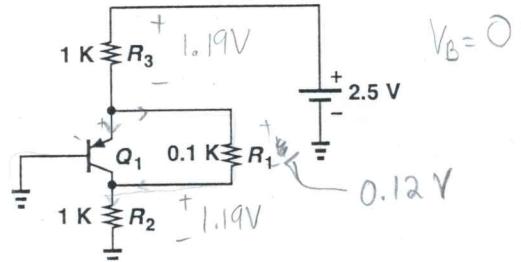

(e)

a)  $V_B = 2V$

$V_{BE} \approx 0.75V$

$V_C \approx 1.25V$

$V_B > V_C$  npn

saturation because  
collector and emitter  
are forward biased. 3)

b)  $V_E = 2V$

off current cannot  
flow from emitter  
to collector.

2.5

c) off current cannot  
flow from 2.5 to  
ground. transistor  
is PNP 2.5

d)  $V_B = 2V$

off no supply  
voltage source

2.5

e)

off E-B bias

justify

collector base voltage is reversed biased  
base emitter voltage is reversed biased

$I_C = 0$


5)

3. Consider the circuit shown below, where  $I_{S1} = 3I_{S2} = 5 \times 10^{-16}$  A,  $\beta_{npn} = 2\beta_{pnp} = 100$ , and  $V_A = \infty$ . You can assume the collector and emitter currents are equal.  $I_c = I_E$

(a) We wish to forward-bias the collector-base junction of  $Q_2$  by no more than 200 mV. Determine the maximum allowable value of  $V_{in}$ .

(b) Suppose  $V_{in} = 1.5$  V. What is the maximum value of  $R_C$  that forward-biases the collector-base junction of  $Q_2$  by no more than 200 mV?

0/10

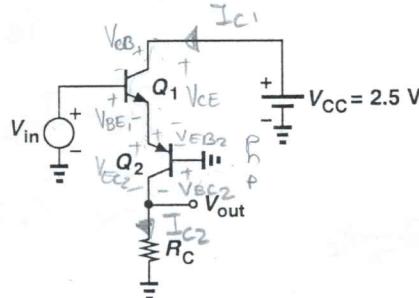

$$V_{C1} = 2.5 \text{ V}$$

$$V_{B1} = V_{in}$$

$$V_{E1} =$$

$$V_{E2} =$$

$$V_{B2} = 0$$

$$V_{C2} =$$

$$I_{C1} = I_{C2}$$

$$\neq$$

$$V_{CE1} =$$

$$I_C$$

$$\begin{aligned} a) \quad V_{CC} &= V_{CE1} + V_{EB2} \\ V_{CC} &= V_{CB1} + V_{in} \\ V_{CC} &= V_{CE1} + V_{EC2} + I_{G2} R_C \end{aligned}$$

$$V_{in} = 2V_{EB}$$

$$I_{C1} = I_{S1} \exp\left(\frac{V_{EB}}{V_T}\right) \quad V_{EB} = V_T \ln\left(\frac{I_{C1}}{I_{S1}}\right)$$

$$V_{CC} = V_{CE1} + V_T \ln\left(\frac{I_{C1}}{I_{S2}}\right)$$

$$I_{C2} R_C = -V_{BC2} \quad V_{CE1} = V_{CC} - V_T \ln\left(\frac{I_{C1}}{I_{S2}}\right)$$

$$V_{CC} = 2(V_{CC} - V_T \ln\left(\frac{I_{C1}}{I_{S2}}\right)) + I_C R_C$$

$$V_{CC} = -I_C R_C + 2V_T \ln\left(\frac{I_{C1}}{I_{S2}}\right)$$

$$Q_2 \text{ is } I_C = 1 \text{ mA}$$

$$2.5 + I_C R_C =$$

$$-I_C R_C = V_{BC} < 200 \text{ mV}$$

$$V_{CC} - 2V_T \ln\left(\frac{I_{C1}}{I_{S2}}\right) = V_{BC} < 200 \text{ mV}$$

$$2.5 - 2V_T \ln\left(\frac{I_{C1}}{I_{S2}}\right) < 200 \text{ mV}$$

$$2V_T \ln\left(\frac{I_{C1}}{I_{S2}}\right) > 2.3$$

$$\ln\left(\frac{I_{C1}}{I_{S2}}\right) > 44$$

$$I_{C1} > 2142 \text{ A}$$

$$V_{EB} = 1.14 \text{ V}$$


$$V_{in} = 2.29 \text{ V}$$

maximum


(b)  
over

2

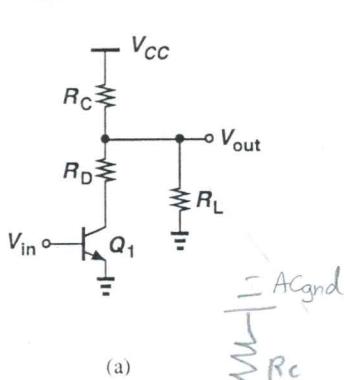
4. Compute the voltage gain of the circuits shown below, assuming that all transistors are biased in the forward active region and  $V_A < \infty$  and  $\beta \gg 1$ .




(a)

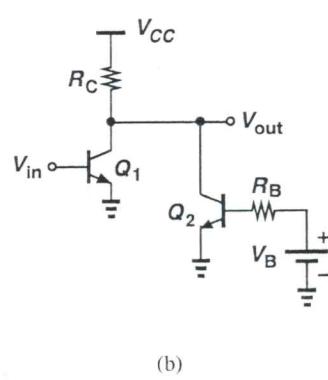


(b)

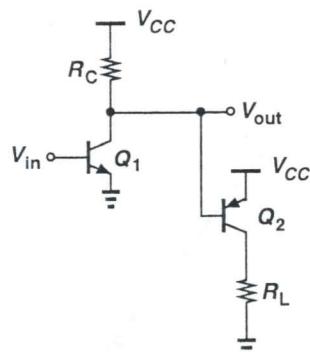

a)

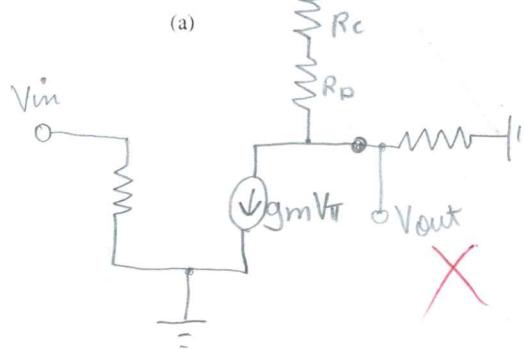


$$A_V = -g_m \times (R_C + R_D)$$

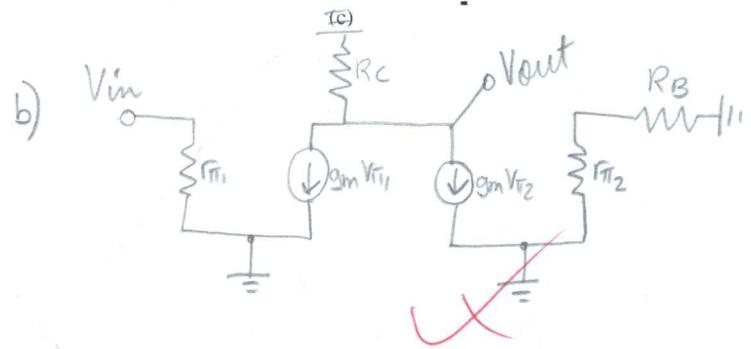

$$A_V = \frac{R_C \parallel (R_B + R_L)}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$



c)

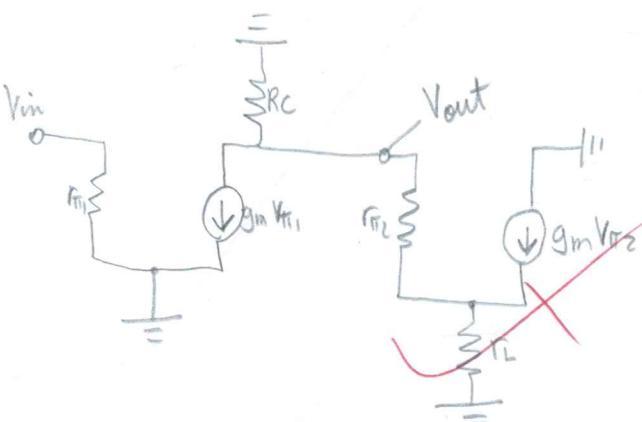

$$A_V = \frac{R_C}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

