

**EE 115A
Winter 2011
Midterm Exam
Feb 7th 2010**

Instructions: This exam consists of five problems, blank sheets for the solutions and additional blank sheets. You have 1 hour 45 minutes to finish your exam.

Name:

UID:

Left student's name:

Right student's name:

Problem1:	18 /20
Problem2:	20 /30
Problem3:	20 /20
Problem4:	30/30
Problem5 (Bonus):	0 /20

Total: 88

The professor did not provide solutions to #2, so I included mine. They are 2/3 correct.


Problem 1 (20)

For the circuit in the following figure, please plot the input – output characteristics (V_{out} vs. V_{in}) for $-5V < V_{in} < 5V$. Please find the important break-points and the slope (show steps), and label them on the waveform.

(a) Assume ideal diodes.

(b) Assume constant-voltage diode model ($V_{D,on} = 0.7V$).



(10 + 10 = 20 points)

 


Problem 2 (30)

For the circuits in the following figure, each utilizes an ideal diode. Please sketch the output in the steady-state for the shown input. Label the most positive and the most negative output levels and mathematically justify your sketch. Please provide two sets of outputs for a) $RC \ll T$, b) $T < RC < \infty$.


(15 + 15 = 30 points)

  

(a)

 


(b)

 

(c)

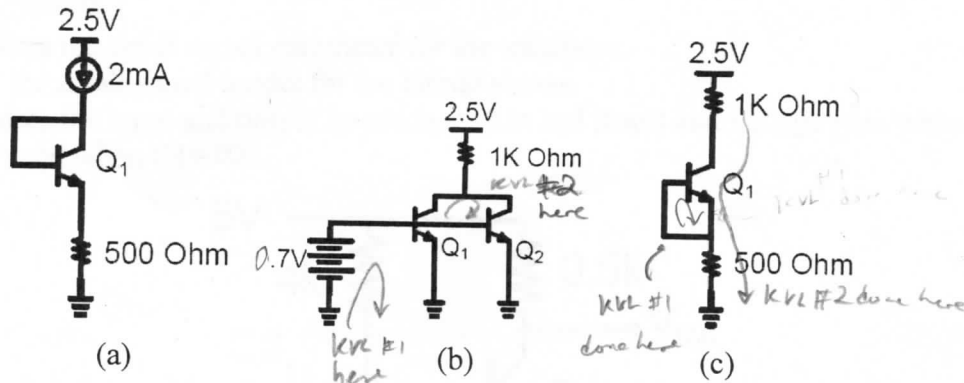Problem 3 (20)

Assume $I_s = 8 \cdot 10^{-16}$, $\beta = 100$, $V_A = \infty$, $V_{CE,SAT} = 0.2$ V. Find I_C , V_{BE} , V_{CE} and identify the region of operation.




Problem 4 (30)

For the amplifier circuit shown below, assume that $I_s(\text{pnp}) = 5 \cdot 10^{-16}$, $\beta(\text{pnp}) = 100$, $V_A(\text{pnp}) = \infty$, $I_s(\text{nnp}) = 5 \cdot 10^{-16}$, $\beta(\text{nnp}) = 80$, $V_{CE,SAT} = 0.2$ V, and $V_A(\text{nnp}) = \infty$.

(a) For $R_{C2} = 2\text{K}\Omega$, solve for the voltages of all three terminals of both transistors Q_1 and Q_2 (V_E , V_C , and V_B for both the npn and pnp).

 (b) For what values of R_{C2} will the device Q_2 be in saturation region?


*You may neglect I_B with respect to I_R .



 Problem 5 (Bonus, 20 total)

For the circuit in the following figure, $I_s=5 \cdot 10^{-16}A$, $\beta=100$, $V_{CE(sat)} = 0.2V$, $V_{D,on}=0.7V$ and $V_A = \infty$, $C_2 = \infty$.


- Calculate the small signal parameter for the transistor.
- Draw the small signal model for the circuit shown.
- Calculate the input and output impedance (R_{in} and R_{out}) and voltage gain when $C_1=0$; and when $C_1 = \infty$.




Midterm

(P1) a) for $V_i = -5$


D_2 & D_3 are on, D_1 & D_4 are off

 

 
$$V_o = -V_i \times \frac{R}{5R} = \frac{-V_i}{5}$$



 as V_i increases, @ $V_i = 0$ D_2 & D_3 turn off & D_1 & D_4 turn on



 
$$V_o = V_i \times \frac{R}{3R} = \frac{V_i}{3}$$



(b) for $v_i = -5$, D_2 & D_3 are on & D_1 & D_4 are off

$$v_o = -(v_i + 1.4) \times \frac{R}{5R}$$

$$v_o = -\frac{v_i}{5} - 0.28$$


 


as v_i increases to $-1.4 \rightarrow I = 0 \rightarrow D_2$ & D_3 turn off
and D_1 & D_4 are still off
 $I = 0 \rightarrow v_o = 0$

@ $v_i = 1.4$ V $\rightarrow D_1$ & D_4 turn on



$$v_o = (v_i - 1.4) \times \frac{R}{3R}$$

$$= \frac{v_i}{3} - 0.466$$

  


(This page is not entirely correct, but the professor did not give solutions for #2)

Cap doesn't discharge quickly

 
 


when $v_{in} < 0$, cap charges up, and $v_{out} = 0 + v_{cap}$ since grounded
 when $v_{in} > 0$, $v_{out} = v_{in} + v_{cap} = 5 + 5 = 10V$

cap acts like a wire

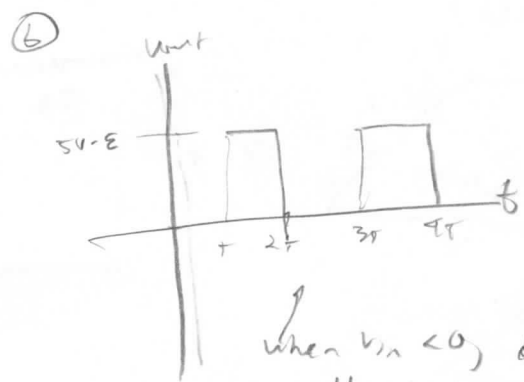


  when $v_{in} < 0$, diode is a wire/shunt
 \therefore no voltage when $v_{in} > 0$ v_{out} is v_{in} minus small change on resistor.





When $v_{in} < 0$, no current flows, so no charge on cap. when $v_{in} > 0$, cap charges up

Ⓛ

 


  When $v_{in} < 0$, no current flows
 when $v_{in} > 0$, $v_{out} = v_{in}$ by KVL



value 1 > value 2 since resistor $4R > R$

Ⓛ

 

When $v_{in} < 0$, $v_{out} = \frac{R}{R+R} v_{in} = \frac{1}{2} v_{in}$
 by voltage division
 when $v_{in} > 0$, $v_{out} = \frac{4R}{4R+R} v_{in} = \frac{4}{5} v_{in}$


(P3) (a)

$$I_C + I_B = 2 \text{ mA} = I_E$$

$$I_C = \alpha I_E = \frac{\beta}{\beta + 1} I_E = 1.98 \text{ mA}$$

$$\rightarrow V_{BE} = V_T \ln \frac{I_C}{I_S} = 0.742 \text{ V}$$

$$\& V_{CE} = V_{BE} = 0.742 \text{ V}$$

 


Transistor in (Active)

(b) $V_{BE1} = V_{BE2} = 0.7 \text{ V}$

$$I_{C1} = I_{C2} = I_S e^{V_{BE}/V_T}$$

$$= 0.394 \text{ mA}$$

 

$$\rightarrow V_{CE1} = 2.5 - 1\text{k} \times 2 \times 0.394 \text{ mA} = 1.712 \text{ V} = V_{CE2}$$

Q_1 & Q_2 are in (Active)

(c)


$V_{BE} = 0 \rightarrow I_C = 0$ as BE junction is in reverse

$$V_C = 2.5 \text{ V}, V_E = 0$$

$$\rightarrow V_{CE} = 2.5 \text{ V}$$

\rightarrow CB junction is in reverse

\rightarrow transistor is (off)

 

Assume $I_B \ll \left(\frac{10V}{10k\Omega} = 1mA\right)$ $\therefore \beta \gg 1 \Rightarrow I_E \approx I_C = \beta I_B$

(a)

$$\therefore V_{B_1} = \frac{10 \times 9}{9+1} = 9V$$

KVL: $10V = I_{E_1} \times 100 + V_{EB_1} + 9V$

$$\therefore 1 = 100 I_E e^{V_{EB_1}/V_T + V_{EB_1}}$$

$$V_{EB} = 0.7 \Rightarrow RHS = 0.725$$

$$V_{EB} = 0.75 \Rightarrow RHS = 0.87$$

$$V_{EB} = 0.8 \Rightarrow RHS = 1.95$$

$$V_{EB} = 0.78 \Rightarrow RHS = 1.12$$

$$V_{EB} = 0.755 \Rightarrow RHS = 0.96V \neq$$

$$\therefore V_{E_1} = V_{B_1} + V_{EB_1} = 9 + 0.96 = 9.96V$$

$$\therefore I_E = \frac{10 - 9.96}{100} = \frac{245mV}{100} = 2.45mA = 400\mu A$$

$$I_C \approx I_E \Rightarrow V_{C_1} = I_{C_1} \times 3000 = 7.35V \quad \text{"Assume } I_{B_2} \ll I_{E_1} \text{"}$$


Check 1: $V_{C_1} < V_{B_1} \Rightarrow$ Active Region

Check 2: $I_{B_1} = \frac{2450\mu A}{100} = 24\mu A \ll 1mA \Rightarrow \left(I_B \ll \frac{10V}{10k\Omega}\right)$
is a valid assumption

KVL₂:

$$V_{c1} = 7.35V = V_{BE2} + I_E \times 1000$$
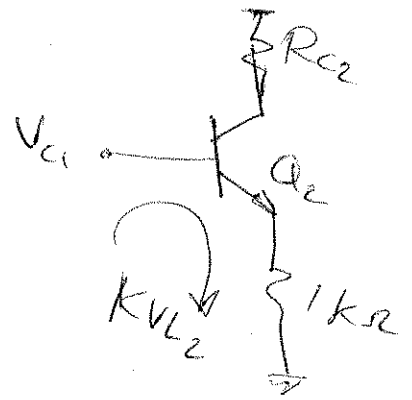
$$\begin{aligned} 7.35 &= V_{BE2} + 1000 I_{S_n} \times e^{V_{BE2}/V_T} \\ &= V_{BE2} + 5 \times 10^{-13} e^{V_{BE2}/V_T} \end{aligned}$$



$$V_{BE2} = 0.7V \Rightarrow \text{RHS} = 0.95$$

$$V_{BE2} = 0.75V \Rightarrow \text{RHS} = 2.44$$

$$V_{BE2} = 0.73V \Rightarrow \text{RHS} = 1.51V$$

$$V_{BE2} = 0.72V \Rightarrow \text{RHS} = 1.25V \neq$$

$$V_{BE2} = 0.785V \Rightarrow \text{RHS} = 7.26$$

$$\therefore V_{B2} = 7.35V, \quad V_{E2} = 7.35 - 0.785 = 6.57V$$

$$\therefore I_{E2} = \frac{6.57V}{1k} = 6.57 \text{ mA}$$

$$\begin{aligned} I_{C2} \approx I_{E2} = 6.57 \text{ mA} &\Rightarrow V_{C2} = 10 - I_{C2} R_{C2} \\ &= 10 - 0.96 = 3.03V \end{aligned}$$

X

Check 1: $V_{C2} > V_{B2} \Rightarrow$ Active Region

Check 2: $I_{B2} = \frac{I_{C2}}{\beta_n} = 6 \mu A \ll (I_{C1} = 400 \mu A)$

(b) Edge of Sat. $\Rightarrow V_{C2} = V_{B2} = 7.35V$

$$\therefore R_{C2} = \frac{10 - 7.35}{6.57 \text{ mA}} = 0.4 \text{ k}\Omega$$

#

5