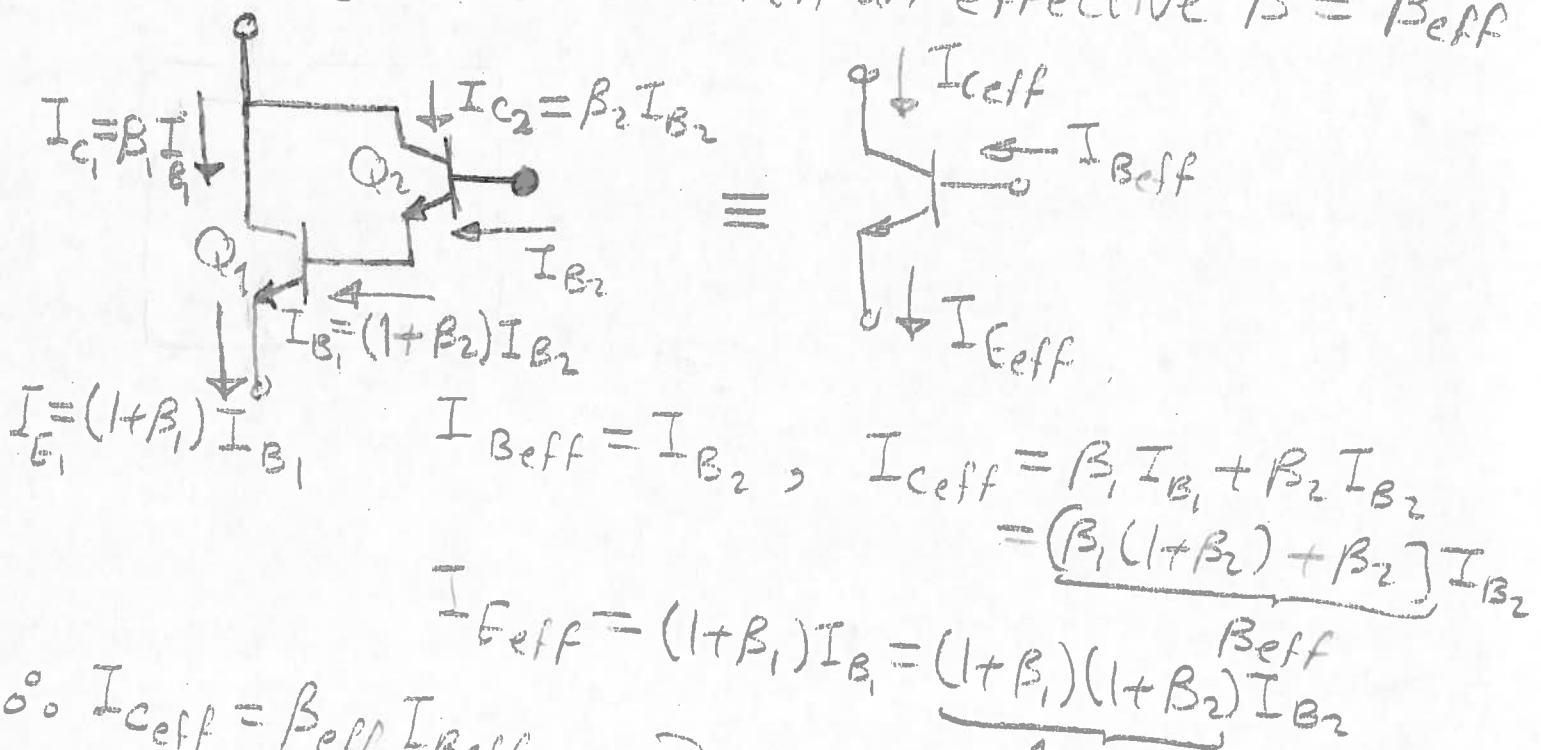


# EE 115B

## Mid-term Solution :


1- A) A Darlington pair can be represented using a single BJT with an effective  $\beta = \beta_{eff}$



$$I_{B_{eff}} = I_{B_2} \Rightarrow I_{C_{eff}} = \beta_1 I_{B_1} + \beta_2 I_{B_2} = (\beta_1(1 + \beta_2) + \beta_2) I_{B_2}$$

$$I_{E_{eff}} = (1 + \beta_1) I_{B_1} = (1 + \beta_1)(1 + \beta_2) I_{B_2}$$
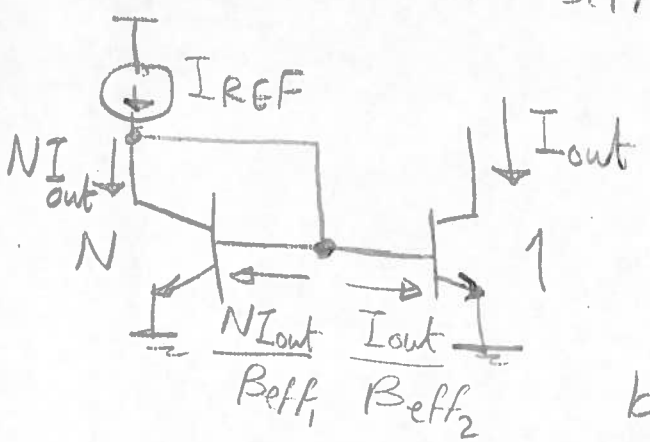
$$\begin{cases} I_{C_{eff}} = \beta_{eff} I_{B_{eff}} \\ I_{E_{eff}} = (1 + \beta_{eff}) I_{B_{eff}} \end{cases} \Rightarrow \beta_{eff} = \beta_1 + \beta_2 + \beta_1 \beta_2$$




$$I_{REF} = NI_{out} + \frac{NI_{out}}{\beta_{eff1}} + \frac{I_{out}}{\beta_{eff2}}$$

$$\therefore I_{out} = \frac{I_{REF}}{N + \frac{N}{\beta_{eff1}} + \frac{1}{\beta_{eff2}}}$$

but  $\beta_{eff1} = \beta_1 + \beta_2 + \beta_1 \beta_2$   
 $\beta_{eff2} = \beta_3 + \beta_4 + \beta_3 \beta_4$

$$\therefore I_{out} = \frac{I_{REF}}{N + \frac{N}{\beta_1 + \beta_2 + \beta_1 \beta_2} + \frac{1}{\beta_3 + \beta_4 + \beta_3 \beta_4}}$$

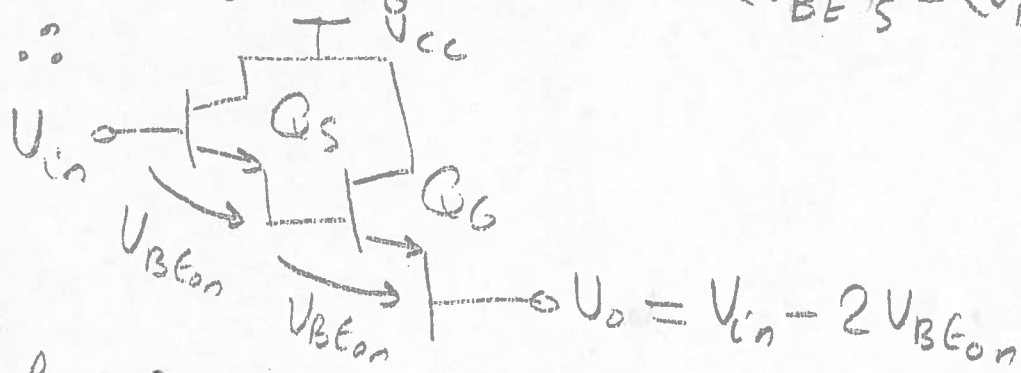B) For  $Q_5$  &  $Q_6$  to be on  $(V_{BE})_5 = (V_{BE})_6 = V_{BEon}$




Also for  $Q_3$  &  $Q_4$  to be in active

$(V_{CE})_4 \geq V_{CEsat} \Rightarrow V_{c4} \geq V_{CEsat}$

Also,  $(V_{CE})_3 \geq V_{CEsat}$

But  $V_{E3} = V_{BEon}$

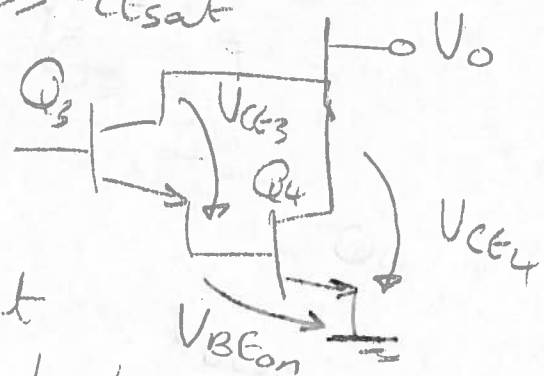$\therefore V_{c3} \geq V_{BEon} + V_{CEsat}$




Since both devices need to be active we take the larger of the two constraints

$\therefore U_o \geq V_{BEon} + V_{CEsat}$

$\therefore U_{o\min} = V_{BEon} + V_{CEsat}$

$U_{in\min} = 3V_{BEon} + V_{CEsat}$

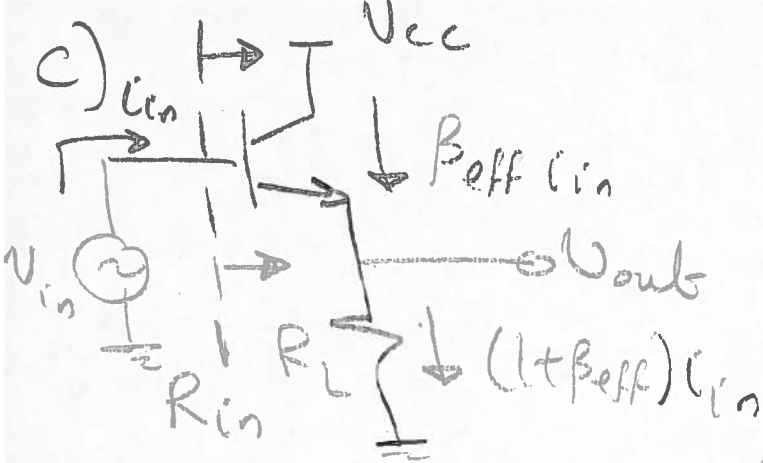


$$i_{in} = \frac{V_{in}}{R_{in}}$$

$$V_{out} = (1 + \beta_{eff}) i_{in} R_L$$

$$\therefore V_{out} = \frac{(1 + \beta_{eff}) R_L V_{in}}{R_{in}}$$

$$\therefore A_v = \frac{(1 + \beta_{eff}) R_L}{R_{in}}$$

But

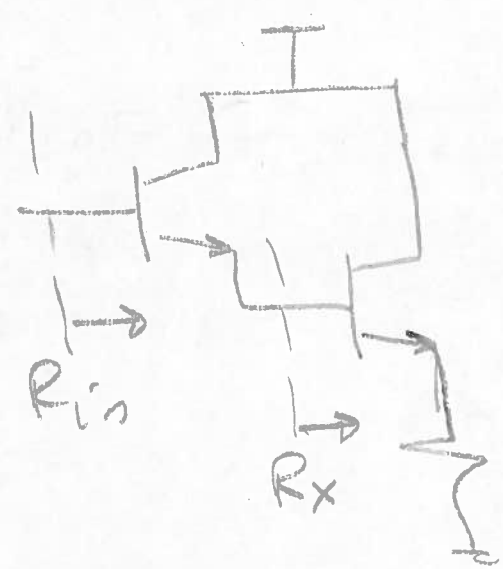

$$R_x = \underbrace{r_{\pi_6} + (1 + \beta_1) R_L}_{\text{reflection rule}}$$

$$R_{in} = \underbrace{r_{\pi_5} + (1 + \beta_2) R_x}_{\text{reflection rule}}$$

$$R_{in} = r_{\pi_5} + (1 + \beta_2) [r_{\pi_6} + (1 + \beta_1) R_L]$$




Also,  $\beta_{eff} = \beta_1 + \beta_2 + \beta_1 \beta_2$

$$\therefore A_v = \frac{(1 + \beta_1 + \beta_2 + \beta_1 \beta_2) R_L}{r_{\pi_5} + (1 + \beta_2) [r_{\pi_6} + (1 + \beta_1) R_L]}$$

You may also use:  $r_{\pi_5} = \frac{V_T}{I_{B_5}}$  &  $r_{\pi_6} = \frac{V_T}{I_{B_6}}$

But  $I_{B_6} = (1 + \beta_2) I_{B_5} \Rightarrow r_{\pi_6} = \frac{r_{\pi_5}}{1 + \beta_2}$
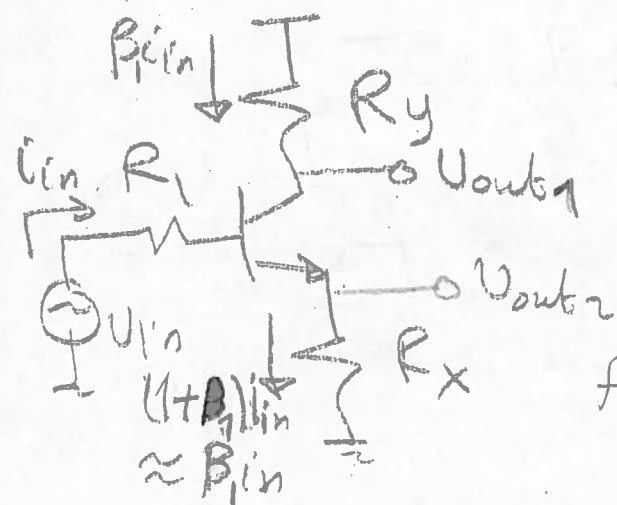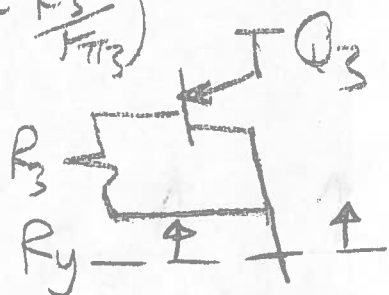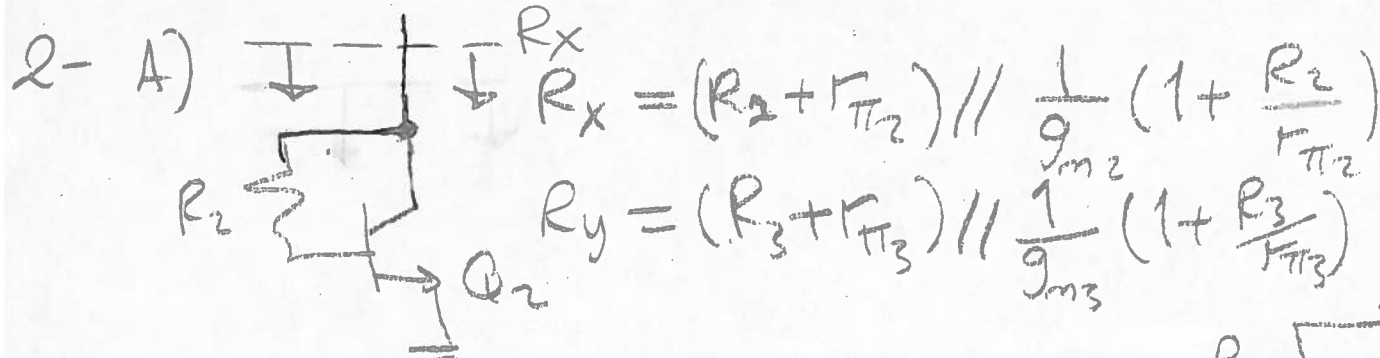
$$\therefore A_v = \frac{(1 + \beta_1)(1 + \beta_2) R_L}{2r_{\pi_5} + (1 + \beta_1)(1 + \beta_2) R_L} = \frac{r_{\pi_5} = \frac{\beta_2 V_T}{I_{C_5}}}{(1 + \beta_2)(1 + \beta_1) V_T} = \frac{I_{C_5}}{I_{out}}$$



$V_{out1} = -\beta_1 I_{in} R_y$   
 $V_{out2} = (1 + \beta_1) I_{in} R_x, \beta_1 \gg 1$   
 $\approx \beta_1 I_{in} R_x$

For  $V_{out1} = -V_{out2}$   
 $R_x = R_y$

$R_x = (R_2 + r_{\pi 2}) \parallel \frac{1}{g_{m2}} \left(1 + \frac{R_2}{r_{\pi 2}}\right) = \frac{R_2 + r_{\pi 2}}{1 + \beta_2}$   
 But because  $\beta_2 \gg 1 \Rightarrow R_x = \frac{R_2 + r_{\pi 2}}{\beta_2}$   
 $= \frac{R_2}{\beta_2} + \frac{1}{g_{m2}}$


Similarly,  $R_y = \frac{R_3}{\beta_3} + \frac{1}{g_{m3}}$   
 $\frac{1}{g_{m2}} = \frac{V_T}{I_{c2}} \quad \& \quad \frac{1}{g_{m3}} = \frac{V_T}{I_{c3}}$

But  $I_{c2} = I_{c3}$  because  $\beta_1, \beta_2, \beta_3 \gg 1$

$\therefore$  For  $R_x = R_y$  we need:

$\frac{R_2}{\beta_2} = \frac{R_3}{\beta_3}$


B)

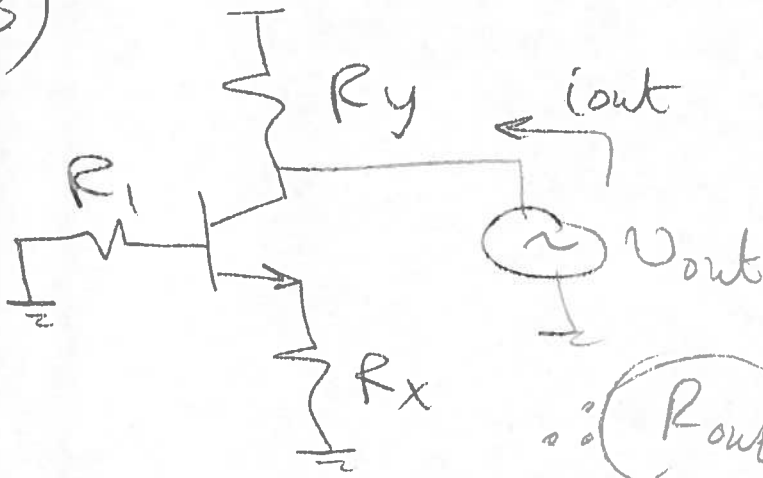

Because  $r_{o1} = \infty$

$$\therefore \frac{V_{out}}{i_{out}} = R_y$$
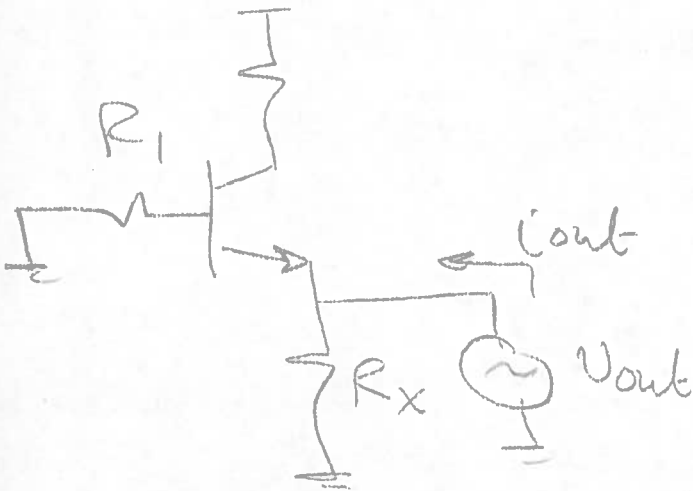
$$\therefore R_{out1} = (R_3 + r_{\pi3}) \parallel \frac{1}{g_{m3}} \left(1 + \frac{\beta_3}{r_{\pi3}}\right)$$




Because  $r_{o1} = \infty$

$$R_{out} = \frac{R_1 + r_{\pi1}}{(1 + \beta_1)} \parallel R_x$$



reflection rule

$$R_{out2} = \frac{R_1 + r_{\pi1}}{(1 + \beta_1)} \parallel \left[ (R_2 + r_{\pi2}) \parallel \frac{1}{g_{m2}} \left(1 + \frac{\beta_2}{r_{\pi2}}\right) \right]$$



3-

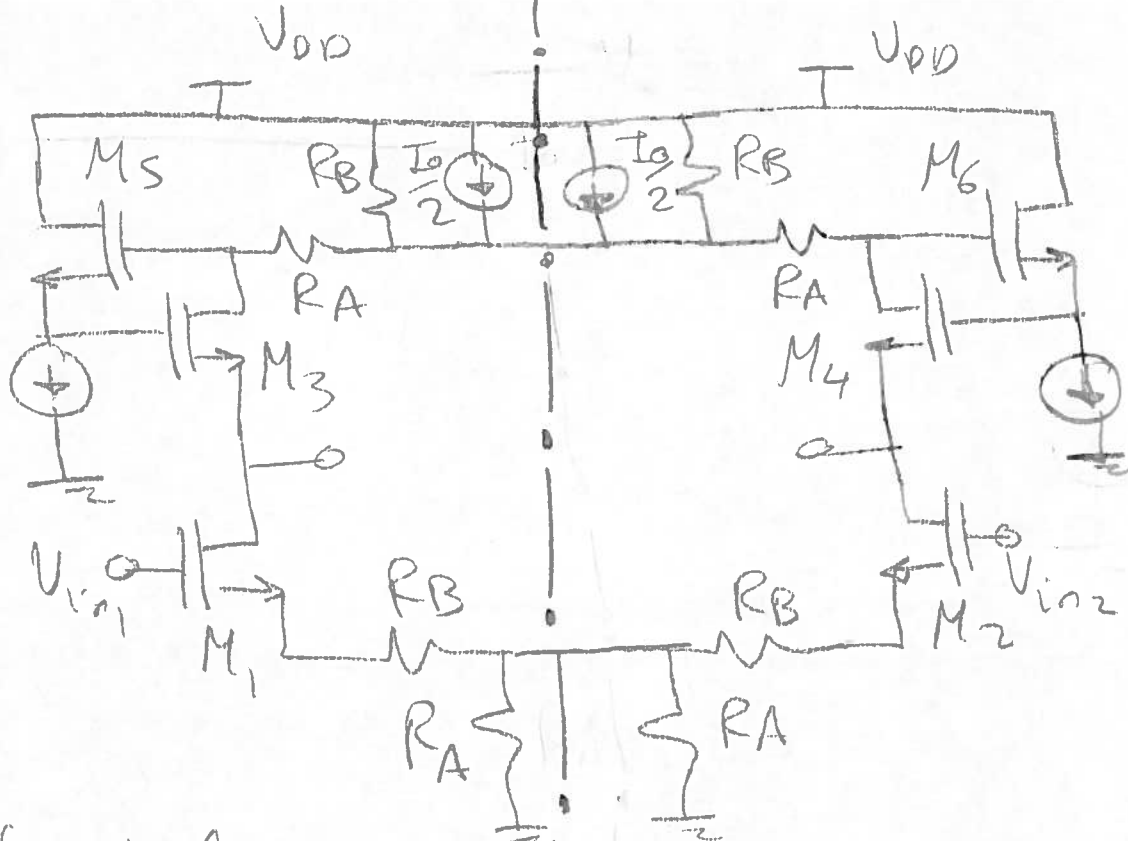

Differential Half-circuit

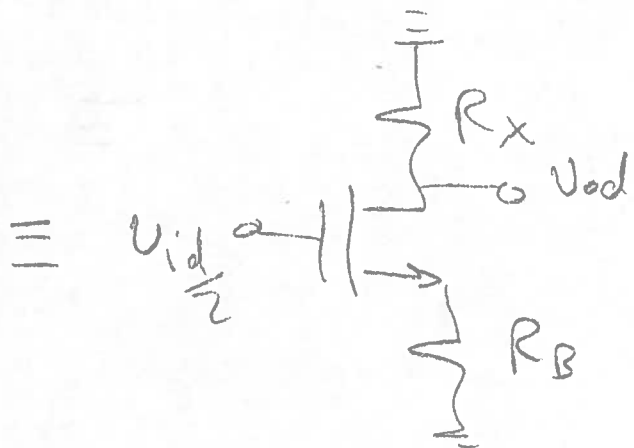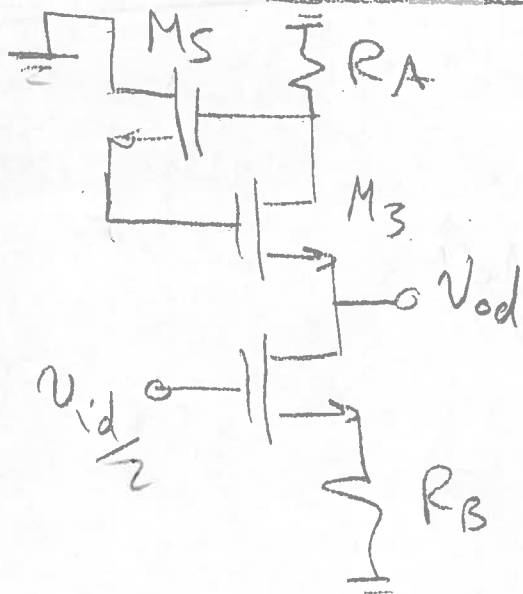

Common Mode Half-circuit

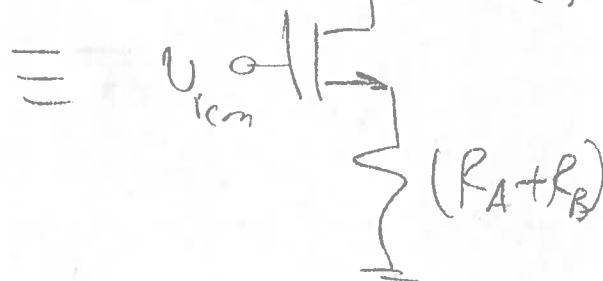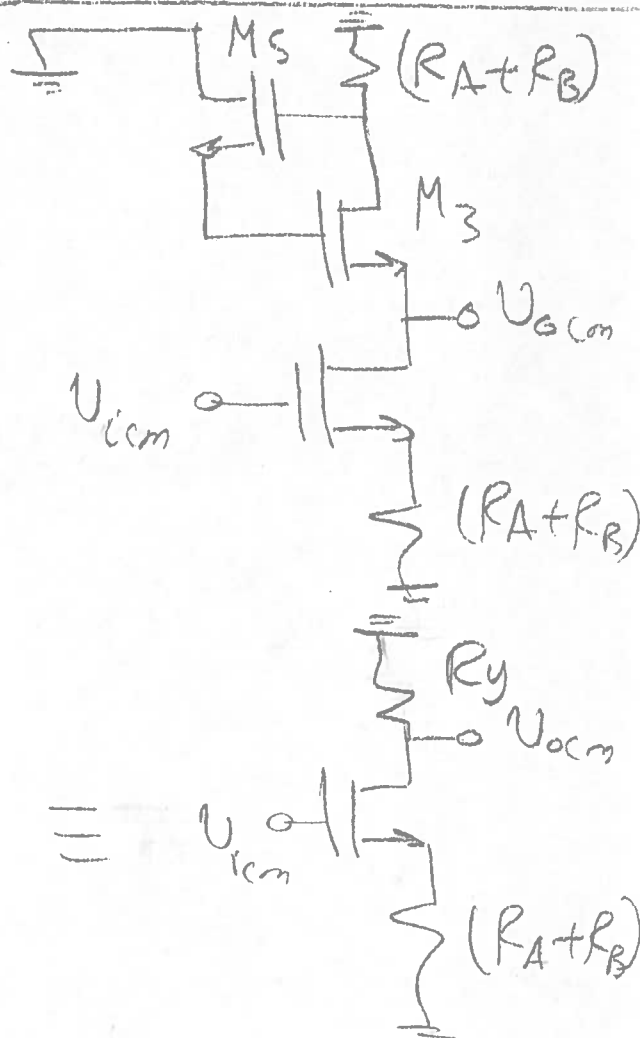

$$A_{vd} = -G_m \cdot R_{out}$$

(ignoring  $r_{o1} \Rightarrow G_m = \frac{g_{m1}}{2(1+g_{m1}R_B)}$

$$R_{out} = R_x$$

$$\therefore A_{vd} = - \frac{g_{m1} R_x}{2(1+g_{m1}R_B)}$$


Also  $A_{cm} = -G_m R_{out}$

ignoring  $r_{o1} \Rightarrow G_m = \frac{g_{m1}}{1+g_{m1}(R_A+R_B)}$

$$\therefore A_{cm} = \frac{-g_{m1} R_y}{1+g_{m1}(R_A+R_B)}$$

$$\therefore CMRR = \frac{A_d}{A_{cm}} = \frac{R_x}{2R_y} \left( \frac{1+g_{m1}(R_A+R_B)}{1+g_{m1}R_B} \right)$$

Now, we need to find  $R_x$  &  $R_y$ :

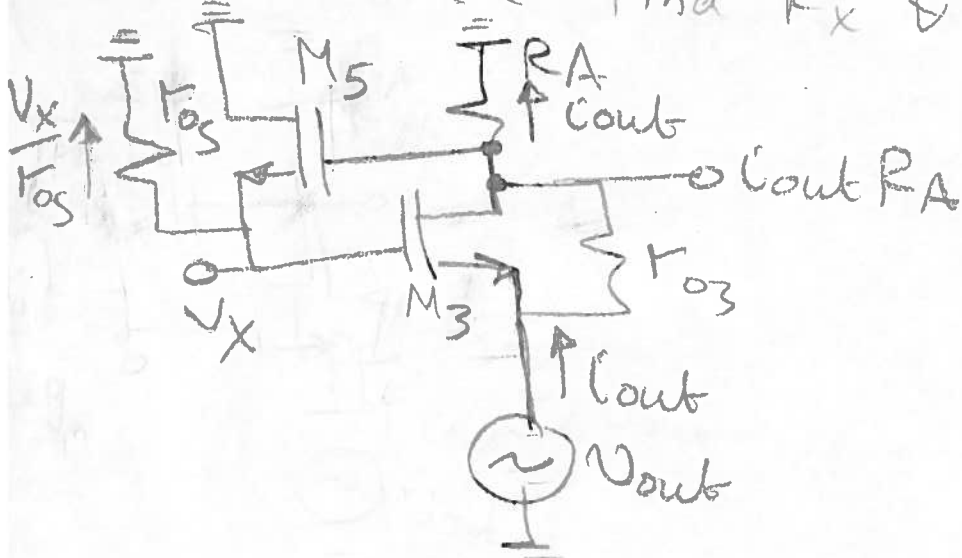

Apply KCL @ source of  $M_5$

$$\frac{V_x}{r_{o5}} = g_{m5}(V_{out} R_A - V_x)$$

$$\therefore V_x \left( \frac{1}{r_{o5}} + g_{m5} \right) = g_{m5} V_{out} R_A$$

$$V_x = \frac{g_{m5} r_{o5}}{1 + g_{m5} r_{o5}} V_{out} R_A$$

Apply KCL @ source of  $M_3$

$$I_{out} = \frac{V_{out} - V_{out} R_A}{r_{o3}} - g_{m3}(V_x - V_{out})$$

$$= \frac{V_{out}}{r_{o3}} - \frac{V_{out} R_A}{r_{o3}} - \frac{g_{m3} g_{m5} r_{o5}}{1 + g_{m5} r_{o5}} V_{out} R_A + g_{m3} V_{out}$$

$$I_{out} \left[ 1 + \frac{R_A}{r_{o3}} + \frac{g_{m3} g_{m5} r_{o5}}{1 + g_{m5} r_{o5}} R_A \right] = V_{out} \left[ \frac{1}{r_{o3}} + g_{m3} \right]$$

$$\therefore R_x = \frac{r_{o3} + R_A + \frac{g_{m3} g_{m5} r_{o5} r_{o3}}{1 + g_{m5} r_{o5}} R_A}{1 + g_{m3} r_{o3}}$$

but  $g_{m3} r_{o3} \gg 1$  &  $g_{m5} r_{o5} \gg 1$

$$\therefore R_x \approx \frac{1}{g_{m3}} + \frac{R_A}{g_{m3} r_{o3}} + R_A \approx R_A + \frac{1}{g_{m3}}$$

Similarly  $R_y \approx (R_A + R_B) + \frac{1}{g_{m3}}$

$$\therefore CMRR = \frac{1}{2} \frac{1 + g_{m3} R_A}{1 + g_{m3} (R_A + R_B)} \cdot \frac{1 + g_{m1} (R_A + R_B)}{1 + g_{m1} R_B}$$