



University of California, Los Angeles  
Henry Samueli School of Engineering and Applied Science  
Department of Electrical Engineering

Danijela Cabric

Tue, Feb 18<sup>th</sup>, 10:00 am – 11:50 am

## EE115C: WINTER 2014—MIDTERM

NAME	SOLUTION	
	Last	First

UID	
-----	--

Please write answers in the box provided.

*Answers elsewhere will not be graded.*

*You have 110 minutes.*

*The test is planned so that you roughly spend 1.5 minutes per point + 20 minutes to check your answers.*

*Budget your time properly.*

*If you get stuck, move on...*

*Good luck!*

Problem 1 \_\_\_\_\_/10

Problem 2 \_\_\_\_\_/10

Problem 3 \_\_\_\_\_/15

Problem 4 \_\_\_\_\_/10

Problem 5 \_\_\_\_\_/15

Total (60)	
------------	--

Problem 1	MOS Operation	10 pts
-----------	---------------	--------

1A For figure 1(a), if  $V_{in}$  is a waveform as shown below, plot  $V_{out}$  as a function of time, if the capacitor  $C_L$  is initially fully discharged. Assume  $V_{TN} = 0.3 V$ ,  $R_{on,N}C_L \ll T_0$ . (3 pts)


 


Figure 1(a)

 

- 1B** For figure 1(b), if  $V_{in}$  is a waveform as shown below, plot  $V_{out}$  as a function of time, if the capacitor  $C_L$  is initially fully discharged. Assume  $V_{TP} = -0.3 V$ ,  $R_{on,P}C_L \ll T_0$ . (3 pts)


 


Figure 1(b)

 

- 1C For figure 1(c), if  $V_{in}$  is a waveform as shown below, plot  $V_{out}$  as a function of time, if the capacitor  $C_L$  is initially charged such that initial value of  $V_{out} = 1.3V$ . Assume  $V_{TP} = -0.3V, R_{on,p}C_L \ll T_0$ . (4 pts)


 


Figure 1(c)

 

<b>Problem 2</b>	<b>Voltage Transfer Characteristics</b>	<b>10 pts</b>
------------------	---	---------------

Consider the CMOS inverter shown in Figure 2. Assume there is **no sub-threshold conduction**.  $V_{DD} = 0.5\text{ V}$ ,  $V_{TN} = |V_{TP}| = 0.3\text{ V}$ .


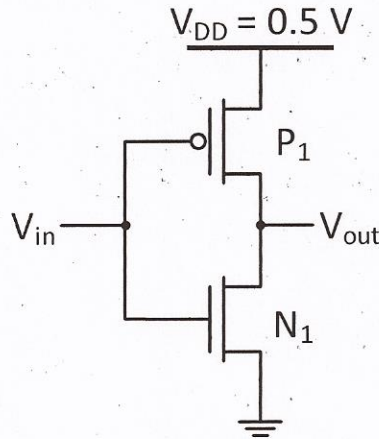


Figure 2

 - 2A Sketch the **Voltage Transfer Characteristics (VTC)** with all relevant points marked on the graph. Also, mark on the graph, the regions where the NMOS and PMOS are ON/OFF. (Hint: Sweep  $V_{in}$  from 0 to 0.5V and back to 0V, and plot  $V_{out}$ .) (7 pts)



2B Find  $V_{OL}$ ,  $V_{OH}$  and  $V_M$ .

(3 pts)

$$V_{OL} = 0V$$

$$V_{OH} = V_{DD} = 0.5V$$

$V_M$  cannot be uniquely found because, in the middle region, both PMOS and NMOS are OFF and changing  $V_{in}$  does not change  $V_{out}$ .

$V_{OL} = 0$	(1)
$V_{OH} = 0.5V$	(1)
$V_M = \text{Does not exist}$	(1)

**Problem 3**

**Power Consumption**

15 pts

A 5-stage ring oscillator is shown below (built with static CMOS gates with sizes shown, all inverters of the same size). Assume  $C_{S/D} = C_G = 2fF/\mu m$ ,  $V_{DD} = 1V$ .


 


Figure 3

3A For  $A: 0 \rightarrow 1$ , determine the energy taken out of supply.

(5 pts)

 

Total capacitance at each of the intermediate nodes is  $(6\mu m + 6\mu m) \times \frac{2fF}{\mu m} = 24fF$  (2)

When  $A: 0 \rightarrow 1$ ,  $C: 0 \rightarrow 1$  &  $E: 0 \rightarrow 1$

Thus, energy taken out of supply

$$= 3 \times 24fF \times V_{DD}^2 \quad (2)$$

$$= 3 \times 24fF \times 1^2$$

$$= 72fJ$$

$E_{tot} = 72fJ$	(1)
------------------	-----

3B For A:  $0 \rightarrow 1$ , determine the energy dissipated as heat.

(5 pts)

Inverters 2, 4, and 5: Energy dissipated by PMOS (1)

Inverters 1 and 3: Energy dissipated by NMOS

Thus, in total, 5 transistors release heat (1)

$$(1) E_{NMOS} = E_{PMOS} = \frac{1}{2} \times 24 \text{ fF} \times 1^2 = 12 \text{ fJ}$$

$$E_{\text{heat tot}} = 5 \times 12 \text{ fJ} = 60 \text{ fJ} \quad (1)$$

$E_{\text{heat tot}} = 60 \text{ fJ}$	(1)
---------------------------------------	-----

3C Assume the single-stage delay  $t_p = 50 \text{ ps}$  ( $V_{DD} = 1 \text{ V}$ ), determine the average power dissipation. (5 pts)

$$P_{\text{avg}} = f_{\text{osc}} \cdot C_{\text{tot}} \cdot V_{DD}^2 \quad (2)$$

$$= \frac{1}{2 \times 5 \times 50 \text{ ps}} \times 5 \text{ inverters} \times \frac{24 \text{ fF}}{\text{inverter}} \times 1^2 \quad (2)$$

$$= 240 \text{ } \mu\text{W}$$

$P_{\text{avg}} = 240 \text{ } \mu\text{W}$	(1)
---	-----



**Problem 4**

**CMOS Logic and Logical Effort**

**10 pts**

Assume the mobility ratio  $\mu_n : \mu_p = 2$ ,  $C_{S/D} = C_G = C_0$ .

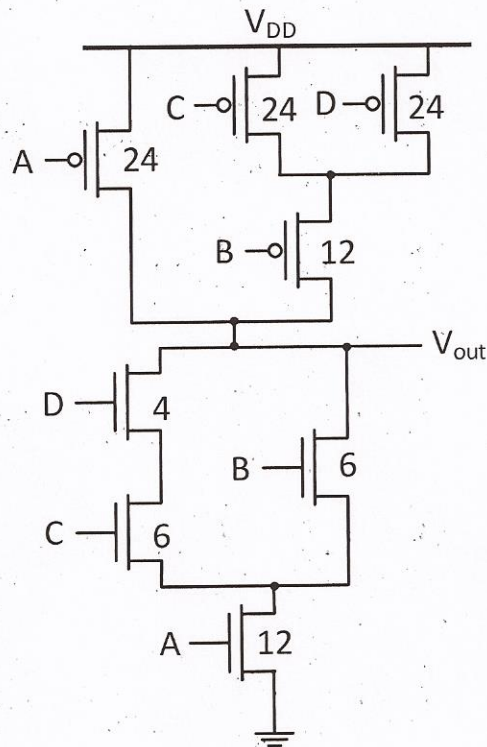


Figure 4

4A What is the logic function of Out? (2 pts)

Out =  $\overline{A \cdot (B + CD)}$  (2)

4B Which input has the lowest average delay to the output? (4 pts)

A (B) C D (2)

Justification: Closest to the output (2)

- 4C What are the largest  $g_{avg}$  (average worst-case  $g_{up}$  and  $g_{down}$  for an input) and largest  $p_{avg}$  (average worst-case  $p_{up}$  and  $p_{down}$  for an input)? You may ignore the capacitances at intermediate nodes. (4 pts)

Since, A and C have the largest input capacitance and the second largest input capacitance, respectively, one of those will tend to have the largest  $g_{avg}$ .

For input A:

$$g_{A\ up} = \frac{36}{36} = 1$$

$$g_{A\ down} = \frac{36}{6} = 6$$

$$g_{A\ avg} = 3.5$$

For input C:

$$g_{C\ up} = \frac{30}{12} = 2.5 \quad (0.5)$$

$$g_{C\ down} = \frac{30}{6} = 5 \quad (0.5)$$

$$g_{C\ avg} = 3.75$$

For inputs B and D, it is easy to verify that the  $g_{avg}$  is lower than 3.75.

$$\begin{array}{l} (0.5) \quad p_{up} = \frac{46}{12} \\ (0.5) \quad p_{down} = \frac{46}{6} \end{array} \left. \vphantom{\begin{array}{l} p_{up} \\ p_{down} \end{array}} \right\} \begin{array}{l} \text{Independent of} \\ \text{input} \end{array}$$

$$p_{avg} = 5.75$$

$$\boxed{\text{Max}(g_{avg}) = 3.75} \quad (1)$$


$$\boxed{\text{Max}(p_{avg}) = 5.75} \quad (1)$$

Problem 5

Logical Effort Delay

15 pts

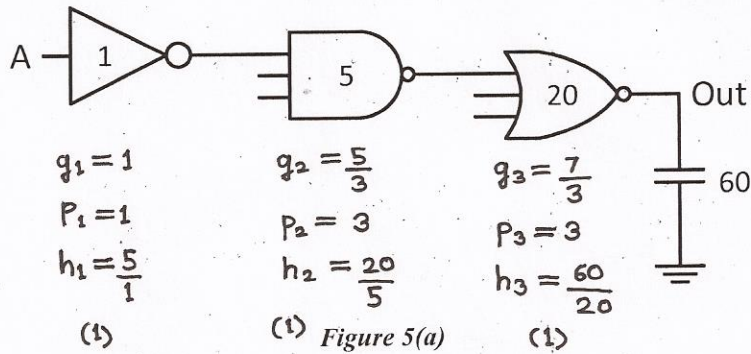5A For the logic path from A to Out shown below, find the **total path delay** using logical effort. Assume  $\mu_n: \mu_p = 2$ . (5 pts)



$$\begin{aligned}
 \text{Total path delay } D &= (g_1 h_1 + p_1) + (g_2 h_2 + p_2) + (g_3 h_3 + p_3) \quad (1) \\
 &= 5 + 1 + \frac{20}{3} + 3 + \frac{7}{3} \cdot 3 + 3 \\
 &= 25.67
 \end{aligned}$$

$D = 25.67$	(1)
-------------	-----

- 5B For the same logic circuit in figure 5(a), without changing the load and the sizing of the first inverter, resize other gates such that the total path delay from A to Out is minimized. In other words, find the **sizes x and y**. Also, find the **minimum delay** from A to Out.

(10 pts)

 


Figure 5(b)

$$G = g_1 g_2 g_3 = \frac{5}{3} \cdot \frac{7}{3} = \frac{35}{9} \quad (1)$$

$$H = \frac{C_{out}}{C_{in}} = \frac{60}{1} = 60 \quad (1)$$

No branching.

$$F = GH = \frac{35}{9} \times 60 = 233.33 \quad (1)$$

$$P = p_1 + p_2 + p_3 = 1 + 3 + 3 = 7 \quad (1)$$

$$f_{opt} = \sqrt[N]{F} = \sqrt[3]{233.33} = 6.156 \quad (1)$$

$$D = Nf_{opt} + P \quad (1)$$

$$= 3(6.156) + 7$$

$$= 25.47$$

$$f_{opt} = g_1 h_1 = g_2 h_2 = g_3 h_3 \quad (1)$$

$$\Rightarrow 6.156 = x = \frac{5}{3} \frac{y}{x} = \frac{7}{3} \frac{60}{y}$$

$$\Rightarrow x = 6.156, y = 22.74$$

$x = 6.156$	(1)
-------------	-----

$y = 22.74$	(1)
-------------	-----

$D_{min} = 25.47$	(1)
-------------------	-----