



University of California, Los Angeles
Henry Samueli School of Engineering and Applied Science
Department of Electrical Engineering

D. Marković

Mon, May 2, 8:00 – 9:50 am

EE115C: SPRING 2011—MIDTERM

NAME	Last SOLUTION First
SID	

Please write answers in the box provided.

Answers elsewhere will not be graded.

<p><i>You have 110 minutes.</i></p> <p><i>The test is planned so that you roughly spend 2 minutes per point + 10 minutes to check your answers.</i></p> <p><i>Budget your time properly.</i></p> <p><i>If you get stuck, move on...</i></p> <p><i>Good luck!</i></p>
--

Problem 1 ____/10

Problem 2 ____/10


Problem 3 ____/20

Problem 4 ____/10

Total (50)	
-------------------	--

 PROBLEM 1: MOS Transistor – Regions of Operation (10 pts)

Determine the region of operation for devices (a) and (b) for the V_X values listed in the tables below. If you find that a device is on the boundary of two regions, write both regions in the table. For example, for a device on the boundary of linear and saturation region write (linear/saturation). Assume $V_{SB} = 0$ for both devices (no body bias).



Parameters:
 $V_{TN} = 0.17V, V_{TP} = -0.2V$
 $\epsilon_{CN} = 3V/\mu m, |\epsilon_{CP}| = 4V/\mu m$
 For both transistors: $L_d = 110nm, x_d = 15nm$

Device (a) (5 pts)

- $|V_{DSATP}| = |\epsilon_{CP}| \times L_{effP} = 0.32V.$
 $|V_{GT}| = |V_{GS}| - |V_{TP}| = |V_{GS}| - 0.2 \leq 0$: cutoff
 $V_{min} = \min(|V_{GT}|, |V_{DS}|, |V_{DSATP}|)$
- $V_{min} = |V_{GT}|$: saturation
 - $V_{min} = |V_{DS}|$: linear
 - $V_{min} = |V_{DSATP}|$: vel-saturation

$V_X = 0 V$	$V_X = 0.6 V$	$V_X = 0.7 V$	$V_X = 1.1 V$
Saturation	Saturation	Linear/Saturation	Linear


Device (b) (5 pts)

- $V_{DSATN} = \epsilon_{CN} \times L_{effN} = 0.24V.$
 $V_{GT} = V_{GS} - V_{TN} = V_{GS} - 0.17 \leq 0$: cutoff
 $V_{min} = \min(V_{GT}, V_{DS}, V_{DSATN})$
- $V_{min} = V_{GT}$: saturation
 - $V_{min} = V_{DS}$: linear
 - $V_{min} = V_{DSATN}$: vel-saturation

$V_X = 0.4 V$	$V_X = 0.2 V$	$V_X = 0.09 V$	$V_X = 0 V$
Cutoff	Saturation	Saturation/Vel-Sat	Vel-Sat

 PROBLEM 2: VTC (10 pts)

Consider the circuit below, with the input at the gate of the NMOS transistor M_1 . M_2 is also an NMOS transistor, but its gate voltage is fixed at 0.4V.



Parameters:

$$\begin{aligned} V_{DD} &= 1V, \\ V_{DSAT} &= 0.3V, V_{T0} = 0.17V, \\ k_n' &= 130\mu A/V^2, \gamma = 0, \lambda = 0. \end{aligned}$$

(a) Calculate V_{out} for $V_{in} = V_{DD}$. (3 pts)

Since M_1 is diode-connected, assume M_1 is in velocity saturation (v-sat).

Since M_2 has very low V_{GS} , assume M_2 is in saturation.

From $I_{M1} = I_{M2}$,

$$130 \times 4 \times \left((V_{in} - V_{out} - 0.17) \times 0.3 - \frac{0.3^2}{2} \right) = 130 \times 2 \times \frac{(0.4 - 0.17)^2}{2}$$

$$V_{out} = 0.64V$$

Check: based on V_{out} , we confirm that M_1 is v-sat and that M_2 is sat.

$V_{out} = 0.64 V$

(b) Calculate V_{out} for $V_{in} = 0.7V$. (3 pts)

Assume M_1 is in v-sat (could be v-sat or sat, but $V_G = 0.7V$ is quite high, so assume v-sat)

Assume M_2 is in saturation for the same reason as in (a).

From $I_{M1} = I_{M2}$,

$$130 \times 4 \times \left((V_{in} - V_{out} - 0.17) \times 0.3 - \frac{0.3^2}{2} \right) = 130 \times 2 \times \frac{(0.4 - 0.17)^2}{2}$$

$$V_{out} = 0.34V$$

Check: based on V_{out} , we confirm that the assumptions are valid.


$V_{out} = 0.32V$

(c) Sketch the VTC for this circuit. (4 pts)

As long as M_1 is in v-sat and M_2 is in saturation like in parts (a) and (b), we have a level-shifter:


$$V_{out} = V_{in} - 0.36V$$

When V_{in} is reduced such that M_2 enters linear region ($V_{out} < 0.4 - 0.17 = 0.23V$), current equation has V_{out}^2 term. Below $V_{in} = 0.23V + 0.36V = 0.59V$, the circuit is a non-linear level shifter down to $V_{in} = 0.17V$ below which $V_{out} = 0$.

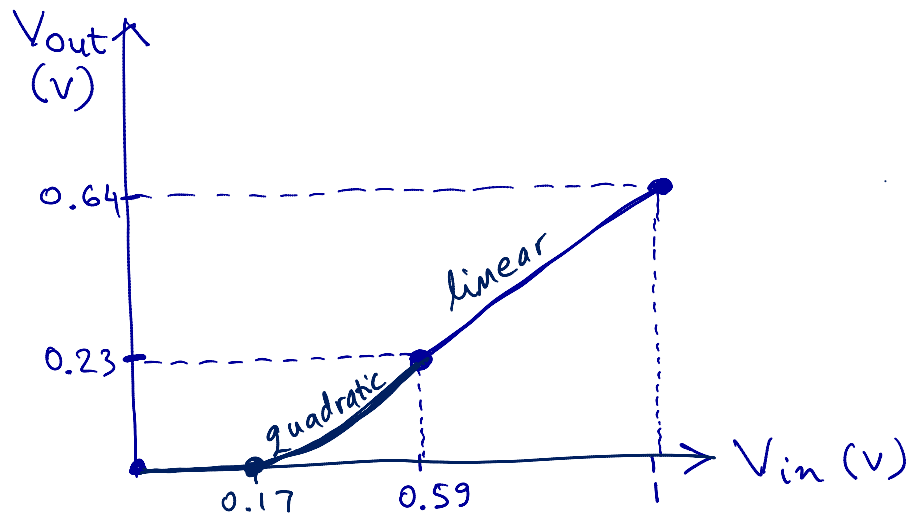

 PROBLEM 3: Delay and Power (20 pts)

Consider the following circuit, with NAND, NOR gates and two NMOS transistors.



(a) What logic function is implemented by this circuit (inputs: A, B, C, D, E; output: F)? (4 pts)


$$F = E \cdot X + \bar{E} \cdot Y$$

$$X = \text{NAND}(A,B)$$

$$Y = \text{NOR}(C,D)$$

$$F = E \cdot \overline{A \cdot B} + \bar{E} \cdot \overline{C + D}$$

 - (b) Assume the NAND and NOR gates are static CMOS gates with device sizes such that NMOS transistors all have $R_{on} = 10\text{ k}\Omega$ and PMOS transistors all have $R_{on} = 12\text{ k}\Omega$. Capacitance: $C_X = C_Y = 0$, $C_F = 40\text{ fF}$, any other capacitance not explicitly drawn is neglected (including capacitance at NAND and NOR gate internal nodes). Suppose now we have input transition from $(A, B, C, D, E) = (0, 1, 1, 0, 1)$ to $(A, B, C, D, E) = (0, 1, 1, 0, 0)$. Assuming ideal step transition at input E, calculate t_{pHL} for this transition at output F. **(6 pts)**



The discharging path goes through \bar{E} -controlled and C-controlled NMOS transistors. So the pull-down resistance is:

$$R_{dn} = R_{on} + R_{on} = 20\text{ k}\Omega$$

Since $C_Y = 0$, the pull-down delay t_{pHL} is given by:

$$t_{pHL} = 0.69R_{dn}C_F = 0.69 \times 20\text{ k}\Omega \times 40\text{ fF} = 552\text{ ps}$$

$t_{pHL} = 552\text{ ps}$

- (c) Assume $C_X = C_Y = 10 \text{ fF}$, $C_F = 40 \text{ fF}$, any other capacitance not explicitly drawn is neglected (including capacitance at NAND and NOR gate internal nodes). Assume the probability of logic 1 for inputs: $p(A = 1) = 0.5$, $p(B = 1) = 0.4$, $p(C = 1) = 0.2$, $p(D = 1) = 0.3$, $p(E = 1) = 0.6$. $f_{clk} = 100 \text{ MHz}$, $V_{DD} = 1\text{V}$, threshold voltage $V_{TN} = 0.2 \text{ V}$, $V_{TP} = -0.2 \text{ V}$. Calculate the average switching power P_{sw} of the circuit (logic inputs A-E have 0 to V_{DD} swing and gates are powered from V_{DD}). **(10 pts)**

We can calculate switching probabilities of nodes X and Y in order to calculate power due to switching of C_X and C_Y .

$$p(X = 0) = p(A = 1)p(B = 1) = 0.5 * 0.4 = 0.2$$

$$p(X = 1) = 1 - 0.2 = 0.8$$

$$\alpha_{X:0 \rightarrow 1} = 0.2 \times 0.8 = 0.16$$

$$p(Y = 1) = p(C = 0)p(D = 0) = 0.8 * 0.7 = 0.56$$

$$p(Y = 0) = 1 - 0.56 = 0.44$$

$$\alpha_{Y:0 \rightarrow 1} = 0.44 \times 0.56 = 0.2464$$

$$P_{sw,X} = \alpha_{X:0 \rightarrow 1} \times f_{clk} \times C_X \times V_{DD}^2 = 0.16 \times 100\text{MHz} \times 10\text{fF} \times (1\text{V})^2 = 0.16\mu\text{W}$$

$$P_{sw,Y} = \alpha_{Y:0 \rightarrow 1} \times f_{clk} \times C_Y \times V_{DD}^2 = 0.2464 \times 100\text{MHz} \times 10\text{fF} \times (1\text{V})^2 = 0.2464\mu\text{W}$$

Now we calculate switching probability of the output node F and the corresponding power.

$$p(F = 1) = p(X = 1)p(E = 1) + p(Y = 1)p(E = 0) = 0.8 * 0.6 + 0.56 * 0.4 = 0.704$$

$$p(F = 0) = 1 - 0.704 = 0.296$$


$$\alpha_{F:0 \rightarrow 1} = 0.296 \times 0.704 = 0.208$$

$$P_{sw,F} = \alpha_{F:0 \rightarrow 1} \times f_{clk} \times C_F \times V_{DD} \times (V_{DD} - V_{TN})$$

$$= 0.208 \times 100\text{MHz} \times 40\text{fF} \times 1\text{V} \times (1\text{V} - 0.2\text{V}) = 0.6656\mu\text{W}$$

$P_{sw,X} = 0.16\mu\text{W}$
$P_{sw,Y} = 0.25\mu\text{W}$
$P_{sw,F} = 0.67\mu\text{W}$

 PROBLEM 4: Gate Sizing of a Multi-Stage Network (10 pts)



Consider such a multi-stage logic shown above. The numbers represent relative input gate capacitance. For example, the inverter with “1” has input capacitance of C_{in} , the inverter with “21” has input capacitance of $21C_{in}$ because it is 21 times as wide. Output is loaded with $60 C_{in}$.

(a) Find the minimum delay from input to output using logical effort. **(4 pts)**

We calculate stage effort f^* that minimizes delay:

$$G = g_{NAND} \times g_{NOR} = \frac{4}{3} \times \frac{5}{3} = \frac{20}{9}, H = \frac{21+60}{1} = 81$$

$$F = GH = 180, \text{ therefore optimal stage effort is } f^* = \sqrt[3]{180} = 5.65$$

Since all stages have equal stage effort at minimum delay,

$$D_{min} = 3f^* + P = 16.95 + 5 = 21.95$$

$D_{min} = 21.95$

(b) Find the size of the NAND and NOR gates x and y (NAND has input capacitance $x C_{in}$ and NOR has input capacitance $y C_{in}$) that minimize the delay from input to output. **(6 pts)**

Now start from the output and work backwards to calculate size of the gates:

$$y = \frac{5}{3} \times \frac{81}{5.65} = 23.9, x = \frac{4}{3} \times \frac{23.9}{5.65} = 5.64$$

$x = 5.64$

$y = 23.9$
