



University of California, Los Angeles
Henry Samueli School of Engineering and Applied Science
Department of Electrical Engineering

D. Marković

Tue, Feb 14, 8:00 – 9:50 am

EE115C: WINTER 2012—MIDTERM

NAME	Last SOLUTION First
SID	

Please write answers in the box provided.

Answers elsewhere will not be graded.

<p><i>You have 110 minutes.</i></p> <p><i>The test is planned so that you roughly spend 2 minutes per point + 10 minutes to check your answers.</i></p> <p><i>Budget your time properly.</i></p> <p><i>If you get stuck, move on...</i></p> <p><i>Good luck!</i></p>

Problem 1 ____/10

Problem 2 ____/10


Problem 3 ____/15

Problem 4 ____/15



Total (50)	
-------------------	--

 Problem 1: MOS Transistor – Regions of Operation (10 pts)

Determine the V_x ranges for different regions of operation to occur. If a region of operation is not possible, demark the case with DNE (does not exist).



  Parameters:
 $V_T = 0.2 \text{ V}$
 $V_{DSAT} = 0.3 \text{ V}$
 $V_x \text{ range: } -1 \text{ V} \leq V_x \leq 1 \text{ V}$




Vmin condition

- $V_{DSAT} = 0.3 \text{ V}$ 1. starts here
- $V_{GT} = -0.3 \text{ V} - V_x$ 2. enters sat @ $V_x = -0.6 \text{ V}$
 ($V_{GT} < V_{DS}$)
- $V_{DS} = 0.5 \text{ V} - V_x$ 3. cuts off @ $V_x = -0.3 \text{ V}$

$V_{GT} < 0 \Rightarrow \text{off}$


Therefore:

 

V_x range
mode of operation

Cutoff	Linear	Saturation	Velocity - Saturation
$-0.3 \text{ V} \leq V_x \leq 1 \text{ V}$	DNE	$-0.6 \text{ V} \leq V_x \leq -0.3 \text{ V}$	$-1 \text{ V} \leq V_x \leq -0.6 \text{ V}$

Problem 2: VTC (10 pts)

 

This figure shows the voltage transfer characteristic (VTC) of a standard CMOS inverter. Note that VTC is approximated with a straight line between $V_{in} = V_{IL}$ and $V_{in} = V_{IH}$.

Parameters:

$$V_{DD} = 1 \text{ V}, V_{OH} = 1 \text{ V}, V_{OL} = 0 \text{ V}, V_M = 0.5 \text{ V}.$$

- (a) Determine V_{IL} and V_{IH} given that the gain around the V_M point is $g = -2$. (2 pts)

$$V_{IL} = V_M - \frac{V_{OH} - V_M}{|g|} = 0.25 \text{ V}$$

$$V_{IH} = V_{IL} + \frac{V_{OH} - V_{OL}}{|g|} = 0.75 \text{ V}$$

$V_{IL} = 0.25 \text{ V}$

$V_{IH} = 0.75 \text{ V}$

- (b) Determine V_{TN} and V_{TP} assuming that the NMOS transistor is strictly off for $V_{GS} < V_{TN}$ and the PMOS transistor is strictly off for $V_{GS} > V_{TP}$. (2 pts)

$$V_{TN} @ V_{IL}$$

$$V_{TP} @ V_{DD} - V_{IH} \quad (\text{negative, PMOS})$$

$V_{TN} = 0.25 \text{ V}$

$V_{TP} = -0.25 \text{ V}$

- (c) Determine the High and Low noise margins of the inverter. (2 pts)


$$NM_H = V_{OH} - V_{IH} = 0.25 \text{ V}$$

$$NM_L = V_{IL} - V_{OL} = 0.25 \text{ V}$$


$NM_H = 0.25 \text{ V}$

$NM_L = 0.25 \text{ V}$

(d) Suppose V_{DD} is reduced to 0.4 V and also assume that $V_{TN} = |V_{TP}| = 0.3$ V. Sketch the new VTC with all relevant voltage points marked on the graph. Also mark where NMOS and PMOS devices are ON. (4 pts)

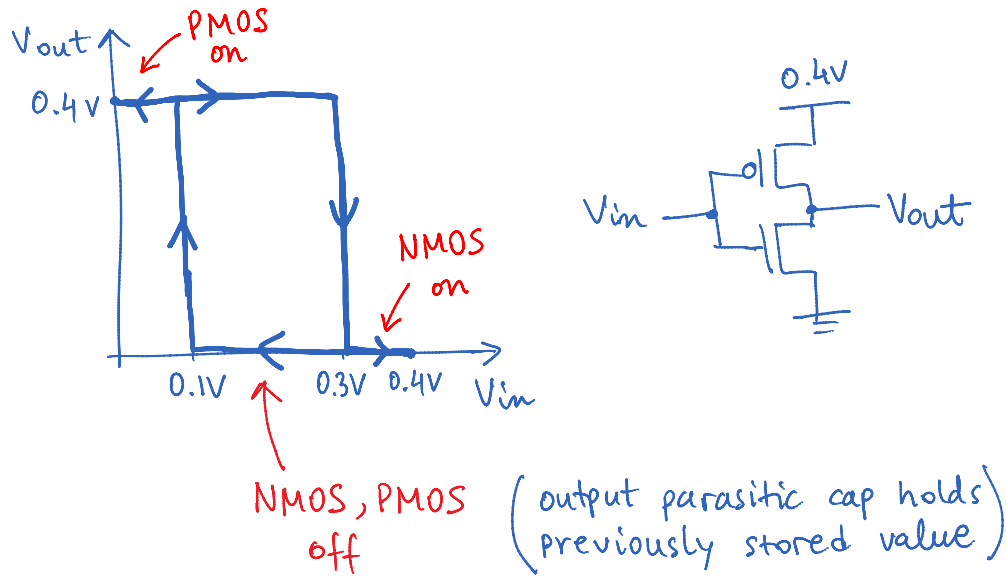

Problem 3: Power and Energy (15 pts)

 

(a) What logic function F is implemented by this circuit (inputs: A , B , and C)? (2 pts)

$F = (A+B) \cdot C$

(b) Assume the probability of logic 1 for inputs: $p(A = 1) = 0.3$, $p(B = 1) = 0.25$, $p(C = 1) = 0.3$, capacitances $C_Y = 10$ fF, $C_F = 40$ fF, frequency $f = 200$ MHz, $V_{DD} = 1$ V, threshold voltage $V_{TN} = 0.2$ V and $V_{TP} = -0.3$ V. Calculate the average switching power P_{sw} of the circuit (input C is a full swing signal). Calculate all results with 2 digits of precision. (10 pts)

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

$$P(Y=0) = p(A=0) \cdot p(B=0) = (1-0.3) \cdot (1-0.25) = 0.53$$

$$P(Y=1) = 1 - P(Y=0) = 0.47$$

$$\alpha_{Y:0 \rightarrow 1} = P(Y=0) \cdot P(Y=1) = 0.25$$

$$P_{sw,Y} = \alpha_{Y:0 \rightarrow 1} \cdot f \cdot C_Y \cdot V_{DD}^2 = 0.5 \mu W$$

$p(Y = 1) = 0.47$
$\alpha_{Y:0 \rightarrow 1} = 0.25$

$P_{sw,Y} = 0.50 \mu W$

Y	C	F	Value
0	0	0	$\rightarrow V_{TP1} (0^*)$
0	1	0	$\rightarrow 0$
1	0	0	$\rightarrow V_{TP1} (0^*)$
1	1	1	$\rightarrow V_{DD} - V_{TN}$

$$P(F=1) = P(Y=1) \cdot P(C=1) = 0.14$$

$$\alpha_{F:0 \rightarrow 1} = P(F=1) \cdot P(F=0) = 0.12$$

$$P(F = V_{TP1}) = 0.7$$

$$P(F = 0) = 0.16$$

$$\alpha_{0^* \rightarrow 1} = 0.7 \cdot 0.14 = 0.10$$

$$\alpha_{0 \rightarrow 1} = 0.16 \cdot 0.14 = 0.02$$

$$P_{sw,F} = \alpha_{F:0 \rightarrow 1} \cdot f \cdot C_F \cdot V_{DD} \cdot V_{swing}$$

$$V_{swing} \begin{cases} 0 \rightarrow V_{DD} - V_{TN} : 0.13 \mu W \\ V_{TP1} \rightarrow V_{DD} - V_{TN} : 0.4 \mu W \end{cases}$$

$p(F = 1) = 0.14$
$\alpha_{F:0 \rightarrow 1} = 0.12 \begin{pmatrix} 0.10 \\ 0.02 \end{pmatrix}$

$P_{sw,F} = 0.53 \mu W$

(c) Calculate the heat energy dissipation for one cycle (charge + discharge) associated with C_Y and C_F . (3 pts)

$$E_Y = C_Y \cdot V_{DD}^2 = 10 \text{ fJ}$$

$$E_F = C_F \cdot V_{DD} \cdot (V_{DD} - V_{TN}) = 32 \text{ fJ} \quad (0 \rightarrow 1)$$

$$C_F \cdot V_{DD} \cdot (V_{DD} - V_{TN} - |V_{TP}|) = 20 \text{ fJ} \quad (0^* \rightarrow 1) \quad \text{5x more frequent}$$

Node Y (C_Y)	$E_{\text{heat}} = 10 \text{ fJ}$
Node F (C_F)	$E_{\text{heat}} = 32 \text{ fJ} / 20 \text{ fJ}$


Extra credit: what is the average heat energy dissipation associated with C_F ? (3 pts)

$$\text{Average } E_{\text{heat}} = \frac{5 \cdot 20 \text{ fJ} + 1 \cdot 32 \text{ fJ}}{6} = 22 \text{ fJ}$$

$E_{\text{heat,avg}}(C_F) = 22 \text{ fJ}$

Problem 4: Logical Effort (15 pts)

 
- (a) Draw the schematic of the 3-input NAND gate, and size all the transistors such that the worst-case delay is equal to that of a unit-sized inverter ($W_P:W_N = 2:1$). Find the logical effort of the 3-input NAND gate. (3 pts)



$$g = \frac{5}{3}$$

$g = 5/3$

 - (b) For the logic path from In to Out shown below, find the *path* logical effort, *path* branching effort, *path* electrical effort, and the total *path* effort. What is the optimum effort per stage f_{opt} for minimizing delay? (7 pts)



$$G = 1 \times \frac{4}{3} \times \frac{5}{3} \times 1 \times \frac{5}{3} \times \frac{4}{3} = \frac{400}{81} = 4.94$$

$$B = 1 \times 2 \times 3 \times 1 \times 1 \times 1 = 6$$


$$H = \frac{100}{1} = 100$$

$$F = G \times B \times H = 2963$$

$$f_{opt} = \sqrt[6]{F} = 3.79$$

$G = \frac{400}{81} = 4.94$
$B = 6$
$H = 100$
$F = 2963$
$f_{opt} = 3.79$

 (c) Find scaling factors (x, y, z, w, v) in the path in order to minimize delay (circuit drawing repeated for convenience). (5 pts)



From Out to In:

$$v = \frac{4}{3} \frac{100}{3.79} = 35.2$$

$$w = \frac{5}{3} \frac{35.2}{3.79} = 15.5$$

$$z = 1 \frac{15.5}{3.79} = 4.09$$

$$y = \frac{5}{3} \times 3 \times \frac{4.09}{3.79} = 5.4$$

$$x = \frac{4}{3} \times 2 \times \frac{5.4}{3.79} = 3.79 \quad (= f_{opt})$$

x =	3.8
y =	5.4
z =	4.1
w =	15.5
v =	35.2