

ECE3 Spring 2020

Name _____
Family (Last) Name | Given (First) Name


Final Exam

UID _____

**DO NOT OPEN UNTIL
INSTRUCTED TO DO SO.**

- We will copy some graded exam papers for archival purposes!
- Put your name in the blank on EVERY page.
- Show your setup.
- Circle your answers.
- Add notes to help the graders determine your intentions.

Problem	Value	Score	Problem	Value	Score
1a	1		4	25	
1b	1		5	15	
1c	1		6a	5	
1d	1		6b	5	
1e	4		7a	8	
2	20		7b	8	
3	6		TOTAL	100	

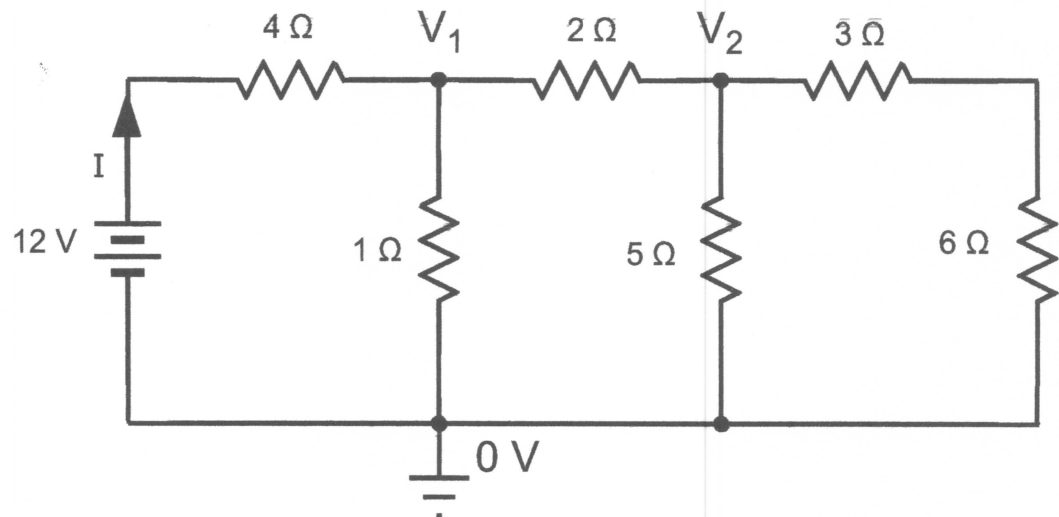

1

•IF YOU ARE PRINTING THE TEST AND WRITING ON IT, USE THE NEXT PAGE FOR ANSWERS.

- Using Node Voltage Analysis, write an Ohm's Law expression (in terms of V_1 and V_2) for the current going through the $4\ \Omega$ resistor.
- Under the same assumption, write an Ohm's Law expression (in terms of V_1 and V_2) for the current through the $1\ \Omega$ resistor.
- Continuing, write an expression (in terms of V_1 and V_2) for the current through the $2\ \Omega$ resistor.
- Now, combine the answers to 1a,b,c into a KCL equation for Node 1.
- Write the KCL equation for Node 2 (in terms of V_1 and V_2).

2

You now have 2 equations in 2 unknowns. Solve them for V_1 and V_2 .

3

Now that you know V_1 , you can compute I .

USE THIS PAGE FOR CALCULATIONS

1a) $V = 12$

$$(V_1 - 12V) = I(4\Omega)$$

$$I = \frac{(V_1 - 12V)}{(4\Omega)}$$

if we assume the current is leaving V_1

$$I = \frac{(12V - V_1)}{4\Omega}$$

if the current is entering V_1

1b) Assuming current is leaving V_1

$$(V_1 - 0V) = I(1\Omega)$$

$$I = \frac{V_1}{1\Omega} = V_1$$

1c) Assuming current is leaving V_1

$$V = 12$$

$$(V_1 - V_2) = I(2\Omega)$$

$$I = \frac{(V_1 - V_2)}{2\Omega}$$

1d) KCL: currents in a node add up to zero
(assume all are exiting)

$$\frac{V_1 - 12}{4} + V_1 + \frac{V_1 - V_2}{2} = 0$$

1e) Node 2: All currents leaving

$$\frac{V_2 - V_1}{2} + \frac{V_2 - 0}{5} + \frac{V_2 - 0}{3+6} = 0$$

$$\frac{V_2 - V_1}{2} + \frac{V_2}{5} + \frac{V_2}{9} = 0$$

USE THIS PAGE FOR CALCULATIONS

2) two equations

$$\frac{V_1 - 12}{4} + V_1 + \frac{V_1 - V_2}{2} = 0 \rightarrow V_1 - 12 + 4V_1 + 2V_1 - 2V_2 = 0$$

$$7V_1 - 2V_2 = 12$$

$$\frac{V_2 - V_1}{2} + \frac{V_2}{5} + \frac{V_2}{9} = 0 \rightarrow 45V_2 - 45V_1 + 18V_2 + 10V_2 = 0$$

$$-45V_1 + 73V_2 = 0$$

$$45V_1 = 73V_2$$

$$V_1 = \frac{73}{45} V_2$$

$$V_1 = \frac{73}{45} (1.28 \text{ V})$$

$$7\left(\frac{73}{45} V_2\right) - 2V_2 = 12$$

$$\frac{511}{45} V_2 - \frac{90}{45} V_2 = 12$$

$$\frac{421}{45} V_2 = 12$$


$$V_2 = 1.28 \text{ V}$$

$$\boxed{\begin{array}{l} V_1 = 2.08 \text{ V} \\ V_2 = 1.28 \text{ V} \end{array}}$$

3) $I =$ current across 4Ω resistor entering the node V_1

$$I = \frac{(12 \text{ V} - 2.08 \text{ V})}{4 \Omega} = \boxed{2.48 \text{ A}}$$

4

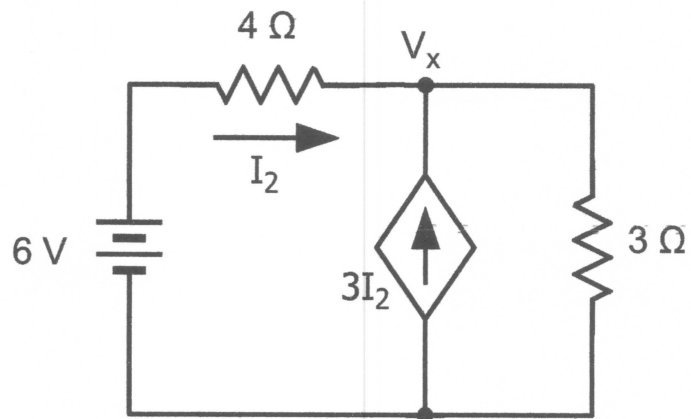Find V_x .

node voltage analysis V_x

~~~~~

$$\frac{(V_x - 6V)}{4\Omega} - 3I_2 + \frac{V_x - 0}{3\Omega} = 0$$

$$I_2 = \frac{(6V - V_x)}{4}$$

$$3V_x - 18 - 36I_2 + 4V_x = 0$$

$$7V_x - 18 - 36I_2 = 0$$

$$7V_x - 18 - 36\left(\frac{6 - V_x}{4}\right) = 0$$

$$7V_x - 18 - 54 + 9V_x = 0$$

$$16V_x = 72$$

$$\boxed{V_x = 4.5V}$$

5

Find  $V_o$ .

BY KCL


$$\frac{V_n - V_o}{4.7 \text{ k}\Omega} - 1 \text{ mA} = 0$$

$$\text{CONSTRAINTS: } V_n = 0$$

$$\frac{-V_o}{4.7 \text{ k}\Omega} - 1 \text{ mA} = 0$$

$$\begin{aligned} -V_o &= 1 \text{ mA} (4.7 \text{ k}\Omega) \\ &= (1 \times 10^{-3} \text{ A}) (4.7 \times 10^3 \Omega) \\ &= 4.7 \text{ V} \end{aligned}$$


$$\boxed{V_o = -4.7 \text{ V}}$$

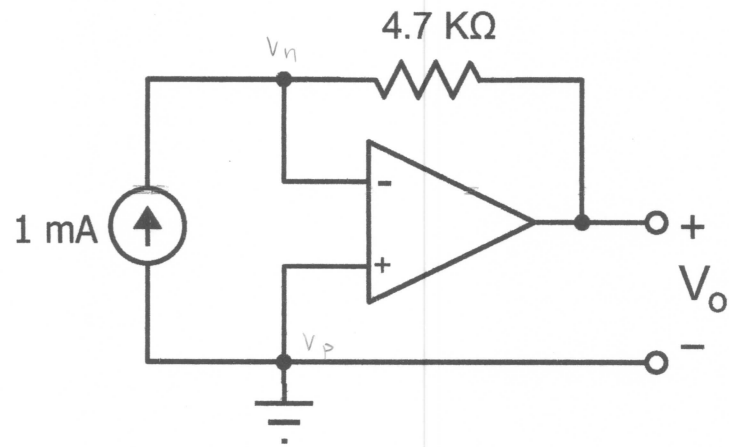

6

The switch has been in position A for a Long Time. At  $t=0$ , it moves instantaneously from A to B. Find the trajectory of the current  $i(t)$ .

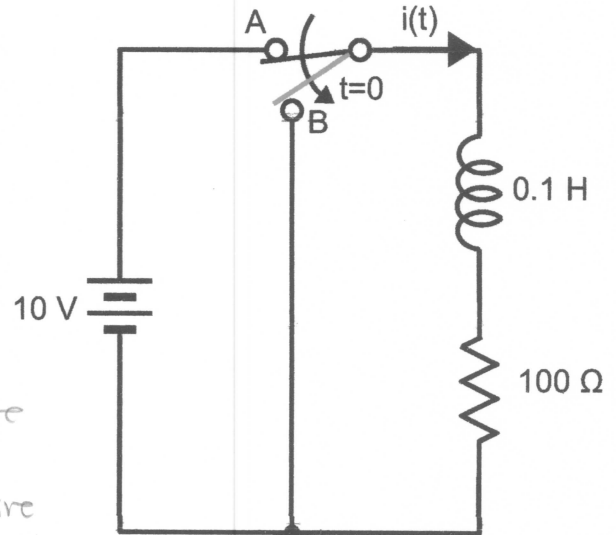- What is the current  $i(0^-)$ ?
- What is the current  $i(0^+)$ ?



- a) Before the switch is flipped + long time series circuit  
After a long time, inductors act like a wire

$$V = IR$$

$$(10V) = I (100 \Omega)$$

$$i(0^-) = 0.10 A$$

- b) immediately after the switch is flipped, the inductor resists change in current, so


$$i(0^+) = i(0^-) = 0.10 A$$

7

In this circuit,  $\omega = 6283 \text{ rad/s}$ .

a. Find  $Z_L$ .

b. Find  $Z_C$ .

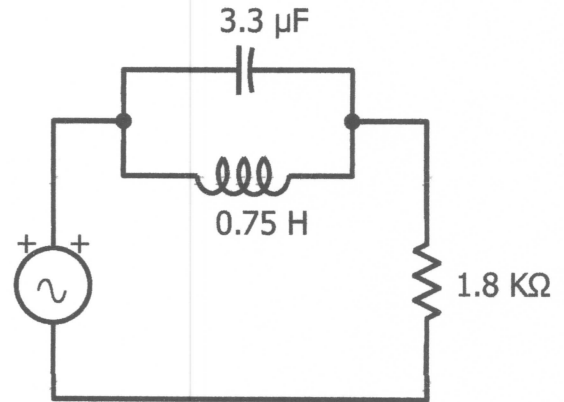

$$a) z_L = j\omega L$$

$$= j(6283 \text{ rad/s})(0.75 \text{ H})$$

$$= j(4712.25)$$

$$b) z_C = \frac{1}{j\omega C}$$

$$= \frac{1}{j(6283 \text{ rad/s})(3.3 \times 10^{-6} \text{ F})}$$

$$= -j(48.23)$$



ECE3 Spring 2020

Name \_\_\_\_\_  
Family (Last) Name | Given (First) Name

Final Exam

UID \_\_\_\_\_

USE THIS PAGE FOR OVERFLOW CALCULATIONS.