

ECE3 Spring 2020

Name

Family (Last) Name

Given (First) Name

Final Exam

UID

**DO NOT OPEN UNTIL  
INSTRUCTED TO DO SO.**

- We will copy some graded exam papers for archival purposes!
- Put your name in the blank on EVERY page.
- Show your setup.
- Circle your answers.
- Add notes to help the graders determine your intentions.

Problem	Value	Score	Problem	Value	Score
1a	1		4	25	
1b	1		5	15	
1c	1		6a	5	
1d	1		6b	5	
1e	4		7a	8	
2	20		7b	8	
3	6		<b>TOTAL</b>	<b>100</b>	

ECE3 Spring 2020


Name \_\_\_\_\_

Family (Last) Name

Given (First) Name

Final Exam

UID \_\_\_\_\_

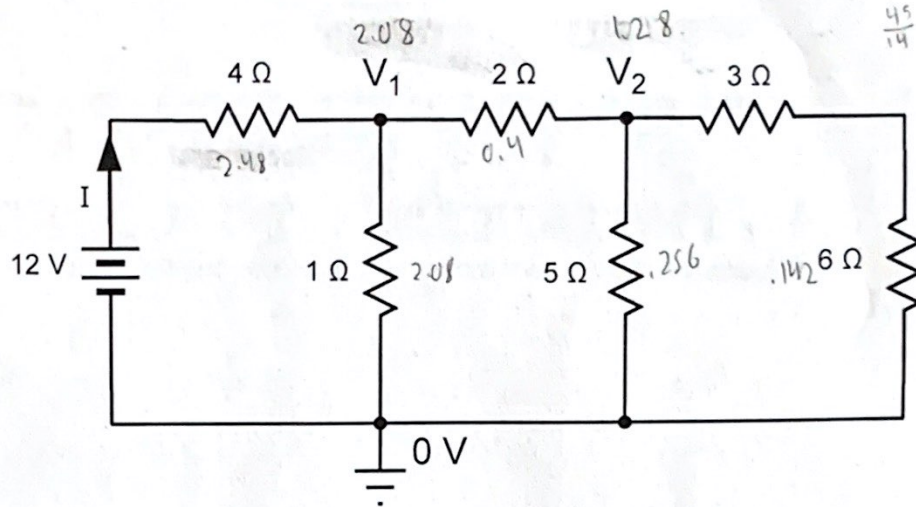

1

•IF YOU ARE PRINTING THE TEST AND WRITING ON IT, USE THE NEXT PAGE FOR ANSWERS.

- Using Node Voltage Analysis, write an Ohm's Law expression (in terms of  $V_1$  and  $V_2$ ) for the current going through the 4 Ω resistor.
- Under the same assumption, write an Ohm's Law expression (in terms of  $V_1$  and  $V_2$ ) for the current through the 1 Ω resistor.
- Continuing, write an expression (in terms of  $V_1$  and  $V_2$ ) for the current through the 2 Ω resistor.
- Now, combine the answers to 1a,b,c into a KCL equation for Node 1.
- Write the KCL equation for Node 2 (in terms of  $V_1$  and  $V_2$ ).

2

You now have 2 equations in 2 unknowns. Solve them for  $V_1$  and  $V_2$ .

3

Now that you know  $V_1$ , you can compute  $I$ .

ECE3 Spring 2020

Name

Family (Last) Name

Given (First) Name

Final Exam

UID

USE THIS PAGE FOR CALCULATIONS

1) a)  $I_{4\Omega} = \frac{12V - V_1}{4\Omega}$

b)  $I_{1\Omega} = \frac{V_1}{1\Omega}$

c)  $I_{2\Omega} = \frac{V_1 - V_2}{2\Omega}$

d)  $\frac{V_1 - 12V}{4\Omega} + \frac{V_1}{1\Omega} + \frac{V_1 - V_2}{2\Omega} = 0$

e)  $\frac{V_2 - V_1}{2\Omega} + \frac{V_2}{5\Omega} + \frac{V_2}{9\Omega} = 0$

2)  $V_1$  node:  $V_1 - 12 + 4V_1 + 2V_1 - 2V_2 = 0 \rightarrow 7V_1 - 2V_2 = 12$

$V_2$  node:  $45V_2 - 45V_1 + 18V_2 + 10V_2 = 0 \rightarrow -45V_1 + 73V_2 = 0$

$V_1 = 2.08 \text{ V}$

$V_2 = 1.28 \text{ V}$

3)  $I = \frac{12V - V_1}{4\Omega} = \frac{12 - 2.08}{4}$

$I = 2.48 \text{ A}$

ECE3 Spring 2020

Name

Family (Last) Name

Given (First) Name

Final Exam

UID

4 Find  $V_x$ .

$$I_2 = \frac{6V - V_x}{4\Omega}$$


$$V_x \text{ node: } -I_2 - 3I_2 + \frac{V_x}{3\Omega} = 0$$

$$-4 \left( \frac{6V - V_x}{4} \right) + \frac{V_x}{3} = 0$$

$$-3V_x - 18 + V_x = 0$$

$$4V_x = 18$$

$$V_x = 4.5V$$

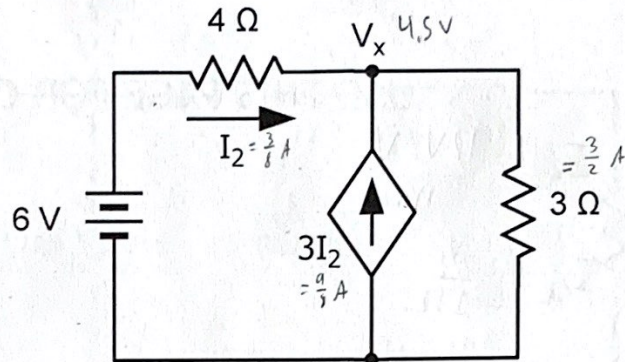

check:

$$\frac{3}{8} + \frac{9}{8} = \frac{12}{8} = \frac{3}{2}A \checkmark$$

ECE3 Spring 2020

Name

Family (Last) Name


Given (First) Name

Final Exam

UID

5

Find  $V_o$ .

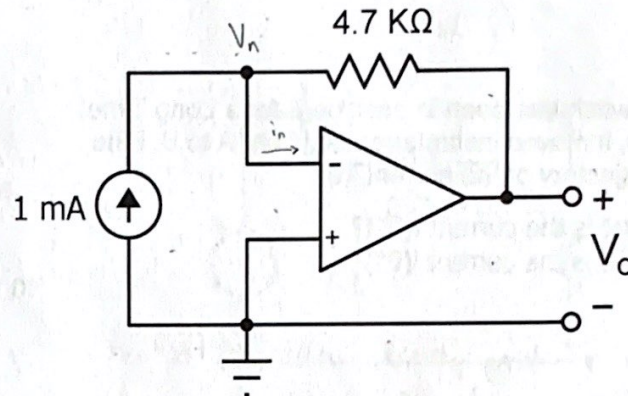

$$-1\text{mA} + i_n + \frac{V_n - V_o}{4.7\text{k}\Omega} = 0$$

Summing point constraints:

$$i_n = i_p = 0$$

$$V_n = V_p = 0$$

$$V_p = 0 \Rightarrow V_n = 0$$

$$\Rightarrow -1\text{mA} + \frac{0 - V_o}{4.7\text{k}\Omega} = 0$$

$$V_o = (-1\text{mA})(4.7\text{k}\Omega)$$

$$V_o = -4.7\text{V}$$

6

The switch has been in position A for a Long Time. At  $t=0$ , it moves instantaneously from A to B. Find the trajectory of the current  $i(t)$ .

- What is the current  $i(0^-)$ ?
- What is the current  $i(0^+)$ ?

a) After a long time, the effective impedance of the inductor is 0

$$\text{So } i(0^-) = \frac{10\text{V}}{100\Omega} = 0.1\text{A} = i(0^-)$$

b) Inductors resist changes in current, so

$$i(0^+) = i(0^-) = 0.1\text{A} = i(0^+)$$

$$\text{KVL: } L \frac{di}{dt} + iR = 0$$

$$\text{Let } i = Ae^{st}$$

$$L(Ase^{st}) + (Ae^{st})R = 0$$


$$Ae^{st}(Ls + R) = 0$$

$$Ls + R = 0$$

$$s = -\frac{R}{L} = -\frac{100}{0.1} = -1000$$

$$A = i(0^+) = 0.1\text{A}$$

$$i(t) = 0.1e^{-1000t}$$

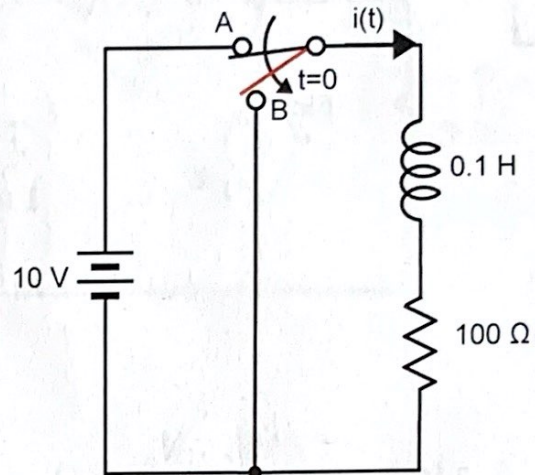

ECE3 Spring 2020

Name

Family (Last) Name

Given (First) Name


Final Exam

UID

7

In this circuit,  $\omega = 6283$  rad/s.

- Find  $Z_L$ .
- Find  $Z_C$ .

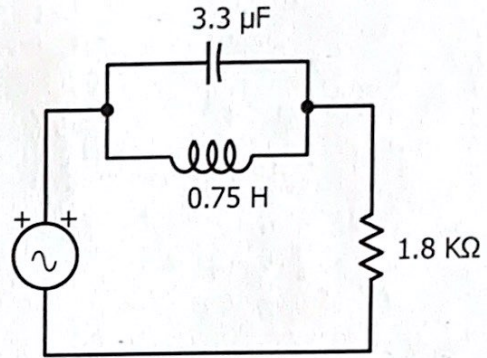

$$a) Z_L = j\omega L = j(6283)(0.75)$$

$$Z_L = 4712.25j \Omega$$

$$b) Z_C = \frac{1}{j\omega C} = -j \frac{1}{(6283)(3.3 \times 10^{-6})} = -48.23j \Omega$$

$$Z_C = -48.23j \Omega$$

$$Z_{tot} = \frac{Z_L Z_C}{Z_L + Z_C} + Z_R$$

$$= \frac{(4712.25j)(-48.23j)}{4712.25j - 48.23j} + 1.8k$$

$$= 1800 - 48.73j \Omega$$