

EE 3 Final Exam w'13 Solutions

1. a) series resistors $\Rightarrow 20\Omega$

20 parallel to $20: 10\Omega$

$$2 \quad 10\Omega + 10\Omega = 20\Omega$$

b) parallel impedances $j\omega L$ and $(R + \frac{1}{j\omega C})$

$$\Rightarrow \frac{j\omega L (R + \frac{1}{j\omega C})}{R + j\omega L + \frac{1}{j\omega C}} = \frac{1 + j10\omega}{10 + j(\omega - 1/\omega)}$$

$$2 \quad \therefore Z_{eq} = 10 + \frac{1 + j10\omega}{10 + j(\omega - 1/\omega)}$$

c) For the second part, $R_{eq} = 20\Omega$

$$1 \quad \therefore V_2 = 20i_2$$

$$\text{since } V_1 = V_2 \frac{N_1}{N_2}, \quad V_1 = \frac{1}{2} 20i_2 = 10i_2$$

$$1 \quad \frac{i_2}{i_1} = \frac{1}{2}; \quad i_2 = \frac{i_1}{2}; \quad V_1 = 10i_1/2 = 5i_1$$

$$1 \quad \text{By KVL} \quad 1 = 20i_1 + 5i_1; \quad i_1 = \frac{1}{25}; \quad V_1 = \frac{1}{5}$$

$$1 \quad \text{Thus } i_2 = \frac{1}{50}; \quad V_2 = \frac{2}{5}$$

The parallel resistors equally divide the current

$$1 \quad i_3 = i_4 = \frac{1}{600}$$

1) ~~voltage~~ is stepped up to reduce resistive losses in transmission lines and then stepped down for safety in local distribution.

2. a) $10\ \Omega$ resistor prevents damaging currents through motor & $1k\Omega$ prevents large currents through base
-  We require $V_{BE} > V_{th}$ for current to flow from C \rightarrow E.
- b) A DC motor would change directions with the current changing directions. But in any case the transistor would only be active in positive phases.
- we want $e^{-T/RC}$ to be ~ 1 for $T = \frac{1}{f_c} = 10^{-3}$
- so $RC \approx 10^{-4}$ would work (value = .9)
- $C = -1\ \mu F$
- c) wavefront spreading, transducer losses, obstructions
- need $\frac{R_f}{R_i} = 10$. Given other resistor values, $R_i = 1k\Omega$, $R_f = 10k\Omega$ would be good
- d) Basis for most digital logic (Computers)
most amplifiers use them
(could name particular classes of consumer products \rightarrow radio, TV, etc.)

3. a) $L = 100^2 = 10^4$

Thus $G = 10^4$

b) Always put the lowest noise figure amplifiers first

| Start with gains $10 + 10$:

| $F = 8 + \frac{8-1}{10} = 8.7$

| Then add gain 100

| $F = 8.7 + \frac{10-1}{100} = 8.7 + .09 = 8.79$

c) Their noise figure for one link is

| $F = 10^4 + \frac{8.79-1}{10^4} = 10^4 + 7.79 \times 10^{-4} = 8.79 \times 10^4$

| For the second link

| $F = 8.79 \times 10^4 + \frac{8.79 \times 10^4 - 1}{10^4} \approx 2 \times 8.79 \times 10^4$

| Thus 10 links are needed for a degradation by a factor of 10.

d) Digital repeaters increase error rate linearly with the number of links, rather than decreasing SNR. This is far more favorable when the error rate per link is low. (We can additionally use multiple modulation formats) Analog systems were used until relatively recently due to cost; Moore's Law has pushed it down.

| If in (c) amplifier is first, $F_1 = 8.79 + \frac{10^4 - 1}{10^4} = 9.79$

| $F_2 = 9.79 + \frac{9.79 - 1}{10^4} = 9.79 + 8.79 ; F_n = 9.79 + (n-1)8.79$
 $n \approx 11$]