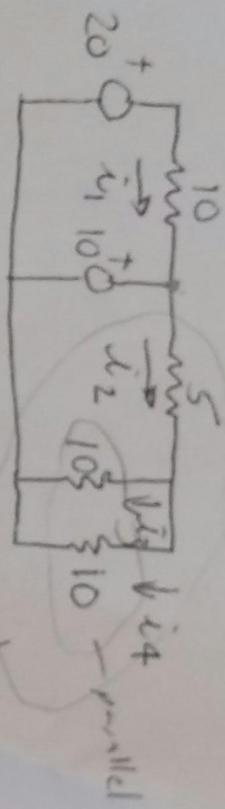


Prof. G. R. P. H. H. e


Instructions: attempt all parts. A sheet of useful formulae is attached. Calculators are permitted.

a) By means of series and parallel resistor relations, reduce the following circuit to a simple form and then determine the currents i_1 and i_2



b) Determine i_3 and i_4 .

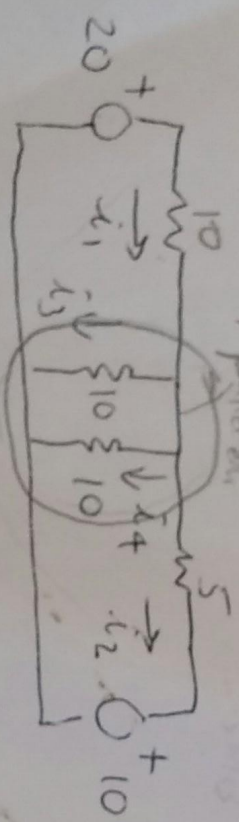c) Reduce the following circuit as far as you can using series + parallel resistor relations




d) Using node or mesh equations, solve for the currents in the reduced circuit, and then use those results to solve for all the currents in the original circuit.

1a) parallel 10Ω resistors

$$\frac{1}{R} = \frac{1}{10} + \frac{1}{10}$$

$$R = 5\Omega$$

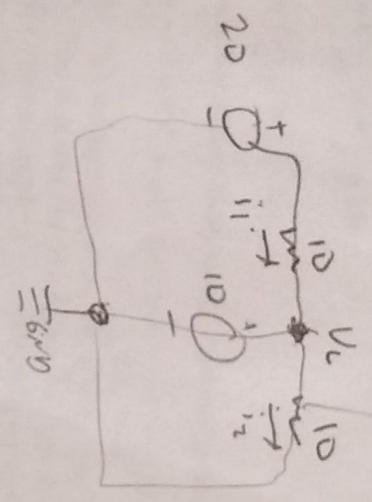Series 5Ω resistors:
 $5\Omega + 5\Omega = 10\Omega = R_{eq}$



$$V_C = 10V$$

$$i_1 = \frac{20-10}{10}$$

$$i_1 = 1A$$

$$i_2 = \frac{V_C - 0}{10} = 1A = i_2$$


b) since $i_3 + i_4$ combined receive the same amount of current as i_2 and the have equivalent resistors $i_3, i_4 = 0.5i_2$

$$i_3 = 0.5A$$

$$i_4 = 0.5A$$

c) parallel 10Ω resistors

$$R = 5\Omega$$

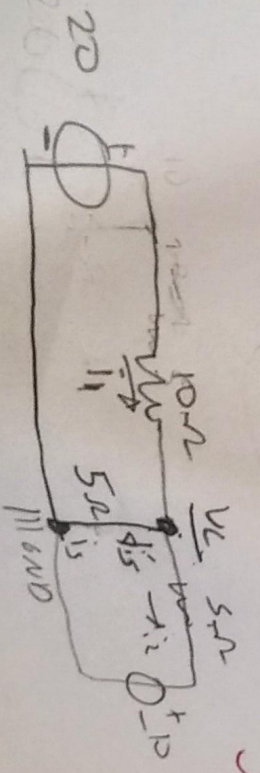

$$i_1 = \frac{20-8}{10} = 1.2A$$

$$i_2 = \frac{8-10}{5} = -\frac{2}{5}A$$

$$i_5 = \frac{8}{5}A$$

for same resistors in B, 10Ω resistors are each half of i_5

$$i_3 = 5i_5 = \frac{4}{5}A$$

$$i_4 = 5i_5 = \frac{4}{5}A$$

d) $i_1 = i_3 + i_4 = 0$

Node eqn: $i_1 - i_3 - i_4 = 0$

$$i_5 = \frac{V_C}{5\Omega}$$

$$i_2 = \frac{V_C - 10}{5\Omega}$$

$$i_1 = \frac{20 - V_C}{10\Omega}$$

$$\frac{20 - V_C}{10\Omega} - \frac{V_C}{5\Omega} - \left(\frac{V_C - 10}{5\Omega}\right) = 0$$

$$2 - \frac{V_C}{10} - \frac{V_C}{5} - \frac{V_C - 10}{5} + 2 = 0$$

$$V_C = 8V$$