

EE 3 F'13 Quiz 2 Solution

2 a) This is an adder circuit

$$v_o = - (10v_1 + 10v_2) = -10(v_1 + v_2)$$

b) This is a series RLC circuit and so

$$v_o = \bar{i} \left(R + j\omega L + \frac{1}{j\omega C} \right)$$

3

$$\bar{i} = \frac{v_o}{R + j\left(\omega L - \frac{1}{\omega C}\right)} = \frac{-10(v_1 + v_2)}{100 + j(10^{-3}\omega - 10^9/\omega)}$$

c) For the circuit to be purely resistive, the imaginary part must go to zero.

2 Thus $10^{-3}\omega_0 - 10^9/\omega_0 = 0$; $\omega_0^2 = 10^{12}$
 $\omega_0 = 10^6$ rad/s.

d) The response due to the sinusoid at ω_0 is proportional to $\frac{1}{100}$

3 The response at ω_1 is proportional to

$$\frac{1}{\sqrt{100^2 + (1.1 \times 10^3 - 1/1.1 \times 10^{-3})^2}} = \frac{1}{215}$$

Thus it is down by a factor of $20 \log \left(\frac{215}{100} \right)$

or 6.6 dB