

**UCLA**  
**Department of Electrical Engineering**  
**EEM16 – Fall 2011**  
**Final Exam**  
**December 7, 2011**  
**(The final contains 7 problems)**

1. Exam is closed book. You are allowed **two 8 ½ x 11” double-sided cheat sheet**.
2. Calculators are allowed.
3. Show the intermediate steps leading to your final solution for each problem.
4. You can use both sides of the sheets to answer questions.

Problem	Points	Your Score	Comments
1	10		
2	10		
3	15		
4a	10		
4b	10		
5	15		
6	15		
7	15		
	Total: 100		

**Problem 1 (10 points)**

State minimization

Find an equivalent finite state machine with a minimum number of states. Show all partitions and the minimal state table.

PS	$x = 0$	$x = 1$
A	E,0	C,0
B	C,0	A,0
C	B,0	G,0
D	G,0	A,0
E	F,1	B,0
F	E,0	D,0
G	D,0	G,0

~~$P_1 = (A, B, C, D, F, G)(E)$~~   $\alpha$

For  $P_1$ :

	Group 1	Group 2
	A B C D F G	E
0	2 1 1 1 2 1	1
1	1 1 1 1 1 1	1

~~$P_2 = (A, F)(B, C, D, G)(E)$~~   $\alpha$

For  $P_2$ :

	Group 1	Group 2	Group 3
	A F	B C D G	E
0	3 3	2 2 2 2	1
1	2 2	1 2 1 2	2

~~$P_3 = (A, F), (B, D), (C, G), (E)$~~   $\alpha$

For P4

	Group 1 A, F	Group 2 B, D	Group 3 C, G	Group 4 E
0	4 4	3 3	2 2	1
1	3 2	1 1	3 3	0

~~P4 = (A), (F), (B, D), (C, G), (E)~~ J

For P5

	Group 1 A	Group 2 F	Group 3 B, D	Group 4 C, G	Group 5 E
0	5	5	4 4	3 3	2
1	4	3	1 1	4 4	3

PJ = P4. Stop.

Denote  $S_1$   $S_2$   $S_3$   $S_4$   $S_5$   
~~A F B, D C, G E~~ ✓

State table.

PS	$x=0$	$x=1$
$S_1$	$S_5, 0$	$S_4, 0$
$S_2$	$S_5, 0$	$S_3, 0$
$S_3$	$S_4, 0$	$S_1, 0$
$S_4$	$S_3, 0$	$S_4, 0$
$S_5$	$S_2, 1$	$S_3, 0$

2.


✓

10 min

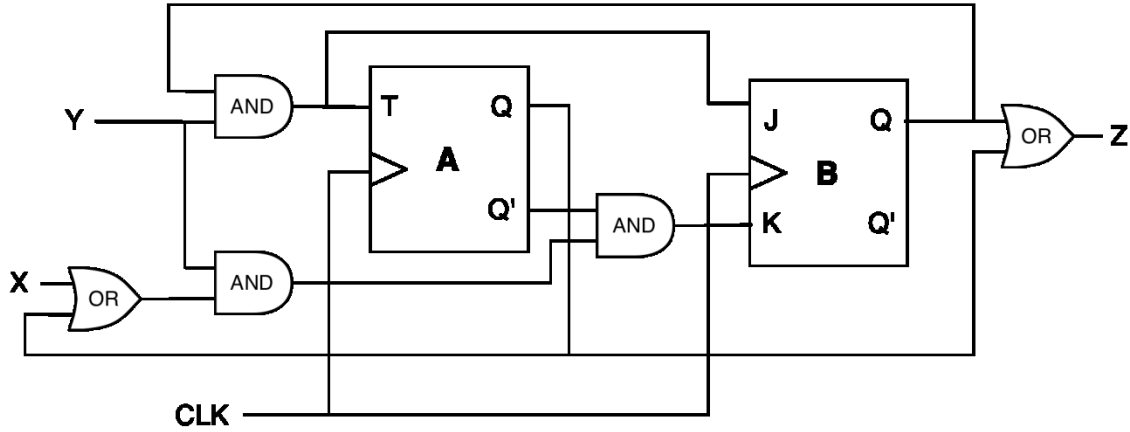**Problem 2 (10 points)**

Analysis of a sequential network


For the following design, draw the state transition diagram.



$T_1 = Q_2 \cdot Y$  ,  $T_2 = Q_1 \cdot Y$      $K = X \cdot Q_1 \cdot A'$      $\begin{matrix} (2/1) \\ \text{---} \end{matrix}$      $\begin{matrix} (3/1) \\ \text{---} \end{matrix}$   
 $J_1 = Q_2 \cdot Y$  ,  $J_2 = Q_1 \cdot Y$      $Z = Q_1 + Q_2$   
 $K_0 = Q_1' \cdot A = Q_1' \cdot (Y \cdot B) = Q_1' \cdot (Y \cdot (X + Q_1)) = X \cdot Y \cdot Q_1'$   
 $Z = Q_2 + Q_1$

PS $Q_2 Q_1$	Input X Y				Input X Y				Z
	00	01	10	11	00	01	10	11	
00	000,0	000,0	000,000	1,0	00	00	00	00	0
01	000,1	000,1	000,1000	1	01	01	01	01	1
10	000,1	110,1	000,1111	1	10	11	10	0,1	1
11	000,1	110,1	000,1110	1	11	10	11	10	1
	T <sub>1</sub> J <sub>2</sub> K <sub>2</sub> , Z				NS ( $Q_2(t+1), Q_1(t+1)$ )				Z

State transition diagram:

 

15 min.



**Problem 3 (15 points)**

Design an 8 to 3 priority encoder with the following priority order (from lowest to highest priority): 3, 5, 2, 1, 0, 6, 7, 4. Use only NAND gates. The encoder should have an enable input signal E and an output signal A that's 0 when no input is active.

E	x <sub>7</sub>	x <sub>6</sub>	x <sub>5</sub>	x <sub>4</sub>	x <sub>3</sub>	x <sub>2</sub>	x <sub>1</sub>	x <sub>0</sub>	y <sub>2</sub>	y <sub>1</sub>	y <sub>0</sub>	A
1	0	0	0	0	1	0	0	0	0	1	1	1
1	0	0	1	0	-	0	0	0	1	0	1	1
1	0	0	-	0	-	1	0	0	0	1	0	1
1	0	0	-	0	-	-	1	0	0	0	1	1
1	0	0	-	0	-	-	-	1	0	0	0	1
1	0	1	-	0	-	-	-	-	1	1	0	1
1	1	-	-	0	-	-	-	-	1	1	1	1
1	-	-	-	1	-	-	-	-	1	0	0	1
1	0	0	0	0	0	0	0	0	0	0	0	0
0	-	-	-	-	-	-	-	-	0	0	0	0

$$\Rightarrow A' = E' + E \cdot (x_7'x_6'x_5'x_4'x_3'x_2'x_1'x_0')$$

$$A' = E' + (x_7'x_6'x_5'x_4'x_3'x_2'x_1'x_0')$$

$$A = [E' + (x_7'x_6'x_5'x_4'x_3'x_2'x_1'x_0')]'$$

$$A = E \cdot (x_7'x_6'x_5'x_4'x_3'x_2'x_1'x_0')$$

$$y_2 = E \left[ (x_7'x_6'x_5'x_4'x_3'x_2'x_1'x_0') + (x_7'x_6'x_4') + (x_7'x_4') + x_4 \right]$$

$$= E \left[ ( \quad ) + x_7'x_6 + x_7 + x_4 \right]$$

$$y_2 = E \left[ (x_5'x_6'x_4') + x_6 + x_7 + x_4 \right]$$

$$y_1 = E \left[ (x_7'x_6'x_5'x_4'x_3'x_2'x_1'x_0') + (x_7'x_6'x_4'x_2'x_0') + (x_7'x_6'x_4') + (x_7'x_4') \right]$$

$$y_1 = E \left[ ( \quad ) + ( \quad ) + (x_7'x_6 + x_7) \cdot x_4' \right]$$


$$y_1 = E \left[ ( \quad ) + ( \quad ) + (x_6 + x_7) \cdot x_4' \right]$$

$$y_1 = E \cdot x_4' \left[ x_7'x_6'x_5'x_3'x_2'x_1'x_0' + x_7'x_6'x_2'x_1'x_0' + x_6 + x_7 \right]$$

$$y_1 = E \cdot x_4' \left[ x_5'x_3'x_2'x_1'x_0' + x_6'x_1'x_0' + x_6 + x_7 \right]$$

$$y_0 = E \left[ x_7'x_6'x_5'x_4'x_3'x_2'x_1'x_0' + x_7'x_6'x_5'x_4'x_2'x_1'x_0' + x_7'x_6'x_4'x_1'x_0' + x_7'x_4' \right]$$
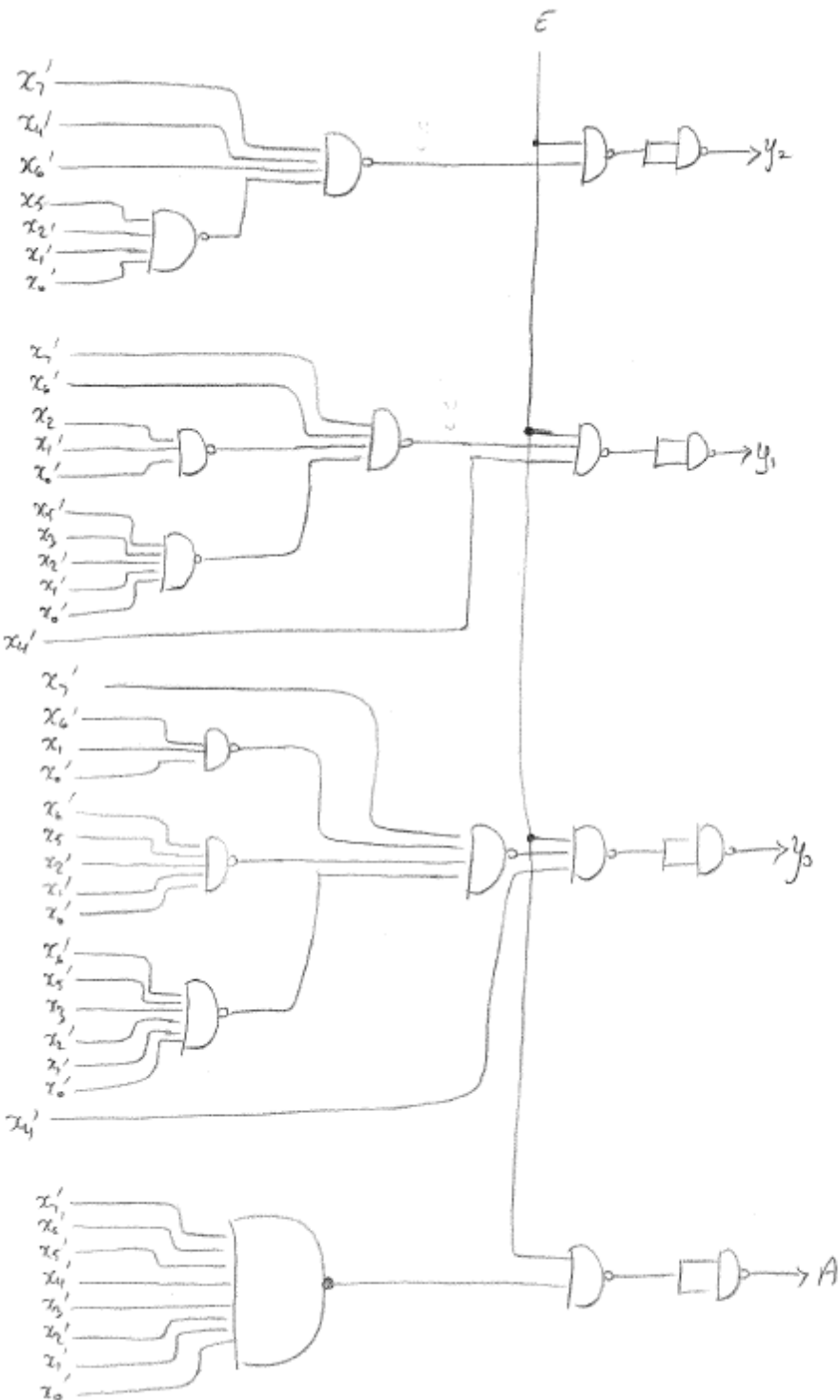
$$y_0 = E \cdot x_4' \left[ x_5'x_3'x_2'x_1'x_0' + x_6'x_5'x_2'x_1'x_0' + x_6'x_1'x_0' + x_7 \right]$$



**Problem 4** (10+10=20 points)

Implement the function  $f(a, b, c, d) = \text{one-set}(1,3,4,9,14,15)$  using

- An eight-input multiplexer;
- A four-input multiplexer and NOR gates (use inputs  $a$  and  $b$  as select inputs to the multiplexer, the NOR gates for functions  $f(0,0, c, d)$ ,  $f(0,1, c, d)$ ,  $f(1,0, c, d)$  and  $f(1,1, c, d)$ , and connect the outputs of these networks to the corresponding data input of the multiplexer).

**Exercise 9.15**

$f(a, b, c, d) = \text{oneset}(1, 3, 4, 9, 14, 15)$

	$abcd$	$f(a, b, c, d)$
0	0000	0
1	0001	1
2	0010	0
3	0011	1
4	0100	1
5	0101	0
6	0110	0
7	0111	0
8	1000	0
9	1001	1
10	1010	0
11	1011	0
12	1100	0
13	1101	0
14	1110	1
15	1111	1

(a) the implementation using 8-input multiplexer is presented in Figure 9.14. The expression can be manipulated as follows:

$$f(a, b, c, d) = a'b'c'd + a'b'cd + a'bc'd' + ab'c'd + abcd' + abcd$$

$$f(a, b, c, d) = m_0(a, b, c)d + m_1(a, b, c)d + m_2(a, b, c)d' + m_4(a, b, c)d + m_7(a, b, c)(d' + d)$$



 


Figure 9.14: Implementation for Exercise 9.15 (a)

(b) the implementation using 4-input multiplexer is presented in Figure 9.15. The expression for this implementation is:

$$f(a, b, c, d) = m_0(a, b)(c'd + cd) + m_1(a, b)c'd' + m_2(a, b)c'd + m_3(a, b)(cd + cd')$$

$$f(a, b, c, d) = m_0(a, b)d + m_1(a, b)(c + d)' + m_2(a, b)(c + d')' + m_3(a, b)c$$

 


Figure 9.15: Network for Exercise 9.15 (b)

**Problem 5** (15 points)

Design a sequential network described by the following state/output table, using the ‘one flip-flop per state’ approach.

<i>PS</i>	Input	
	$x = 0$	$x = 1$
A	B, a	F, b
B	C, a	A, c
C	D, a	B, b
D	E, b	C, c
E	F, b	D, b
F	A, c	E, c
	<i>NS, z</i>	

**Exercise 8.33** Each state is represented by one flip-flop. Consider that the input of these FFs are represented as  $NA, NB, NC, ND, NE$ , and  $NF$  respectively. The switching expressions for these variables are:

$$NA = Fx' + Bx$$

$$NB = Ax' + Cx$$

$$NC = Bx' + Cx$$

$$ND = Cx' + Ex$$

$$NE = Dx' + Fx$$

$$NF = Ex' + Ax$$

For the following output encoding

	$z_1z_0$
<i>a</i>	00
<i>b</i>	01
<i>c</i>	10

the switching expressions for the output are:

$$z_0 = Dx' + Ax + Cx + E$$

$$z_1 = Bx + Dx + F$$

The network that corresponds to these expressions is shown in Figure 8.38.

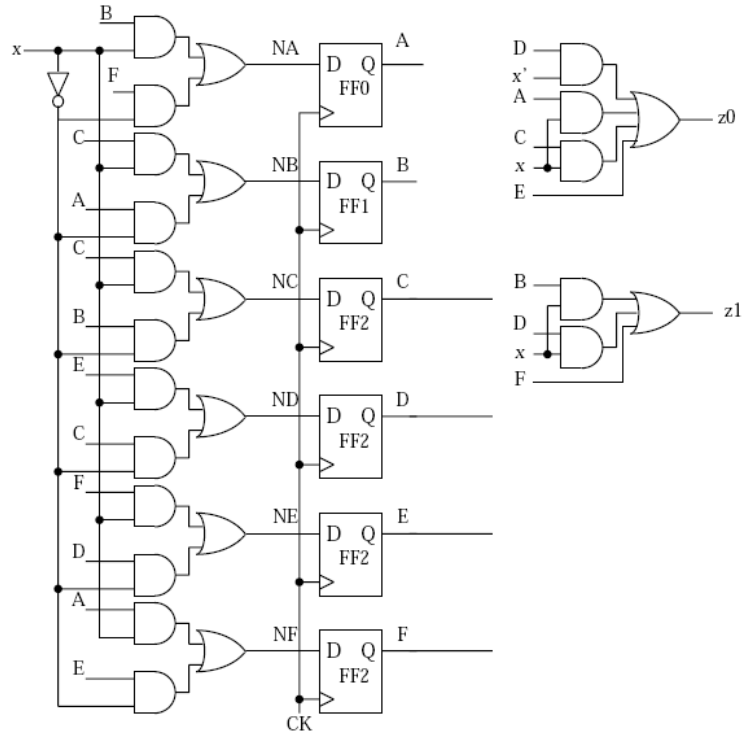


Figure 8.38: Network for Exercise 8.33

**Problem 6 (15 points)**

Design a one-digit decimal adder in BCD code. Use four-bit binary adder modules and NAND gates.

**Exercise 10.4** BCD Addition

When we add two BCD digits (0..9), considering a carry-in bit, the range of values obtained is from 0 to 19. The output consists of a carry out and a digit coded in BCD also.

$$s = (a + b + C_{IN}) \bmod 10$$

$$C_{OUT} = \begin{cases} 1 & \text{if } (a + b + C_{IN}) \geq 10 \\ 0 & \text{if otherwise} \end{cases}$$

where  $s$ ,  $a$  and  $b$  are BCD digits.

When the integers  $a$  and  $b$  are applied to the inputs of the binary adder, the output is:

$$z = (a + b + C_{IN}) \bmod 2^4$$

$$C_0 = \begin{cases} 1 & \text{if } (a + b + C_{IN}) \geq 2^4 \\ 0 & \text{if otherwise} \end{cases}$$

So, looking at the binary adder output and comparing to the expected output for the BCD adder, we must consider three cases:

(i)  $C_0 = 0$  and  $z < 10$ : the output of the binary adder does not need correction

(ii)  $10 \leq z \leq 15$  and  $C_0 = 0$ : in this case we convert the sum as follows:

$$s = z \bmod 10 = (z - 10) = (z + 6) \bmod 16$$

As the operation is done with 4 bits, adding 6 is equivalent to subtracting 10.

$$C_{OUT} = 1$$

(iii)  $C_0 = 1$ : in this case  $z = (A + B + C_{in}) - 16$  and we want  $s = (A + B + C_{in}) \bmod 10$ . For this range of values we have  $(A + B + C_{in}) \bmod 10 = (A + B + C_{in}) - 10$ , so we make:

$$s = z + 6$$

$$C_{OUT} = 1$$

Therefore, to obtain the BCD adder, the following operations must be performed to the binary adder output ( $z$ ):

$$s = \begin{cases} z & \text{if } z \leq 9 \text{ and } C_0 = 0 \\ (z + 6) \bmod 16 & \text{if } 10 \leq z \leq 15 \text{ or } C_0 = 1 \end{cases}$$

$$C_{OUT} = \begin{cases} 0 & \text{if } z \leq 9 \text{ and } C_0 = 0 \\ 1 & \text{if } z \geq 10 \text{ or } C_0 = 1 \end{cases}$$

The condition  $z \geq 10$  or  $C_0 = 1$  is described by the switching expression:

$$w = (z_1 z_3 + z_2 z_3 + C_0)$$

The circuit is shown in Figure 10.2.

 


Figure 10.2: BCD adder (Exercise 10.4)

**Problem 7 (15 points)**

Implement a sequential (bit-serial) network for converting an  $n$ -bit representation of an integer from binary code to Gray code. Use the fact that  $g_i = b_i \oplus b_{i+1}$ , where  $b_i$  is the  $i$ th bit of the binary representation and  $g_i$  is the corresponding bit of the Gray code.

**Exercise 8.10:**

To implement a sequential network that performs a Binary-to-Gray code conversion we use the given equation:

$$g_i = b_i \oplus b_{i+1}, i = 1, \dots, n - 1$$

$$g_n = b_n$$

Thus, the conversion is done from left to right, storing a new binary-code bit in each clock cycle. Initially the internal variable is 0 ( $b_{i+1} = 0$ ).

The sequential network is shown in Figure 8.11.

 


Figure 8.11: Binary-to-Gray converter

