

**Problem 1** (10 points)

Reduce the following expression using Boolean algebra postulates and theorems. The simplified expression should have the minimum number of gates. Show the intermediate steps.


$$\begin{aligned}
 f(a, b, c, d) &= \overline{(acd)(\bar{a} + \bar{b} + \bar{d})(\bar{a}d + c) + \bar{a}b(\bar{a} + \bar{b}c + \bar{b}c)} \\
 &= \left( \overline{(acd)}' + \overline{(a' + b'd)'} + \overline{(bd)' + c}' + \overline{(a' + b)'} \right) (a' + b'c + b'c') \\
 &= acd + abd + (ad)'c' + (a' + b)(a' + b'c + b'c') \\
 &= acd + abd + ac'd + (a' + a'b'c + a'b'c' + a'b + b'c + b'c') \\
 &= ad(\underline{c+c'}) + abd + a'(\underline{1+b}) + a'b'(\underline{c+c'}) \\
 &= ad + abd + a' + a'b' \\
 &= ad(\underline{1+b}) + a'(\underline{1+b'}) \\
 &= ad + a' \\
 &= \textcircled{6}
 \end{aligned}$$

**Problem 2** (15 points)


Consider the following function

$$f(a, b, c, d) = \Sigma m(1, 7, 9, 11, 13, 15).$$

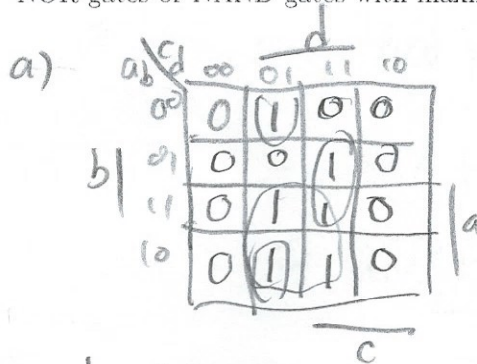- (a) (8 points) Use K-maps to minimize **both** the sum of products and products of sums forms. Write the Boolean expressions.
- (b) (7 points) Implement the function using the minimal number of gates. You can use either NOR gates or NAND gates with maximum number of four inputs per gate.




$$ad + b'c'd + bcd$$

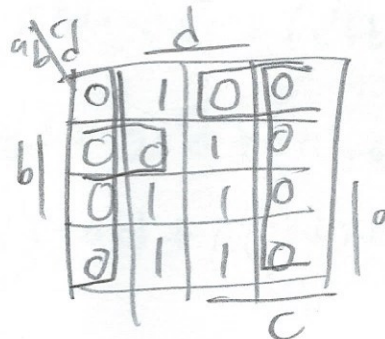


$$(d)(a+b+c')(a+b'+c)$$

8

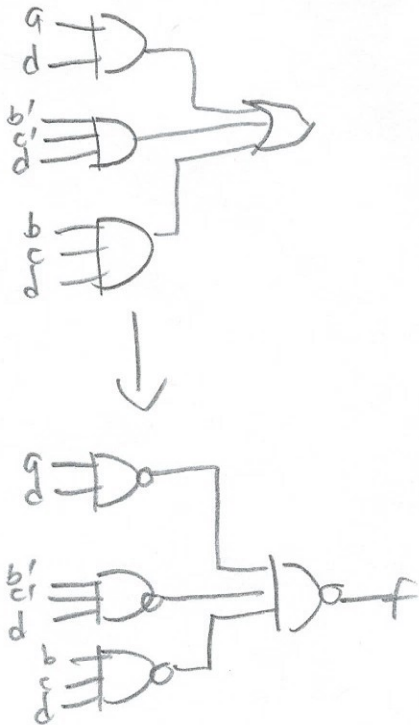

or

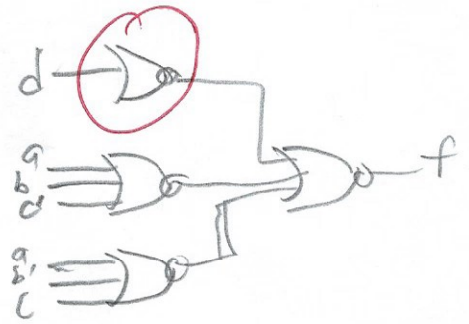


6

19.5


**Problem 3** (20 points)

Consider the following function shown below.

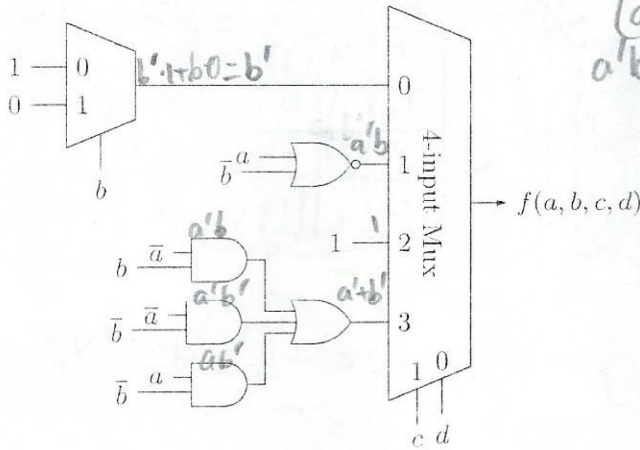- (a) (3 points) Write the switching expression for the multiplexer circuit below. The multiplexers have binary select inputs. The expression need not be simplified.
- (b) (3 points) Determine the prime implicants and the essential prime implicants for this expression.
- (c) (8 points) Find the minimal sum-of-product for the switching expression  $f$ .
- (d) (6 points) Does this function have a unique minimal sum-of-products? If not, list any other minimal sum-of-products expressions.



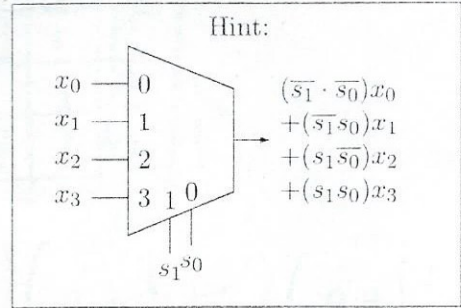$(a+b) = a'b$   
 $a'b + a'b + ab' + a'b' = a'b + ab' = a + b'$



a)

$f(a, b, c, d) = c'd'(b') + c'd(a'b) + cd'(1) + cd(a'+b')$   
 $= b'c'd' + a'b'cd + cd' + a'cd + b'cd$

b)

		d			
	a <b>b</b>	00	01	11	10
b	00	1	0	1	1
	01	0	1	1	1
	11	0	0	0	1
	10	1	0	1	1
		c			

EPI:  $a'bd, cd', b'c, b'd'$   
 PI:  $a'bd, cd', b'c, b'd', \bar{a}c, 1, 0, 1, 0$


c)  $f = a'bd + cd' + b'c + b'd'$

d) ~~Yes~~, since all PIs are EPIs

10
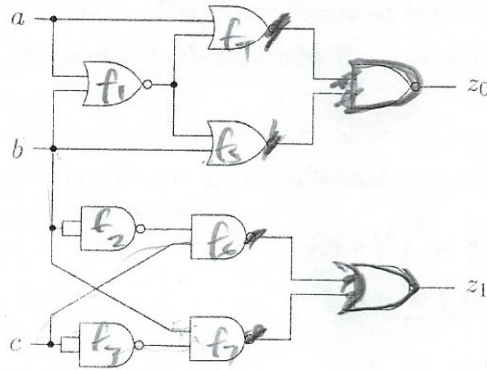
## Problem 4 (10 points)

Analyze the NAND-NOR network shown in the figure below. Obtain switching expressions for the outputs  $z_0$  and  $z_1$ .



$$f_1 = (a + b)' = a'b'$$

$$f_2 = (bb)' = b'$$

$$f_3 = (cc)' = c'$$

$$f_4 = a + f_1 = a + a'b'$$

$$f_5 = b + f_1 = b + a'b'$$

$$f_6 = f_2 c = b'c$$

$$f_7 = b f_3 = bc'$$

$$z_0 = f_4 f_5 = (a + a'b')(b + a'b')$$

$$= ab + 0 + 0 + a'b'$$

$$= \underline{ab} + a'b' \quad (\text{XNOR}) \\ = (a \oplus b)'$$

$$z_1 = f_6 + f_7 = \underline{b'c} + bc'$$

$$(\text{XOR}) \\ (b \oplus c)$$

**Problem 5** (15 points)


Design a combinational circuit that converts a 3-bit sign-and-magnitude number,  $a$ , into a 3-bit one's complement number,  $b$ . You are allowed to use any combination of the following blocks:

- Decoders: 1 → 2 and 2 → 4 decoders
- Encoders: 2 → 1 and 4 → 2 encoders
- Logic gates: Use either OR gates or AND gates, but not both

Every block or wire must be clearly labeled.

Decimal	Sign-Magnitude $a_2 a_1 a_0$	One's Complement $b_2 b_1 b_0$
-3	111	100
-2	110	101
-1	101	110
-0	100	111
0	000	000
1	001	001
2	010	010
3	011	011

$a_2 a_1 a_0$	$b_2 b_1 b_0$
0 0 0	0 0 0
0 0 1	0 0 1
0 1 0	0 1 0
0 1 1	0 1 1
1 0 0	1 1 1
1 0 1	1 1 0
1 1 0	1 0 1
1 1 1	1 0 0

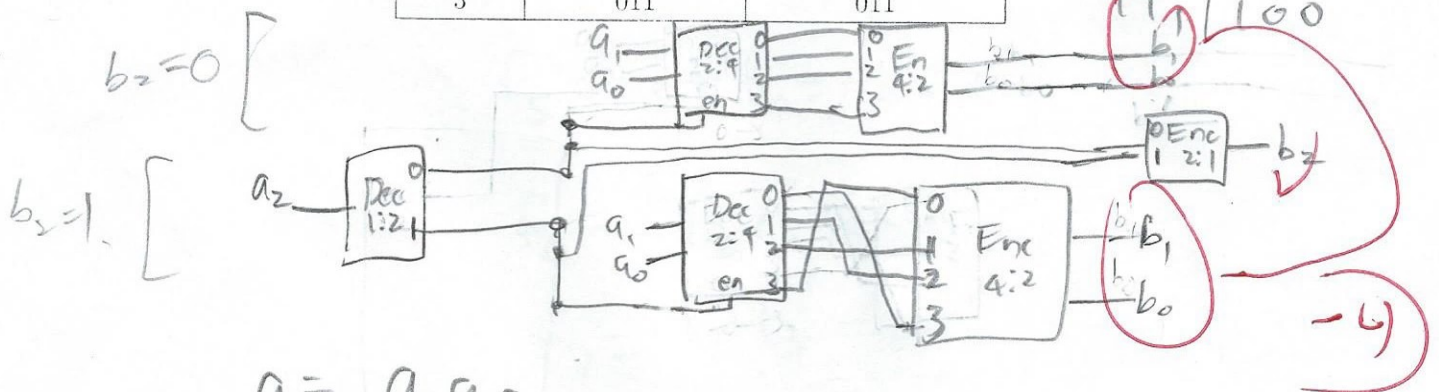

0000 00 11  
 1111 11 00 +1  
 1111 11 01

**Problem 6** (15 points)

Compute  $z = (a - b) + (c - d)$  in 2's complement.

- (a) (4 points) Fill up the table given below.  
 (b) (2 points) How many bits should  $z$  have to represent the correct result?  
 (c) (9 points) Perform calculations on bit-vectors representing  $a, b, c$  and  $d$  (all in 2's complement) and show every step of your work.  $z$  should be given in **both** decimal representation and 2's complement. **If you want**, you can extend the table below.

	Decimal	Sign-Magnitude	2's Complement
a	-13	1 1101	1 0011
b	-10	1 1010	1 0110
c	-6	1 110	1010
d	82	0 1010010	01010010

$\frac{82}{2} = 41r0$   
 $\frac{41}{2} = 20r1$   
 $\frac{20}{2} = 10r0$   
 $\frac{10}{2} = 5r0$   
 $\frac{5}{2} = 2r1$   
 $\frac{2}{2} = 1r0$   
 $\frac{1}{2} = 0r1$

$\frac{13}{2} = 6r1$   
 $\frac{6}{2} = 3r0$   
 $\frac{3}{2} = 1r1$   
 $\frac{1}{2} = 0r1$

$1 \times 2^3 + 0 + 1 \times 2^1 + 0 = 8 + 2 = 10$   
 $16 - 10 = 6 = (110)_2$   
 $32 - 10 = 22 = 1$

$10 \rightarrow 01010 \rightarrow 10101 \rightarrow 1.0110$   
 $16 - 13 = 3 = (0011)_2$

b)

8 bits

c)

	Decimal	2's Comp.	Use range extension
a	-13	11110011	
b	-10	11110110	
-b	10	00001010	$-10 \rightarrow 10$ $00001001 + 1 \Rightarrow 00001010$
a-b	-3	11111101	(a-b): $11110011$ $+ 00001010$ <hr/> $11111101$
c	-6	11111010	
d	82	01010010	
-d	-82	10101110	$-82 \rightarrow 82$ $10101101 + 1 \Rightarrow 10101110$
(c-d)	-88	10101000	(c-d): $11111010$ $+ 10101110$ <hr/> $11010100$
(a-b)+(c-d)	-91	10100010	

3  
 $(a-b) + (c-d)$   
 $11111101$   
 $+ 10101000$   


---

 $10100101$   
 $128$   
 $- 37$   


---

 $91$

Problem 7 (15 points)

Design a combinational network that has 4-bit inputs  $a$  and  $b$ , and a four-bit output  $z$ . All inputs and outputs are given in two's complement representation. The function of the system is

$$z = \max\{a + b, 0\} \pmod 8$$

For example, if  $a = 3$  and  $b = 7$ , then  $z = 2$ . If  $a = 3$  and  $b = -7$ , then  $z = 0$ .

You are allowed to use only magnitude comparators, adders, and/or multiplexers. Every block and wire must be clearly labeled.

Handwritten notes at the top of the page:

- 1010 0111
- 1000 1111
- 1010 0000
- 0110 0111
- 1110
- 1110
- 1110
- 1110
- 1110


Handwritten notes on the left side:

- is
- 0110
- 0001
- 0001
- 0001
- 0001
- 0001
- 0001
- 0001

Handwritten notes on the right side:


- Let  $c = c_3 c_2 c_1 c_0$
- where  $c_3 = 0$
- $c_2 = 0$
- $c_1 = 0$
- $c_0 = 0$

Let  $a+b=d = d_3 d_2 d_1 d_0$

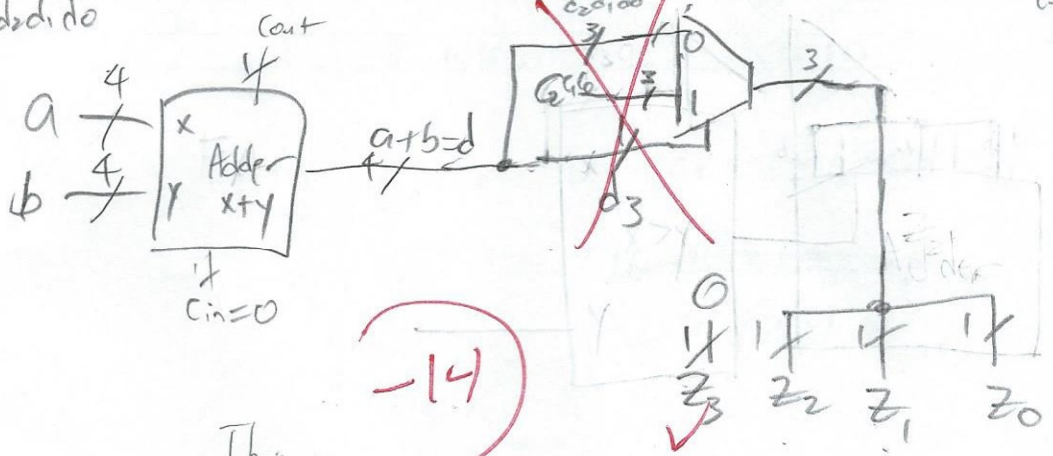

This is assuming no overflow

If  $a, b > 0$

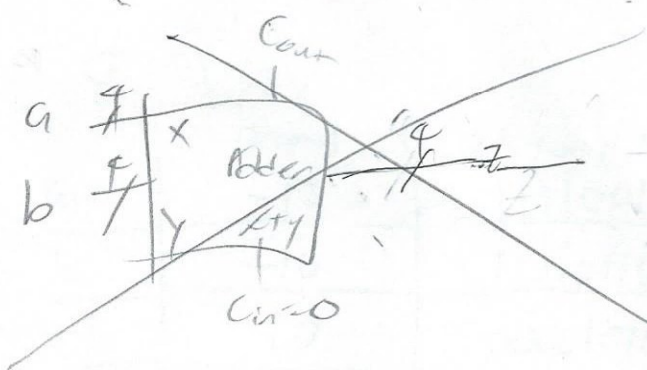

but there could be overflow!