


UCLA  
 Department of Electrical Engineering  
 EEM16 – Fall 2010  
 Quiz 3  
 (This quiz contains 1 problem)

Solution

1. (a) How many 8-input decoders are needed to implement a 32-input decoder using tree decoding?

$$1 + 2^8 + 2^{16} + 2^{24} = \frac{2^{32} - 1}{2^8 - 1}$$

(b) Sketch the implementation.

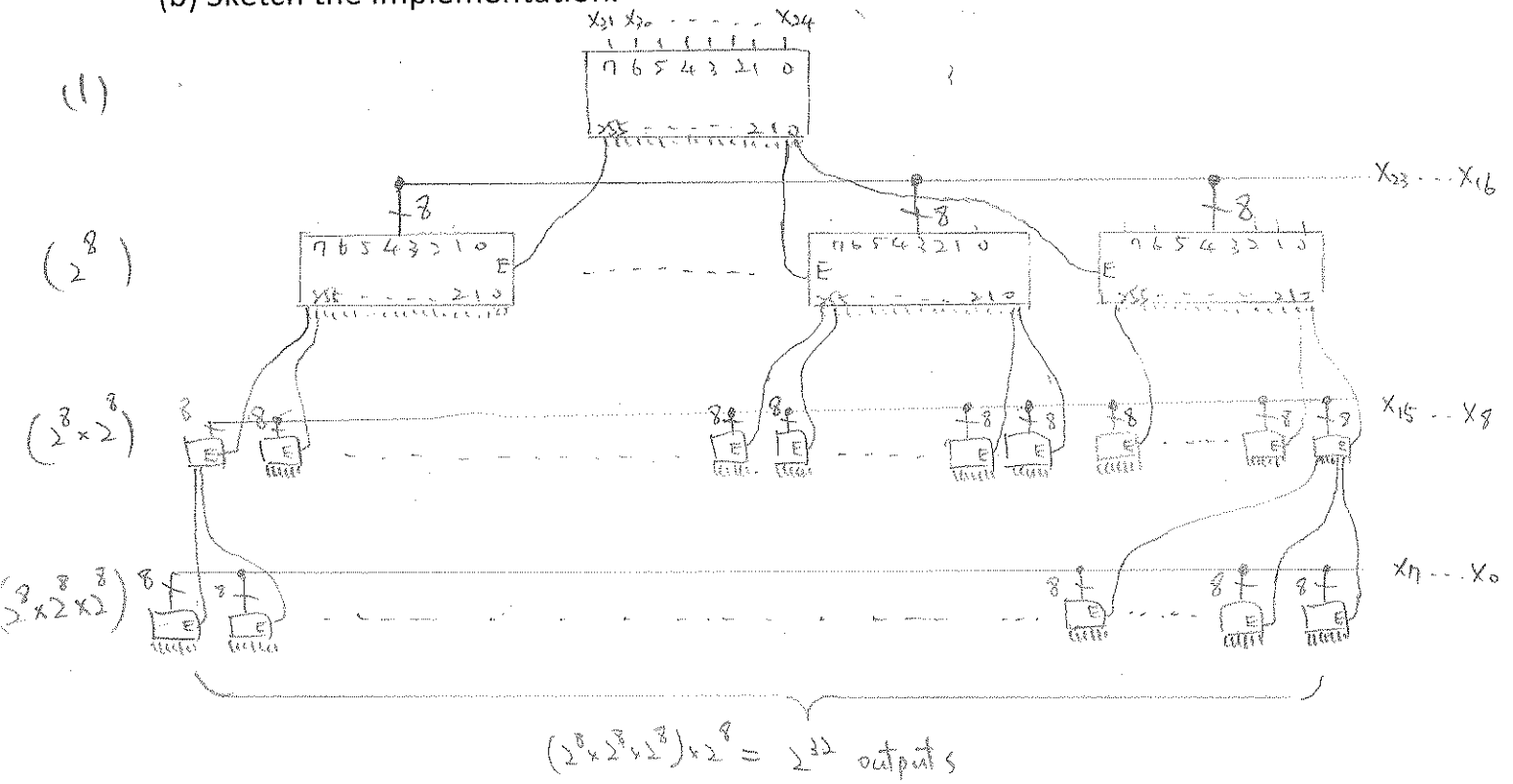

(c) How many levels are necessary?

4 levels

UCLA  
 Department of Electrical Engineering  
 EEM16 – Fall 2010  
**Quiz 3 (15 minutes)**  
 Dec 01, 2010


Solution

**Problem 1**

How many 8-input decoders are needed to implement a 32-input decoder using coincident decoding?

Sketch the implementation.

How many AND gates are needed?

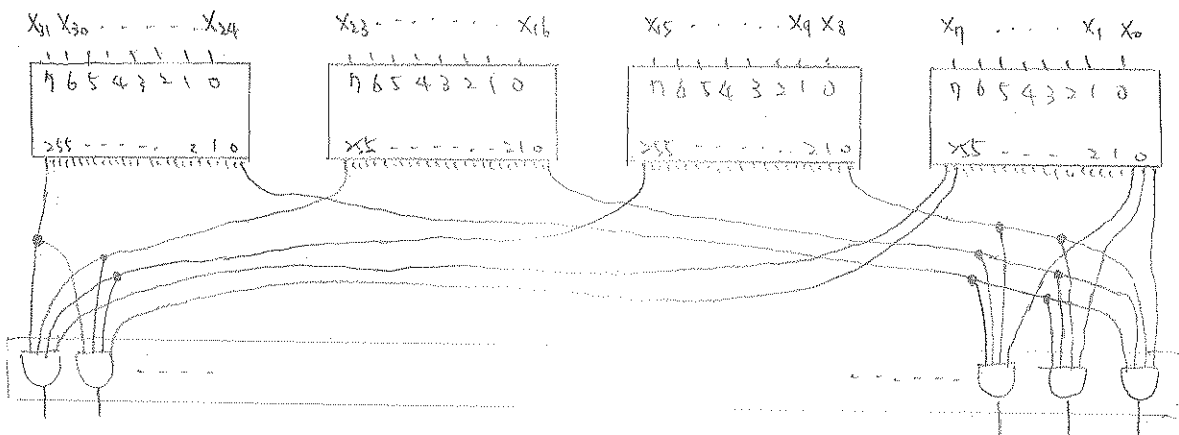

$2^{32} \times$  4-input AND gates

ANS: 4 x 8-input decoders are required!  
 $2^{32} \times$  4-input AND gates