

Midterm Exam

Name (Last, First): *Solution*

Student Id #:

Student to Left:

Student to Right:

Do not start working until instructed to do so.

1. You must answer in the **space provided** for answers after every question. We will ignore answers written anywhere else in the booklet. **All pages in this booklet must be accounted** for otherwise it will not be graded.
2. You are permitted 1 page of notes 8.5x11 (front and back).
3. You may not use any electronic device.

Following table to be filled by course staff only

	Maximum Score	Your Score
Question 1	15	
Question 2	25	
Question 3	25	
Question 4	35	
Question 5 (EC)	+5	
TOTAL	100	

Question #1 (15 pts)

Consider the following Karnaugh Map for the Boolean function, Y. A blank truth table is provided for your convenience.

AB

	"00"	"01"	"11"	"10"
"00"	0	0	1	1
"01"	0	1	0	1
"11"	0	1	0	0
"10"	1	1	X	X

A	B	C	D	Y
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

(a) Circle the prime implicants on the map. (5 pts)

How many prime implicants are there? 5

(b) Write the Boolean (sum-of-product) expression of the essential prime implicants of (b) (if any). (5 pts)

EssentialPrimeImplicants = $C\bar{D} + \bar{A}BD + A\bar{D} + A\bar{B}\bar{C}$

4 essential prime implicants

- ① $C\bar{D}$
- ② $\bar{A}BD$
- ③ $A\bar{D}$
- ④ $A\bar{B}\bar{C}$

(c) Express as a minimal sum of product, $\neg Y$. (5 pts)
 The K-map is provided for your convenience.

		AB			
		"00"	"01"	"11"	"10"
CD	"00"	0	0 ^①	1	1
	"01"	0	1	0 ^③	1
	"11"	0 ^②	1	0	0
	"10"	1	1	X	X ^④

- ① $A + C + D$
- ② $A + B + \bar{D}$
- ③ $\bar{A} + \bar{B} + \bar{D}$
- ④ $\bar{C} + \bar{A}$

~~AAA~~ $(A + C + D)(A + B + \bar{D})(\bar{A} + \bar{B} + \bar{D})(\bar{A} + \bar{C}) \rightarrow Y$ as product of sums

$$\bar{Y} = \overline{(A + C + D)(A + B + \bar{D})(\bar{A} + \bar{B} + \bar{D})(\bar{A} + \bar{C})}$$

$$\bar{Y} = \bar{A}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{D} + ABD + AC$$

Question #2 (25 pts)

(a) Is DeMorgan's theorem still true with more than two variables? If so, prove it in the case of three variables x, y and z. (5 pts) *Yes; Multiple ways to prove this (truth table, Venn diagram, 2 variable DeMorgan's theorem)*

Using De Morgan's theorem with 2 variables: 4 possible cases

① $\overline{x \vee y \vee z}$	② $\overline{x \wedge y \wedge z}$	③ $\overline{(x \wedge y) \vee z}$	④ $\overline{(x \vee y) \wedge z}$
$\overline{(x \vee y)} \wedge \bar{z}$	$\overline{(x \wedge y)} \vee \bar{z}$	$\overline{(x \wedge y)} \wedge \bar{z}$	$\overline{(x \vee y)} \vee \bar{z}$
$\bar{x} \wedge \bar{y} \wedge \bar{z}$	$\bar{x} \vee \bar{y} \vee \bar{z}$	$\bar{x} \vee \bar{y} \wedge \bar{z}$	$\bar{x} \wedge \bar{y} \vee \bar{z}$

- All other combinations of x, y, z work because of the commutative property.

(b) Rewrite the following Boolean equation in (Disjunctive) Normal form. (6 pts)

$$f = \overline{A \oplus B} + \overline{B \oplus C}$$

where \oplus means XOR operation, i.e., $A \oplus B = \overline{A}B + A\overline{B}$

* Note: Fully disjunctive normal form was intended but credit will be given for any valid disjunctive form

Answer: $f = \overline{(\overline{A}B + A\overline{B})} + \overline{(\overline{B}C + B\overline{C})}$

$$= (\overline{A} + B)(A + \overline{B}) + (\overline{B} + C)(B + \overline{C})$$

$$= (\overline{A}A + \overline{A}B + AB + B\overline{B}) + (\overline{B}B + \overline{B}C + BC + C\overline{C})$$

$$= 0 + \overline{A}B + AB + 0 + 0 + \overline{B}C + BC + 0$$

$$= \overline{A}B + AB + \overline{B}C + BC$$

$$= (\overline{A}BC + \overline{A}B\overline{C}) + (ABC + AB\overline{C}) + (A\overline{B}C + A\overline{B}\overline{C}) + (ABC + \overline{A}BC)$$


$$f = \overline{A}BC + \overline{A}B\overline{C} + ABC + AB\overline{C} + A\overline{B}C + \overline{A}BC$$

(c) Simplify f from (b) to a minimum sum-of-products. List which Boolean properties you use at each step of the simplification. Hint: you may use K-map to **verify** your answer. (6 pts)

Answer: $f = (\overline{A}BC + \overline{A}B\overline{C}) + (ABC + AB\overline{C}) + (A\overline{B}C + A\overline{B}\overline{C}) + (ABC + \overline{A}BC) \rightarrow X + X = X$ (Idempotence)

$$= \overline{A}B + AB + \overline{B}C + BC \rightarrow XY + X\overline{Y} = X$$
 (Combining)
$$= \overline{A}B + AB(C + \overline{C}) + (A + \overline{A})\overline{B}C + BC \rightarrow X + \overline{X} = 1$$
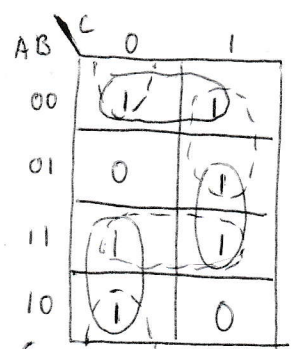
$$= \overline{A}B + \overline{A}BC + \overline{A}B\overline{C} + \overline{A}BC + \overline{A}B\overline{C} + BC \rightarrow$$
 distributive
$$= (\overline{A}B + \overline{A}B\overline{C}) + (ABC + BC) + (A\overline{B}C + A\overline{B}\overline{C}) \rightarrow$$
 commutative
$$= \overline{A}B + BC + A\overline{C} \rightarrow$$
 combining and absorption



$$f = \overline{A}B + BC + A\overline{C} \text{ (could also be)}$$

should be either: $\overline{A}B + BC + A\overline{C}$
or
 $A\overline{C} + AB + \overline{B}C$

Should be 3 terms!

- solution to find alternative SOP is similar

(d) With only 2-input NOR gates, implement f with a minimal number of gates. Draw the gate diagram. (Note: no complemented inputs are given) (8 pts)


Using the minimum SOP from c)

$$f = \bar{A}\bar{B} + BC + A\bar{C}$$

$$= \overline{(A+B)(\bar{B}+\bar{C})(\bar{A}+C)}$$

$$= \overline{[(A+B) + (\bar{B}+\bar{C})] (\bar{A}+C)}$$

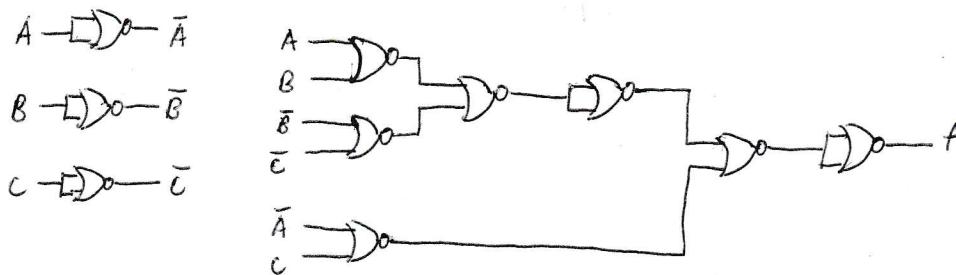
$$= \overline{\overline{[(A+B) + (\bar{B}+\bar{C})]} + (\bar{A}+C)}$$



$3 + 3 + 2 + 2 = 10$ gates required

Alternatively, $f = \bar{A}C + AB + \bar{B}\bar{C}$
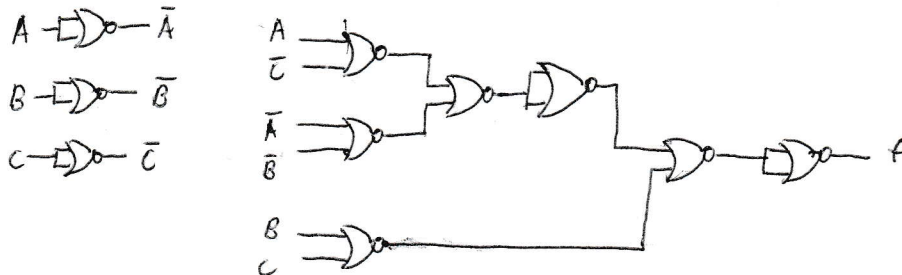
$$= \overline{\overline{[(A+\bar{C}) + (\bar{A}+\bar{B})]} + (B+C)}}$$



Question #3 (25 pts)

The following 12-bit word can be used to represent different numbers depending on the encoding

$$12b'1110_0110_1101 \rightarrow \overset{1's \text{ complement}}{0001_1001_0010} \rightarrow \overset{2's \text{ complement (+1)}}{0001_1001_0011}$$

$$2^8 + 2^7 + 2^4 + 2^1 + 2^0 = 256 + 128 + 16 + 2 + 1$$

(a) If the word is 2's complement, what is the corresponding integer? (4 pts) -403 = 384 + 19

(b) If we convert the word (treated as unsigned) into base-4, what is the represented number? (3 pts) = 403

$$\begin{array}{cccccc} 11 & 10 & 01 & 10 & 11 & 01 \\ \hline 3 & 2 & 1 & 2 & 3 & 1 \\ \hline 321231 \end{array}$$

(c) If we take answer in (b), extending how we define 1's complement for base-2, write the 3's complement of the base-4 number. (4 pts)

012102

(d) What is this word in Hexadecimal? (3 pts) E6D

(e) In base-20 system, assume each digit is now 00, 01, 02, ... 09, 10, 11, ... 19 (each called a "vigint"). For example, 01,19 is 39 in decimal. Using 3 "vigints":

How would one represent a base-10 integer 1246? (4 pts) 3, 2, 6

$$\begin{array}{r} 1246 \\ -1200 \quad \leftarrow 20^2 \times 3 \\ \hline 46 \\ -40 \quad \leftarrow 20^1 \times 2 \\ \hline 6 \quad \leftarrow 20^0 \times 6 \end{array}$$

What's the 20's complement representation of -1246 (i.e. the 20's complement of the 1246)?

(4 pts) 16, 17, 14 \leftarrow 19's complement: 16, 17, 13
+1

Using the first vigint as the sign vigint, what is the most positive value in base-10 integer that can be represented? (3 pts) 3999




$$\begin{aligned} \text{Max value: } & 9, 19, 19 \quad (\text{1st vigint still has range } 0-19) \\ & = 9 \times 400 + 19 \times 20 + 19 \\ & = 3600 + 380 + 19 \\ & = 3999 \end{aligned}$$

(a) Implement a one-bit "half-subtractor" from gates. The carry-out of this subtractor is 1 when the result is -1. The truth table for this is shown below: (8 pts)

a	b	a - b	"carry"
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

2 methods: ① by inspection of the truth table
 ② by K-map

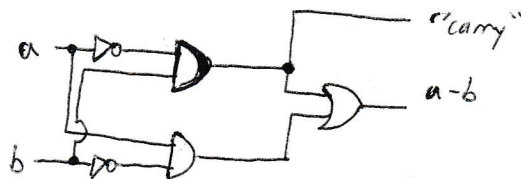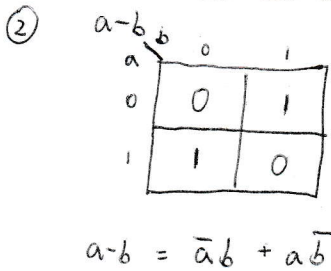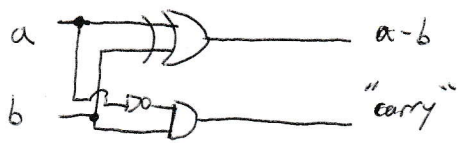
① Notice $a-b$ is True only when a and b are different \rightarrow XOR gate
 "carry" is True only when $a=0$ and $b=1 \rightarrow \bar{a}b$



Either solution is valid

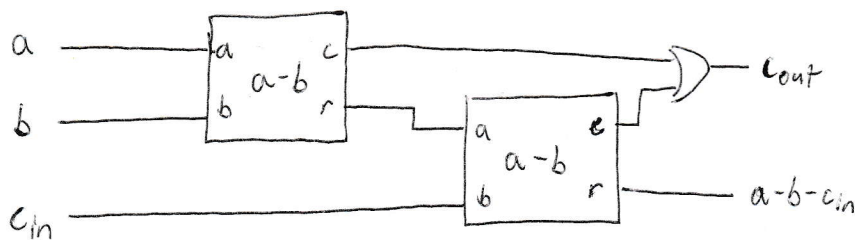(b) Implement a "full-subtractor" from "half-subtractor" blocks. (6 pts)

\hookrightarrow 3 inputs: $a, b, \text{"carry in"}$ 2 outputs: $a-b, \text{"carry out"}$




a	b	c_{in}	$a-b-c_{in}$	c_{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

- Just like a full adder from half adders

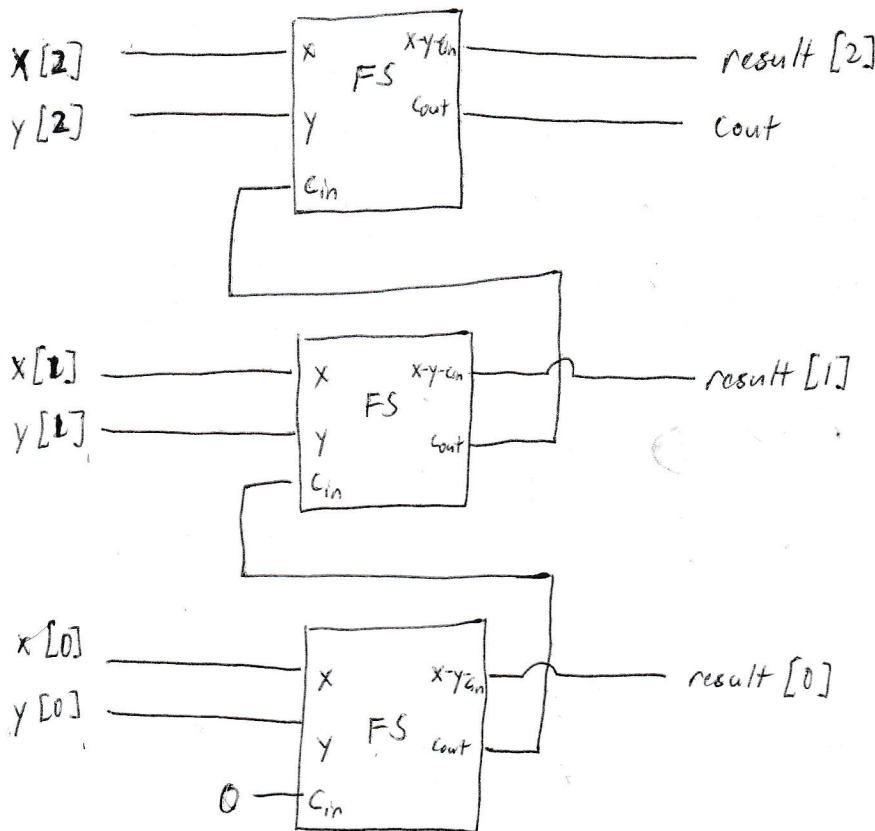(c) Implement a 3-bit "subtractor" from 1-bit "full-subtractor" blocks. (7 pts)

Implementing $X[2:0] - Y[2:0]$ (Index 2 is MSB, Index 0 is LSB)
 = result $[2:0]$ with overflow in cout



* Note: This solution works if inputs are assumed to be unsigned and the outputs are in 2's complement format.


(d) Processors use a block called an ALU (Arithmetic Logic Unit) as part of their processing capability. Here we will implement a very basic ALU with a total of 4 functions, selected by a 2-bit code. Using the building blocks discussed in lecture and the 3-bit subtractor block, implement a 3-bit ALU that can add, subtract, negate one argument, and multiply by 2. The select codes are listed in the table below. Note that there are 3 inputs (3-bit a, 3-bit b, and the 2-bit select code) and 2 outputs (3-bit result and a 1-bit carry). (14 pts)

Hint: Multiplying a number is like shifting the bits to the left and using 0 as the lowest bit. An example: $a = 1 = 3'b001 \rightarrow 2a = 2 = 4'b0010$

Select Code	Result (3-bits)	Carry bit
00	$a + b$	carry out
01	$a - b$	carry out
10	$-a$	0
11	$2 \cdot a$	Product MSB

- ↕ Adder
- ↕ "Subtractor"
- ↕ invert and add 1
- ↕ change order of wires

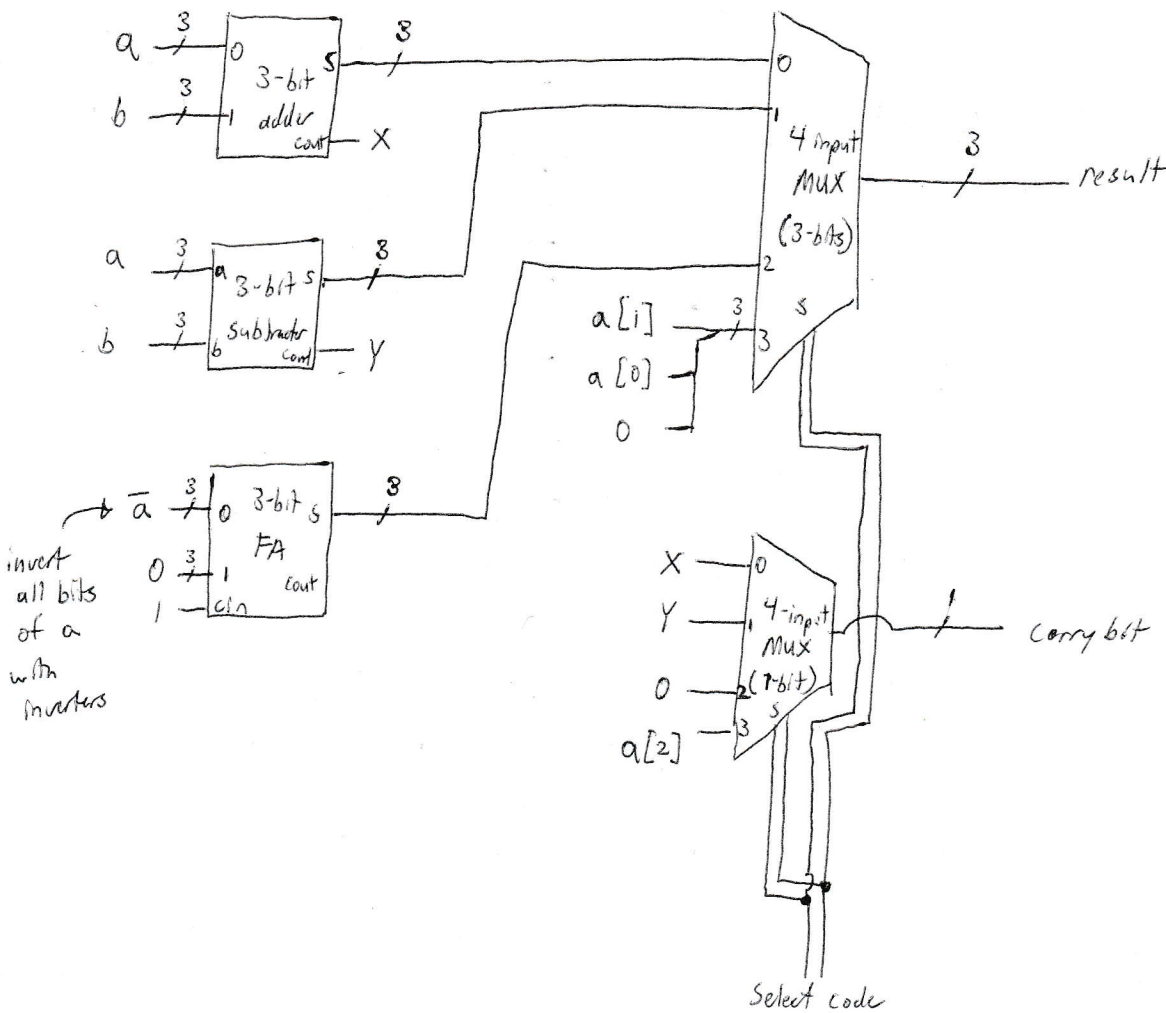- Combine all of these functions with MUXs



* Note: Ideally, $-a$ actually requires 4-bits since $-4 \rightarrow +4$ cannot be represented in 3-bits. This is a mistake in the problem and thus the -4 case will not work.

Question #5 (Extra Credit - 5 pts)

Implement a 4-bit Gray code +1 incremator using building blocks (no gates). The 4-bit Gray codes are shown below.

Decimal Number	Gray Code
0	0000
1	0001
2	0011
3	0010
4	0110
5	0111
6	0101
7	0100
8	1100
9	1101
10	1111
11	1110
12	1010
13	1011
14	1001
15	1000

Unsigned Int. interpretation

0
1
3
2
6
7
5
4
12
13
15
14
10
11
9
8

increment by 1 by switching to the next unit value
ex: 0 → 1 and 8 → 0 (wrap around)

