

## EE M16 Digital System Design

### Midterm Exam

Closed Book, 1 sheet of notes allowed

Name: \_\_\_\_\_

Student ID No.: \_\_\_\_\_

1) 5 / 5

2) 20 / 20

3) 11 / 11

4) 14 / 14

5) 10 / 10

TOTAL 60 / 60

5 pts

**Problem 1:**

Given a logic family with

$$V_{OL} = 0.15V_{DD}; \quad V_{IL} = 0.35V_{DD}; \quad V_{IH} = 0.7V_{DD}; \quad V_{OH} = 0.9V_{DD}$$

What is the lowest value of  $V_{DD}$  such that the gate can tolerate noise up to 100 mV.

$$V_{NML} = V_{IL} - V_{OL}$$

$$V_{NMH} = V_{OH} - V_{IH}$$

$$V_{NML} = 0.35V_{DD} - 0.15V_{DD}$$

$$V_{NMH} = 0.9V_{DD} - 0.7V_{DD}$$

$$0.100 = 0.20V_{DD}$$

$$0.100 = 0.2V_{DD}$$

$$V_{DD} = \frac{1}{2}V$$

$$V_{DD} = \frac{1}{2}V$$

$$V_{DD} = \frac{1}{2}V$$

20  
15 pts

**Problem 2:**

6 pts



(a) Sketch out the labeled signals assuming that all gates have a unit delay.

7 pts

(b) Is there a hazard in the circuit? If so, please identify it and explain the cause of it.


7 pts

 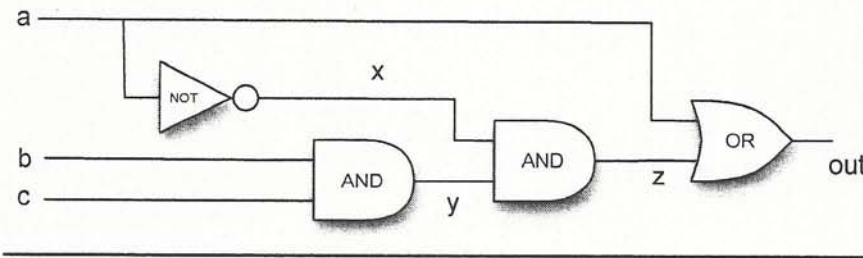(c) Can the hazard be eliminated? If so how?




b) Yes there is a 1-0-1 hazard. When a is changed to low while b and c are high, the output should be 1, but the output temporarily drops to 0 because of the delays where 'a' propagates to 'x' which propagates to 'z' which finally propagates to the output.



c)  $f = aV(\bar{a} \wedge b \wedge c)$

 

 To fix the hazard, add another implicant to overlap the implicants



$f = aV(b \wedge c)$

  

If 'a' switches to low at the same time 'b', 'c' switch to high there is still a hazard as 'b' and 'c' still need to go through one more AND gate than 'a'. Fix this by making 'a' go through AND gate.



11 pts

Problem 3:

- 3 pts (a) express the number -87 in 8-bit 2's complement notation
- 3 pts (b) express 11001101 in 8-bit 2's complement to decimal
- 5 pts (c) find the closest 6-bit two's complement fractional representation of the decimal number: -4.51

a)

$87 \div 2 = 43$	1	$87: 01010111$ $1 + 2 + 4 + 16 + 64$ $23 + 64 = 87$
$43 \div 2 = 21$	1	
$21 \div 2 = 10$	1	
$10 \div 2 = 5$	0	
$5 \div 2 = 2$	1	
$2 \div 2 = 1$	0	
$1 \div 2 = 0$	1	
sign	0	

$-87_{10} = 10101000$

+ 1

10101001

b)

$11001101$	
$00110010$	
+	1
$00110011$	$= 1 + 2 + 16 + 32 = 51$

-51

c)

sign is 1 bit

4  $\rightarrow$  100

2 bits for fraction (LSB =  $\frac{1}{4}$ )

4  $\cdot$  4.51 = 18  $\rightarrow$  010010

4.51 = 0100.10

-4.51 = 1011.01

+

1011.10

6 of 13



14 pts

**Problem 4:**

Design an efficient multiple of 3 circuit that takes in a decimal number between 0 and 11 represented as a 4-bit binary number  $x_3x_2x_1x_0$  ( $x_3$  is the MSB) and outputs a '1' if the input is 0, 3, 6, 9.

3 pts

(a) write the truth table

3 pts

(b) draw the Karnaugh Map

3 pts

(c) identify the prime implicants

5 pts

(d) Draw the logic diagram for a circuit that uses the minimum number of gates to implement this function.

a)

$x_3$	$x_2$	$x_1$	$x_0$	O/P
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	x
1	1	0	1	x
1	1	1	0	x
1	1	1	1	x

b)

$x_3x_2$	$x_1x_0$ 00	01	11	10
00	1	0	1	0
01	0	0	0	1
11	x	x	x	x
10	0	1	0	0

c) Implicants

Prime implicants

$$(x_3 \wedge \bar{x}_1 \wedge x_0) \vee$$


$$(x_2 \wedge x_1 \wedge \bar{x}_0) \vee$$

$$(\bar{x}_3 \wedge \bar{x}_2 \wedge x_1 \wedge x_0) \vee$$

$$(\bar{x}_3 \wedge \bar{x}_2 \wedge \bar{x}_1 \wedge \bar{x}_0)$$



D)

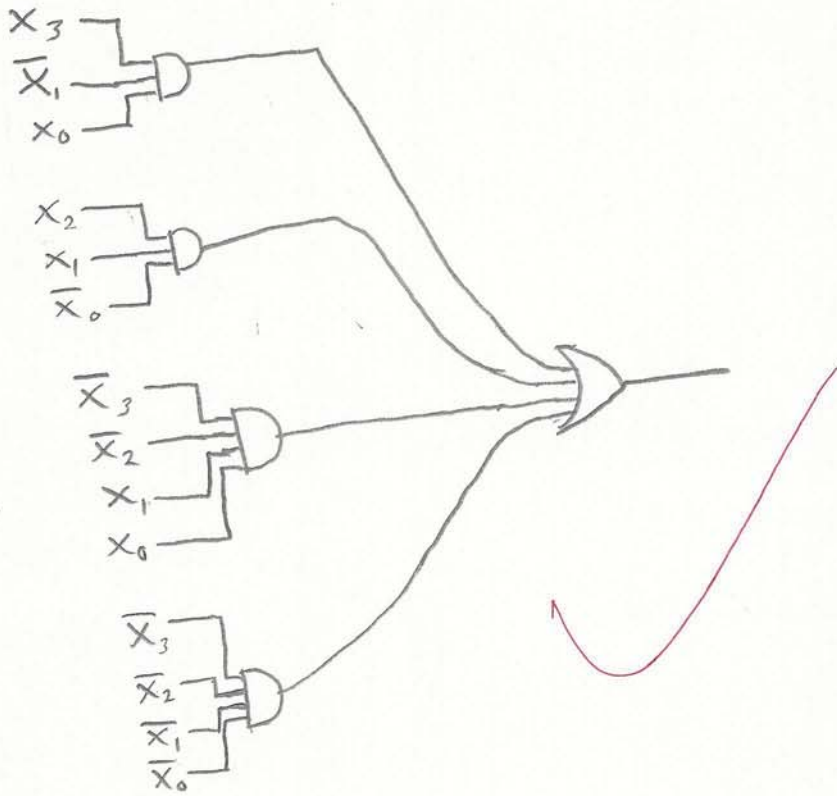




**Problem 5:**


10 pts

Implement the following Boolean expression using only 2:1 multiplexer gates
 
$$F = (A \wedge B' \wedge C \wedge D') \vee (A' \wedge B \wedge C \wedge D') \vee (A \wedge B' \wedge C' \wedge D) \vee (A' \wedge B \wedge C' \wedge D)$$



D	C	F
0	0	0
0	1	$a \oplus b$
1	0	$a \oplus b$
1	1	0

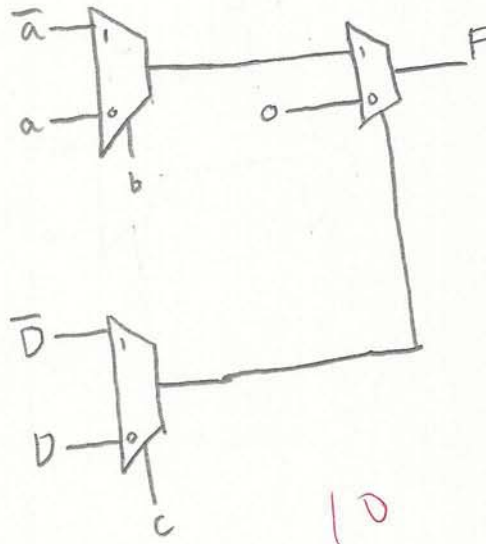

10



