

1. (40 points) Quickly testing the basics.

Note: Only write answers in the boxes, and use the extra sheet at the end of the question for any scratch work.

- (a) (4 points) The 7-bit 2's complement number representation of -11 is:

1110101

- (b) (4 points) 6'b110101, when treated as a 6-bit signed magnitude number, has a decimal representation of:

-21

- (c) (4 points) 8'b10011101 has a hexadecimal representation of:

unsigned : 9D / signed : -1D

- (d) (4 points) If 8'b10011101 is a fixed point 1001.1101, the corresponding number is:

unsigned : 9.8125 / signed : -1.8125

- (e) (4 points) If 8'b10011101 was a 4E3 floating point number (IEEE format), bias is:

3

- (f) (4 points) If 8'b10011101 was a 4E3 floating point number (IEEE format), corresponding real number is:

$-\frac{31}{64}$

- (g) (4 points) True or false: A boolean function of N variables with greater than $2^N - 1$ product terms can always be simplified to an expression using fewer product terms.

True

- (h) (4 points) What is the maximum number of product terms in a minimal sum-of-products expression with three variables?

4

- (i) (4 points) What is the minimum number of 2-input NAND gates that would suffice for you to be able to build an implementation of any arbitrary 2-input boolean function?

5

- (j) (4 points) You are treating the 8-bit numbers $A[7:0]$ and $B[7:0]$ as unsigned numbers. If you set $B[3:0]=A[7:4]$ and $B[7:4]=0$, what is the numeric value of B as a function of A ?

$B = A/16$ if $/$ is viewed as integer division

or $\text{floor}(A/16)$ if $/$ is viewed as real division

2. (10 points) Reduce the following expression. The simplified expression should have the minimum number of gates. Show the intermediate steps.

$$f(a, b, c, d) = \neg(\neg(a \wedge c \wedge d) \wedge (\neg a \vee \neg b \vee \neg d) \wedge (\neg(a \wedge d) \vee c)) \vee \neg(a \wedge \neg b) \wedge (\neg a \vee (\neg b \wedge c) \vee (\neg b \wedge \neg c))$$

$$\begin{aligned} f(a, b, c, d) &= \overline{\overline{acd}(\overline{a+b+d})(\overline{ad+c})} + \overline{a\overline{b}}(\overline{a} + \overline{b}c + \overline{b}\overline{c}) \\ &= acd + \overline{(\overline{a+b+d})} + \overline{(\overline{ad+c})} + (\overline{a} + \overline{b})(\overline{a} + \overline{b}(c + \overline{c})) \\ &= acd + abd + a\overline{c}d + (\overline{a} + \overline{b})(\overline{a} + \overline{b}) \\ &= ad(c + b + \overline{c}) + \overline{a} \\ &= ad + \overline{a} \\ &= ad + \overline{a}d + \overline{a}d + \overline{a}\overline{d} \\ &= d + \overline{a} \end{aligned}$$

3. (20 points) Consider the following function

$$f(a, b, c, d) = (\neg a \wedge \neg b \wedge c) \vee (b \wedge \neg c \wedge \neg d) \vee (\neg a \wedge c \wedge \neg d) \vee (a \wedge b \wedge \neg d) \vee (a \wedge \neg b \wedge d)$$

(a) (5 points) Complete the Karnaugh Map shown below, circuit the prime implicants.

	ab	00	01	11	10
cd	00	0	1	1	0
	01	0	0	0	1
	11	1	0	0	1
	10	1	1	1	0

How many prime implicants are there?

5

(b) (5 points) Show a combinational circuit that implements f using minimum number of inverters and NAND gates only. The maximum number of inputs per gate is less than 4.

According to K-map, using sum-of-products

$$f = \bar{a}\bar{b}c + a\bar{b}d + b\bar{d}$$


$$= (\bar{a}\bar{b}c) \cdot (\bar{a}\bar{b}d) \cdot c\bar{b}\bar{d}$$


(c) (5 points) Show a combinational circuit that implements f using minimum number of inverters and NOR gates only. The maximum number of inputs per gate is less than 4.

According to K-map, using product-of-sums

$$f = \bar{a}\bar{b}\bar{c} + a\bar{b}\bar{d} + bd$$

 
$$= \overline{a+b+c} + \overline{\bar{a}+b+d} + \overline{\bar{b}+\bar{d}}$$



 

- (d) (5 points) Show an 8-input Multiplexer that implements f . The select signal is $s[2:0] = \{B, C, D\}$ where $s = 3'b100$ is $B = 1$ and $C = D = 0$ selecting the input $mux_in[4]$. Constants, A or $\neg A$ are permissible as inputs, $mux_in[7:0]$. Write the desired inputs on the figure below.

BCD	A	
	0	1
000	0	0
001	0	1
010	1	0
011	1	1
100	1	1
101	0	0
110	1	1
111	0	0

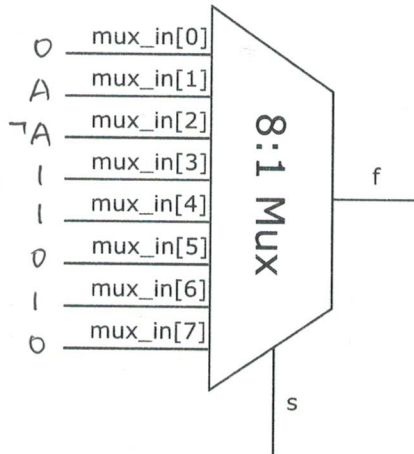


4. (10 points) Design a combinational network that has a three-bit input x representing the digits 0 to 7, and a three-bit output y representing the same set of integers. The function of the system is $y = (x + 3) \pmod 8$. You may use any building blocks and gates you have learnt.

input (x)	output (y)
0	3
1	4
2	5
3	6
4	7
5	0
6	1
7	2

We use a binary 3-to-8 decoder to obtain a 1-hot representation, and then connect the output of the decoder to the input of a 8-to-3 encoder, as shown below.

First, create an input-output table.
 Note that each input has a unique output.

 5. (20 points) A standard decoder typically has an additional input pin E called Enable. The rough idea of using E in a decoder design is shown in the following figure. A 0 value



on E turns decoder off, setting all d_i s to 0. Value 1 on E turns decoder on. Design a combinational circuit that converts a 3-bit sign-and-magnitude number, a , into a 3-bit one's complement number, b . You are allowed to use any number and any combination of the following building blocks:

- Decoders with enable pins: $1 \rightarrow 2$ and $2 \rightarrow 4$ decoders
- Encoders: $2 \rightarrow 1$ and $4 \rightarrow 2$ encoders
- Logic gates: Use either OR gates or AND gates, but not both

Every block and wire must be clearly labeled.

decimal	sign-and-magnitude	one's complement
-3	111	100
-2	110	101
-1	101	110
-0	100	111
0	000	000
1	001	001
2	010	010
3	011	011

Observe that if the input is positive, then output b is the same as a . If input is negative, then the bits ~~a~~ are flipped.

