

EEM16 Midterm

TOTAL POINTS

65 / 65

QUESTION 1

1 Problem #1 18 / 18

- ✓ - 0 a) is Correct
- ✓ - 0 b) is correct
- ✓ - 0 c) is correct
- ✓ - 0 d) is correct
- ✓ - 0 e) is correct
- 1 a) added don't cares as minterms
- 3 a) is incorrect
- 2 b) is partially correct
- 5 b) is incorrect
- 3 c) is incorrect
- 3 d) is incorrect
- 2 e) is partially incorrect
- 4 e) is incorrect
- 1 d) partially incorrect
- 2 c) partially incorrect

QUESTION 2

2 Problem #2 14 / 14

- ✓ - 0 all correct
- 2 Part (a): answer other than 2, 3 or 4
- 1 Part (b): deduct for wrong demorgan
- 0.5 Part(b): partial improper SoP
- 1 Part(b): For improper SoP form
- 2 Part(b) quite wrong SoP
- 4 Part(b): all wrong
- 1.5 Part(c): if Not distributive
- 2 Part(c) no 6 SoP
- 1 Part(c). For each wrong SoP term
- 4 Part(c): all wrong
- 0.5 Part(d): Partial wrong reduced expression
- 1 Part(d): quite wrong reduced expression
- 1 Part(d): For one missing property
- 2 Part(d): For two missing properties

QUESTION 3

3 Problem #3 22 / 22

- ✓ - 0 Correct. Good Job.
- 1 (a) math error
- 2 (a) incorrect
- 1 (a) (b) or (c) math error
- 2 (b) incorrect
- 2 (c) incorrect = -105
- 0.5 (c) negative error for 2's complement
- 2 (d) incorrect hex
- 2 (e) incorrect BCD
- 1 (f) partial credit
- 2 (f) incorrect
- 2 (g) incorrect bias
- 2 (g) incorrect real number
- 1 (g) partial credit for error
- 6 (h) incorrect
- 2 (h) incorrect floating point choice
- 1 (h) partially incorrect min bits for mantissa
- 2 (h) incorrect min bits for mantissa
- 1 (h) partially incorrect min bits for exponent
- 2 (h) incorrect min bits for exponent

QUESTION 4

4 Problem #5 11 / 11

- ✓ - 0 (a) Correct. Nice Job!
- 7 (a) incorrect
- 5.5 (a) partial for ok attempt
- 3 (a) Too much excessive logic
- 0 (a) No or incorrect Hit logic
- 0.5 (a) Some unnecessary logic
- ✓ - 0 (b) Correct. Nice Job!
- 4 (b) incorrect
- 3.5 (b) Partial credit for attempt
- 1 (b) incorrect bit weight (hop and adder cnt)
- 1 (b) no or incorrect adder count or hop

- **0.5** (b) Good attempt but slightly too many FA
- **1.5** (b) ok attempt but incorrect design
- **3** (b) partial credit for attempt

Midterm Exam

Name (Last, First):



Student Id #:

**Do not start working until instructed to do so.**

1. You must answer in the **space provided** for answers after every question. We will ignore answers written anywhere else in the booklet. **All pages in this booklet must be accounted** for otherwise it will not be graded.
2. You are permitted 1 page of notes 8.5x11 (front and back).
3. You may not use any electronic device.

Following table to be filled by course staff only

	Maximum Score	Your Score
Question 1		
Question 2		
Question 3		
Question 4		
Question 5		
TOTAL	100	

Question #1

Consider the Boolean function defined by the truth table below where A, B, C, and D are inputs, and Y is the sole output.

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	X
1	1	1	0	1
1	1	1	1	X

(a) Complete the following statements

$$Y = \sum m(0, 4, 5, 6, 7, 8, 9, 11, 14)$$

(b) Complete the Karnaugh Map shown below, **circle** the prime implicants.


		AB			
		"00"	"01"	"11"	"10"
CD	"00"	1	1	0	1
	"01"	0	1	X	1
	"11"	0	1	X	1
	"10"	0	1	1	0

How many prime implicants are there? 7

(c) Write the Boolean (sum-of-product) expression for the essential prime implicants (if any).

EssentialPrimeImplicants = $(B \wedge C) \vee (A \wedge D)$

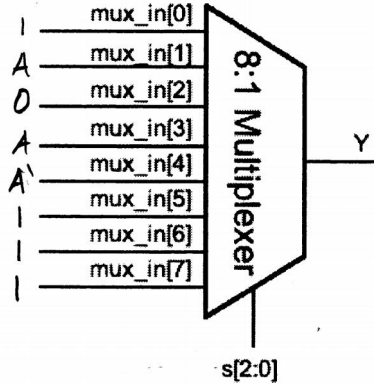(d) Implement the function Y using an 8-input multiplexer. The select signal is $s[2:0]=\{B,C,D\}$ where $s=3'b100$ is $B=1$ and $C=D=0$ selecting the input $mux_in[4]$. A or $\sim A$ are permissible as inputs, $mux_in[7:0]$. Write the desired inputs on the figure below.




(e) Implement $\sim Y$ using the minimum # of NOR gates with fewest # of inputs (minimize literals and terms).

POS

$$Y = (B \wedge C) \vee (A \wedge D) \vee (\bar{A} \wedge \bar{B}) \vee (\bar{B} \wedge \bar{C} \wedge \bar{D})$$
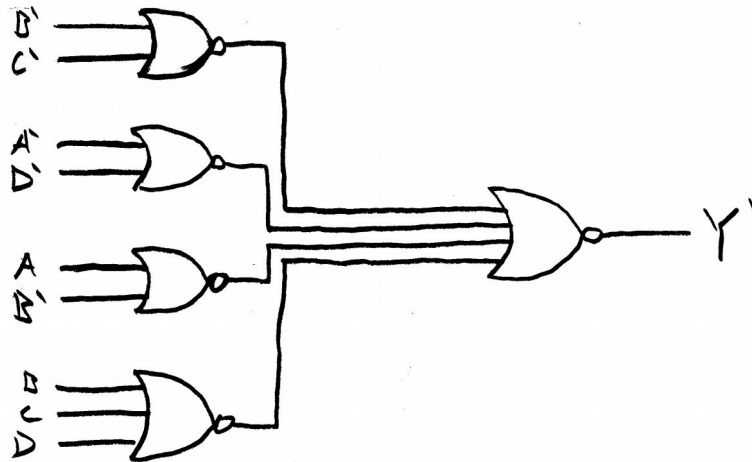
$$\bar{Y} = (\bar{B} \vee \bar{C}) \wedge (\bar{A} \vee \bar{D}) \wedge (A \vee \bar{B}) \wedge (B \vee C \vee D)$$



$$\begin{aligned}
 (a \wedge \bar{b}) \wedge (\bar{c} \vee d \vee e) &= (a \wedge \bar{b} \wedge \bar{c}) \vee (a \wedge \bar{b} \wedge d) \vee (a \wedge \bar{b} \wedge e) \\
 &\uparrow \\
 (\bar{a} \vee b) \vee (c \wedge \bar{d} \wedge \bar{e}) & \\
 &\uparrow \uparrow \\
 Y = \neg(\neg(a \wedge \neg b) \vee (c \wedge \neg(d \vee e))) &\rightarrow \overline{(\overline{a \wedge \bar{b}}) \vee (c \wedge \bar{d} \wedge \bar{e})}
 \end{aligned}$$

(a) For the above Boolean function, if you were to convert the above expression into a sum-of-product representation, how many times did you have to apply DeMorgan's theorem?

3

(b) For part (a), what is the resulting function?

$$Y = \underline{(a \wedge \bar{b} \wedge \bar{c}) \vee (a \wedge \bar{b} \wedge d) \vee (a \wedge \bar{b} \wedge e)}$$

(c) The following expression can be written as a 6-term sum-of-product, $(a \vee b) \wedge a$

$$Y = (a \vee b) \wedge (a \vee \neg b \vee \neg c)$$

What Boolean property do you need to apply to do this?

Distributive Property

Without reducing, what are the 6 product terms?

$$\underline{(a \wedge a) \vee (a \wedge \bar{b}) \vee (a \wedge \bar{c}) \vee (b \wedge a) \vee (b \wedge \bar{b}) \vee (b \wedge \bar{c})}$$

(d) The 6-term sum-of-product of part (c) can obviously be reduced.

What is the reduced expression?

$$\underline{a \vee (b \wedge \bar{c})}$$

What Boolean axioms or properties are needed for the reduction?

Absorption, idempotence, convergence

$$\begin{aligned}
 a \vee (a \wedge \bar{b}) \vee (a \wedge b) \\
 \vee (a \wedge \bar{c}) \vee (b \wedge \bar{c})
 \end{aligned}$$

$$\begin{aligned}
 a \vee (a \wedge \bar{c}) \vee (b \wedge \bar{c}) \\
 a \vee (b \wedge \bar{c})
 \end{aligned}$$

$$(a \wedge b) \vee (a \wedge \bar{b})$$

$$= a$$

convergence?

97

1101001
bit 5 8 1 105

$144 + 7 = 151$

Question #3

(a) The following 8 bits can be used to represent different numbers depending on the encoding
8b'10010111

If this was unsigned, what is the corresponding integer? 151

$1 + 2 + 4 + 16 + 128 = 151$

(b) If the 8 bits in (a) was sign magnitude, what is the corresponding integer? -23

$-(16 + 4 + 2 + 1) = -23$

(c) If the 8 bits in (a) was 2's complement, what is the corresponding integer? -105

$(-128) + 23 = -105$

(d) If the 8 bits in (a) was hexadecimal, what is the corresponding hexadecimal? 97_{Hex}

$1001 = 9, \quad 0111 = 7$

(e) If the 8 bits in (a) was binary coded decimal, what is the corresponding integer? 97

(f) If the 8 bits is fixed point 1001.0111, what is the corresponding number? 9.4375

$1001 = 9, \quad .0111 = 2^{-2} + 2^{-3} + 2^{-4} = 0.4375$

(g) If the 8 bits in (a) was a 4E3 floating point number (IEEE format S+EEE+MMMM),

What is the bias? 3

$-1 \cdot 2^{1-3} \cdot (1 + 2^{-2} + 2^{-3} + 2^{-4})$

What is the corresponding real number? -0.359375

(h) Military temperature range is -55°C to +125°C with 1% accuracy.

LM. mag. 0.25°C

Would you choose floating point or fixed point? floating point

If you are to represent this in floating point, what is the minimum # of bits for mantissa? 6

$125 - (-55) = 180$

$2^{5.6} = 2^6$

And, what is the minimum # of bits for exponent? 4


9 bits $\Rightarrow 7,$

$15 - 7 = 8$


$0.01 \approx 2^{-7}$

Question #5

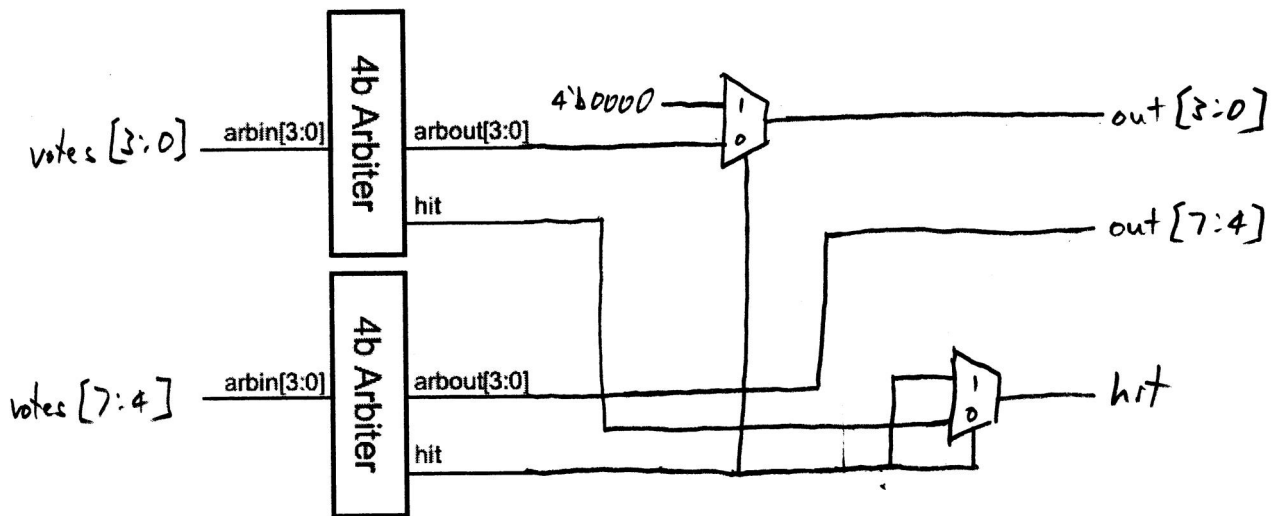- (a) Given 8-bit input, $votes[7:0]$, in which any number of the inputs can be a 1'b1. Build an **arbiter** that provides an 8-bit output, $arbout[7:0]$, that is 1-hot. The hot signal corresponds to the position with the highest priority. Note that $votes[7]$ has higher priority than $votes[6]$ etc. You have available to you a module ARB that is a 4-bit arbiter already built that you **must** use. ARB accepts as inputs $arbin[3:0]$ and outputs $arbout[3:0]$ and a *hit* signal to indicate that one or more of the signals is a 1'b1. You also have available to you INV (inverters), and 2-input MUX (multiplexers). Recall that you can implement considerable arbitrary logic with 2-input MUXs.





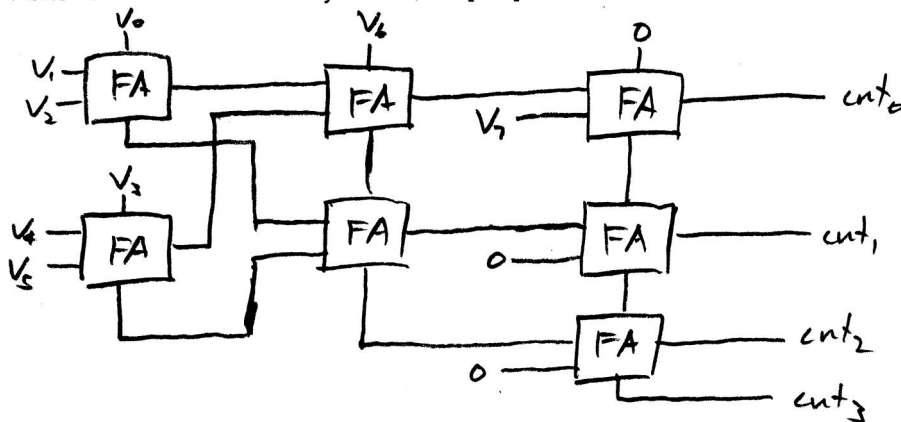- (b) Now, the $votes[7:0]$ need to be counted. You have available Full Adders (FA) as building blocks for implementing a design. If the delay of the logic is determined by the number of hops where each hop is the traversal of a Full-Adder from any input ($a, b,$ and c) to any output ($sum, carry$). Design your block to minimize this delay. Note that your design should output 4 bits to indicate the binary count, $cnt[3:0]$.



How many Full Adders to you need? 7
 How many hops is your design? 4

Blank page for scratch work

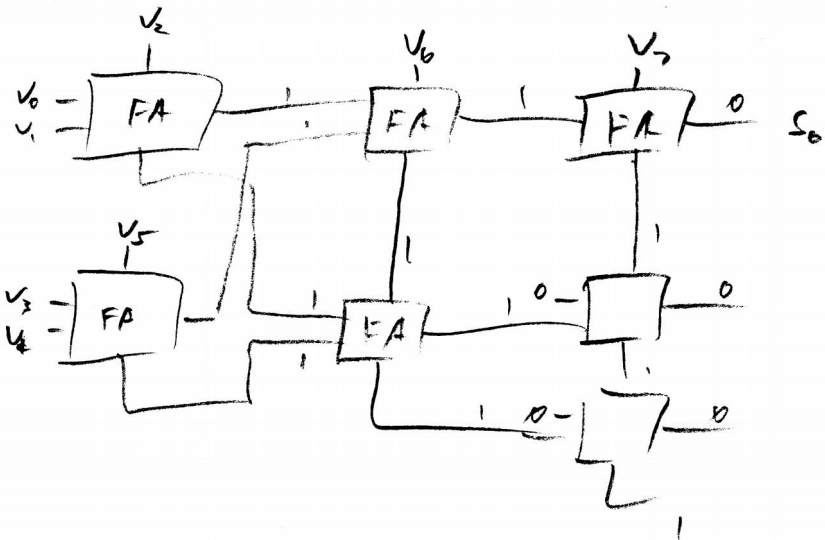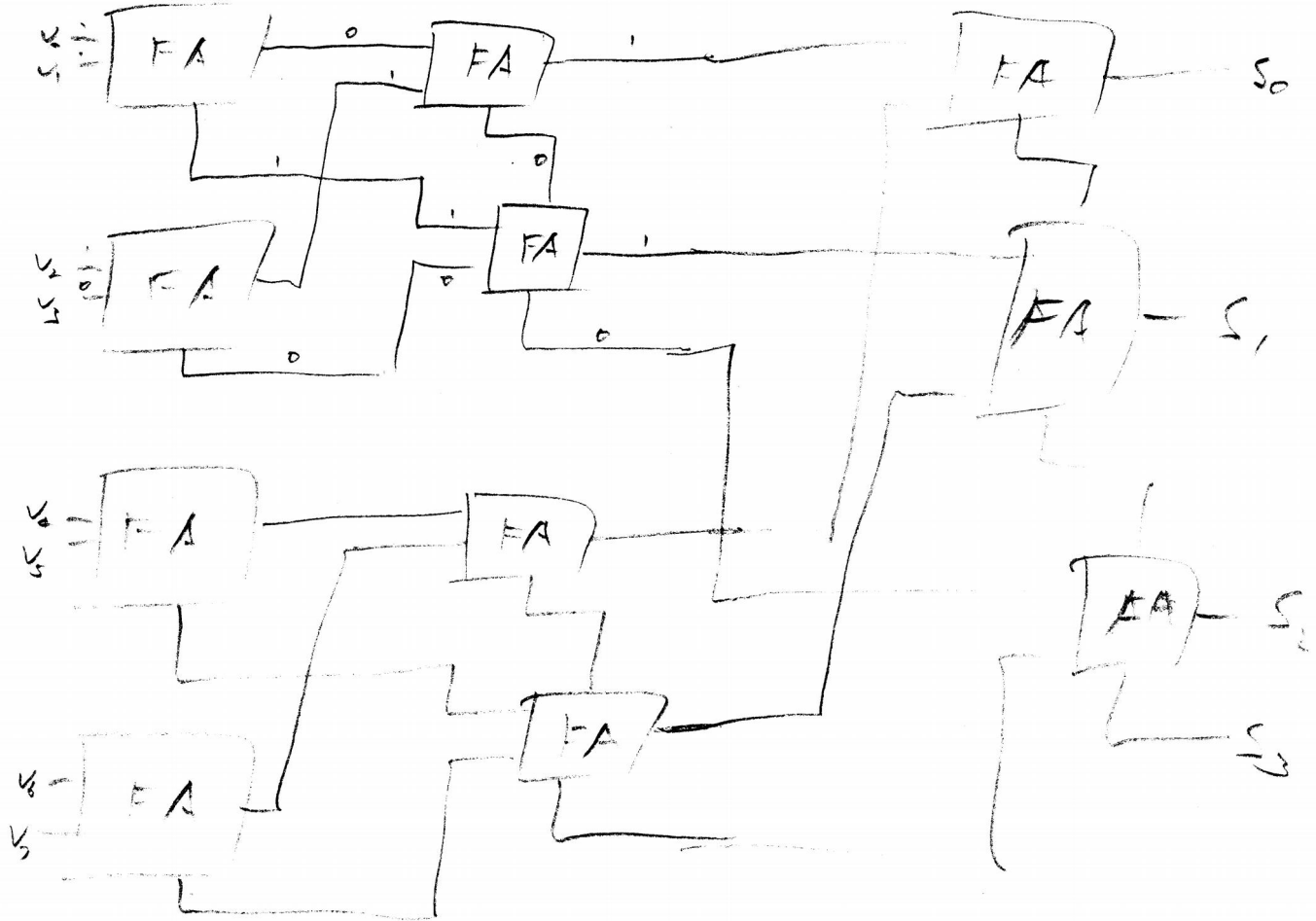

UCLA | EEM16/CSM51A | Spring 2017
Blank page for scratch work

Prof. C.K. Yang