

Midterm Exam

Name (Last, First):

Student Id #:

Do not start working until instructed to do so.

1. You must answer in the **space provided** for answers after every question. We will ignore answers written anywhere else in the booklet. **All pages in this booklet must be accounted** for otherwise it will not be graded.
2. You are permitted 1 page of notes 8.5x11 (front and back).
3. You may not use any electronic device.

Following table to be filled by course staff only

	Maximum Score	Your Score
Question 1		
Question 2		
Question 3		
Question 4		
TOTAL	100	

Question #1

Consider the following Karnaugh Map for the Boolean function, Y. A blank truth table is provided for your convenience.

	AB			
	"00"	"01"	"11"	"10"
"00"	0	0	1	1
"01"	1	1	X	X
"11"	0	0	1	1
"10"	1	1	X	0

xx01

) 11XX

1X0X

1XX1

0X10

A	B	C	D	Y	Y'	Y''
0	0	0	0	0	1	0
0	0	0	1	1	0	X
0	0	1	0	1	0	1
0	0	1	1	0	1	0
0	1	0	0	0	1	0
0	1	0	1	1	0	1
0	1	1	0	1	0	X
0	1	1	1	0	1	0
1	0	0	0	1	0	1
1	0	0	1	X	X	0
1	0	1	0	0	1	0
1	0	1	1	1	0	1
1	1	0	0	1	0	1
1	1	0	1	X	X	0
1	1	1	0	X	X	0
1	1	1	1	1	0	1

- (a) Circle the prime implicants on the map.
How many prime implicants are there? 5
- (b) Write the Boolean (sum-of-product) expression of the essential prime implicants of (b) (if any).

EssentialPrimeImplicants = $(\bar{C}D) \vee (A\bar{C}) \vee (AD) \vee (\bar{A}C\bar{D})$

- * (c) Complete the following statement

$\neg Y = \prod M()$

This seems like the covers of 0's

ABCD
0X00
0X11
1X10

$\bar{A}\bar{C}\bar{D} \vee \bar{A}C\bar{D} \vee A\bar{C}\bar{D}$

How do you get inverse, product of sums

- (d) Express as a minimal sum of product, $\neg Y$.
The K-map is provided for your convenience.

		AB			
		"00"	"01"	"11"	"10"
CD	"00"	0	0	1	1
	"01"	1	1	X	X
	"11"	0	0	1	1
	"10"	1	1	X	0

$C \times 00$
 0×11
 1×10

$\bar{A}\bar{C}\bar{D}$
 $A\bar{C}\bar{D}$

$$\neg Y = (\bar{A}\bar{C}\bar{D}) \vee (\bar{A}C\bar{D}) \vee (A\bar{C}\bar{D})$$

- (e) Is the dual of this function itself? Circle one: Yes No

Justify your answer:

If it weren't for don't care values it would obviously be a dual.
It still is however, because you would get the identical logic

Y, Y^D if you write a boolean expression and flipped $\vee \leftrightarrow \wedge$, For don't cares we can assume they are any value, because it doesn't matter.

Is it a dual if there are don't care values?

Yes

- * (f) If the logic is implemented using its minimal sum-of-product expression, is there a risk of a static hazard?

Circle one: Yes No

Under what input conditions?

What product term(s) would you add to remove the risk? _____

What is a static hazard?

Question #2

(a) Rewrite the following Boolean equation as a sum-of-products or product-of-sum. Hint: apply DeMorgan's theorem.

$$W = \neg(\neg(c \vee \neg(a \wedge \neg b)) \vee (d \wedge \neg e)) \quad ((c + (ab)') + (d\bar{e}))'$$

Answer:

$$= (c \vee \neg(a \wedge \neg b)) \wedge (\overline{d \wedge \neg e}) = (c + (ab)')(d\bar{e})'$$

$$= (c \vee (\bar{a} \vee b)) \wedge (\bar{d} \vee e) = (c + (ab)')(d' + e)$$

$$(c \vee \bar{a} \vee b) \wedge (\bar{d} \vee e) \quad (c + (a' + b))(d' + e)$$

$$W = \underline{(c \vee \bar{a} \vee b) \wedge (\bar{d} \vee e)} \quad \text{SOP: } cd' + d'd' + bd' + ce + d'e + be$$

(b) Rewrite the following Boolean equation as a sum-of-products or product-of-sum.

$$X = (c \vee (a \wedge b)) \vee (d \wedge e)$$

Answer: Find logical equivalent of $c \vee (a \wedge b)$ in SOP form

$$= (c \wedge (a \wedge b)) \vee (c \wedge \overline{(a \wedge b)}) \vee (\bar{c} \wedge (a \wedge b))$$

$$(c \wedge a \wedge b) \vee (c \wedge (\bar{a} \vee \bar{b})) \vee (\bar{c} \wedge a \wedge b)$$

$$(c \wedge a \wedge b) \vee (c \wedge \bar{a}) \vee (c \wedge \bar{b}) \vee (\bar{c} \wedge a \wedge b) \vee (d \wedge e)$$





$$X = \underline{(c \wedge a \wedge b) \vee (c \wedge \bar{a}) \vee (c \wedge \bar{b}) \vee (\bar{c} \wedge a \wedge b) \vee (d \wedge e)}$$

(c) Implement the following function using NOR gates only and the fewest NOR gates possible.

You may use true and complemented versions of the a-f inputs,


$$Y = (a \wedge b \wedge c \wedge d \wedge e) \vee (c \wedge d \wedge f)$$

    Simplified logic is
 $= (abcde) + (cdf)$
 $= cd(obe + f)$



$$A \wedge B \Rightarrow \overline{\overline{A \wedge B}} = \overline{\overline{A} \vee \overline{B}}$$
 
$$A - B = \overline{A} \Rightarrow \overline{\overline{A}} = \overline{\overline{A}}$$



The following 12-bit word can be used to represent different numbers depending on the encoding

12b'1011_1101_0110

(a) If the word is 2's complement, what is the corresponding integer? -1066

(b) If we convert the word into base-4, what is the represented number?

233112 2 bits needed for 1-3 10-11-11-01-01-10
2 3 3 1 1 2

(c) If we take answer in (b), write the 3's complement of the base-4 number.

3100221
3 3 3 3 3 3 3
-0 -2 -3 -3 -1 -1 -2
0 1 0 0 2 2 1 +1 = 100221

(d) If the word is unsigned fixed point 6.6, what is the corresponding number?

47.6875
10 1111 01 01 10
 $2^5 + 2^4 + 2^3 + 2^2 = 32 + 8 + 4 + 2 = 47$ 47
 $2^{-1} + 2^{-2} + 2^{-3} + 2^{-4} = .5 + .25 + .125 + .0625 = .9375$

What is the absolute accuracy of this representation? .015625

(e) What is this word in Hexadecimal? BDS

1011 1101 0110
B D 5

(f) If the word is 6E5 floating point number (IEEE format S+EEEE+MMMMMM),

What is the bias? 2
bias = $\lfloor \frac{5}{2} \rfloor + 1 = 2$ 0111 010110

What is the corresponding real number? -22×10^{13} $(-1)^S (1.M) \cdot 2^{(E-bias)}$

(g) In base-20 system and using 3 "vigits" (base-20 digits) in 20's complement:

How would one represent a base-10 integer -1616? _____

What is the most positive value in base-10 integer that can be represented?

3999

20
20
~~20~~

$20^3/2 - 1$
 $20^2 - 1$
 $400 - 1$

9 19 19

Number is negative
Exponent is 15 bias 2
Mantissa is

$19 \cdot 20^2 + 19 \cdot 20^1 + 9 \cdot 20^0$

HEX bias $(\frac{5}{2}) = 2$

400
200
8000

-1616
 $1616/2 = 808$
 $808/2 = 404$
 $404/2 = 202$
 $202/2 = 101$
 $101/2 = 50$
 $50/2 = 25$
 $25/2 = 12$
 $12/2 = 6$
 $6/2 = 3$

$\frac{1}{2} = 0.1$
11001010000

10110
 $2^4 + 2^2 + 2^1$
 $16 + 4 + 2 = 22$

1 10010 10000
1 18 16

400
9
3600

Question #4

(a) Two 4-bit binary inputs, $b_1[3:0]$ and $b_2[3:0]$, are ^{needed} ~~needed~~ to be decoded into a single 2-hot output vector, $twoh[15:0]$. This 2-hot vector has up to two positions of 1's and the remainder are 0's. If b_1 is the same as b_2 , then only a single 1 is asserted. Design this logic. You may use 2:4 Decoders as building blocks and any number of AND, OR, or INV gates. Try to minimize the amount you use. You may describe connections to avoid an overly complex drawing of every signal and line.


00	0004	0001
01	0010	0010
10	0100	0100
11	1000	1000

$b_1[3]$ $b_1[2]$ $b_1[1]$ $b_1[0]$ $b_2[3]$ $b_2[2]$ $b_2[1]$ $b_2[0]$


0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	0	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0
1	0	1	0	0	0	0	0
1	0	1	1	0	0	0	0
1	1	0	0	0	0	0	0
1	1	0	1	0	0	0	0
1	1	1	0	0	0	0	0
1	1	1	1	0	0	0	0

For each decoder there a 64


16 rows

 

All possible permutations

 

 (b) Next, you are tasked to code the $twoh[15:0]$ signals into a vector that indicates a range, similar to a thermometer code. The 16-bit input, $twoh[15:0]$, produces 16-bit outputs, $rangeh[15:0]$, whereby the positions in between the 2 asserted signals of the $twoh[15:0]$ are all 1's. For instance, with $b1[3:0]=4'b0110$ and $b2[3:0]=4'b0010$, $rangeh[15:0]=16b'0000_0000_0011_1110$. You may use any building block we have covered in lecture as well as any number of AND, OR, or INV gates. Again you can describe connections to avoid drawing every signal and line.



if previous is 0
and current is 1, propagate.

if previous is 1
and current is 1, don't propagate


if previous is 1
and current is 0, propagate

previous	current	Propagate	output
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	1


$$prop = \bar{p}c \vee p\bar{c}$$

Output

~~rangeh[i]~~

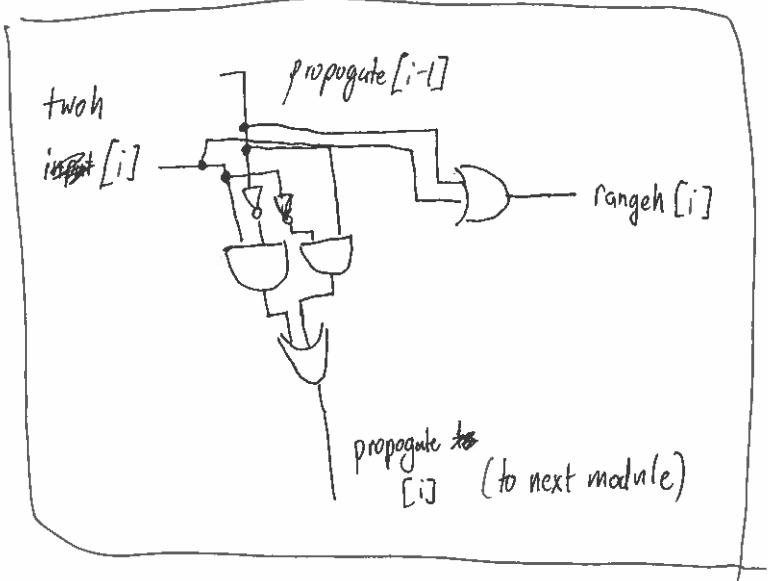

 - (c) Finally, encode inverse the function of (a) by accepting the $twoh[15:0]$ signal as input and output 2 binary values $bo1[3:0]$ and $bo2[3:0]$ to indicate the binary position of the two hot bits. You may use any building block we have covered in lecture as well as any number of AND, OR, or INV gates. Again you can describe connections to avoid drawing every signal and line.



Here, you need to have encoders
and probably a MUX to