

[CS M51A FALL 14] MIDTERM EXAM

Date: 11/04/14

- Please show all your work and write legibly, otherwise no partial credit will be given.
- This should strictly be your own work; any form of collaboration will be penalized.

Name :



Student ID :



Problem	Points	Score
1	10	2
2	10	4
3	20	20
4	20	20
5	10	10
6	30	30
Total	100	86

Problem 1 (10 points) 2

$X = (x, y, z)$ is a 3-digit weighted mixed-radix number system: x is a radix-16 digit, y is a radix-3 digit, and z is a radix-12 digit.

1. (5 points) Convert $X = (6, 1, 11)$ to a decimal number.

$$16 \cdot 6 + 3 \cdot 1 + 12 \cdot 11$$

$$\begin{array}{r} 3 \\ 16 \\ \hline 16 \\ 96 \\ 16 \\ \hline 3 \ 256 \\ 6 \\ \hline 1536 \end{array}$$

$$6 \ 1 \ 11$$

$$6 \cdot 16^2 + 1 \cdot 3^1 + 11 \cdot 12^0$$

$$1536_0 + 3_0 + 11_{00} = (1550) \times$$

2. (5 points) 2 What is the largest number of X in decimal?

$$X = (15, 2, 11) + 2$$

$$15 \cdot 16^2 + 2 \cdot 3^1 + 11 \cdot 12^0$$

$$3840 + 6 + 11 = 3857$$

$$\begin{array}{r} 2 \ 2 \\ 256 \\ \hline 15 \\ 1280 \\ 2560 \\ \hline 3840 \end{array}$$

Problem 2 (10 points)

Simplify the following boolean expression by using postulates of Boolean Algebra.

$$(a+b)' = a'b'$$

$$(ab)' = a'+b'$$

$$(a'b' + c)(a+b)(b' + a'c)'$$

$$((a'b' + c)(a+b)(b'(a'c)'))'$$

$$(a'b' + c)(a+b)(b(a+c))'$$

$$((a+b)' + c)(a+b)(b(a+c))$$

$$(a+b)' + c = a' + b' + c$$

$$(a' + b' + c)(a+b)(b(a+c))$$

no bc...

~~$$ac + cb + b' + a'c'$$~~

~~$$ac + c + b' + a'c'$$~~


~~$$c + b' + a'c'$$~~

~~$$c + a' + b'$$~~

4

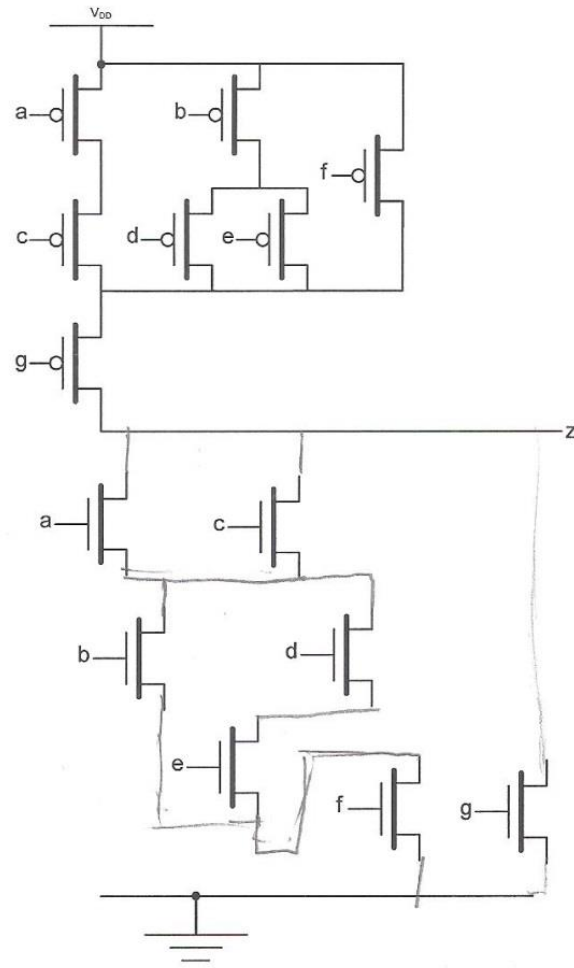Problem 3 (20 points)

We are given the following partial CMOS network.



1. (10 points) Write the expression for the pull-up network. From this, derive the expression for the pull-down network using switching algebra.

pull-up

$$Z = \left((a'c') + f' + (d'e')b' \right) g'$$

$$Z' = \left[(a'c') + f' + (d'e')b' \right] g''$$

$$\left((a'c') + f' + (d'e')b' \right)' + g$$

$$(a'c')' f' ((d'e')b')' + g$$

$$(a+c) f' ((d'e')' + b) + g$$

pull-down

$$(a+c) f (de + b) + g$$


2. (10 points) Connect the NMOS transistors in page 4 to complete the pull-down network so that it corresponds to the expression obtained from part 1 and drives the output z to a valid output - i. e. either V_{DD} or ground - for any combination of inputs.

You can directly draw on the CMOS implementation on page 4.

Problem 4 (20 points)

We would like to determine the propagation delay of the gate network shown here. The output is z with a input x . The necessary gate characteristics are given in the table below.

Gate Type	Fan-in	Propagation Delays (ns)		Load Factor
		t_{pLH}	t_{pHL}	I
NOT	1	$0.02 + 0.038L$	$0.05 + 0.017L$	1.0
AND	2	$0.15 + 0.037L$	$0.16 + 0.017L$	1.0
NAND	2	$0.05 + 0.038L$	$0.08 + 0.027L$	1.0
NAND	3	$0.07 + 0.038L$	$0.09 + 0.039L$	1.0
XOR	2	$0.30 + 0.036L$	$0.30 + 0.021L$	1.1
		$0.16 + 0.036L$	$0.15 + 0.020L$	2.0

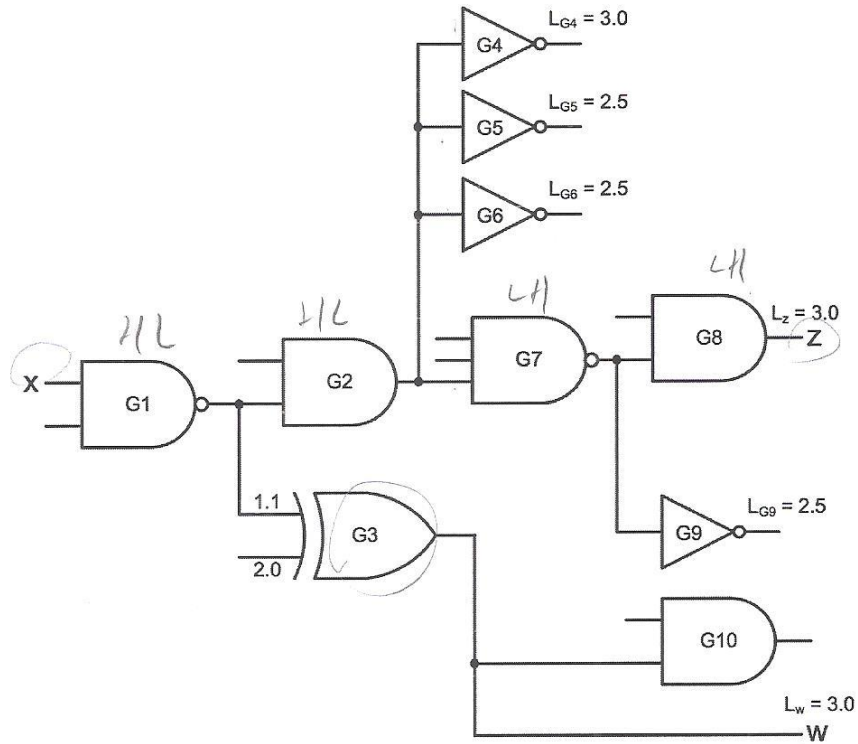

1. (10 points) (a) Determine the output load of gate G3. 10
(b) If the fanout factor of gate G3 is 8, then how many additional gate inputs with load factor of 2 can be connected to the output of gate G3?

a) $1 + 3 = 4$

b) $8 - 4 = 4 \div 2 = 2$

10

2. (10 points) Find the worst case value of $t_{pLH}(x \rightarrow z)$. Fill in the blanks below with the appropriate values.

Gate type and fan-in G1: NAND, 2 → G2: AND, 2 → G7: NAND, 3 → G8: AND, 2

LH / HL G1: HL → G2: HL → G7: LH → G8: LH

Output load L G1: 2.1 → G2: 4 → G7: 2 → G8: 3

Propagational delay G1: .08 + .027(2.1) → G2: .16 + .017(4) → G7: .07 + .038(2) → G8: .15 + .037(3)

$t_{pLH}(x \rightarrow z)$ _____

Problem 5 (10 points)

Decide whether the function E defined in (a) and (b) are universal functions.. If Yes, show your proof. You can use constant 0 or 1 as your input.

10


(a) (5 points)

x	y	$E(x,y)$
0	0	1
0	1	1
1	0	0
1	1	1

NOR ←
 "OR" ←
 XOR ←
 OR ←


00 → NAND
 01 → NAND
 10 → AND
 11 → AND

NOT ✓

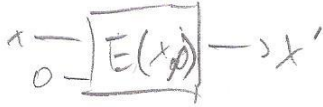

x	$E(x,0)$
0	1
1	0

← NOT gate

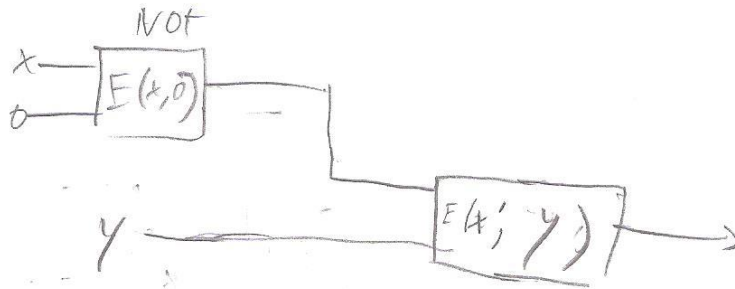

x	y	output
0	0	0
0	1	1
1	0	1
1	1	1

OR ✓

Universal

(b) (5 points)

x	y	z	E(x,y,z)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

$E(1,0,z) \rightarrow \text{NOT}$

z	E(1,0,z)
0	1
1	0

$\in \underline{\text{NOT}}$

$E(0,y,z) \rightarrow \text{AND}$

y	z	E(0,y,z)
0	0	0
0	1	0
1	0	0
1	1	1

AND

{AND, NOT}

Universal set

Problem 6 (30 points)

$z \rightarrow dc$




30

F is a function that accepts inputs $x \in \{0, 1, 2\}$, $y \in \{0, 1, 2, 3\}$, and outputs $z = x^2 + y$. Suppose you use binary code to encode x , y , and z . x is encoded as x_1x_0 , y is encoded as y_1y_0 , z is encoded as $z_2z_1z_0$.

(a) (5 points) Fill in the following truth table.

	x_1	x_0	y_1	y_0	z_2	z_1	z_0	
0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	1	1
2	0	0	1	0	0	1	0	2
3	0	0	1	1	0	1	1	3
4	0	1	0	0	0	0	1	1
5	0	1	0	1	0	1	0	2
6	0	1	1	0	0	1	1	3
7	0	1	1	1	1	0	0	4
8	1	0	0	0	1	0	0	5
9	1	0	0	1	1	0	1	5
10	1	0	1	0	1	1	0	6
11	1	0	1	1	1	1	1	7
12	1	1	0	0	1	1	1	
13	1	1	0	1	1	1	1	
14	1	1	1	0	1	1	1	
15	1	1	1	1	1	1	1	

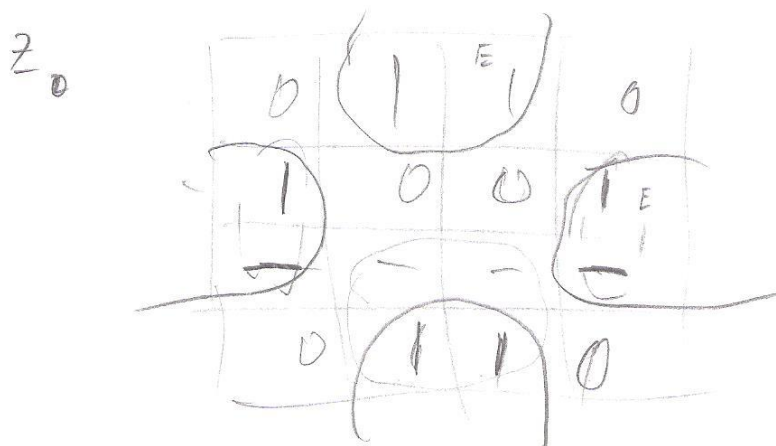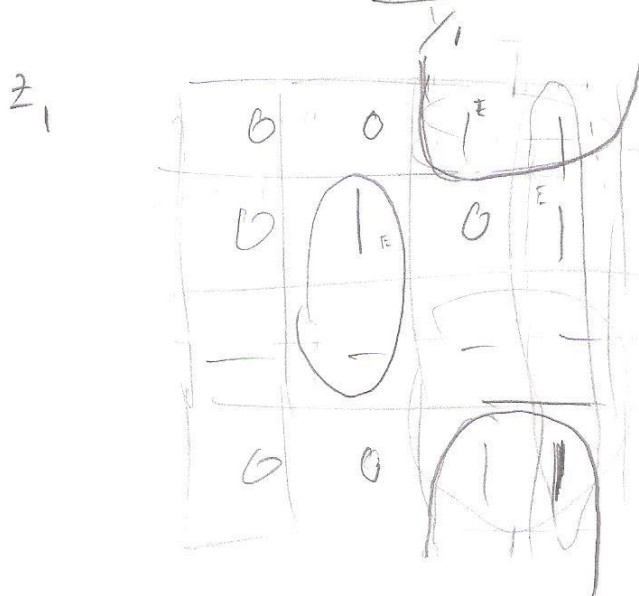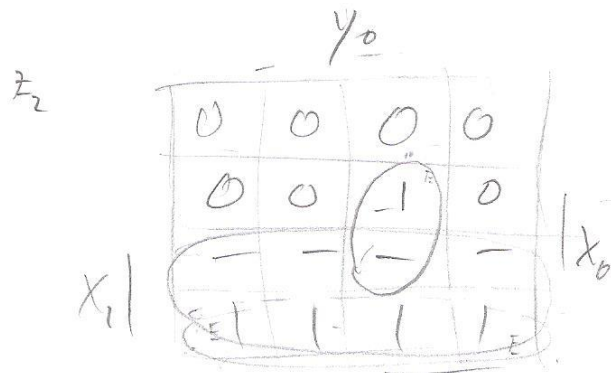(b) (5 points) Based on the truth table in (a), draw the K-map for z_2 , z_1 , and z_0 .



(c) (5 points) Use the K-maps in (b) to find all the prime implicants for z_2 , z_1 , and z_0 respectively.

z_2

x_1	0	0	0	0
	0	0	1	0
	-	-	-	-
	1	1	1	1
				x_0

$$z_2 = x_0 y_1 y_0, x_1 y_0'$$

z_1

0	0	1	1
0	1	0	1
-	-	-	-
0	0	1	1

$$z_1 = x_1 y_1, y_1 y_0', x_0 y_0', x_0 y_1'$$

$$z_0 = x_0 y_0', x_0 y_0, x_1 y_0$$

(d) (5 points) Use the K-maps in (b) to find all the essential prime implicants for z_2 , z_1 , and z_0 respectively.

$$z_2 = x_0 y_1 y_0, x_1 y_0'$$

$$z_1 = x_0 y_1 y_0, y_1 y_0', x_0 y_0'$$

$$z_0 = x_0 y_0', x_0 y_0$$

(e) (5 points) Give minimal SOP expression for z_2 , z_1 , and z_0 . State if the expressions are unique.

$$z_2 = (x_0 y_1 y_0) + (x_1)$$

unique

$$z_1 = (x_0 y_1 y_0) + (y_1 y_0) + (x_0 y_1)$$

unique


$$z_0 = (x_0 y_0) + (x_0 y_1)$$

unique

(f) (5 points) Implement z_2 , z_1 , and z_0 using minimal NAND-NAND networks. Note that each output has a separate gate network. You can directly use x_1, x_0, y_1, y_0 as inputs.


$$x_0 y_1 y_0 + x_1$$

$$\left((x_0 y_1 y_0)' (x_1)' \right)'$$

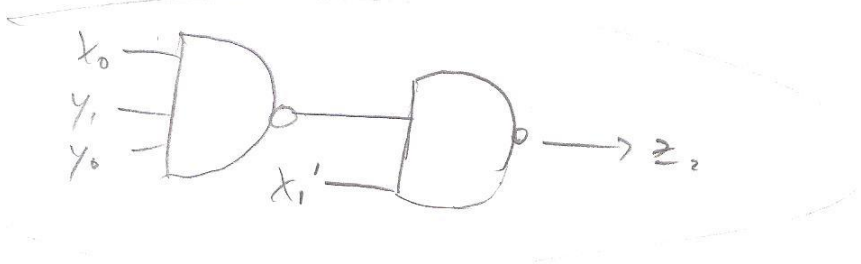

$$x_0 y_1' y_0 + y_1 y_0' + x_0' y_1$$
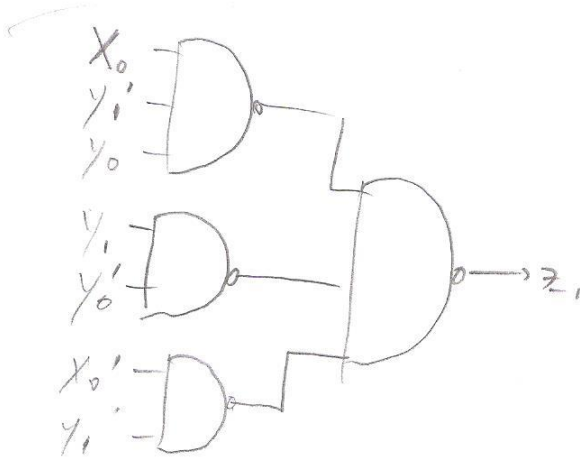
$$\left((x_0 y_1' y_0)' (y_1 y_0')' (x_0' y_1)' \right)'$$



$$x_0 y_0' + x_0' y_0$$

$$\left((x_0 y_0')' (x_0' y_0)' \right)'$$

