

# [CS M51A FALL 15] MIDTERM EXAM

Date: 11/3/15

- The midterm is closed books and notes. Tablets and smartphone are not allowed.
- You can use calculators and have up to 2 sheets (= 4 pages) of summary notes.
- Please show all your work and write legibly, otherwise no partial credit will be given.
- This should strictly be your own work; any form of collaboration will be penalized.

Name : \_\_\_\_\_

Max Chern

Dis 2B

Student ID : \_\_\_\_\_

Problem	Points	Score
1	15	14
2	15	8
3	10	3
4	15	15
5	10	10
6	15	15
7	20	18
Total	100	83

### Problem 1 (15 points)

1. (6 points) Given the following simplification of a boolean expression, identify all right and wrong steps and briefly explain what is wrong for each error.  
(For example, (10)  $\rightarrow$  (11) wrong application of the Identity rule, (11)  $\rightarrow$  (12) correct )

$$\begin{aligned} E_1(w, x, y, z) &= (((w + x + x'y')y + z)' + wx' + y')' & (1) \\ &= ((w + x + x'y')'y'z' + wx' + y')' & (2) \\ &= ((w + x + x'y')'y'z' + (w + y')(x' + y'))' & (3) \\ &= ((w + x' + y')'y'z' + (w + y')(x' + y'))' & (4) \\ &= (w'xyy'z' + (w + y')(x' + y'))' & (5) \\ &= (0 + (w + y')(x' + y'))' & (6) \\ &= wy + xy & (7) \end{aligned}$$

(1)  $\rightarrow$  (2) wrong application of DeMorgan's Law

$\times$  (2)  $\rightarrow$  (3) wrong application of Distributivity

(3)  $\rightarrow$  (4) wrong application of Simplification

(4)  $\rightarrow$  (5) correct

(5)  $\rightarrow$  (6) correct

(6)  $\rightarrow$  (7) wrong application of DeMorgan's Law


-1

2. (5 points) Obtain the minimal sum of products form for  $E_2(w, x, y, z)$  using the identities of Boolean algebra.  
Show all the steps in your derivation.

$$\begin{aligned}
 E_2 &= xy' + xzw + yw \\
 &= xy' + xzw(y + y') + yw \\
 &= xy' + xzw + xzw'y' + yw \\
 &= \overline{xy'} + \overline{xzw} + \overline{yw} + \overline{yw}xz \quad a + ab = a \\
 &= \overline{xy'} + yw
 \end{aligned}$$

✓

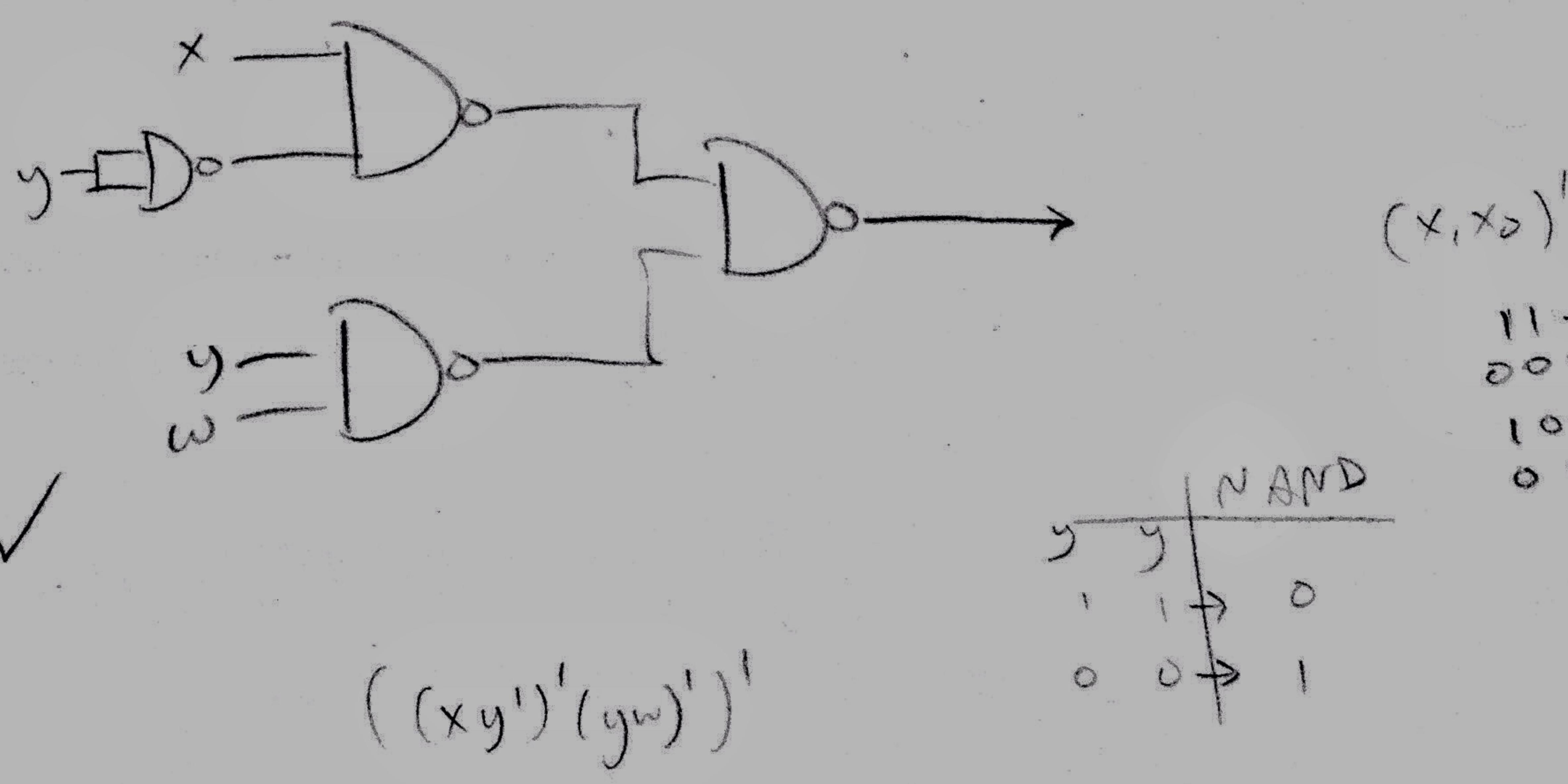
3. (4 points) Using the expression obtained for  $E_2$  from the previous step, obtain the NAND network that uses ONLY NAND gates. Inverted inputs are not available, and no constant inputs are allowed.



$$= (xy') + (yw)$$
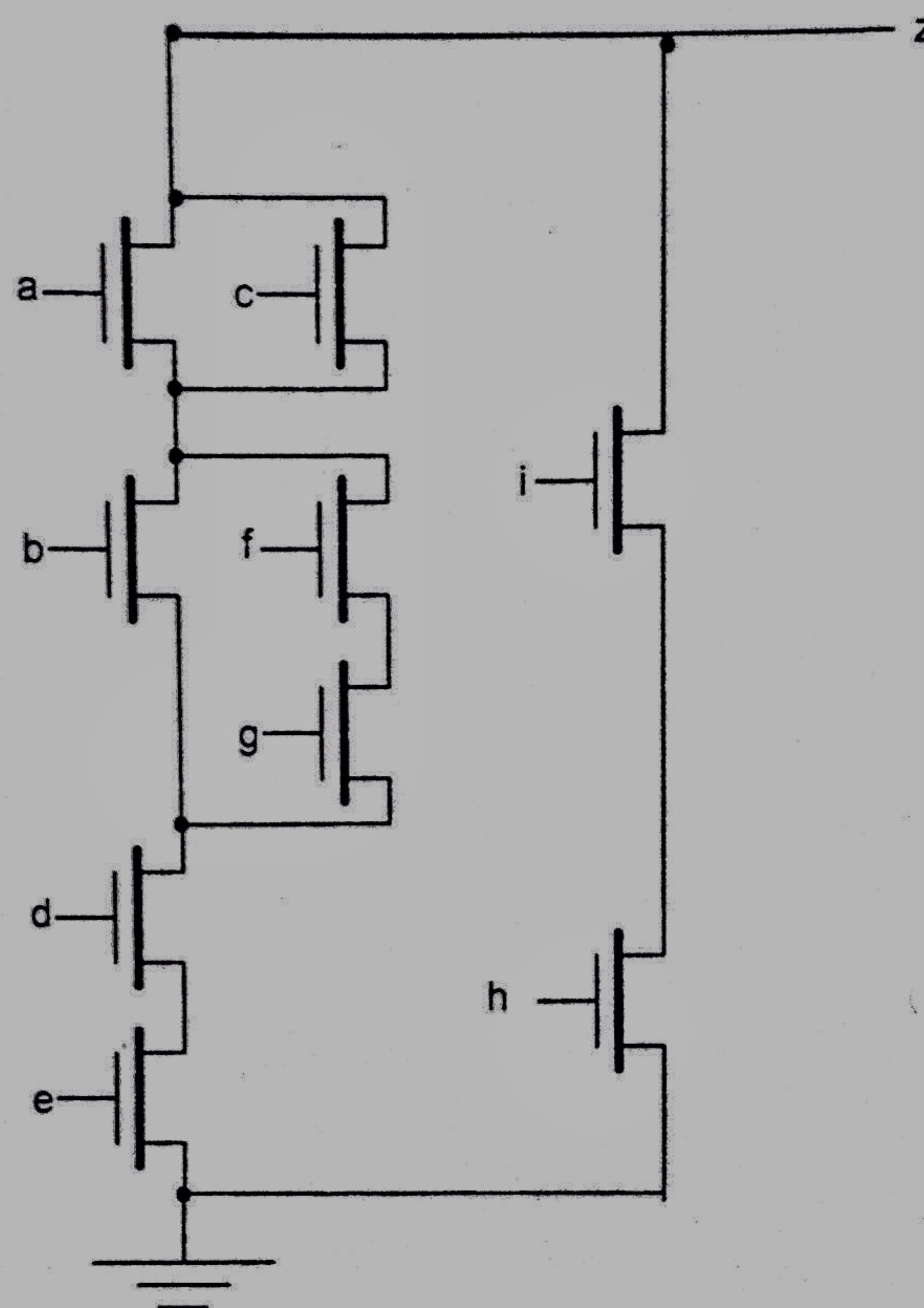
## Problem 2 (15 points)

The following pull-down network is part of a complex CMOS gate that we want to implement.



1. (8 points) (a) Write the expression for the pull-down network.

$$\text{Pull-down network expression : } z' = \frac{[(a+c)(b+fg)de]}{hi}$$

✓

- (b) Obtain the expression for the corresponding pull-up network.

$$\text{Pull-up network expression : } z = \frac{[a'c' + b'(f'+g')] + d' + e'}{h' + i'}$$

$$z = \left( [(a+c)(b+fg)de] + hi \right)'$$


$$= [(a+c)(b+fg)de]'(hi)'$$

$$= [(a+c)' + (b+fg)' + d' + e'] [h' + i']$$


$$= [a'c' + b'(f+g)' + d' + e'] [h' + i']$$

$$= (a'c' + b'(f+g') + d' + e') (h' + i')$$


(c) Draw the pull-up network.

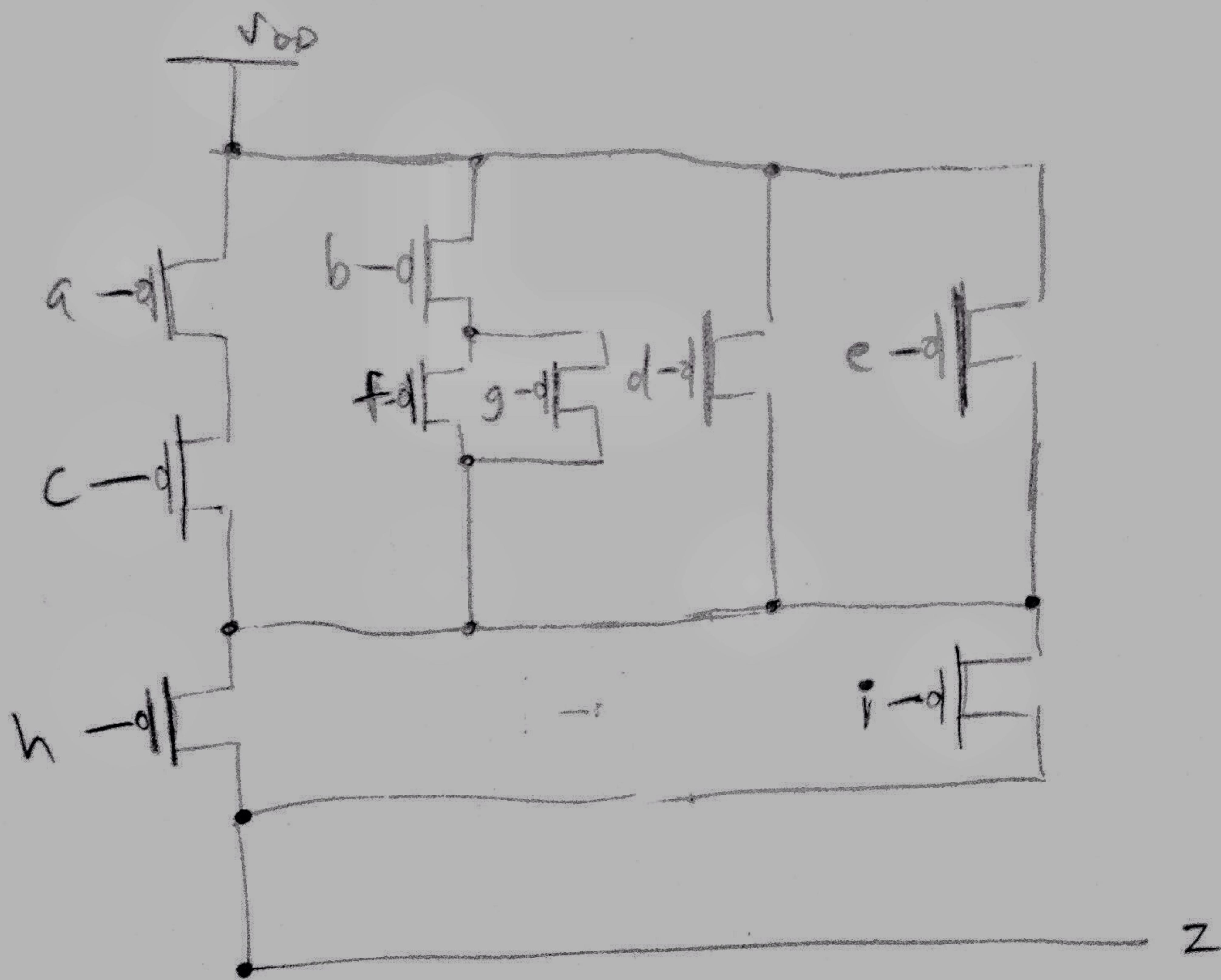

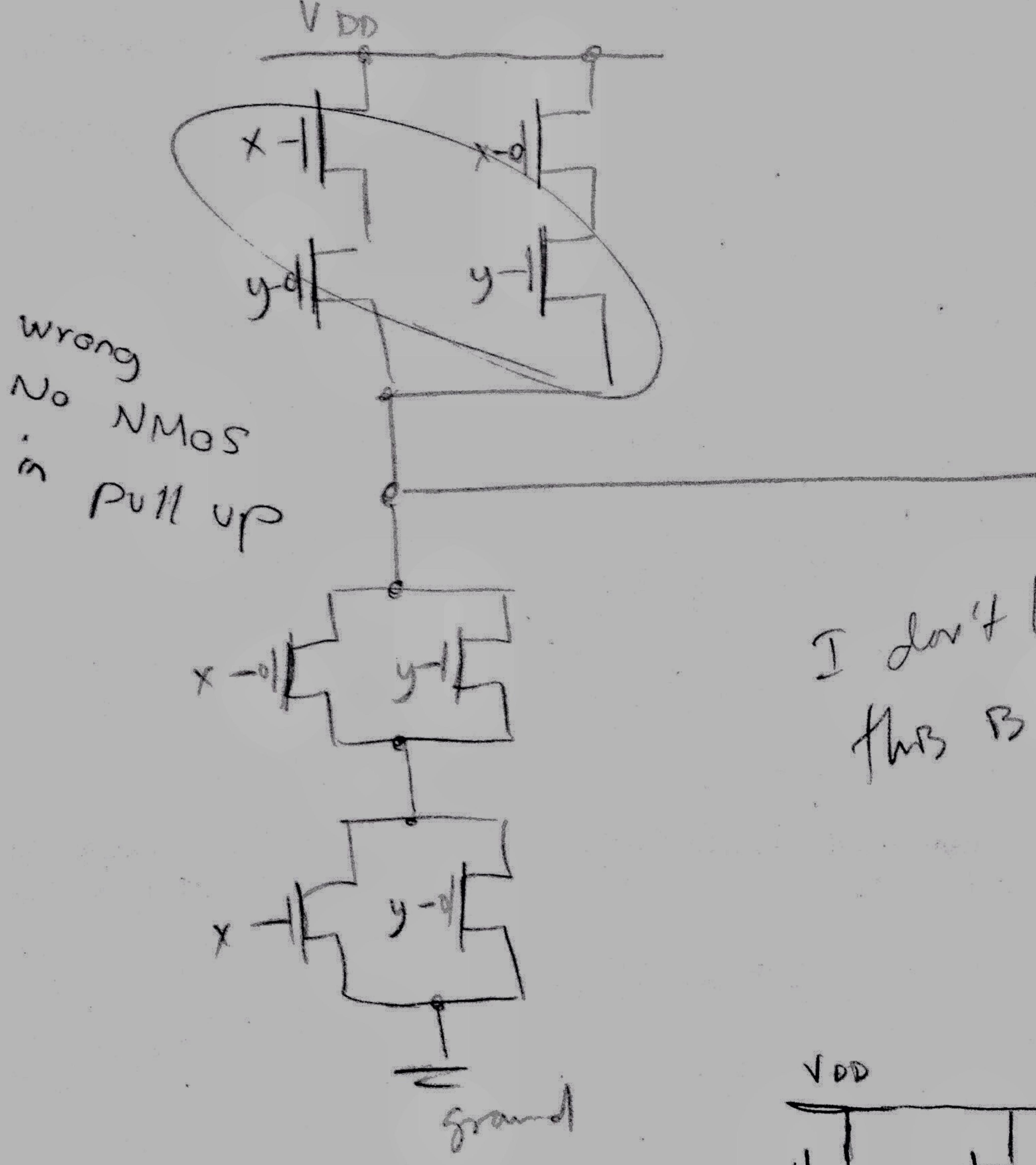2. (7 points) Draw a CMOS network that implements  $f(x,y) = xy' + x'y$  (2-input XOR).  $x'$  and  $y'$  are not available as inputs. Do not use transmission gates. How many transistors does your solution have?  
 OPTIONAL: If you find another solution with fewer transistors, you get 3 extra points. Show your reduced design and explain why it works.



I don't know if  
this is right : (

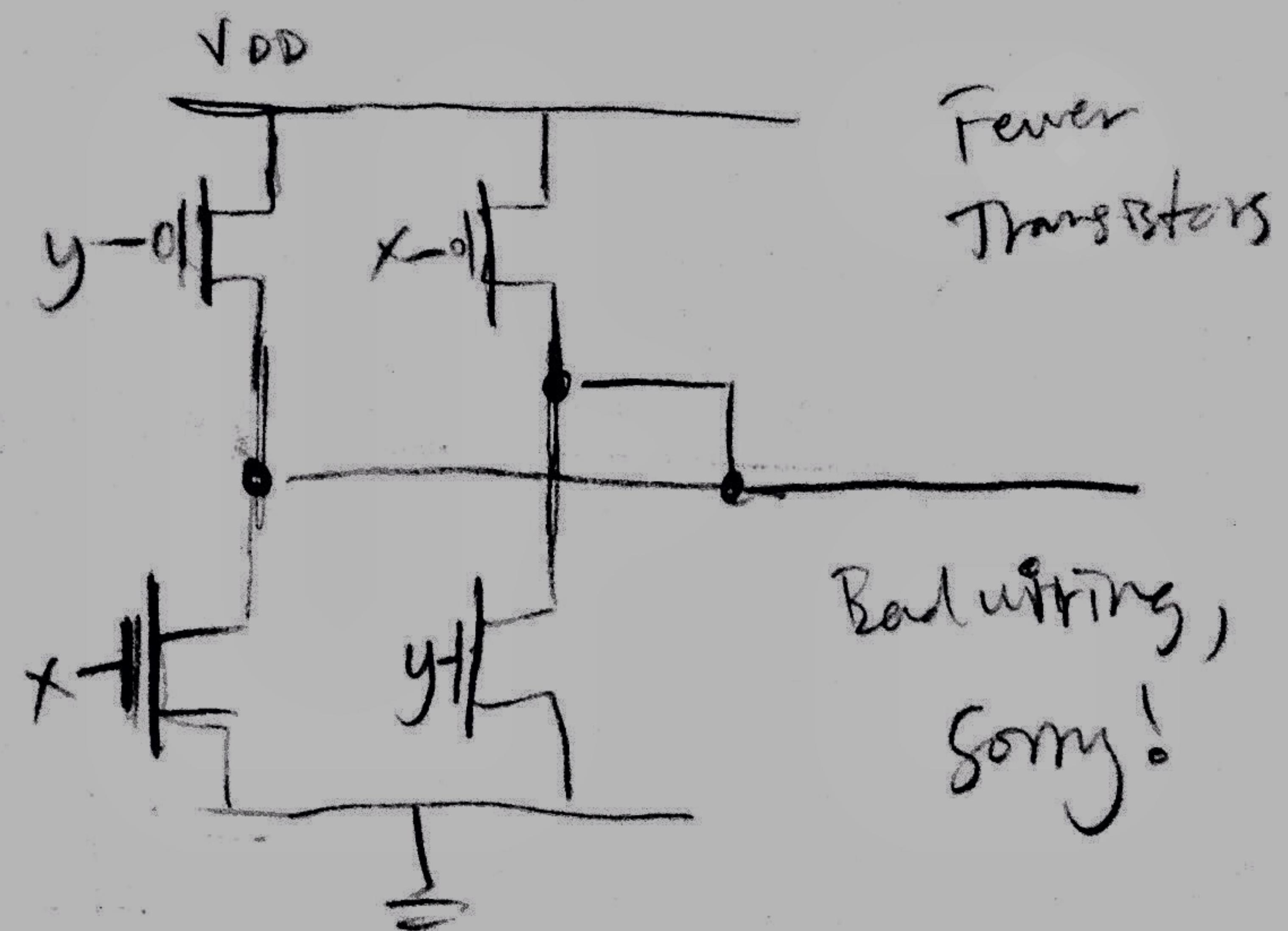

problem 3 (10 points)

3

1. (5 points) A 12-bit vector represents a set of positive integers  $\{0, \dots, N\}$ . Which of the following coding alternatives

- (a) BCD
- (b) 2421 code (a decimal code)
- (c) Excess-3 code (a decimal code)
- (d) Octal
- (e) Binary

provides the largest range? Why? (Give  $N$  for each case).

(a) BCD

each 4 bits has range 16, 0-15

so 12 bit range is  $16^3 = 4096$ ,  $N = 4095$

(b) 2421 code

each 3 bits has range 9

so 12 bit range is  $9^4 = 729$ ,  $N = 728$

(c) Excess-3 code

each 4 bits has range 16 still,  $N = 4095$

(d) Octal

each 3 bits has range 8, 0-7

so 12 bit range is  $8^4 = 4096$ ,  $N = 4095$

(e) binary

same as BCD

$N = 4095$

✓ - 1

Octal has largest range because each bit has a range of 0-7

2. (5 points) Let  $a = (101110010110)$  and  $b = (001110110101)$ . If  $a$  represents a number in the Excess-3 code and  $b$  in the binary code, what is the value in decimal of their sum  $a + b$ ? Show all your work.

$$b = \underline{949} + 2^{5+11(16)+3(256)}$$

$$a = 3 + 6(16) + 8(256)$$

$$= 2147 \times$$


$$a+b = 949 + 2147 = 3096$$

Problem 4 (15 points)

15

We would like to verify that the PLA implementation shown here implements the following switching functions:
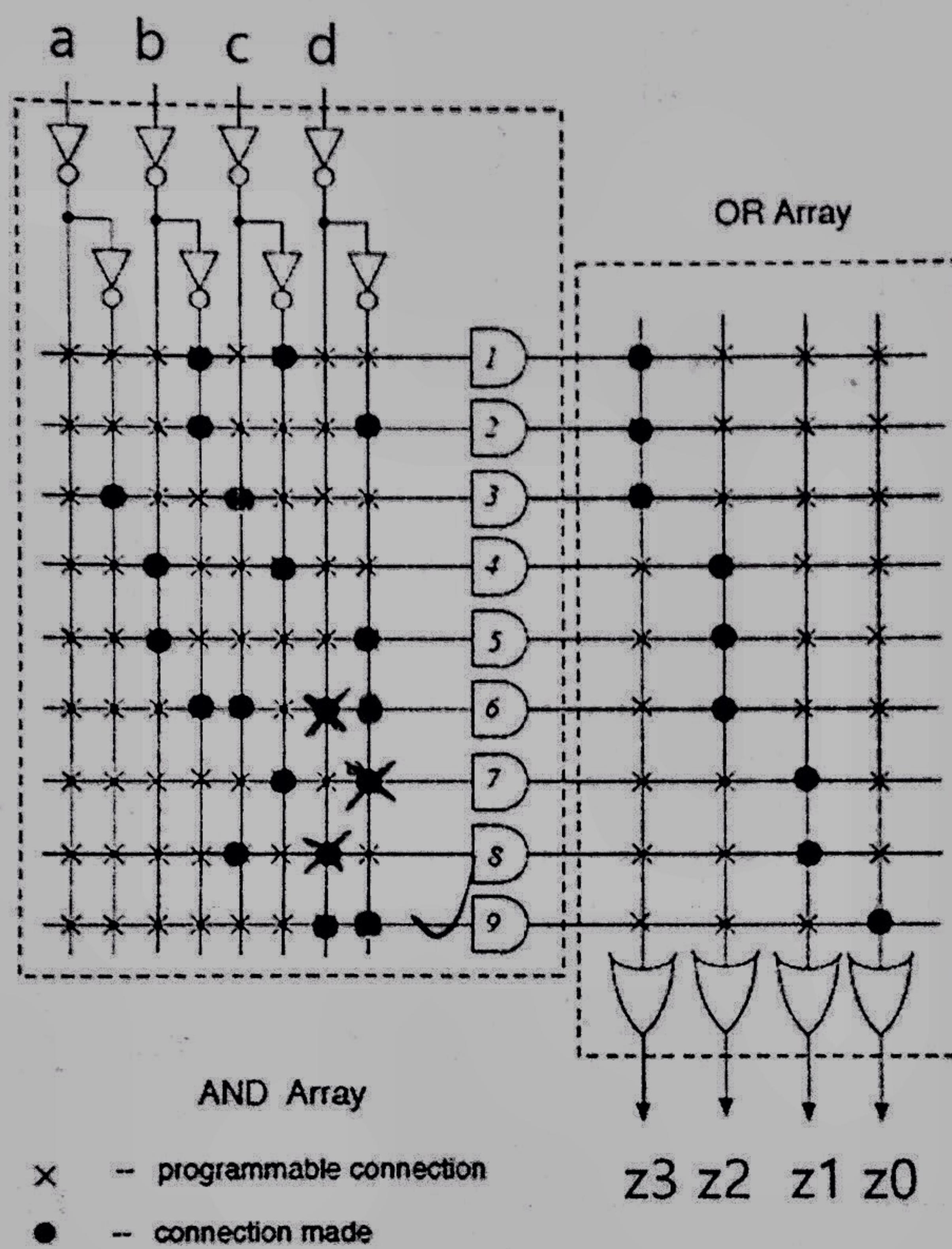
$$\begin{aligned}z_3 &= bc + bd + ac' \\z_2 &= b'c + b'd + bc'd \\z_1 &= 1 \\z_0 &= 0\end{aligned}$$



1. (7 points) Analyze the PLA shown above and show the output expressions.

$$z_3 = bc + bd + a$$

$$z_2 = b'c + b'd + bc'd'$$

$$z_1 = cd + c'd' \quad \checkmark$$

$$z_0 = d$$


2. (8 points) Is the PLA implementation correct? If not, find errors and show the correct implementation (cross out wrong connections and insert correct ones)

Not Correct!

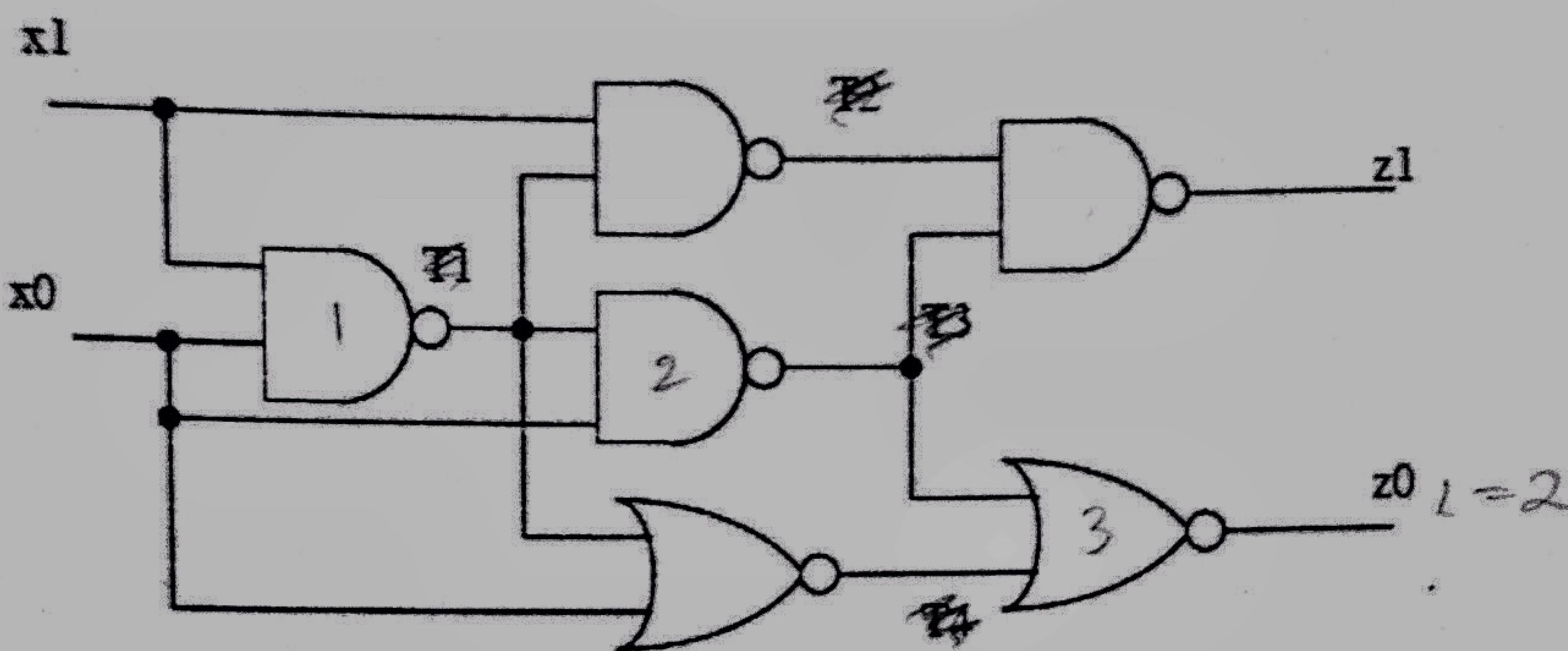Problem 5 (10 points)

0

Calculate the propagation delay  $t_{pLH}(z_0)$  when  $x_0$  changes. Assume that  $z_0$ 's load value is 2. Fill in the blanks below with the appropriate values. You don't need to fill all the blanks.



Gate Type	Fan-in	Propagation Delays (ns)		Load Factor I
		$t_{pLH}$	$t_{pHL}$	
NOT	1	$0.02 + 0.038L$	$0.05 + 0.017L$	1.0
AND	2	$0.15 + 0.037L$	$0.16 + 0.017L$	1.0
OR	2	$0.12 + 0.037L$	$0.20 + 0.019L$	1.0
NAND	2	$0.05 + 0.038L$	$0.08 + 0.027L$	1.0
NOR	2	$0.06 + 0.075L$	$0.07 + 0.016L$	1.0

Gate type & Fan-in

NAND 2 → NAND 2 → NOR 2 → \_\_\_\_\_ → \_\_\_\_\_ → \_\_\_\_\_

LH / HL      LH → HL → LH → \_\_\_\_\_ → \_\_\_\_\_ → \_\_\_\_\_

Output load L

3.0 → 2.0 → 2.0 → \_\_\_\_\_ → \_\_\_\_\_ → \_\_\_\_\_

Prop. Delay

$0.05 + 0.038(3.0)$  →  $0.08 + 0.027(2.0)$  →  $0.06 + 0.075(2.0)$  → ✓ → \_\_\_\_\_ → \_\_\_\_\_

### Problem 6 (15 points)

A gate G is defined by the following expression

15

$$E(a, b, c, d) = cd + a'b'c' + a'b'd' + bcd' + ab'c'd$$

Show that gate G forms a universal set assuming that constants 1 and 0 are available.

Specify a pre-established universal set you are using in the proof, and explicitly show the implementation for each element in the set using gate G with 1 and/or 0 as needed. For example, you can assign  $a=0$  and  $b=1$  in the expression E.

$$c=0, d=0$$

$$E(a, b) = a'b' + a'b' = a'b' = (a+b)'$$

$$\boxed{\text{NOR Gate!} \rightarrow E(a, b, 0, 0) = \text{NOR}(a, b)}$$

{ NOR } is a universal set

Problem 7 (20 points)

18

For the switching function  $f(x_3, x_2, x_1, x_0)$ , we are given the information below for the dc-set and zero-set.

$$\begin{array}{c} 2 \\ 0 \ 0 \ 1 \ 0 \\ (x_3 + x_2 + x_1' + x_0)(x_3 + x_2' + x_1 + x_0') \end{array} \quad \begin{array}{c} 5 \\ 0 \ 1 \ 0 \ 1 \\ (x_3 + x_2' + x_1 + x_0')(x_3 + x_2' + x_1' + x_0) \end{array}$$


dc-set = (4, 15)  
zero-set = zero-set of function

$$(x_3' + x_2 + x_1 + x_0')(x_3' + x_2 + x_1' + x_0)(x_3' + x_2 + x_1' + x_0)(x_3' + x_2' + x_1 + x_0')$$

1. (2 points) Fill out the following K-map.

$$\begin{array}{c} 0 \ 1 \ 1 \ 0 \\ 6 \\ 10 \ 0 \ 1 \\ 9 \\ 10 \ 1 \ 0 \\ 11 \ 0 \ 1 \\ 13 \end{array}$$

		x <sub>0</sub>			
		1	1	1	0
x <sub>3</sub>		-	0	1	0
		1	0	-	1
		1	0	1	0

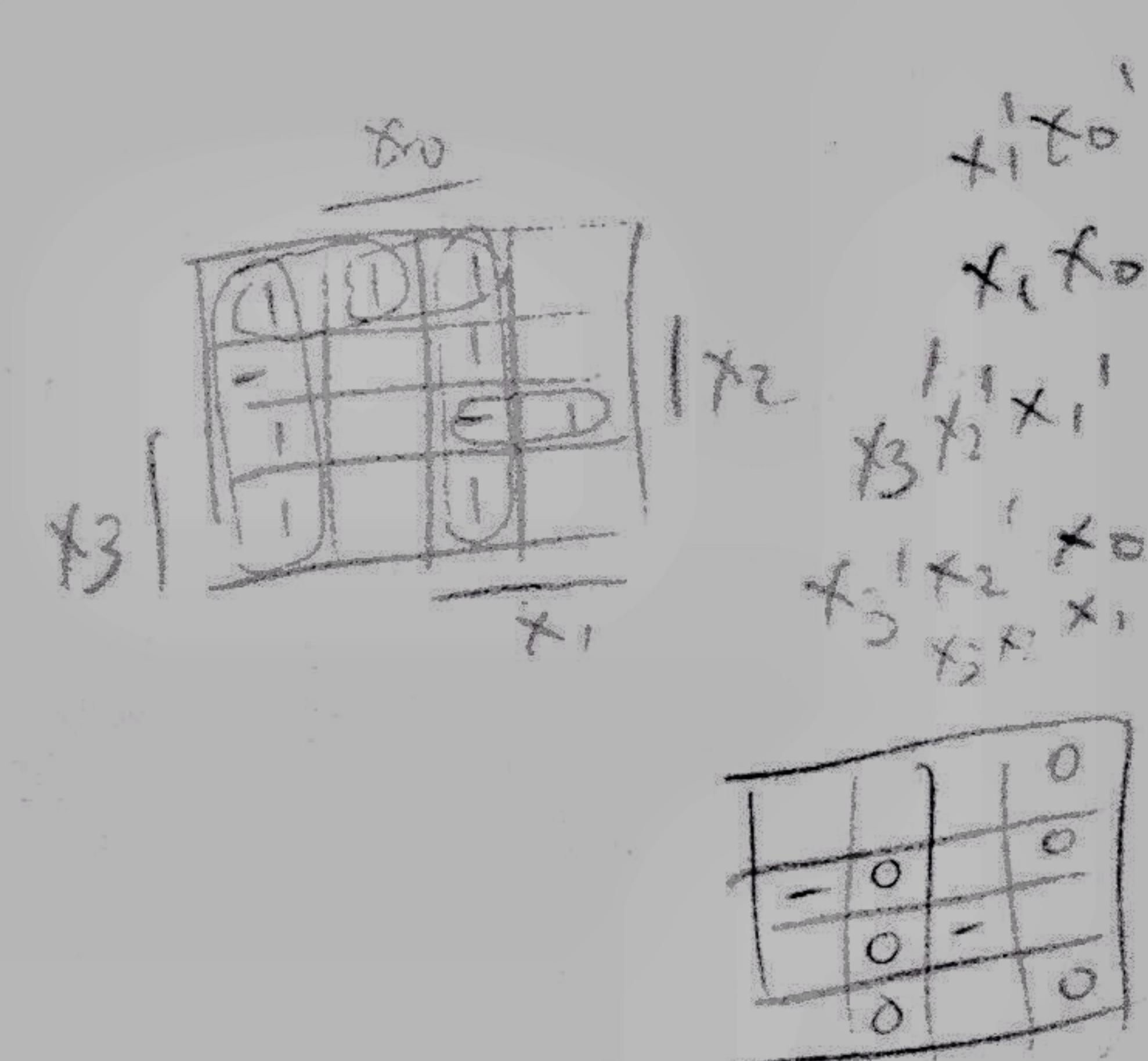

2. (4 points) Which of the given expressions are prime implicants of the function given above? Circle all that apply. Do not circle implicants that are not prime.

- (a)  $x_3x_1$
- (d)  $x_1'x_0'$
- (g)  $x_3'x_2'x_0$
- (j)  $x_3'x_2x_1'x_0$
- (b)  $x_3x_2'$
- (e)  $x_1x_0$
- (h)  $x_3x_2x_1$
- (k)  $x_3x_2'x_1x_0$
- (c)  $x_3'x_1$
- (f)  $x_3'x_2'x_1'$
- (i)  $x_3x_2x_0'$
- (l)  $x_3'x_2x_1x_0'$

3. (3 points) Write down the complete set of essential prime implicants.

$$x_1'x_0', x_1x_0, x_3x_2x_1$$

4. (2 points) Write down the minimal sum of products expressions for  $f$ . If there are multiple forms of minimal sum of products expressions, you only need to write down one of them.

$$x_1'x_0' + x_1x_0 + x_3x_2x_1 + x_3'x_2'x_1'$$

(4 points) Which of the given expressions are prime implicants of the function given above? Circle all that apply. Do not circle implicants that are not prime.

- (a)  $(x_3 + x_2' + x_1)$
- (b)  $(x_3' + x_2')$
- (c)  $(x_2' + x_1 + x_0')$

- (d)  $(x_3' + x_1 + x_0')$
- (e)  $(x_3 + x_2' + x_0)$
- (f)  $(x_3 + x_1' + x_0)$

- (g)  $(x_2 + x_1' + x_0)$
- (h)  $(x_3 + x_1 + x_0)$
- (i)  $(x_3' + x_2' + x_1)$

- (j)  $(x_3' + x_1')$
- (k)  $(x_3 + x_2 + x_1 + x_0')$
- (l)  $(x_3 + x_2' + x_1' + x_0)$


6. (3 points) Write down the complete set of essential prime implicants.

$$x_2 + x_1' + x_0, \quad x_3' + x_1 + x_0'$$

7. (2 points) Write down the minimal product of sums expressions for  $f$ . If there are multiple forms of minimal product of sums expressions, you only need to write down one of them.

$$(x_2 + x_1' + x_0)(x_3' + x_1 + x_0')(x_2' + x_1 + x_0')$$

0	0	0
0	0	0
0	0	0

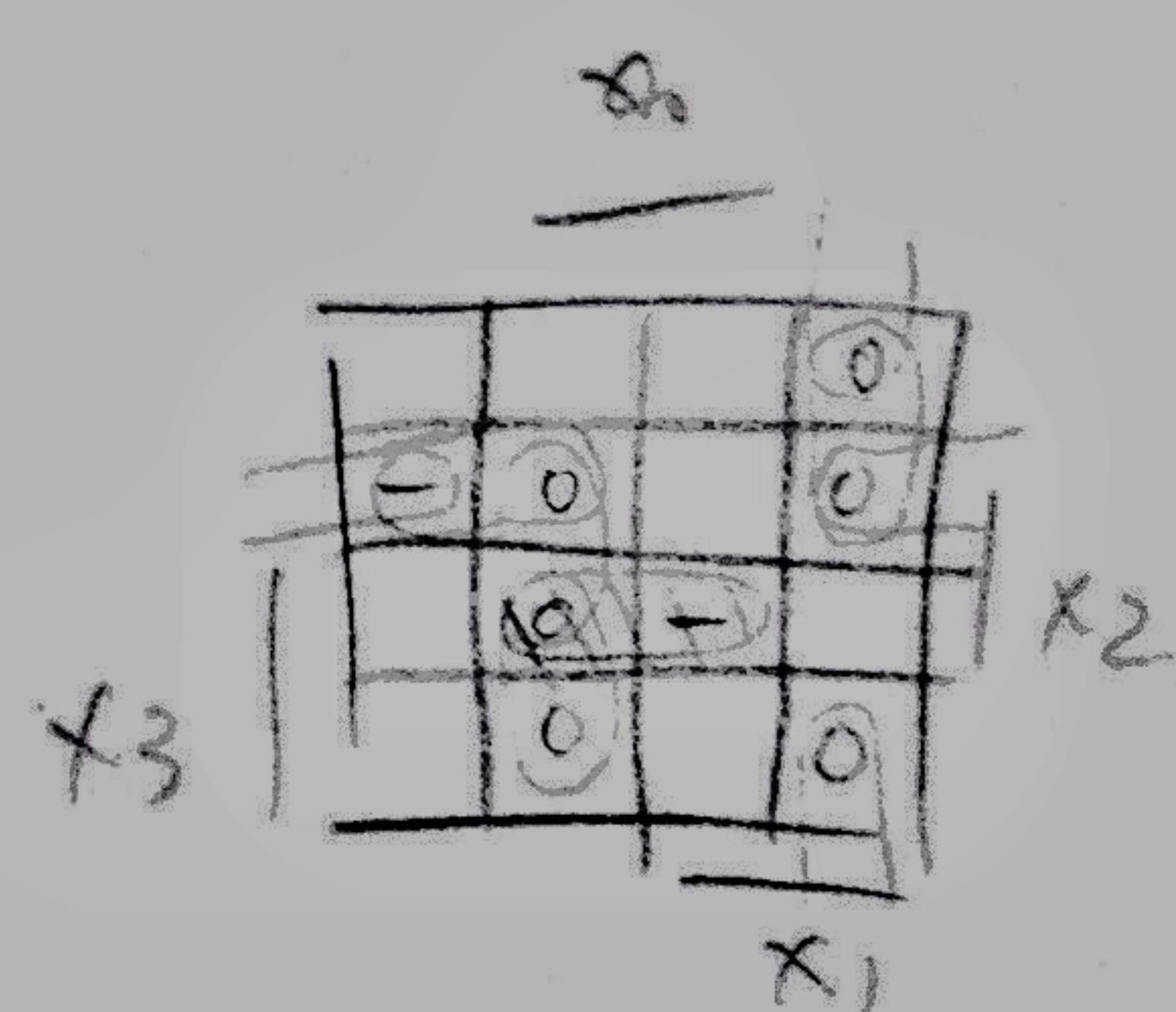

$$x_3 + x_1' + x_0 \quad \boxed{9}$$

$$x_2 + x_1' + x_0 \quad \boxed{A}$$

$$x_3 + x_2' + x_0 \quad \boxed{F}$$

$$x_3 + x_2 + x_1 \quad \boxed{E}$$

$$x_2' + x_1 + x_0' \quad \boxed{B}$$

~~$$x_3 + x_2 + x_1 \quad \boxed{D}$$~~

$$x_3' + x_1 + x_0' \quad \boxed{C}$$