

# [CS M51A FALL 15] MIDTERM EXAM

Date: 11/3/15

- The midterm is closed books and notes. Tablets and smartphone are not allowed.
- You can use calculators and have up to 2 sheets (= 4 pages) of summary notes.
- Please show all your work and write legibly, otherwise no partial credit will be given.
- This should strictly be your own work; any form of collaboration will be penalized.

Name : Yang Hoon Kang

Student ID : 904469956

Discussion 2B

Problem	Points	Score
1	15	15
2	15	17
3	10	3
4	15	11
5	10	10
6	15	15
7	20	20
Total	100	91

Problem 1 (15 points)

1. (6 points) Given the following simplification of a boolean expression, identify all right and wrong steps and briefly explain what is wrong for each error.

(For example, (10)  $\rightarrow$  (11) wrong application of the Identity rule, (11)  $\rightarrow$  (12) correct )

$$E_1(w, x, y, z) = (((w + x + x'y')y + z)' + wx' + y')' \quad (1)$$

$$= ((w + x + x'y')'y'z' + wx' + y')' \quad (2)$$

$$= ((w + x + x'y')'y'z' + (w + y')(x' + y'))' \quad (3)$$

$$= ((w + x' + y')'y'z' + (w + y')(x' + y'))' \quad (4)$$

$$= (w'xyy'z' + (w + y')(x' + y'))' \quad (5)$$

$$= (0 + (w + y')(x' + y'))' \quad (6)$$

$$= wy + xy \quad (7)$$

$$\begin{aligned} & (w+y)'+(x+y)' \\ & w'y + xy \end{aligned}$$

*(faint handwritten notes)*

(1)  $\rightarrow$  (2)

wrong application of DeMorgan's Law

(2)  $\rightarrow$  (3) correct

(3)  $\rightarrow$  (4) wrong application of ~~absorption~~ rule

simplification

(4)  $\rightarrow$  (5) correct

(5)  $\rightarrow$  (6) correct

(6)  $\rightarrow$  (7) wrong application of DeMorgan's Law

2. (5 points) Obtain the minimal sum of products form for  $E_2(w, x, y, z)$  using the identities of Boolean algebra. Show all the steps in your derivation.

$$E_2 = xy' + xzw + yw$$

$$xzw = xzwy' + xzwy$$


$$E_2 = xy' + xzwy' + xzwy + yw$$

$$E_2 = (xy') + (xy')zw + (yw) + (yw)xz$$

$$E_2 = xy' + yw$$




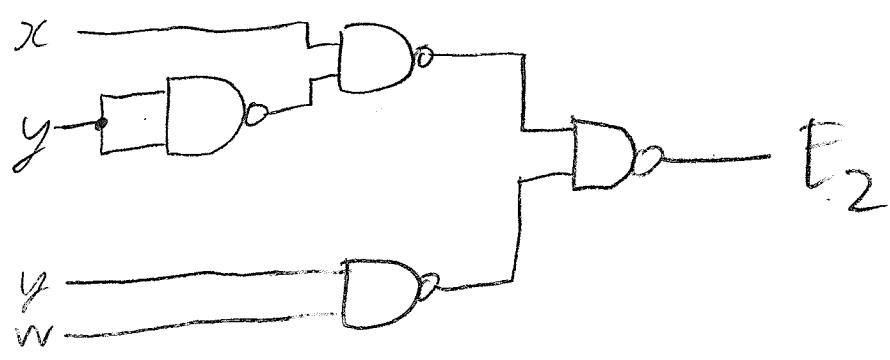3. (4 points) Using the expression obtained for  $E_2$  from the previous step, obtain the NAND network that uses ONLY NAND gates. Inverted inputs are not available, and no constant inputs are allowed.



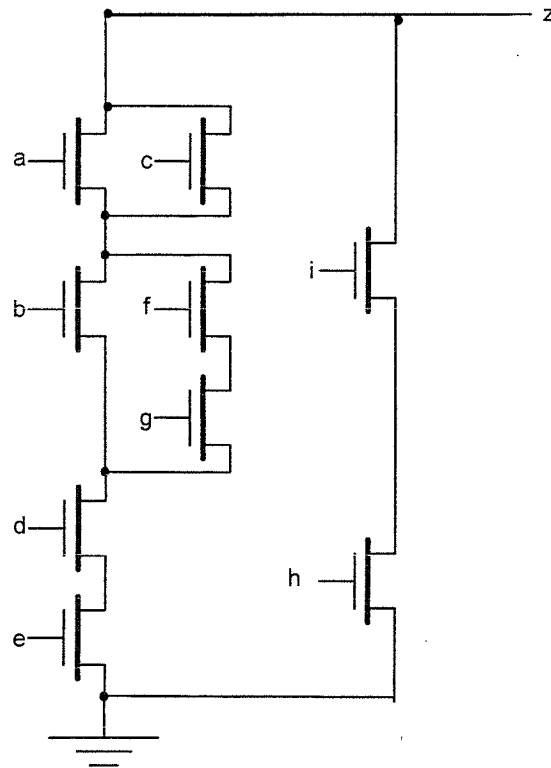Problem 2 (15 points)

The following pull-down network is part of a complex CMOS gate that we want to implement.



1. (8 points) (a) Write the expression for the pull-down network.

Pull-down network expression :  $z' = ((a+c)(b+fg)de) + ih$




- (b) Obtain the expression for the corresponding pull-up network.

Pull-up network expression :  $z = (a'c' + b'(f'+g') + d'+e')(i'+h')$


$$\begin{aligned}
 & ((a+c)(b+fg)de) + ih \\
 &= ((a+c)(b+fg)de)'(i+h) \\
 &= (a+c)' + (b+fg)' + d'+e' (i'+h) \\
 &= (a'c' + b'(f'+g') + d'+e')(i'+h)
 \end{aligned}$$

(c) Draw the pull-up network.

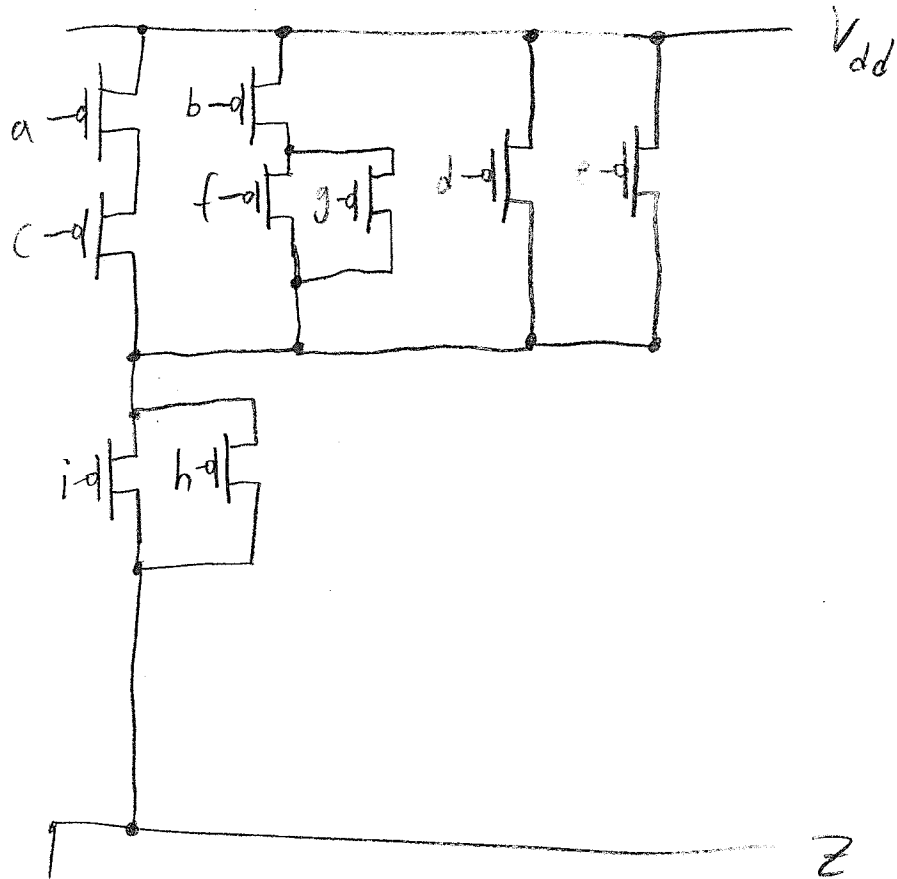

2. (7 points) Draw a CMOS network that implements  $f(x,y) = xy' + x'y$  (2-input XOR).  $x'$  and  $y'$  are not available as inputs. Do not use transmission gates. How many transistors does your solution have?  
 OPTIONAL: If you find another solution with fewer transistors, you get 3 extra points. Show your reduced design and explain why it works.

$$f' = (xy' + x'y)' = xy + x'y'$$

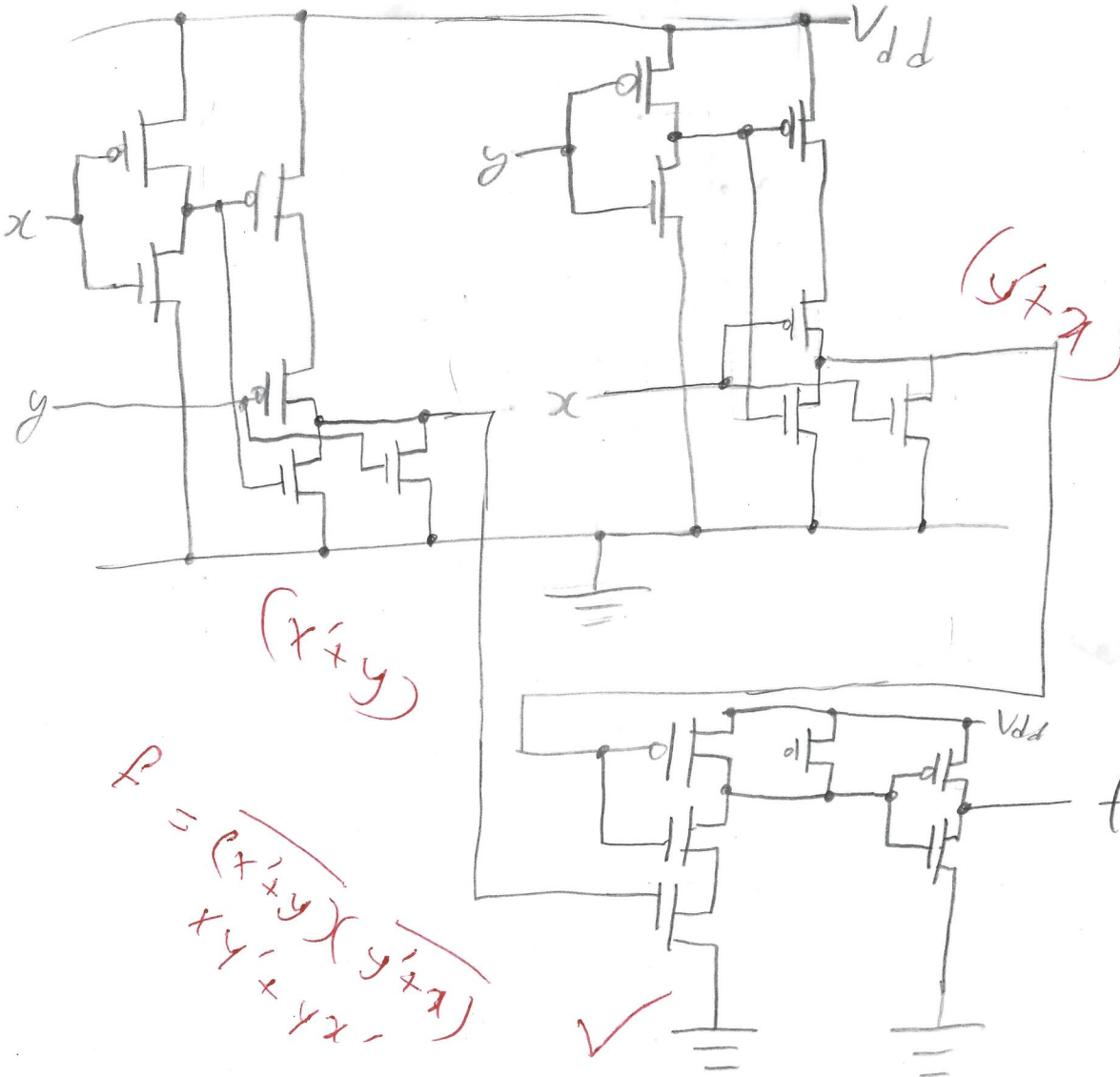

this uses 18 transistors

$$f = \overline{(x+y)(x+y)}$$

$$= \overline{xy + xy + xy + xy}$$

$$= \overline{xy + xy}$$

You could also get a 14 transistor solution:

- $xy$  takes 6
- $x'y'$  takes 4
- $(xy + x'y)'$  takes 4

Problem 3 (10 points)

3

1. (5 points) A 12-bit vector represents a set of positive integers  $\{0, \dots, N\}$ . Which of the following coding alternatives

- (a) BCD  $2^{12} - 1$
- (b) 2421 code (a decimal code)  $10^3 - 1$
- (c) Excess-3 code (a decimal code)  $10^3 - 1$
- (d) Octal  $8^{12} - 1$
- (e) Binary  $2^{12} - 1$

provides the largest range? Why? (Give N for each case).

Octal in this case provides the largest range.

2. (5 points) Let  $a = (101110010110)$  and  $b = (001110110101)$ . If  $a$  represents a number in the Excess-3 code and  $b$  in the binary code, what is the value in decimal of their sum  $a + b$ ? Show all your work.

$a$  in binary = 101110010110  
 $b$  = 001110110101  


---

 111101001000  
 1109876543210

$2^{11} + 2^{10} + 2^9 + 2^8 + 2^6 + 2^3$   
 2048 1024 512 256 64 8

23  
 2048  
 1024  
 512  
 256  
 64  
 8  


---


 3912

3912 X

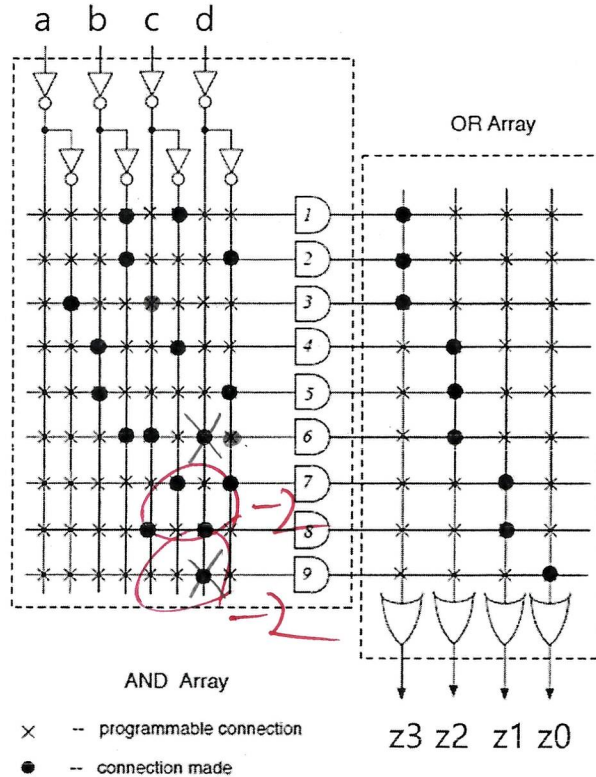Problem 4 (15 points)

We would like to verify that the PLA implementation shown here implements the following switching functions:

$$\begin{aligned} z_3 &= bc + bd + ac' \\ z_2 &= b'c + b'd + bc'd \\ z_1 &= 1 \\ z_0 &= 0 \end{aligned}$$



1. (7 points) Analyze the PLA shown above and show the output expressions.

- term 1:  $bc$
- term 2:  $bd$
- term 3:  $a$
- term 4:  $b'c$
- term 5:  $b'd$
- term 6:  $b'c'd'$
- term 7:  $cd$
- term 8:  $c'd'$
- term 9:  $d'$

$$\begin{aligned} z_3 &= bc + bd + a \\ z_2 &= b'c + b'd + bc'd' \\ z_1 &= cd + c'd' \neq 1 \\ z_0 &= d' \quad \checkmark \end{aligned}$$


2. (8 points) Is the PLA implementation correct? If not, find errors and show the correct implementation (cross out wrong connections and insert correct ones)



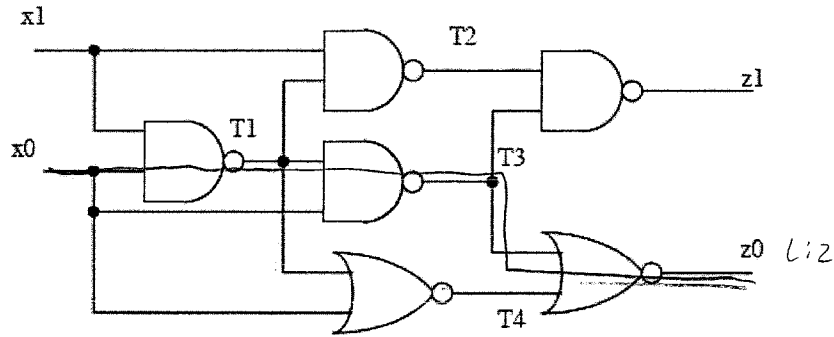Problem 5 (10 points)

10

Calculate the propagation delay  $t_{pLH}(z0)$  when  $x0$  changes. Assume that  $z0$ 's load value is 2. Fill in the blanks below with the appropriate values. You don't need to fill all the blanks.



Gate Type	Fan-in	Propagation Delays (ns)		Load Factor $I$
		$t_{pLH}$	$t_{pHL}$	
NOT	1	$0.02 + 0.038L$	$0.05 + 0.017L$	1.0
AND	2	$0.15 + 0.037L$	$0.16 + 0.017L$	1.0
OR	2	$0.12 + 0.037L$	$0.20 + 0.019L$	1.0
NAND	2	$0.05 + 0.038L$	$0.08 + 0.027L$	1.0
NOR	2	$0.06 + 0.075L$	$0.07 + 0.016L$	1.0

Gate type & Fan-in NAND2 → NAND2 → NOR2 → \_\_\_\_\_ → \_\_\_\_\_ → \_\_\_\_\_

LH / HL LH → HL → LH → \_\_\_\_\_ → \_\_\_\_\_ → \_\_\_\_\_

Output load L 3 → 2 → 2 → \_\_\_\_\_ → \_\_\_\_\_ → \_\_\_\_\_

Prop. Delay  $0.05 + 0.038 \cdot 3$  →  $0.08 + 0.027 \cdot 2$  →  $0.06 + 0.075 \cdot 2$  → \_\_\_\_\_ → \_\_\_\_\_ → \_\_\_\_\_ ✓

• Problem 6 (15 points)

A gate G is defined by the following expression


$$E(a, b, c, d) = cd + a'b'c' + a'b'd' + bcd' + ab'c'd$$

Show that gate G forms a universal set assuming that constants 1 and 0 are available.

Specify a pre-established universal set you are using in the proof, and explicitly show the implementation for each element in the set using gate G with 1 and/or 0 as needed. For example, you can assign  $a=0$  and  $b=1$  in the expression E.

I will be using the NOR universal set

I use k-maps to simplify E:

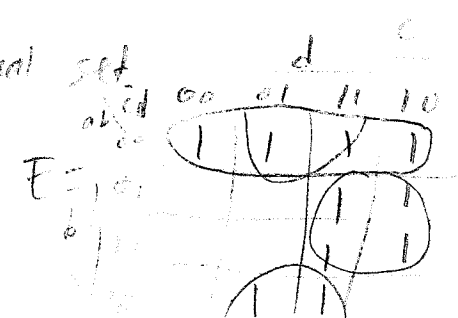

$$E = a'b' + b'd + bc$$

$$\begin{aligned} E(a, b, 0, 0) &= a'b' + b' \cdot 0 + b \cdot 0 \\ &= a'b' = (a+b)' = a \text{ NOR } b \end{aligned}$$

70

Problem 7 (20 points)

For the switching function  $f(x_3, x_2, x_1, x_0)$ , we are given the information below for the dc-set and zero-set.

dc-set = (4, 15)

zero-set = zero-set of function

$(x_3 + x_2 + x_1' + x_0)(x_3 + x_2' + x_1 + x_0')(x_3 + x_2' + x_1' + x_0)(x_3' + x_2 + x_1 + x_0')(x_3' + x_2 + x_1' + x_0)(x_3' + x_2' + x_1 + x_0')$

1. (2 points) Fill out the following K-map.

	00	01	11	10	
	$x_0$				
00	1	1	1	0	$x_2$
01	d	0	1	0	
11	1	0	d	1	
10	1	0	1	0	
		$x_1$			

PI:  $x_1 x_0'$

2. (4 points) Which of the given expressions are prime implicants of the function given above? Circle all that apply. Do not circle implicants that are not prime.

- (a)  $x_3 x_1$
- (b)  $x_3 x_2'$
- (c)  $x_3' x_1$
- (d)  $x_1' x_0'$
- (e)  $x_1 x_0$
- (f)  $x_3' x_2' x_1'$
- (g)  $x_3' x_2' x_0$
- (h)  $x_3 x_2 x_1$
- (i)  $x_3 x_2 x_0'$
- (j)  $x_3' x_2 x_1' x_0$
- (k)  $x_3 x_2' x_1 x_0$
- (l)  $x_3' x_2 x_1 x_0'$

3. (3 points) Write down the complete set of essential prime implicants.

EPI:  $x_1' x_0'$ ,  $x_1 x_0$ ,  $x_3 x_2 x_0'$

4. (2 points) Write down the minimal sum of products expressions for  $f$ . If there are multiple forms of minimal sum of products expressions, you only need to write down one of them.

$f = x_1' x_0' + x_1 x_0 + x_3 x_2 x_0' + x_3' x_2' x_0$

5. (4 points) Which of the given expressions are prime implicants of the function given above? Circle all that apply. Do not circle implicants that are not prime.

- (a)  $(x_3 + x_2' + x_1)$       (d)  $(x_3' + x_1 + x_0')$       (g)  $(x_2 + x_1' + x_0)$       (j)  $(x_3' + x_1')$   
 (b)  $(x_3' + x_2')$       (e)  $(x_3 + x_2' + x_0)$       (h)  $(x_3 + x_1 + x_0)$       (k)  $(x_3 + x_2 + x_1 + x_0')$   
 (c)  $(x_2' + x_1 + x_0')$       (f)  $(x_3 + x_1' + x_0)$       (i)  $(x_3' + x_2' + x_1)$       (l)  $(x_3 + x_2' + x_1' + x_0)$

6. (3 points) Write down the complete set of essential prime implicants.

EPI:  $(x_3' + x_1 + x_0')$ ,  $(x_2' + x_1 + x_0')$ ,  $(x_3 + x_1' + x_0)$ ,  $(x_2 + x_1' + x_0)$

7. (2 points) Write down the minimal product of sums expressions for  $f$ . If there are multiple forms of minimal product of sums expressions, you only need to write down one of them.

$f = (x_3' + x_1 + x_0')(x_2' + x_1 + x_0')(x_3 + x_1' + x_0)(x_2 + x_1' + x_0)$

$x_0$

	1	1	1	0
$x_3$	d	0	1	0
$x_2$	1	0	d	1
$x_1$	1	0	1	0

$x_3' + x_1 + x_0'$        $x_2' + x_1 + x_0'$