

# [CS M51A FALL 15] SOLUTIONS FOR MIDTERM EXAM

Date: 11/3/15

---

## Problem 1 (15 points)

1. (6 points) Given the following simplification of a boolean expression, identify all right and wrong steps and briefly explain what is wrong for each error.  
(For example, (10)  $\rightarrow$  (11) wrong application of the Identity rule, (11)  $\rightarrow$  (12) correct )

$$E_1(w, x, y, z) = (((w + x + x'y')y + z)' + wx' + y')' \quad (1)$$

$$= ((w + x + x'y')'y'z' + wx' + y')' \quad (2)$$

$$= ((w + x + x'y')'y'z' + (w + y')(x' + y'))' \quad (3)$$

$$= ((w + x' + y')'y'z' + (w + y')(x' + y'))' \quad (4)$$

$$= (w'xyy'z' + (w + y')(x' + y'))' \quad (5)$$

$$= (0 + (w + y')(x' + y'))' \quad (6)$$

$$= wy + xy \quad (7)$$

### *Solution*

- (1)  $\rightarrow$  (2) wrong application of DeMorgan's Law  
(2)  $\rightarrow$  (3) correct  
(3)  $\rightarrow$  (4) wrong application of Simplification rule  
(4)  $\rightarrow$  (5) correct  
(5)  $\rightarrow$  (6) correct  
(6)  $\rightarrow$  (7) missing invert sign at wy, should be w'y
2. (5 points) Obtain the minimal sum of products form for  $E_2(w, x, y, z)$  using the identities of Boolean algebra. Show all the steps in your derivation.


$$E_2 = xy' + xzw + yw$$

### *Solution*

$$\begin{aligned} E_2(w, x, y, z) &= xy' + xzw + yw \\ &= xy' + x(y + y')zw + yw \\ &= xy' + xyzw + xy'zw + yw \\ &= xy'(1 + zw) + yw(xz + 1) \\ &= xy' + yw \end{aligned}$$

3. (4 points) Using the expression obtained for  $E_2$  from the previous step, obtain the NAND network that uses ONLY NAND gates. Inverted inputs are not available, and no constant inputs are allowed.

*Solution*

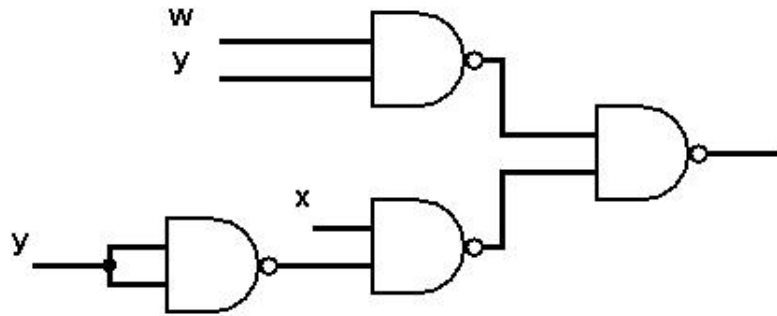

## Problem 2 (15 points)

The following pull-down network is part of a complex CMOS gate that we want to implement.

1. (8 points) (a) Write the expression for the pull-down network.


**Solution** Pull-down network expression :  $z' = ih + (a + c)(b + fg)de$

- (b) Obtain the expression for the corresponding pull-up network.

**Solution** Pull-down network expression :  $z = (i' + h')(a'c' + b'(f' + g') + d' + e')$

- (c) Draw the pull-up network.


**Solution**

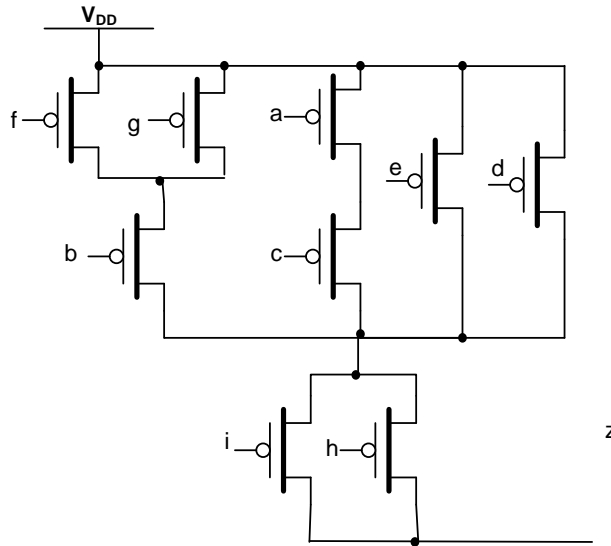

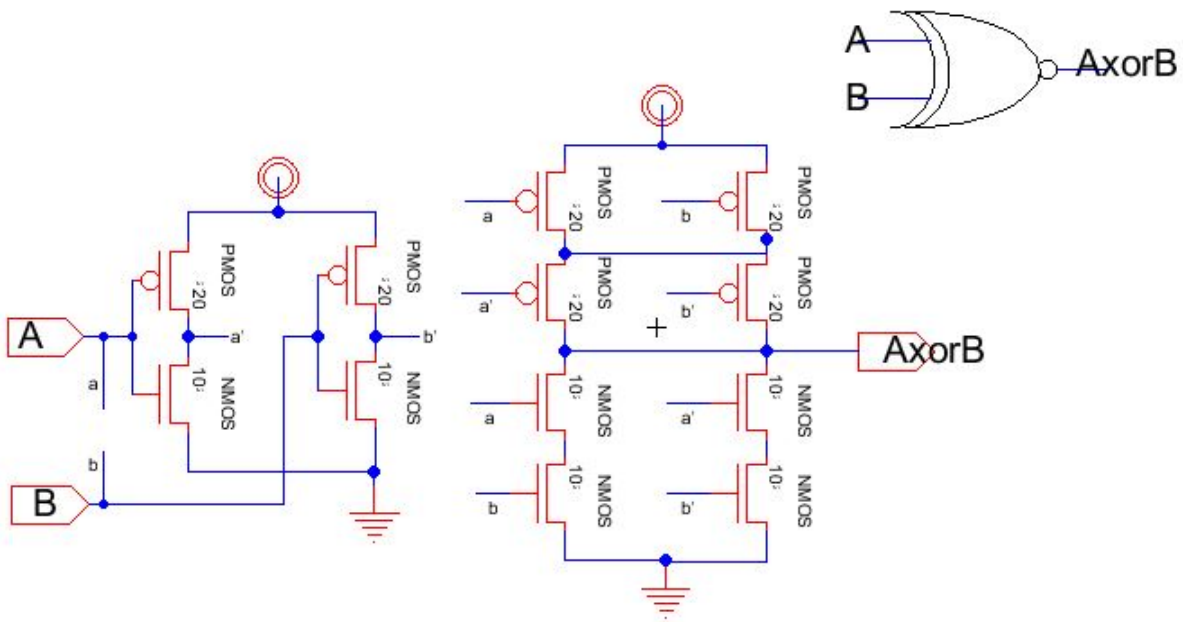
2. (7 points) Draw a CMOS network that implements  $f(x,y) = xy' + x'y$  (2-input XOR).  $x'$  and  $y'$  are not available as inputs. Do not use transmission gates. How many transistors does your solution have?

OPTIONAL: If you find another solution with fewer transistors, you get 3 extra points. Show your reduced design and explain why it works. **Solution**

If implemented correctly with two inverters and a XOR gate with a total of 12 transistors, you get 7 points.



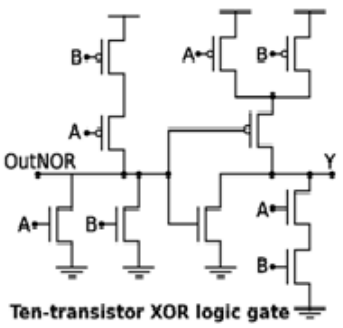but the minimum number of transistors is 10. Using boolean algebra:  
 The pull-down network expression is:  $(XNOR)f' = x'y' + xy = (x + y)' + xy = NOR(x, y) + xy$   
 with this change, now pull-down network expression has no inverted input and has 10 transistors.



**Problem 3 (10 points)**

1. (5 points) A 12-bit vector represents a set of positive integers  $\{0, \dots, N\}$ . Which of the following coding alternatives provides the largest range? Why? (Give N for each case).

**Solution**

- (a) BCD: Max = 100110011001 = 999 → The range is 1,000
  - (b) 2421 code: Max = 111111111111 = 999 → The range is 1,000
  - (c) Excess-3 code: Max = 110011001100 = 999 → The range is 1,000
  - (d) Octal: Max = 111111111111 = 7777<sub>8</sub> = 4,095 → The range is 4,096
  - (e) Binary: Max = 111111111111 = 111111111111<sub>2</sub> = 2<sup>12</sup> - 1 = 4,095 → The range is 4,096
- Thus, the answer is Octal and Binary.

2. (5 points) Let  $a = (101110010110)$  and  $b = (001110110101)$ . If  $a$  represents a number in the Excess-3 code and  $b$  in the binary code, what is the value in decimal of their sum  $a + b$ ? Show all your work.

***Solution***

$$a = 101110010110 = 863$$


$$b = 001110110101_2 = 949$$

$$\text{Thus, } a + b = 863 + 949 = 1,812$$
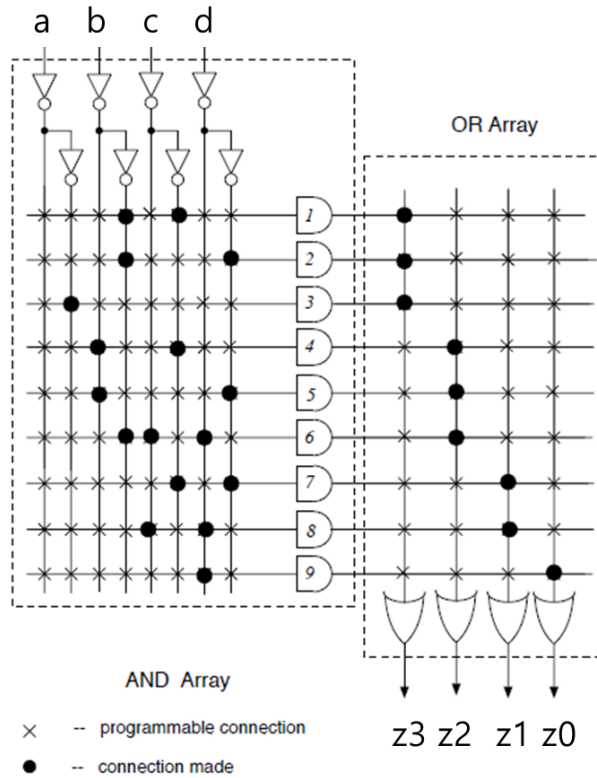
### Problem 4 (15 points)

We would like to verify that the PLA implementation shown here implements the following switching functions:

$$\begin{aligned} z3 &= bc + bd + ac' \\ z2 &= b'c + b'd + bc'd \\ z1 &= 1 \\ z0 &= 0 \end{aligned}$$




- (7 points) Analyze the PLA shown above and show the output expressions.

*Solution*

$$\begin{aligned} z3 &= bc + bd + a \\ z2 &= b'c + b'd + bc'd' \\ z1 &= cd + c'd' \\ z0 &= d' \end{aligned}$$


2. (8 points) Is the PLA implementation correct? If not, find errors and show the correct implementation (cross out wrong connections and insert correct ones)

*Solution*

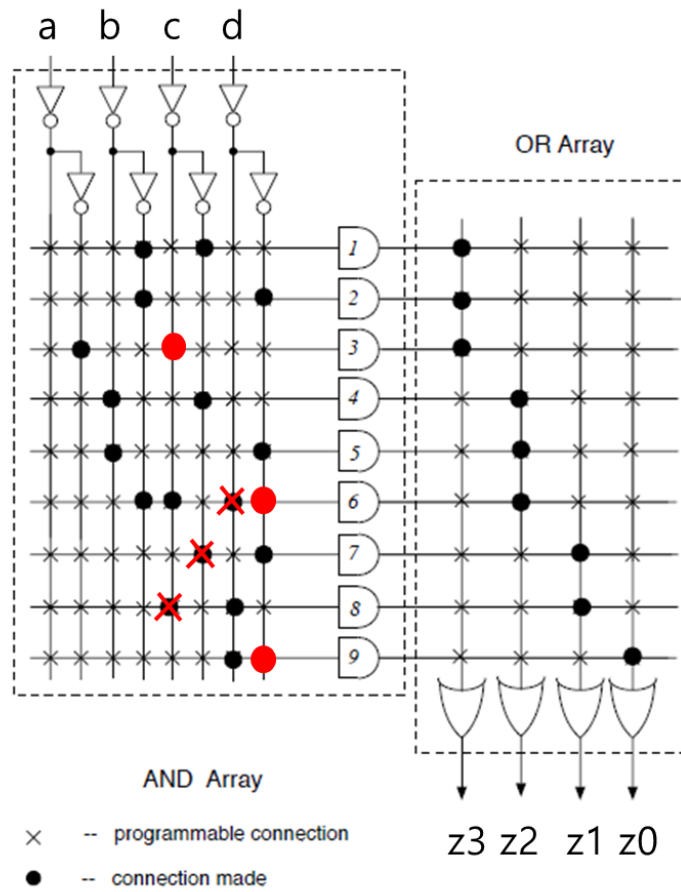
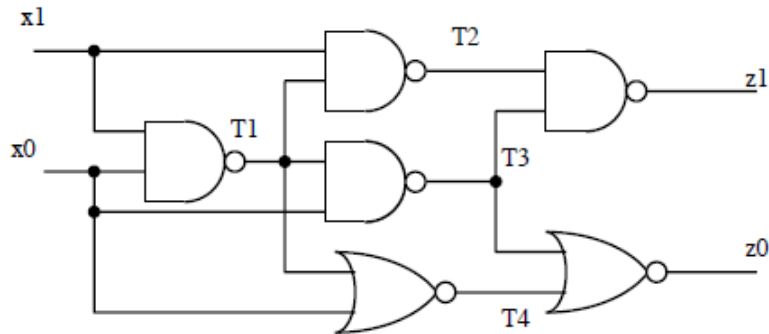
### Problem 5 (10 points)

Calculate the propagation delay  $t_{pLH}(z0)$  when  $x0$  changes. Assume that  $z0$ 's load value is 2. Fill in the blanks below with the appropriate values. You don't need to fill all the blanks.



Gate Type	Fan-in	Propagation Delays (ns)		Load Factor $I$
		$t_{pLH}$	$t_{pHL}$	
NOT	1	$0.02 + 0.038L$	$0.05 + 0.017L$	1.0
AND	2	$0.15 + 0.037L$	$0.16 + 0.017L$	1.0
OR	2	$0.12 + 0.037L$	$0.20 + 0.019L$	1.0
NAND	2	$0.05 + 0.038L$	$0.08 + 0.027L$	1.0
NOR	2	$0.06 + 0.075L$	$0.07 + 0.016L$	1.0

#### Solution

Gate type & Fan-in:            NAND2  $\rightarrow$  NAND2  $\rightarrow$  NOR2  
 LH / HL:                    LH  $\rightarrow$  HL  $\rightarrow$  LH  
 Output load L:             3.0  $\rightarrow$  2.0  $\rightarrow$  2.0  
 Prop. Delay:                 $0.05 + 0.038 \times 3.0 \rightarrow 0.08 + 0.027 \times 2.0 \rightarrow 0.06 + 0.075 \times 2.0$



**Problem 6 (15 points)**

A gate G is defined by the following expression

$$E(a, b, c, d) = cd + a'b'c' + a'b'd' + bcd' + ab'c'd$$

Show that gate G forms a universal set assuming that constants 1 and 0 are available.

Specify a pre-established universal set you are using in the proof, and explicitly show the implementation for each element in the set using gate G with 1 and/or 0 as needed. For example, you can assign a=0 and b=1 in the expression E.

**Solution** Plugging in different input combinations, we can find an input vector that implements a NOR function.

$$E(a, b, 0, 0) = a'b' + a'b' = a'b' = (a + b)'$$

Since {NOR} forms a universal set and we can use  $E(a, b, c, d)$  to implement any switching function and thus G is universal.

**Problem 7 (20 points)**

For the switching function  $f(x_3, x_2, x_1, x_0)$ , we are given the information below for the dc-set and zero-set.

$$\text{dc-set} = (4, 15)$$

$$\text{zero-set} = \text{zero-set of function}$$

$$(x_3 + x_2 + x_1' + x_0)(x_3 + x_2' + x_1 + x_0')(x_3 + x_2' + x_1' + x_0)(x_3' + x_2 + x_1 + x_0')(x_3' + x_2 + x_1' + x_0)(x_3' + x_2' + x_1 + x_0')$$

1. (2 points) Fill out the following K-map.

**Solution** The completed K-map is shown:

		$X_0$				
		1	1	1	0	
		-	0	1	0	
		1	0	-	1	$X_2$
$X_3$		1	0	1	0	
		$X_1$				

2. (4 points) Which of the given expressions are prime implicants of the function given above? Circle **all** that apply. Do not circle implicants that are not prime.

**Solution**  $x_1'x_0'$ ,  $x_1x_0$ ,  $x_3'x_2'x_1'$ ,  $x_3'x_2'x_0$ ,  $x_3x_2x_1$ ,  $x_3x_2x_0'$

3. (3 points) Write down the complete set of **essential** prime implicants.

**Solution**

$x_1'x_0'$  and  $x_1x_0$ .

4. (2 points) Write down the minimal sum of products expressions for  $f$ . If there are multiple forms of minimal sum of products expressions, you only need to write down one of them.

**Solution**  $x_1'x_0' + x_1x_0 + x_3'x_2'x_0 + x_3x_2x_0'$ .

5. (4 points) Which of the given expressions are prime implicants of the function given above? Circle **all** that apply. Do not circle implicants that are not prime.

**Solution**  $(x_3 + x_2' + x_1)$ ,  $(x_2' + x_1 + x_0')$ ,  $(x_3' + x_1 + x_0')$ ,  $(x_3 + x_2' + x_0)$ ,  $(x_3 + x_1' + x_0)$ ,  $(x_2 + x_1' + x_0)$

6. (3 points) Write down the complete set of **essential** prime implicants.

**Solution**  $(x_3' + x_1 + x_0')$  and  $(x_2 + x_1' + x_0)$

7. (2 points) Write down the minimal product of sums expressions for  $f$ . If there are multiple forms of minimal product of sums expressions, you only need to write down one of them.

**Solution**  $(x_3' + x_1 + x_0')(x_2' + x_1 + x_0')(x_2 + x_1' + x_0)(x_3 + x_1' + x_0)$ .