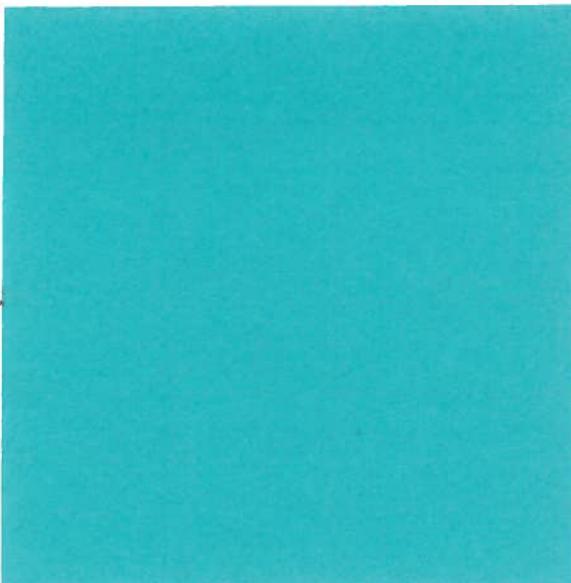


[CS M51A FALL 18] MIDTERM EXAM

Date: 10/30/18

- The midterm is closed book, and up to 4 sheets (= 8 pages) of summary notes are allowed. You can use a calculator but not smart phones.
- For multiple choice questions, wrong answers may have a negative score value so choose carefully. It is possible that questions can have multiple answers.
- Please show all your work and write legibly, otherwise no partial credit will be given.
- This should strictly be your own work; any form of collaboration will be penalized.

Na _____
Student _____



Problem	Points	Score
1	10	7
2	15	15
3	15	7
4	15	15
5	20	16
6	10	7
7	15	9
Total	100	76

94

Problem 1 (10 points)

1. (4 points) How many bits are required to encode a color spectrum capable of supporting 16 million colors using:
- Decimal digits in BCD

24 bits

~~✓~~

- Hexadecimal representation

6 hexadecimal digits ~~✓~~ 24 bits

Which representation is more efficient? Why?

Neither representation is more efficient because losing 7 possibilities per digit (~~16⁸ possibilities~~) is relatively insignificant compared to the overall 16 million possibilities.

2. (6 points) Fill in the missing entries in the table.

Radix	Digit vector \underline{x}	Value x in decimal
16	(5, 1, 7)	1303 /
8	(5, 1, 7)	335 /
7	(4, 5, 3, 2)	1640

Problem 2 (15 points)

$a + b = b + a$	$ab = ba$	Commutativity
$a + (bc) = (a + b)(a + c)$	$a(b + c) = (ab) + (ac)$	Distributivity
$a + (b + c) = (a + b) + c = a + b + c$	$a(bc) = (ab)c = abc$	Associativity
$a + a = a$	$aa = a$	Idempotency
$a + a' = 1$	$aa' = 0$	Complement
$1 + a = 1$	$0a = 0$	
$0 + a = a$	$1a = a$	Identity
$(a')' = a$	$a(a + b) = a$	Involution
$a + ab = a$	$a(a' + b) = ab$	Absorption
$a + a'b = a + b$	$(ab)' = a' + b'$	Simplification
$(a + b)' = a'b'$		DeMorgan's law

Given $E(a, b, c, d) = (ab + c)'(ac + (b' + c' + a'cd)' + a((b + c)(b + d) + c)',$ which of the following represents the same function as $E(a, b, c, d)?$ Show all your work.

1. $a + b + c + d'$
2. $a' + b + c$
3. $b + c' + d$

4. $a'b'c'd$

5. $\textcircled{ab'c'}$

6. $b'cd'$

$$\begin{aligned}
 &= ((a' + b')c') (ac + (bc (a + c' + d')) + a((b'c' + b'd')c')) \text{ Apply DeMorgan's Law} \\
 &\quad (a'c' + b'c') (ac + abc + bcd') + ac'b + ab'cd' \text{ Distributivity} \\
 &\quad \underbrace{\text{All terms cancel out due to } aa' = 0}_{\text{identity}}
 \end{aligned}$$

~~$abc' (1+0)$~~ identity

I showed work on back page

Problem 3 (15 points)

Show if the gate G, described by $G(x, y, z) = \text{one-set}\{3, 4, 6, 7\}$, can implement NOT and AND gates. Assume that 0 and 1 are available. If it can, then use G gates to implement the following expression and show the corresponding network of G gates

$$G = \text{Im}(0, 1, 2, 5) \quad \times \quad E(a, b, c) = (a + b')(b + c')$$

wrong expression

$$G(x, y, z) = x'y'z' + x'y'z + x'yz' + xy'z$$

$$G(1, y, z) = y'z$$

$$G(x, 1, z) = x'z'$$


$$G(x, y, 1) = x'y' + xy'$$

$$G(x, y, 0) = x'y' + x'y$$

Not: $G(1, y, 1) = y'$


AND:
$$\begin{aligned} & G(G(1, x, 1), 1, G(1, z, 1)) \\ &= G(x', 1, z') = xz \end{aligned}$$
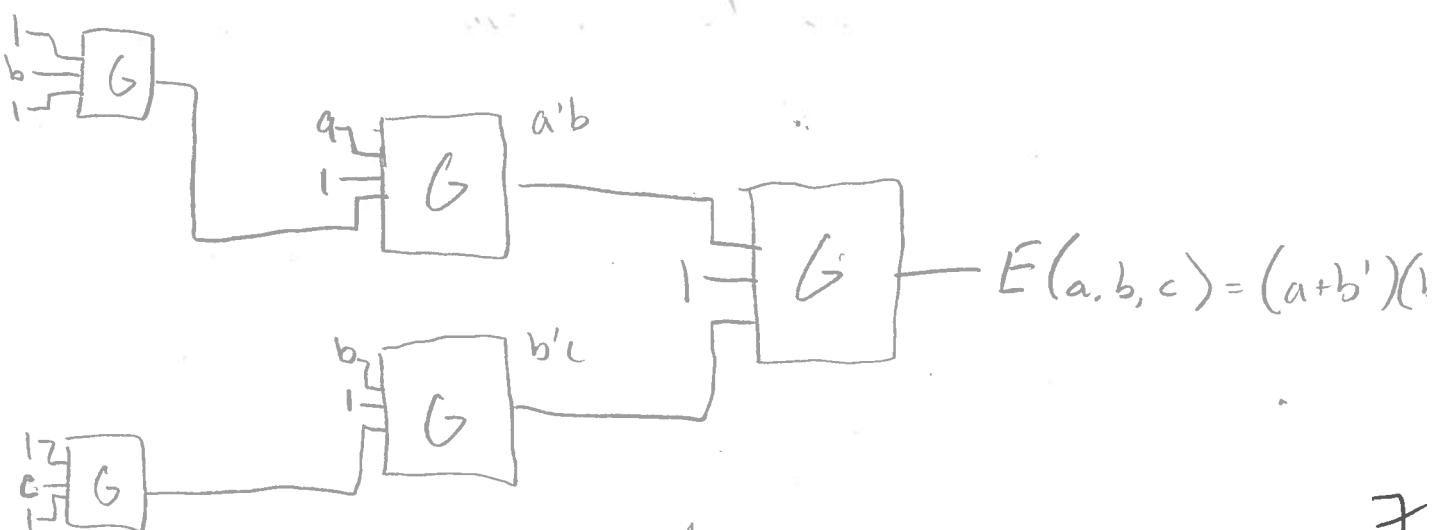
$$E(a, b, c) = G(G(a, 1, G(1, b, 1)), 1, G(b, 1, G(1, c, 1)))$$



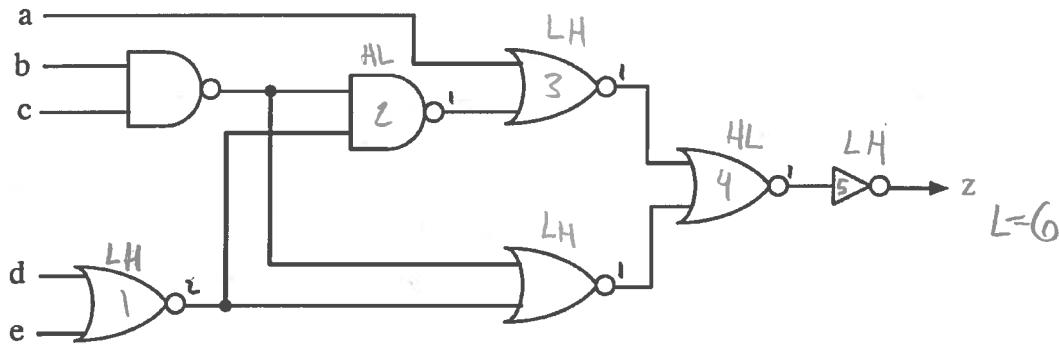Problem 4 (15 points)

With the help of the table below, determine the low to high propagation delay $t_{pLH}(d, z)$ of the output z of the network shown below. Assume the network output has a load of 6.



Gate Type	Fan-in	Propagation Delays (ns)		Load Factor
		t_{pLH}	t_{pHL}	
NOT	1	$0.02 + 0.038L$	$0.05 + 0.017L$	1.0
NAND	2	$0.05 + 0.038L$	$0.08 + 0.027L$	1.0
NOR	2	$0.06 + 0.075L$	$0.07 + 0.016L$	1.0

L	t_p	1	2	3	4	5
1	LH	2	$0.06 + 0.075(z)$			
2	HL	1	$0.08 + 0.027(1)$			
3	LH	1	$0.06 + 0.075(1)$			
4	HL	1	$0.07 + 0.016(1)$			
5	LH	6	$0.02 + 0.038(6)$			

$$t_{pLH}(d, z) = 0.786 \text{ ns}$$

15

Problem 5 (20 points)

Obtain a two-level gate network of the following system.

Inputs: $x, y \in \{0, 1, 2, 3\}$
 Outputs: $z \in \{0, 1, 2, 3\}$
 Function: $z = \{3xy + 1\} \bmod 4$

1. (2 points) Complete the switching table using binary encoding for all values.

$3xy$	x	y	x_1	x_0	y_1	y_0	z_1	z_0
0	0	0	0	0	0	0	0	1
	1	0	0	0	0	1	0	1
	2	0	0	1	0	0	0	1
	3	0	0	1	1	1	0	1
6	0	1	0	0	0	0	1	4
	1	0	1	0	0	1	0	0
	3	0	1	1	0	0	1	6
	6	0	1	1	1	0	1	7
	9	0	1	1	1	1	1	0
12	0	1	1	0	0	0	0	8
	1	1	0	0	1	1	1	9
	2	1	0	1	0	0	0	10
	18	1	0	1	1	1	1	11
18	0	1	1	0	0	0	0	12
	1	1	1	0	1	0	1	13
	18	2	1	1	1	0	1	14
	24	3	1	1	1	1	0	15



2. (5 points) Show the switching expressions of z_1 and z_0 in sum of minterms form.

$$Z_1 = x_1'x_0y_1y_0' + x_1'x_0y_1y_0 + x_1x_0y_1'y_0 + x_1x_0y_1'y_0 + x_1x_0y_1'y_0 + x_1x_0y_1'y_0'$$

$$Z_1 = \sum m(6, 7, 9, 11, 13, 14)$$

$$Z_0 = \sum m(0, 1, 2, 3, 4, 6, 8, 9, 10, 11, 12, 14, 15)$$

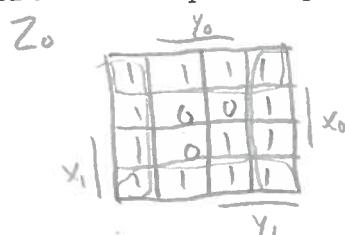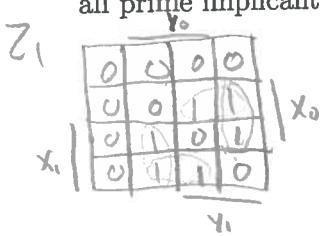3. (8 points) Show the minimal sum of products expressions of z_1 and z_0 . In each case, show a K-map, indicate all prime implicants, and all essential prime implicants. Show NAND-NAND networks.




$$Z_1 = x_0y_1y_0' + x_1'x_0y_1$$

$$+ x_1y_1'y_0 + x_1x_0'y_0$$

$$Z_0 = y_0' + x_0' + x_1y_1$$

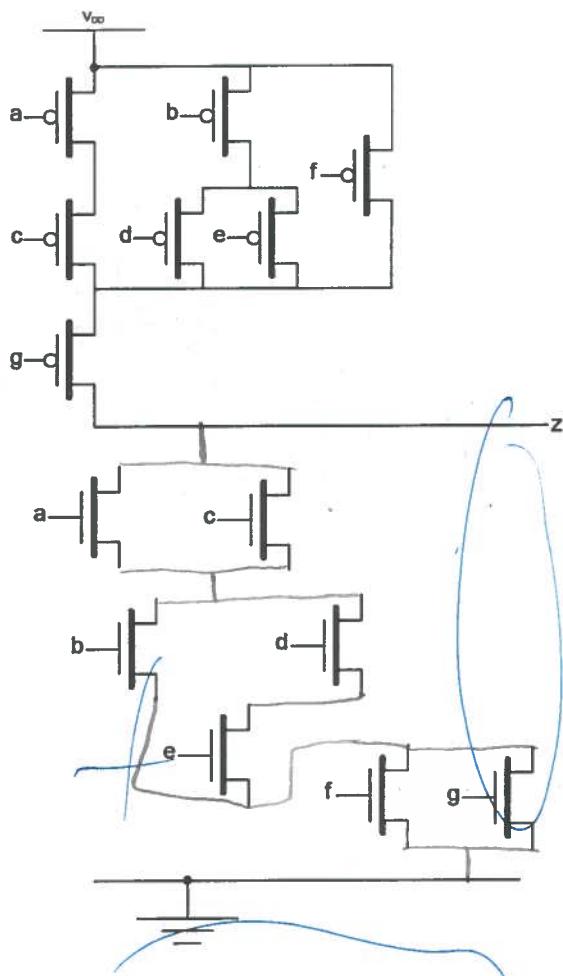Problem 6 (10 points)

We are given the following partial CMOS network.



1. (5 points)

$$Z = ((a+c)(b+de)f) + g$$

Write the expression for the pull-up network. From this, derive the expression for the pull-down network using switching algebra.

$$Z = (a'c' + b'(d+e) + f')g' = a'c'g' + b'd'g' + b'e'g' + f'g'$$


2. (5 points) Connect NMOS transistors to complete the circuit according to the pull-down expression. Please only add missing wires.

Handwritten notes:
 - A dashed line labeled 'a' connects to the drain of the first NMOS transistor.
 - A dashed line labeled 'g' connects to the drain of the last PMOS transistor.
 - A dashed line labeled 'g'' connects to the drain of the fifth NMOS transistor.

Problem 7 (15 points)

For $f(x_3, x_2, x_1, x_0) = (x_3 + x_2' + x_1 + x_0)(x_3 + x_2' + x_1' + x_0)(x_3' + x_2 + x_1 + x_0')(x_3' + x_2' + x_1 + x_0)(x_3' + x_2' + x_1 + x_0')(x_3' + x_2' + x_1' + x_0)$

- Fill out the following K-map.

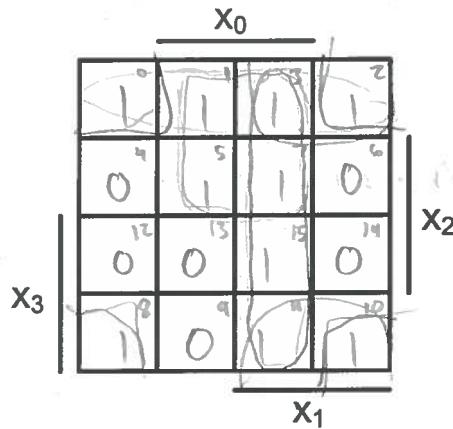

- Which of the given expressions are prime implicants of the function given above? Circle all that apply. Write down any prime implicants that are missing.

- (a) x_1
- (b) x_3x_1
- (c) $x_3'x_2'$
- (d) $x_3'x_1$
- (e) $x_3'x_0$
- (f) x_2x_1
- (g) $x_2'x_0$
- (h) x_1x_0
- (i) x_1x_0'
- (j) $x_3'x_2'x_1$
- (k) $x_2x_1x_0$
- (l) $x_3x_2x_1x_0$

$$x_2' x_0'$$

$$x_2' x_1$$

- Write down the complete set of essential prime implicants.

$$x_3'x_0, x_1x_0, x_2'x_0'$$

- Write the minimal sum of products expression for f . Is it unique?

$$f = x_3'x_0 + x_1x_0 + x_2'x_0'$$

This is unique.

Use of any other implicants would not qualify as the minimal sum of products.

5.3) Z1 prime Implicants essential prime implicants

$x_0 y_1 y_0'$

$x_0 y_1 y_0'$

$x_1' x_0 y_1$

$x_1' x_0 y_1$

$x_1 y_1' y_0$

$x_1 y_1' y_0$

$x_1 x_0' y_0$

$x_1 x_0' y_0$

Zc prime Implicants

y_0'



y_0'

x_0'

x_0'

$x_1 y_1$

$x_1 y_1$

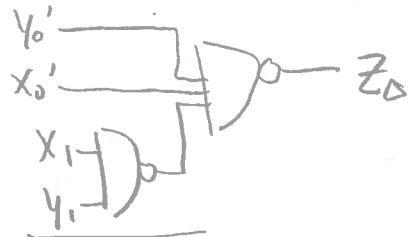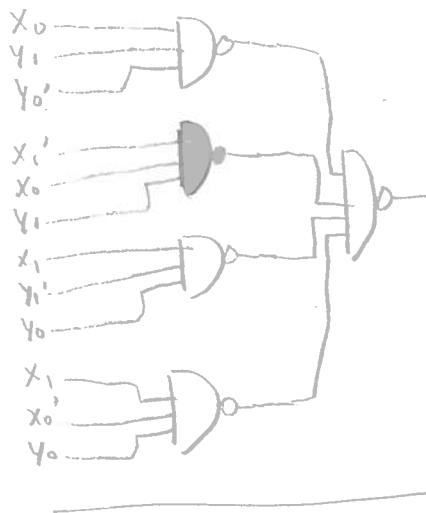

$$2) (ab+c)'(ac+(b'+c'+a'cd)') + a((b+c)(b+d)+c)' \quad \text{Given}$$

$$((ab)' \cdot c')(ac + ((b'+c')'(a'cd)')) + a(((b+c)(b+d))' \cdot c') \quad \text{DeMorgan's Law}$$

$$((a+b') \cdot c')(ac + ((bc)(a+c'+d'))) + a((b+c)' + (b+d)') \cdot c' \quad \text{DeMorgan's Law}$$

$$((a'+b') \cdot c')(ac + ((bc)(a+c'+d'))) + a((b'c') + (b'd')) \cdot c' \quad \text{DeMorgan's Law}$$

$$(a'c' + b'c')(ac + abc + bcc' + bcd') + a(c'c'b' + c'b'd') \quad \text{distributivity}$$

$$(a'c' + b'c')(ac + abc + 0 + bcd') + a(c'b' + c'b'd') \quad \text{Complement \& idempotency}$$

$$(a'c' + b'c')(ac + abc + bcd') + a(c'b' + c'b'd') \quad \text{Identity}$$

$$\begin{aligned} & a'ac'c + a'abc'c + abc'c d' + ab'cc' + abb'cc' + bb'cc'd' \\ & + ac'b'(1+d) \end{aligned} \quad \text{distributivity}$$

$$0 + 0 + 0 + 0 + 0 + ac'b'(1) \quad \text{Complement}$$

$$ac'b' \quad \text{identity}$$

$$ab'c' \quad \text{commutativity} \quad \blacksquare$$

