

# [CS M51A FALL 18] MIDTERM EXAM

Date: 10/30/18

- The midterm is closed book, and up to 4 sheets (= 8 pages) of summary notes are allowed. You can use a calculator but not smart phones.
- For multiple choice questions, wrong answers may have a negative score value so choose carefully. It is possible that questions can have multiple answers.
- Please show all your work and write legibly, otherwise no partial credit will be given.
- This should strictly be your own work; any form of collaboration will be penalized.

Name : \_\_\_\_\_

Student ID : \_\_\_\_\_

Problem	Points	Score
1	10	10
2	15	15
3	15	15
4	15	7
5	20	16
6	10	10
7	15	5
Total	100	78
	94	

### Problem 1 (10 points)

1. (4 points) How many bits are required to encode a color spectrum capable of supporting 16 million colors using:

- a. Decimal digits in BCD

10 colors for every 4 bits.

$$8 \cdot 4 = \boxed{32}$$

$$10^8 = 16 \text{ mil}$$

$$n = \log_2 16 \text{ mil} = 7.2 \rightarrow 8.$$

- b. Hexadecimal representation

$$16^n = 16,000,000$$

$\boxed{6 \text{ bits}}$

$$n = \log_{16} 16,000,000 = 5.98 \rightarrow 6$$

Which representation is more efficient? Why?

Hexadecimal  $\rightarrow$  more efficient because it requires 26 less bits.

2. (6 points) Fill in the missing entries in the table.

Radix	Digit vector $\underline{x}$	Value $x$ in decimal
16	(5, 1, 7)	1303
8	(5, 1, 7)	335
7	(9, 5, 3, 2)	1640

$$5 \cdot 16^2 + 1 \cdot 16^1 + 7 \cdot 16^0$$

$$5 \cdot 8^2 + 1 \cdot 8^1 + 7 \cdot 8^0$$

$$\begin{array}{r} 1640 \\ 7 \overline{)234} \\ 7 \overline{)33} \\ 7 \overline{)4} \end{array}$$

$\rightarrow 4532$  deck

$$4 \cdot 7^3 + 5 \cdot 7^2 + 3 \cdot 7 + 2.$$

## Problem 2 (15 points)

$a + b = b + a$	$ab = ba$	Commutativity
$a + (bc) = (a + b)(a + c)$	$a(b + c) = (ab) + (ac)$	Distributivity
$a + (b + c) = (a + b) + c = a + b + c$	$a(bc) = (ab)c = abc$	Associativity
$a + a = a$	$aa = a$	Idempotency
$a + a' = 1$	$aa' = 0$	Complement
$1 + a = 1$	$0a = 0$	
$0 + a = a$	$1a = a$	Identity
$(a')' = a$		Involution
$a + ab = a$	$a(a + b) = a$	Absorption
$a + a'b = a + b$	$a(a' + b) = ab$	Simplification
$(a + b)' = a'b'$	$(ab)' = a' + b'$	DeMorgan's law

Given  $E(a, b, c, d) = (ab + c)'(ac + (b' + c' + a'cd)') + a((b + c)(b + d) + c)',$  which of the following represents the same function as  $E(a, b, c, d)?$  Show all your work.

1.  $a + b + c + d'$

4.  $a'b'c'd$

2.  $a' + b + c$

5.  $\boxed{ab'c'}$

3.  $b + c' + d$

6.  $b'cd'$

$$E(a, b, c, d) = (ab + c)'(ac + (b' + c' + a'cd)') + a((b + c)(b + d) + c)' \quad (2)$$

(1)

$$(ab + c)'(ac + (b' + c' + a'cd)')$$

$$((a' + b')c') (ac + bc(a + c' + d')) \text{ DeMorgan}$$

$$(a'c' + b'c') (ac + abc + bcc' + bcd') \text{ distribution}$$

$$\cancel{a'c'}ac + \cancel{a'c'}abc + \cancel{a'c'}bcd' + \cancel{b'c'}ac + \cancel{b'c'}abc + \cancel{b'c'}bcd' \text{ distribution}$$

$$= 0 \text{ complete simplification}$$

(2)

$$a((b + c)(b + d) + c)'$$

$$a((b'c' + b'd')c') \text{ DeMorgan}$$

$$a(b'c'(c' + d')) \text{ distribution}$$

$$a(b'(c' + c'd')) \text{ distribution}$$

$$a(b'(c' + c'd')) \text{ Idempotency}$$

$$ab'c' + ab'c'd' \text{ distribution}$$

$$ab'c'(1 + d') \text{ associativity}$$

$$= ab'c'$$

$$\boxed{E(a, b, c, d) = ab'c'}$$

### Problem 3 (15 points)

Show if the gate G, described by  $G(x, y, z) = \text{one-set}\{3, 4, 6, 7\}$ , can implement NOT and AND gates. Assume that 0 and 1 are available. If it can, then use G gates to implement the following expression and show the corresponding network of G gates

$\overline{z}$	$\overline{x}$	$\overline{y}$	$\overline{G}$
0	0	(1)	0
1	0	(1)	1

$$E(a, b, c) = (a + b')(b + c')$$

$$G(x, y, z) = yz + xz'$$


NOT

$$G(1, 0, a) = 0 + 1a' = a'$$

AND

$$G(0, a, b) = ab + 0 = ab$$

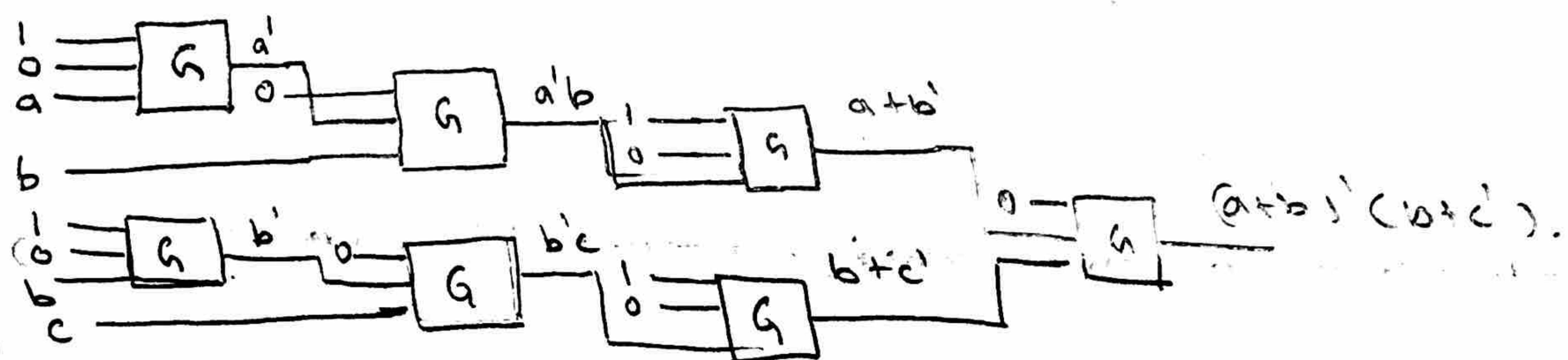
$$\begin{aligned} E(a, b, c) &= ((a+b')')'((b+c')')' \\ &= (a'b)'(b'c)' \end{aligned}$$



15
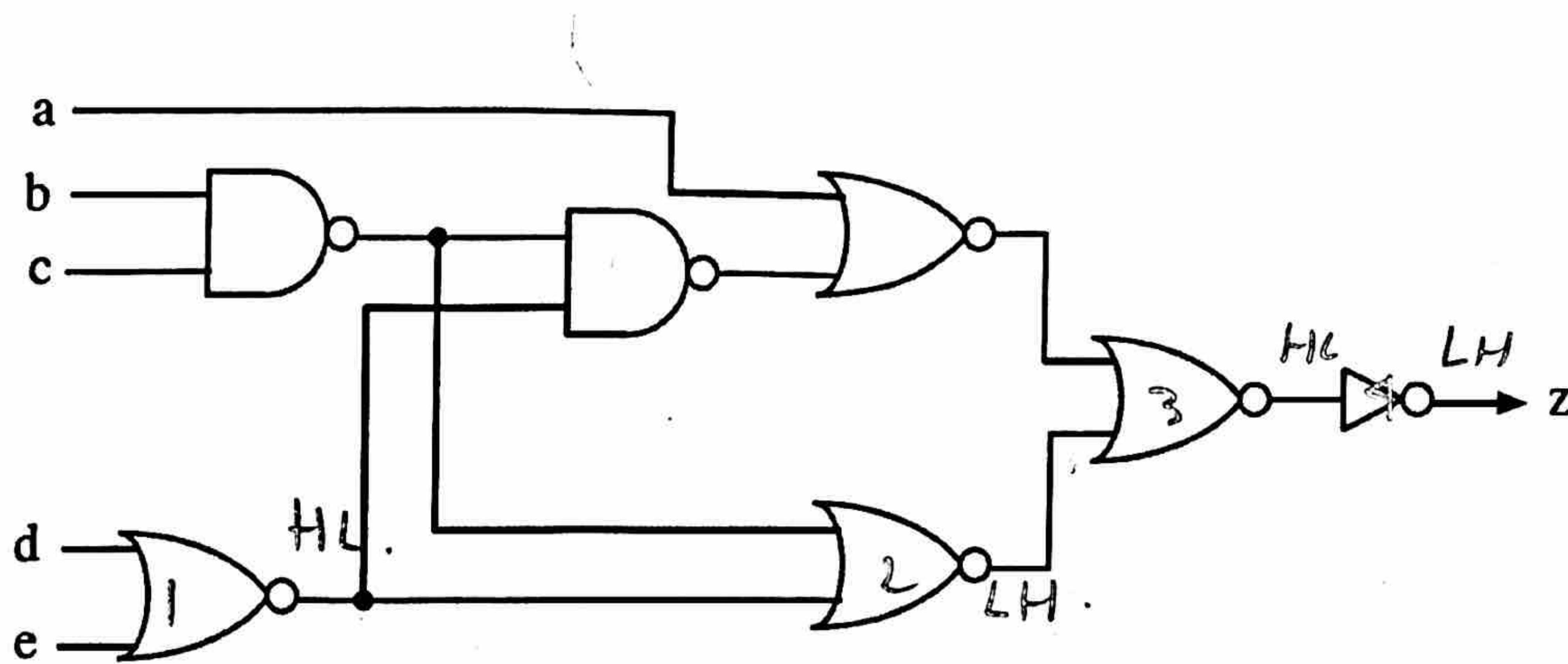
### Problem 4 (15 points)

With the help of the table below, determine the low to high propagation delay  $t_{pLH}(d, z)$  of the output  $z$  of the network shown below. Assume the network output has a load of 6.



Gate Type	Fan-in	Propagation Delays (ns)		Load Factor
		$t_{pLH}$	$t_{pHL}$	
NOT	1	$0.02 + 0.038L$	$0.05 + 0.017L$	1.0
NAND	2	$0.05 + 0.038L$	$0.08 + 0.027L$	1.0
NOR	2	$0.06 + 0.075L$	$0.07 + 0.016L$	1.0

GATE :  $G_1$ : NOR  $\rightarrow$   $G_2$ : NOR  $\rightarrow$   $G_3$ : NOR  $\rightarrow$   $G_4$ : NOT 1.

LH / HL.  $G_1$ : HL  $\rightarrow$   $G_2$ : LH  $\rightarrow$   $G_3$ : HL  $\rightarrow$   $G_4$  : LH.

LOAD.  $G_1$ : 2  $\rightarrow$   $G_2$ : 1  $\rightarrow$   $G_3$ : 1  $\rightarrow$   $G_4$  : 6.

$$t_{pLH}(d, z) = \underbrace{0.07 + 0.016(2)}_{NOR, HL, L=2} + \underbrace{0.06 + 0.075(1)}_{NOR, HL, L=1} + \underbrace{0.02 + 0.038(6)}_{NOT, LH, L=6} + \underbrace{0.07 + 0.016(1)}_{NOR, HL, L=2}$$

$$= \boxed{0.571 \text{ ns}}$$

wrong  
current path

7

### Problem 5 (20 points)

Obtain a two-level gate network of the following system.

Inputs:  $x, y \in \{0, 1, 2, 3\}$   
 Outputs:  $z \in \{0, 1, 2, 3\}$   
 Function:  $z = \{3xy + 1\} \bmod 4$

1. (2 points) Complete the switching table using binary encoding for all values.

$x_1$	$x_0$	$y_1$	$y_0$	$z_1$	$z_0$
0	0	0	0	0	1
0	0	0	1	0	1
0	1	0	0	0	1
0	1	0	1	0	1
0	2	0	0	0	1
0	2	0	1	0	1
0	3	0	0	0	1
0	3	0	1	0	1
1	0	1	0	0	1
1	0	1	1	0	0
1	1	0	0	0	0
1	1	0	1	0	0
1	2	0	0	1	1
1	2	0	1	1	0
1	3	0	0	0	1
1	3	0	1	0	1
2	0	1	0	0	1
2	0	1	1	1	1
2	1	0	0	1	1
2	1	0	1	0	1
2	2	0	0	1	1
2	2	0	1	1	1
2	3	0	0	0	1
2	3	0	1	1	0
3	0	1	0	1	0
3	0	1	1	1	0
3	1	2	0	1	1
3	1	2	1	1	0
3	2	3	0	0	0
3	2	3	1	0	0
3	3	3	0	0	0

2. (5 points) Show the switching expressions of  $z_1$  and  $z_0$  in sum of minterms form.


$$z_1 = \sum m(6, 7, 9, 11, 13, 14)$$

$$z_0 = \sum m(0, 1, 2, 3, 4, 6, 8, 9, 10, 11, 12, 14)$$

$$z_1 = x_1'x_0y_1y_0 + x_1'x_0y_1y_0 + x_1x_0'y_1y_0 + x_1x_0'y_1y_0 + x_1x_0y_1y_0 + x_1x_0y_1y_0$$

$$z_0 = x_1'x_0'y_1y_0 + x_1x_0'y_1y_0 + x_1'x_0y_1y_0 + x_1x_0'y_1y_0 + x_1'x_0y_1y_0 + x_1x_0'y_1y_0 + x_1x_0'y_1y_0 + x_1x_0y_1y_0 + x_1x_0y_1y_0 + x_1x_0y_1y_0 + x_1x_0y_1y_0 + x_1x_0y_1y_0$$

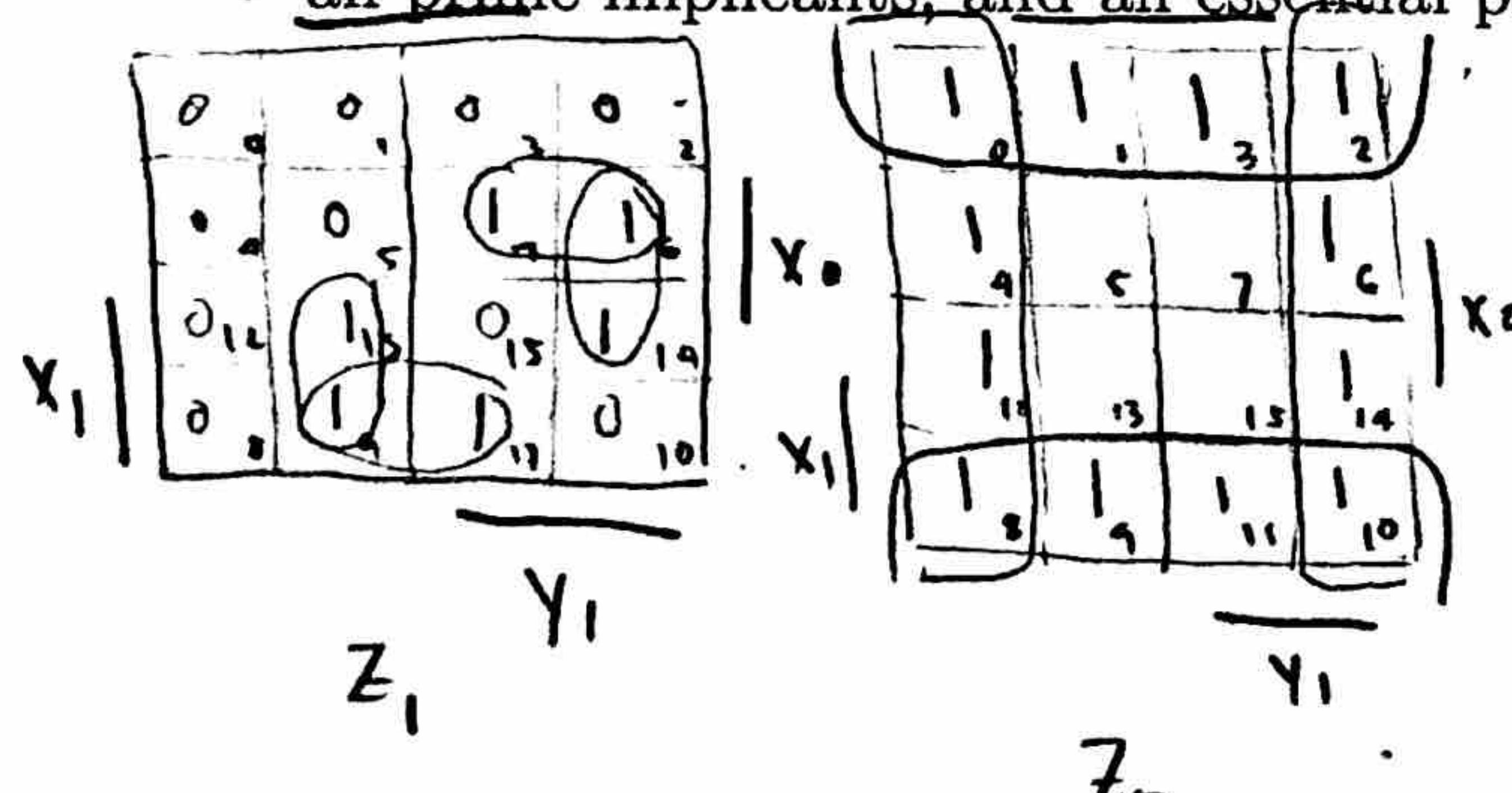3. (8 points) Show the minimal sum of products expressions of  $z_1$  and  $z_0$ . In each case, show a K-map, indicate all prime implicants, and all essential prime implicants. Show NAND-NAND networks.



$$z_1 \rightarrow \text{PIs: } x_1'y_1y_0, x_1x_0'y_0, y_1y_0x_0, y_1x_0'y_0$$

all are essential!


$$z_0 \rightarrow \text{PIs: } x_0 + y_0$$

$$z_1 = \text{NAND}(\text{NAND}(x_1'y_1y_0), \text{NAND}(x_1x_0'y_0), \text{NAND}(y_1y_0x_0), \text{NAND}(y_1x_0'y_0))$$

$$z_0 = \text{NAND}(x_0, y_0)$$
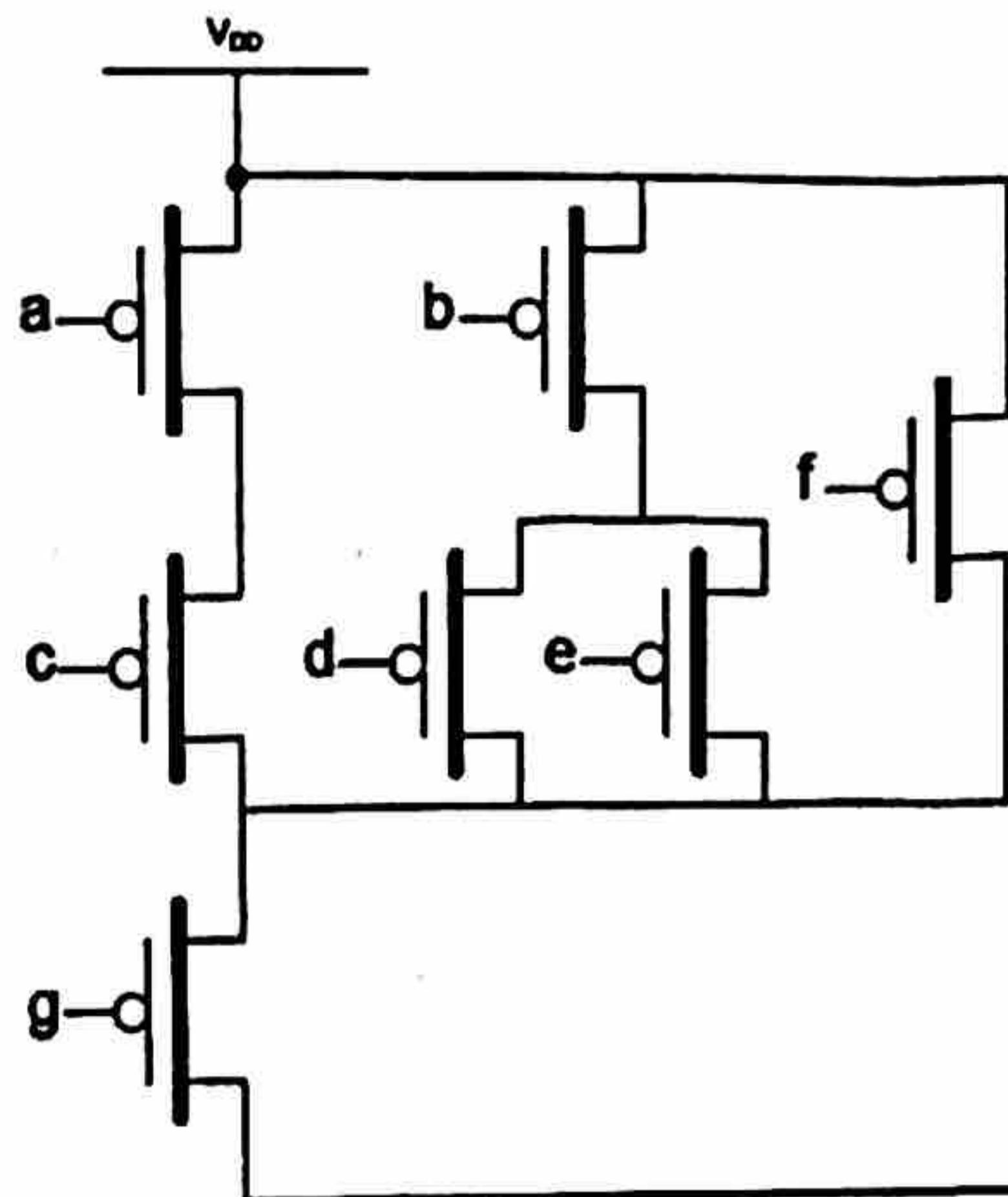
### Problem 6 (10 points)

We are given the following partial CMOS network.




1.

$$\begin{aligned} & g'(a'c' + b'(d'+e')+f') \\ & ((g'(a'c' + b'(d'+e')+f'))') \\ & (g + ((a+c)(b+(de))f)) \end{aligned}$$

PULL DOWN

$$z' = g + ((a+c)(b+de)f)$$

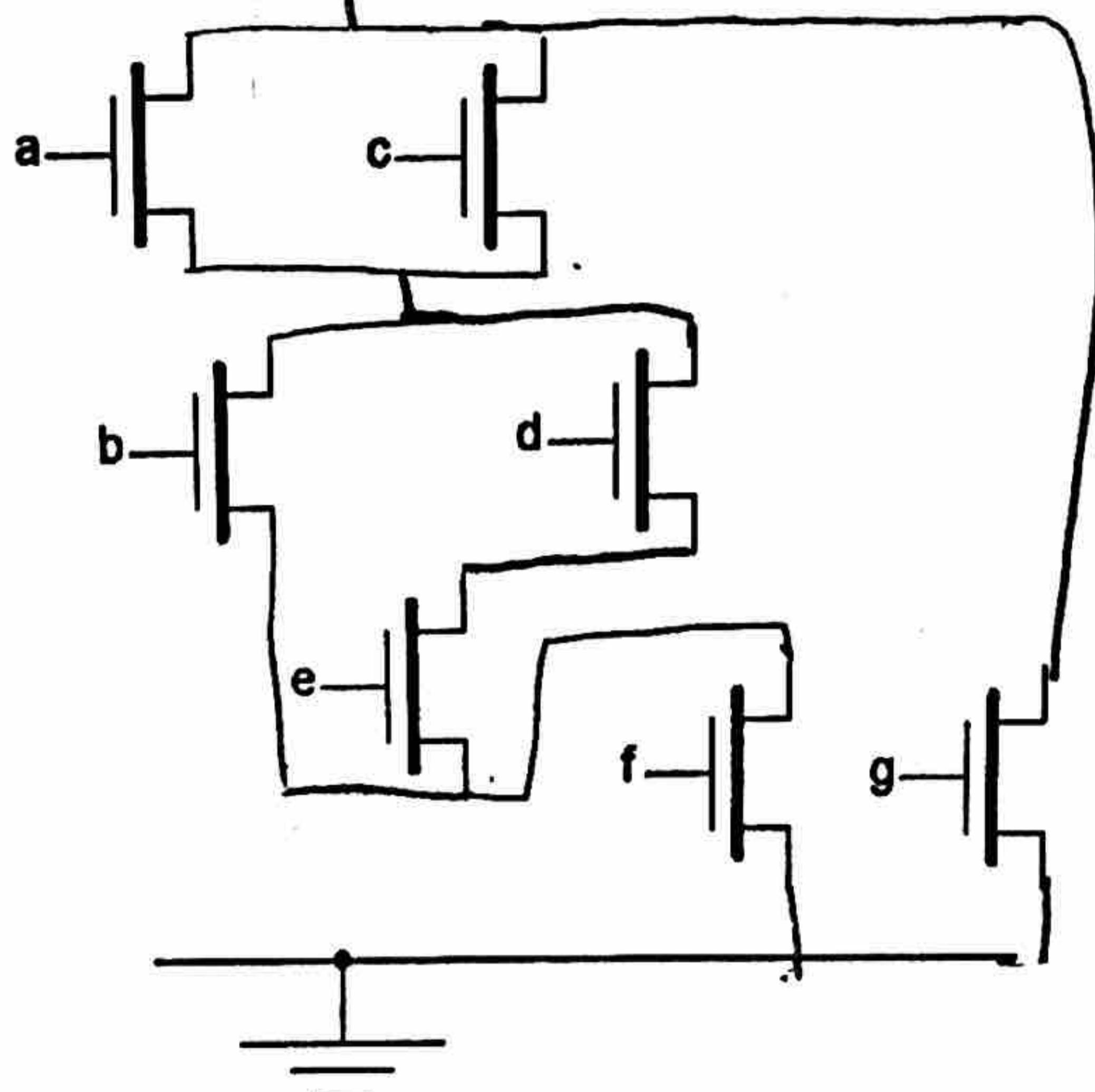

#### 1. (5 points)

Write the expression for the pull-up network. From this, derive the expression for the pull-down network using switching algebra.

#### 2. (5 points) Connect NMOS transistors to complete the circuit according to the pull-down expression. Please only add missing wires.


**Problem 7 (15 points)**

For  $f(x_3, x_2, x_1, x_0) = (x_3 + x_2' + x_1 + x_0)(x_3 + x_2' + x_1' + x_0)(x_3' + x_2 + x_1 + x_0')(x_3' + x_2' + x_1 + x_0')(x_3' + x_2' + x_1' + x_0)$

1. (2 points) Fill out the following K-map.

$$f(x_3, x_2, x_1, x_0)$$

$$\bar{f}M(9, 6, 9, 12, 13, 14)$$

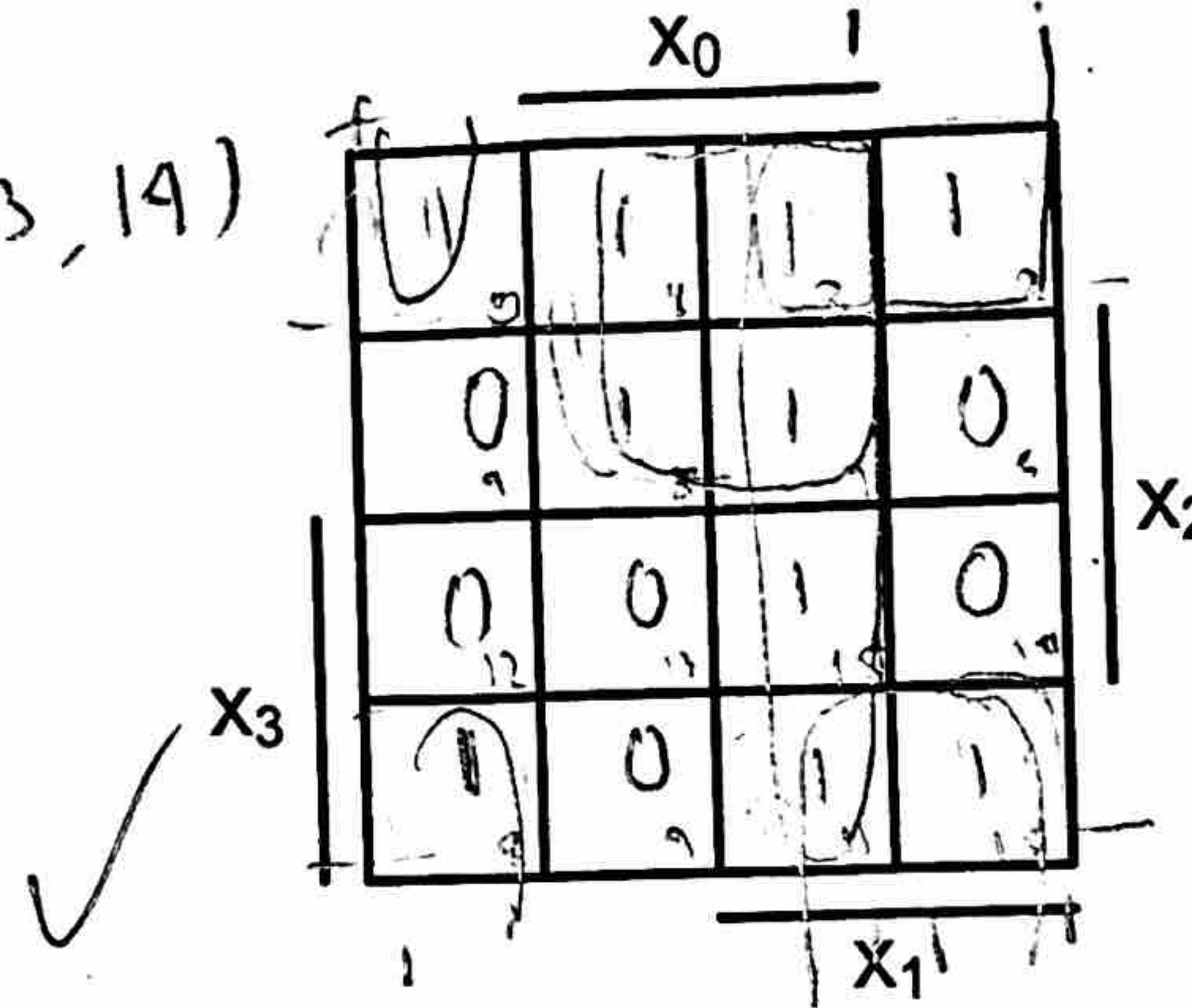

big boys

$$x_3'x_0, x_1x_0, x_3'x_2, x_2x_1$$

small boys

$$x_3x_2x_1, x_3x_2'x_0'$$

$$x_3x_1x_0, x_3'x_2x_0,$$

$$x_3'x_1x_0, x_3'x_1'x_0, x_3'x_2'x_0$$

$$x_3'x_2'x_0', x_3'x_2'x_1$$

2. (4 points) Which of the given expressions are prime implicants of the function given above? Circle all that apply. Write down any prime implicants that are missing.

(a)  $x_1$

(b)  $x_3x_1$

(c)  $x_3'x_2$  ✓

(d)  $x_3'x_1$

(e)  $x_3'x_0$

(f)  $x_2x_1$

(g)  $x_2'x_0$

(h)  $x_1x_0$

(i)  $x_1x_0'$

(j)  $x_3'x_2'x_1$

(k)  $x_2x_1x_0$

(l)  $x_2x_2x_1x_0$

~~st~~ ~~01~~ ~~02~~ ~~032~~  
~~Y5~~ ~~Y3~~ ~~1357~~

~~st~~ ~~32110~~ ~~321111~~ ~~31~~

~~210~~

~~215~~

~~1511~~

~~1110~~

~~100~~

~~2~~

$$x_2'x_1x_0'$$

$$x_3'x_2x_0$$

$$x_3'x_2'x_1'$$

$$x_3'x_1x_0$$

$$x_3'x_2'x_0'$$

$$x_2'x_1$$

$$x_3'x_1'x_0'$$

$$x_2'x_1x_0$$

$$x_3'x_2'x_0$$

$$x_2'x_1x_0'$$

$$x_3x_1x_0$$

3. (2 points) Write down the complete set of essential prime implicants.

$$x_3'x_0, x_1x_0, x_3'x_2, x_3x_2'x_0'$$

✓

✓

✗

✗

$$(x_3x_2'x_1, x_3x_2'x_0)$$

4. (1 point) Write the minimal sum of products expression for  $f$ . Is it unique?

$$f = x_3'x_0 + x_1x_0 + x_3'x_2 + x_3x_2'x_0'$$

✗