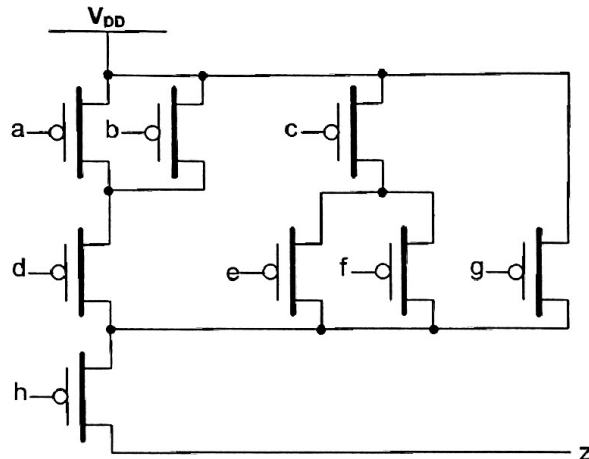


Quiz Problems (50 points total)

Problem 1 (15 points)

12

The following pull-up network is part of a complex CMOS gate that we wish to implement.



1. (5 points) Write the expression for the pull-up network. From this, derive the expression for the pull-down network using switching algebra. Make sure the inverters are on the correct variables.

$$z = ((a' + b')d' + c'(e' + f') + g')h' \quad \checkmark$$

$$z' = [((a' + b')d' + c'(e' + f') + g')h']'$$

$$= ((a' + b')d' + c'(e' + f') + g')'h$$

$$= [((a' + b')d')' (c'(e' + f'))' g']'h$$

$$= ((a' + b')' + d) (c + (e' + f')') gh$$


$$z' = (ab + d)(c + ef)(gh)$$

-1

2. (10 points) Draw the pull-down network of NMOS transistors that correspond to the expression and completes the CMOS gate that drives output z . To keep it minimal, only use one NMOS transistor for each input variable.

$$z' = (ab+cd)(e+fg)$$

Pull-down network

 


Problem 2 (15 points)

13

Answer the following questions on the given switching expression.


$$E(w, x, y, z) = \sum m(0, 1, 4, 5, 7, 11, 14, 15), dc(3, 10)$$

 1. (5 points) Using K-maps, find all the prime implicants for $E(w, x, y, z)$.



prime implicants

$$w'x', yz, wx, w'z$$

 

2. (5 points) Which of these prime implicants are **not** essential?

$$w'z$$

$$yz \rightarrow$$


3. (5 points) Show the minimum sum of minterm for E?

min
SP: $w'x' + wx + yz$

Problem 3 (20 points)

20

Given the circuit shown below,

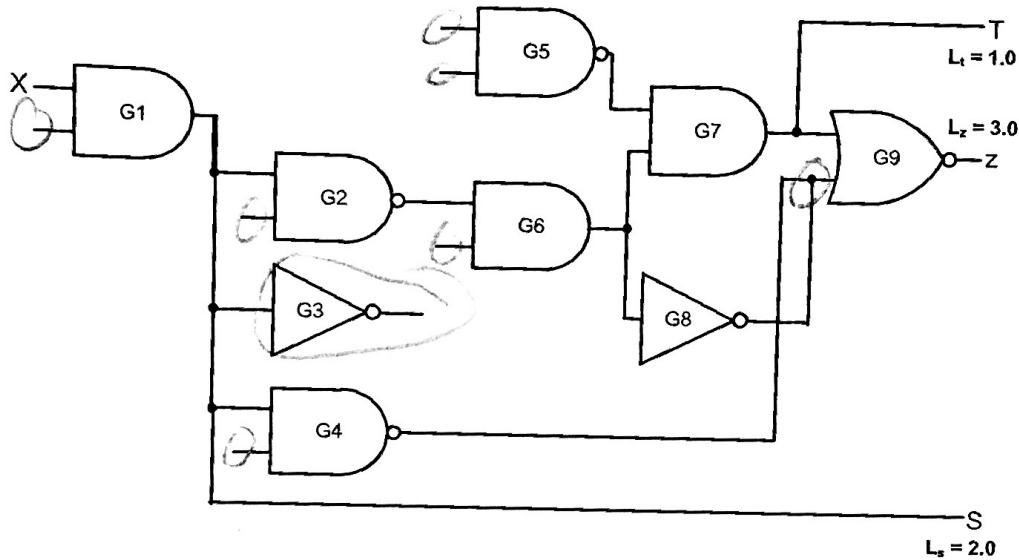

show the items below for the worst case path.

The gate characteristics are listed in the following table.

Gate Type	Fan-in	Propagation Delays (ns)		Load Factor I
		t_{pLH}	t_{pHL}	
AND	2	$0.20 + 0.038L$	$0.18 + 0.018L$	1.0
NOT	1	$0.02 + 0.038L$	$0.05 + 0.017L$	1.0
NAND	2	$0.05 + 0.038L$	$0.08 + 0.027L$	1.0
NOR	2	$0.06 + 0.075L$	$0.07 + 0.016L$	1.0

1. (5 points) Does the given circuit work properly? Answer YES or NO. If your answer is NO, then specify the problems.

(NO)

① G3 goes to nowhere

② G8 intersects the path from G4 incorrectly ✓

*③ Missing many inputs so probably won't do what the spec wanted. Only has X
 → (it is possible we don't care, in which case this is fine)

- In this case we don't care so only ① and ②

15 Xorx

2. (15 points) For $t_{pLH}(x \rightarrow z)$, fill in the blanks with the appropriate information. For the Delay section, write down the equation from the table with the proper L value shown. You do not need to obtain the final delay value for full credit.

Gate type & fan-in	G1: <u>AND 2</u> → G2: <u>NAND 2</u> → G6: <u>AND 2</u> → G7: <u>AND 2</u> → G9: <u>NOR 2</u>
LH / HL	G1: <u>LH</u> → G2: <u>HL</u> → G6: <u>HL</u> → G7: <u>HL</u> → G9: <u>LH</u>
Total load	G1: <u>5</u> → G2: <u>1</u> → G6: <u>2</u> → G7: <u>2</u> → G9: <u>3</u> ✓
Delay	G1: <u>.2 + .038(5)</u> → G2: <u>.08 + .027(1)</u> → G6: <u>.18 + .018(2)</u> → G7: <u>.18 + .018(2)</u> → G9: <u>.06 + .075(3)</u>

G1: .20 + .038(5) → G2: .08 + .027(1) → G6: .18 + .018(2)
 → G7: .18 + .018(2) → G9: .06 + .075(3)

(just in case it is too small to read)

Total delay is sum of