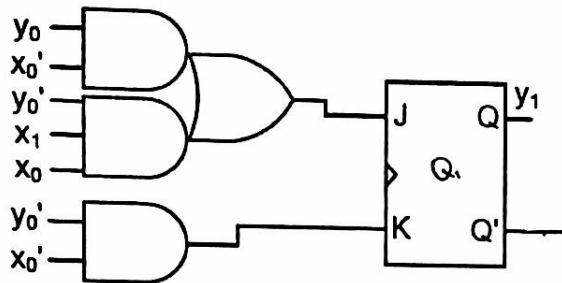



8

Problem 1 (20 points)

Obtain a high-level description (state transition table) of the network shown in the figure below. The system has two input bits x_1 and x_0 , with a single output bit z .



$$Q(t+1) = Q(t) K'(t) + Q'(t) J(t)$$

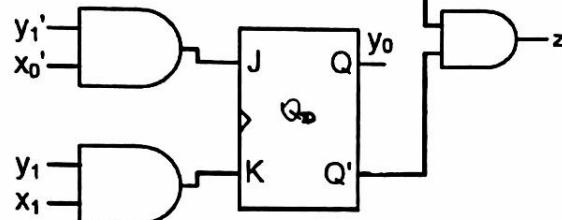

$$\begin{aligned} Q_1 &= y_1 (y_0' x_0')' + x_1 (y_0 x_0 + y_0' x_1 x_0) \\ &= y_1 (y_0 + x_0) + x_1 y_0 x_0' + y_0' x_1 x_0 \end{aligned}$$

$$\begin{aligned} Q_0 &= y_0 (y_1 y_0)' + x_0 (y_1' x_0') \\ &= y_0 (y_1' + y_0') + 0 \\ &= y_0 y_1' \end{aligned}$$

$$\begin{aligned} Q_1 &= (y_1) (y_0' x_0')' + y_1' (y_0 x_0 + y_0' x_1 x_0) \\ &= y_1 (y_0 + x_0) + y_1' y_0 x_0' + y_1' y_0' x_1 x_0 \end{aligned}$$

$$\begin{aligned} Q_0 &= y_0 (y_1 y_0)' + y_0 (y_1' x_0') \\ &= y_0 (y_1' + y_0') + y_0' y_1 x_0' \\ &= y_0 y_1' + y_0' y_1 x_0' \\ &= y_1' (y_0 + y_0' x_0') \\ &= y_1' (y_0 + x_0) \end{aligned}$$


+5

$$Q_1 = y_1 y_0 + y_1 x_0 + y_1' y_0 x_0' + y_1' y_0' x_1 x_0$$

$$Q_0 = x_0 (y_1 + y_1' y_0' x_1) + y_0 (y_1 + y_1' x_0')$$

$$Q_1 = x_0 (y_1 + y_0' x_1) + y_0 (y_1 + x_0')$$

$$z = y_1 y_0 = (y_1 + y_0)'$$

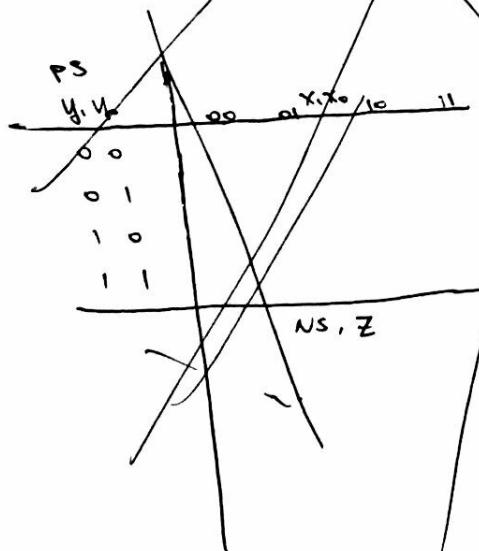

PS	y ₁	y ₀	x ₁	x ₀
0	0	0	0	0
0	0	1	0	1
1	0	0	1	0
1	1	1	1	1


... complete table using
expressions of
 Q_1 , Q_0 , and z

switch table and name inputs to i, j, k, l respectively
name states to a, b, c, d respectively

PS	i	j	k	l
a	b, 1			
b	d, 0			
c	a, 0			
d				

+3

... complete the table
using
NS, output.

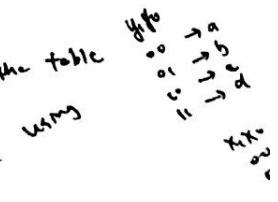

20

Problem 2 (20 points)

Consider the state transition table as shown below. Add 3 new states and their transitions to the table, so that the new table will have 5 states after minimization.

PS	INPUT	
	x=0	x=1
A	B,0	C,0
B	B,0	D,0
C	B,0	A,0
D	C,0	E,1
E	E,1	F,1
F	F,1	E,1
G	F,1	B,1
H	F,1	B,1
I	F,1	B,1

$$k=1 \quad \{A, B, C\}^0 \{D\}^1 \{E, F\}^2$$

$$\begin{array}{ccccccc} A & \oplus & \oplus & \oplus & F & \oplus \\ \oplus & \oplus & \oplus & \oplus & \oplus & \oplus \\ \oplus & \oplus & \oplus & \oplus & \oplus & \oplus \end{array}$$

$$k=2 \quad \{A, C\}^0 \{B\}^1 \{D\}^2 \{E, F\}^3$$

$$\begin{array}{ccccccc} A & \oplus & \oplus & \oplus & E & \oplus & \oplus \\ C & \oplus & \oplus & \oplus & F & \oplus & \oplus \\ \oplus & \oplus & \oplus & \oplus & \oplus & \oplus & \oplus \end{array}$$

$k=3$ same!

add GHI so that they are $k=3$ distinguishable
with $\{E, F\}$

$$k=2 \quad \{A, C\}^0 \{B\}^1 \{D\}^2 \{E, F, G, H, I\}^3$$

$$\begin{array}{ccccccc} E & \oplus & \oplus & \oplus \\ F & \oplus & \oplus & \oplus \\ G & \oplus & \oplus & \oplus \\ H & \oplus & \oplus & \oplus \\ I & \oplus & \oplus & \oplus \end{array}$$

checking $k=1 \quad \{A, B, C\}^0 \{D\}^1 \{E, F, G, H, I\}^2$

$$k=2 \quad \{A, C\}^0 \{B\}^1 \{D\}^2 \{E, F, G, H, I\}^3$$

$$k=3 \quad \underbrace{\{A, C\}}_A \underbrace{\{B\}}_B \underbrace{\{D\}}_D \underbrace{\{E, F\}}_E \underbrace{\{G, H, I\}}_G$$

after minimization:

	$x=0$	$x=1$
A	B,0	A,0
B	B,0	D,0
D	A,0	B,1
E	E,1	E,1
G	E,1	B,1

20

Problem 3 (20 points)

Using RD flip-flops as defined below, design a system as described below. Use only multiplexers to implement your combinational logic.

Input set: $\{a, b, c\}$ $\{a, b, c, d\}$

Output: 1, if $x(t-n, t) = a[b|c]^*d^*$
0, otherwise

Note: * denotes a character can appear 0 to infinite number of times.

+ denotes a character can appear 1 to infinite number of times.

$b|c$ denotes b or c .

For example, given $abcbddaa$, the output should be 1.









		RD			
PS, Q(t)		00	01	10	11
0	0	1	0	0	1
	1	1	0	1	0
NS, Q(t+1)					



RD & excitation table

RD	
0→0	10 → 01
0→1	00 or 11
1→0	-1
1→1	-0

PS		Input x_1x_0			
		$a=00$	$b=01$	$c=10$	$d=11$
S_{00}	S_{0000}	$S_{01}, 0$	S_{0010}	$S_{0001}, 0$	$S_{0000}, 0$
S_{01}	$S_a[b c]^*$	$S_{01}, 0$	$S_{01}, 0$	$S_{01}, 0$	$S_{01}, 0$
S_{10}	$S_d[1 c]^*d^*$	$S_{10}, 1$	$S_{00}, 0$	$S_{00}, 0$	$S_{00}, 0$
S_{11}	-	-	-	-	-

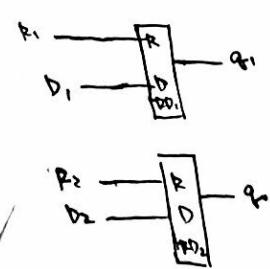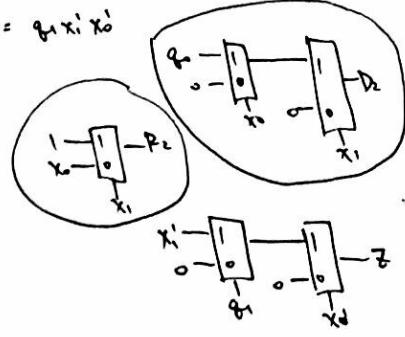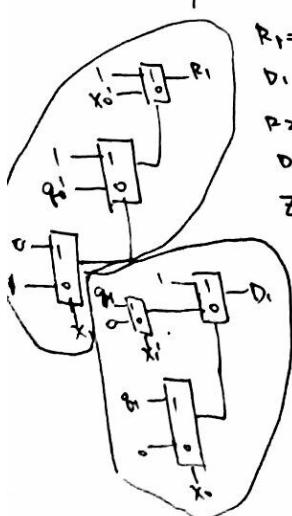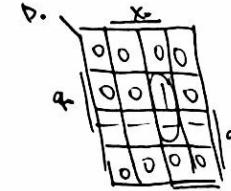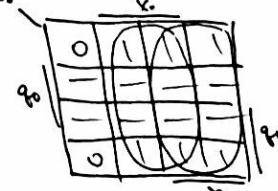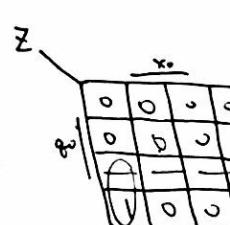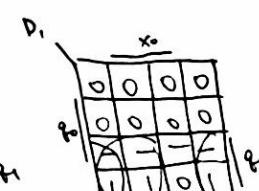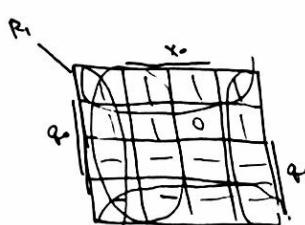


Problem 4 (20 points)

20


Given an input stream of 0s and 1s, design a system that outputs the length, Z , of the largest palindrome found in the last 7 inputs, along with the parity, P , of the length of that palindrome. A palindrome is a string that is spelled the same forwards as it is backwards. For example, the following strings are palindromes: 10101, 11, 1001, 0000. P is equal to 1 when the length of the palindrome is odd, and 0 when its length is even. Your system should only consider palindromes of length 2 to 7.

For example, given the following input stream, 1010101, the output should be $Z=7$ and $P=1$. For the input stream, 1010000, the output should be $Z=4$ and $P=0$.


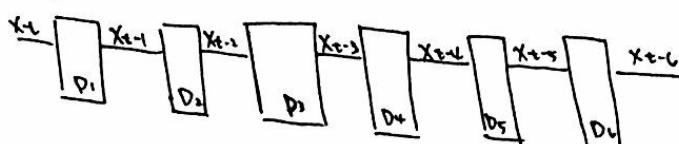
Use any type, any number of flip-flops and combinational gates of your choosing to implement this system.





check if 2-bit palindrome exists:

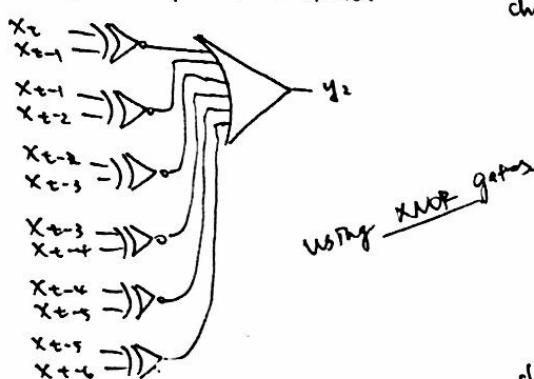




check for 5-bit palindrome:

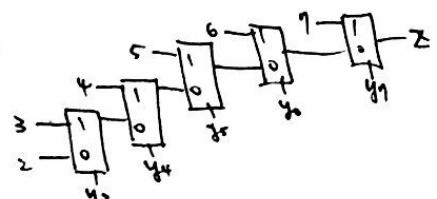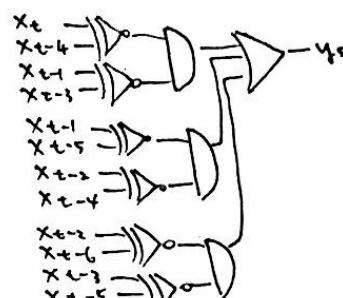

check for 3-bit

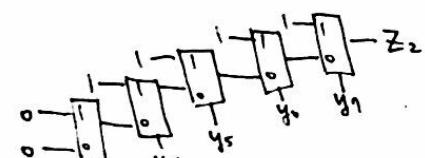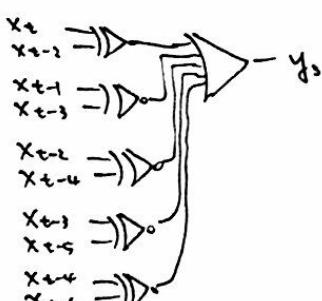

check for 4-bit

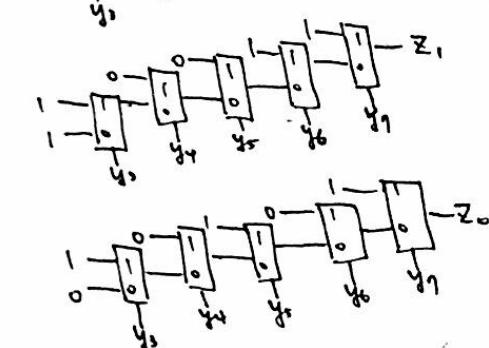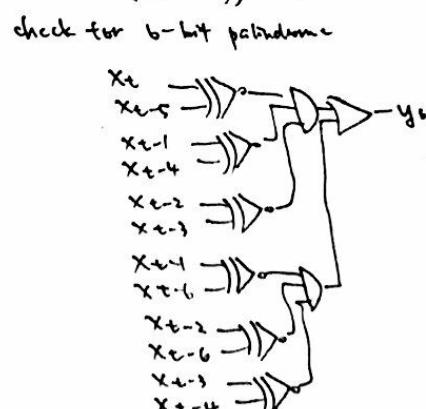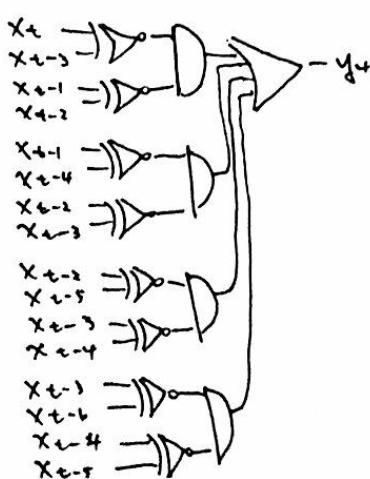

check for 7-bit palindrome:



output:

$$Z = Z_2 Z_3 Z_4$$

$$P = Z_7$$

+5

+5 +5

+5

Problem 5 (20 points)


12

Using at most 1 JK flip-flop, at most 1 SR flip-flop, and at most 8 D flip-flops, design a system as specified below. You may use any gates to implement your combinational logic.
Input set: {0,1}

Output: 1, if $x(t, t-3) = 11\cdot 0$, $x(t-4, t-7) = 1\cdot 10$ or $0\cdot 0$, $x(t-8, t-11) = 1001$
0, otherwise

For example, for the given input sequence $x(t, t-11) = \underline{110010101001}$, output is 1. For the input sequence $x(t, t-11) = \underline{101001011001}$, output is 0.

Implement D ff using JK

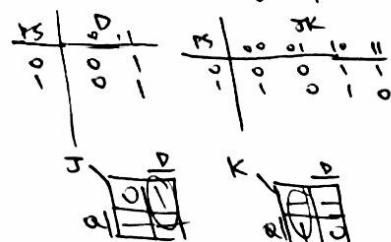

JK	
0 0	0 -
0 1	1 -
1 0	- 1
1 1	- 0



Implement D ff using SR

SR	
0 0	0 -
0 1	1 0
1 0	0 1
1 1	- 0

RS	
0 0	0 0
0 1	1 1
1 0	0 1
1 1	- -

S	
0 0	0 0
0 1	0 1

R	
0 0	0 0
0 1	0 0



Now, combined with the above 2 D-ff, with 8 regular D-ff.



D-FFs
if needed

To get x_{t-11} , use a

