

### Problem 1 (10 points)

1. (4 points) How many bits are required to encode a color spectrum capable of supporting 16 million colors using:

- a. Decimal digits in BCD

28 bits

16000000

$$8 \times 4 = 32$$

- b. Hexadecimal representation

6 bits

Which representation is more efficient? Why?

Hexadecimal representation is more efficient

since it only needs 6 bits while BCD requires 28 bits.

2. (6 points) Fill in the missing entries in the table.

Radix	Digit vector $\underline{x}$	Value $x$ in decimal
16	(5, 1, 7)	1303
8	(5, 1, 7)	335
7	(4, 5, 3, 2)	1640

Q

Item 2 (15 points) ~~✓~~

$a + b = b + a$	$ab = ba$	Commutativity
$a + (bc) = (a + b)(a + c)$	$a(b + c) = (ab) + (ac)$	Distributivity
$a + (b + c) = (a + b) + c = a + b + c$	$a(bc) = (ab)c = abc$	Associativity
$a + a = a$	$aa = a$	Idempotency
$a + a' = 1$	$aa' = 0$	Complement
$1 + a = 1$	$0a = 0$	
$0 + a = a$	$1a = a$	
$(a')' = a$	$a(a + b) = a$	Identity
$a + ab = a$	$a(a' + b) = ab$	Involution
$a + a'b = a + b$	$(ab)' = a' + b'$	Absorption
$(a + b)' = a'b'$		Simplification
		DeMorgan's law

Given  $E(a, b, c, d) = (ab + c)'(ac + (b' + c' + a'cd)') + a((b + c)(b + d) + c)',$  which of the following represents the same function as  $E(a, b, c, d)?$  Show all your work.

1.  $a + b + c + d'$

2.  $a' + b + c$

3.  $b + c' + d$

4.  $a'b'c'd$

5.  $ab'c'$

6.  $b'cd'$

$$E(a, b, c, d) = (ab + c)'(ac + (b' + c' + a'cd)') + a((b + c)(b + d) + c)'$$

$$= (ab)' \cdot c' (ac + b \cdot c \cdot (a'cd)') + a(\frac{b \cdot b + cb + cd + bd + c}{b})'$$

$$= (ab)' \cdot \cancel{c'} \cdot c (a + b \cdot (a'cd)') + a(b + \frac{c(1+b+d)}{+bd})'$$

Demorgan's law  
distributivity

$$= 0 + a(b + c + bd)'$$

Complement

$$= 0 + a(b(1+d) + c)'$$

identity  
distributivity

$$= ab'c'$$

Identity

Demorgan's Law

### Problem 3 (15 points)

Show if the gate G, described by  $G(x, y, z) = \text{one} - \text{set}\{3, 4, 6, 7\}$ , can implement NOT and AND gates. Assume 31st that 0 and 1 are available. If it can, then use G gates to implement the following expression and show the corresponding network of G gates

$$E(a, b, c) = (a + b')(b + c')$$

$$G(x, y, z)$$

$$= x'yz + xy'z' + xyz' + xyz$$

$$= (x' + x)yz + xz'(y' + y)$$

$$\text{NOT}(z) = z' = 0 \cdot z + 1 \cdot z'$$

$$= G(1, 0, z) \quad \checkmark$$

$$= yz + xz'$$

$$\text{AND}(y, z) = y \cdot z = G(0, y, z) \quad \checkmark$$

$\Rightarrow G(x, y, z)$  can implement AND and  
NOT gates.

$$b' = G(1, 0, b)$$

$$c' = G(1, 0, c)$$

$$a' = G(1, 0, a)$$

$$= G(0, a, b) + G(0, G(1, 0, b), c) \quad \cancel{G(1, 0, c)}$$

$$E(a, b, c)$$


$$a'b = G(0, G(1, 0, a), b)$$

$$= (a'b)' \cdot (b'c)'$$

$$b'c = G(0, G(1, 0, b), c)$$

$$= G(0, G(1, 0, G(0, G(1, 0, a), b))),$$
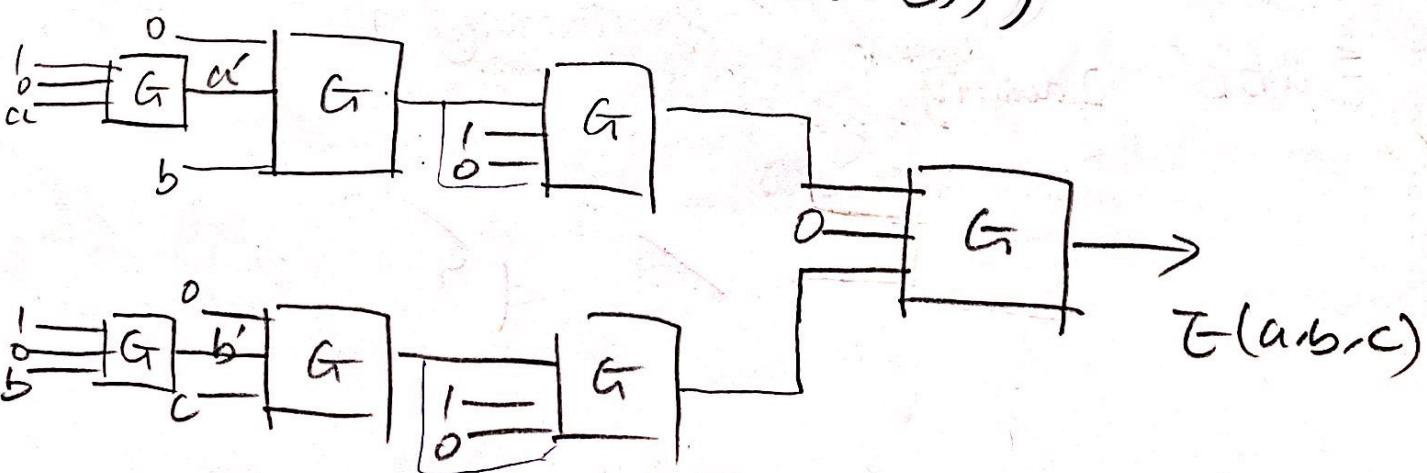
$$G(1, 0, G(0, G(1, 0, b), c))) \quad \checkmark$$




Ordering in  
N/W wrong.

(13)

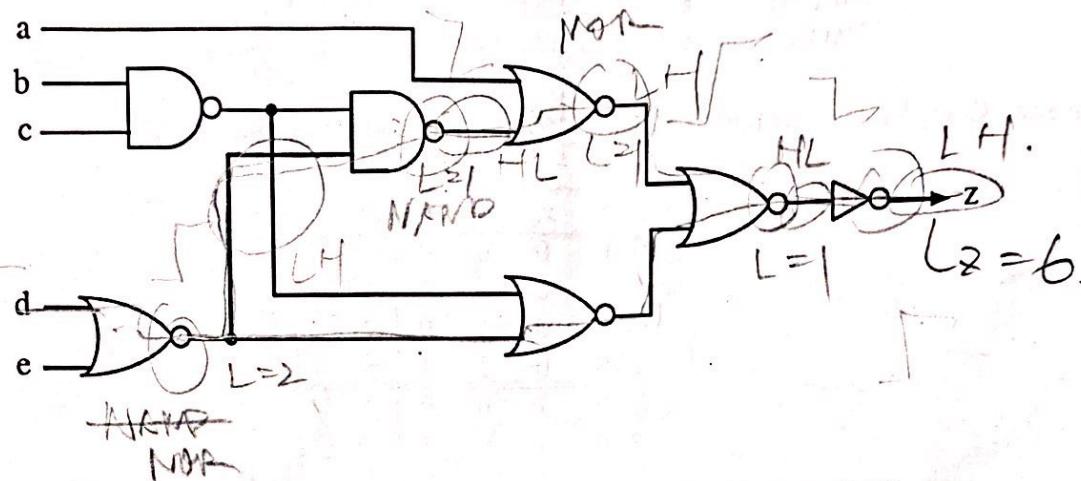Problem 4 (15 points)

With the help of the table below, determine the low to high propagation delay  $t_{PLH}(d, z)$  of the output  $z$  of the network shown below. Assume the network output has a load of 6.



Gate Type	Fan-in	Propagation Delays (ns)		Load Factor
		$t_{PLH}$	$t_{PHL}$	
NOT	1	$0.02 + 0.038L$	$0.05 + 0.017L$	1.0
NAND	2	$0.05 + 0.038L$	$0.08 + 0.027L$	1.0
NOR	2	$0.06 + 0.075L$	$0.07 + 0.016L$	1.0

The longest path from d to  $z$  is  $\text{NOR} \rightarrow \text{NAND} \rightarrow \text{NOR} \rightarrow \text{NOR} \rightarrow \text{NOT}$

$$\begin{aligned}
 t_{PLH}(d, z) &= t_{PLH}(\text{NOR}') + t_{PHL}(\text{NAND}') + t_{PLH}(\text{NOR}') \\
 &\quad + t_{PHL}(\text{NOR}') + t_{PLH}(\text{NOT}) \\
 &= 0.06 + 0.075 \times 2 + 0.08 + 0.027 \times 1 + \\
 &\quad 0.06 + 0.075 \times 1 + 0.07 + 0.016 \times 1 + \\
 &\quad 0.02 + 0.038 \times 6 \\
 &= 0.268 \\
 &= 0.786 \text{ ns}
 \end{aligned}$$

**Problem 5 (20 points)**

Obtain a two-level gate network of the following system.

Inputs:  $x, y \in \{0, 1, 2, 3\}$   
 Outputs:  $z \in \{0, 1, 2, 3\}$   
 Function:  $z = \{3xy + 1\} \bmod 4$

1. (2 points) Complete the switching table using binary encoding for all values.

$x_1$	$x_0$	$y_1$	$y_0$	$z_1$	$z_0$
0	0	0	0	0	1
0	0	0	1	0	1
0	0	1	0	0	1
0	0	1	1	0	1
1	0	1	0	0	1
1	0	1	1	0	0
1	1	1	0	1	1
1	1	1	1	1	0
2	0	0	0	0	1
2	0	0	1	1	1
2	0	1	0	0	1
2	0	1	1	0	0
2	1	0	0	0	1
2	1	0	1	1	1
2	1	1	0	0	1
2	1	1	1	0	0
3	0	0	0	0	1
3	0	0	1	1	1
3	0	1	0	1	1
3	0	1	1	1	0
3	1	0	0	1	1
3	1	0	1	1	0
3	1	1	0	1	1
3	1	1	1	1	1

2. (5 points) Show the switching expressions of  $z_1$  and  $z_0$  in sum of minterms form.

$$z_1 = \sum m(6, 7, 9, 11, 13, 14)$$

$$\checkmark z_0 = \sum m(0, 1, 2, 3, 4, 6, 8, 9, 10, 11, 12, 14)$$

3. (8 points) Show the minimal sum of products expressions of  $z_1$  and  $z_0$ . In each case, show a K-map, indicate all prime implicants, and all essential prime implicants. Show NAND-NAND networks.


The answer is on the last page.

17  
Problem 6 (10 points)

are given the following partial CMOS network.

$$(a' \otimes c')$$

$$+(d'+e') \cdot b' + f'$$

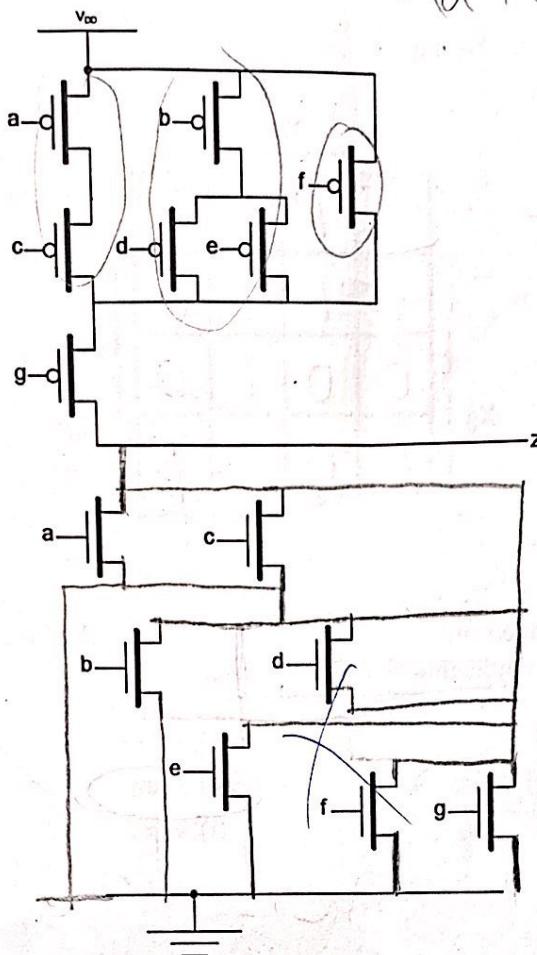

1. (5 points)

Write the expression for the pull-up network. From this, derive the expression for the pull-down network using switching algebra.

2. (5 points) Connect NMOS transistors to complete the circuit according to the pull-down expression. Please only add missing wires.

1. Pull up:  $Z = g' \cdot [a'c' + (d'+e') \cdot b' + f']$

Pull down:  $Z = g'a'c' + g'd'b' + g'e'b' + g'f'$

$$\begin{aligned} Z' &= (g'a'c')' \cdot (g'd'b')' \cdot (g'e'b')' \cdot (g'f')' \\ &= (g+a+c) \cdot (g+d+b) \cdot (g+e+b) \cdot (g+f) \end{aligned}$$

Problem 7 (15 points)

For  $f(x_3, x_2, x_1, x_0) = (x_3 + x_2' + x_1 + x_0)(x_3 + x_2' + x_1' + x_0)(x_3' + x_2 + x_1 + x_0')(x_3' + x_2' + x_1 + x_0)(x_3' + x_2' + x_1' + x_0)$

implies

1. (2 points) Fill out the following K-map.

$x_0$	0	0	0	1
0	1	1	1	0
1	0	0	1	0
$x_3$	1	0	1	1
$x_1$				

2. (4 points) Which of the given expressions are prime implicants of the function given above? Circle all that apply. Write down any prime implicants that are missing.

(a)  $x_1$

(b)  $x_3x_1$

(c)  $x_3'x_2'$

(d)  $x_3'x_1$

(e)  $x_3'x_0$

(f)  $x_2x_1$

(g)  $x_2'x_0$

(h)  $x_1x_0$

(i)  $x_1x_0'$

(j)  $x_3'x_2'x_1$

(k)  $x_2x_1x_0$

(l)  $x_3x_2x_1x_0$

$x_2'x_0' \checkmark$

$x_3x_2 \checkmark$

prime  
missing implicants

3. (2 points) Write down the complete set of essential prime implicants.

$x_2'x_0'$

$x_1x_0 \quad x_3'x_0 \quad \checkmark$

4. (1 point) Write the minimal sum of products expression for  $f$ . Is it unique?

minimal SP =  $x_2'x_0' + x_1x_0 + x_3'x_0$  It is unique

P5.3

$z_1$	$y_0$
$x_1$	$y_1$
0	0
0	1
0	1
1	0
0	0

0 1 3 2  
6 5 7 6  
8 13 18 14  
8 9 11 10

prime implicants:

$$x_1 y_1' y_0$$

$$x_1 x_0' y_0$$

$$x_1' x_0 y_1$$

$$x_0 y_1 y_0'$$

All of them are essential.

$z_0$	$y$
$x_1$	$y_1$
1	1
1	0
1	0
1	1
1	1

prime implicants:

$$y_0'$$

$$x_0'$$

All of them are essential.

$$z_1 = x_1 y_1' y_0 + x_1 x_0' y_0 + x_1 x_0 y_1 + x_0 y_1 y_0'$$

$$z_0 = y_0' + x_0'$$

