

[CS M51A FALL 18] MIDTERM EXAM

Date: 10/30/18

- The midterm is closed book, and up to 4 sheets (= 8 pages) of summary notes are allowed. You can use a calculator but not smart phones.
- For multiple choice questions, wrong answers may have a negative score value so choose carefully. It is possible that questions can have multiple answers.
- Please show all your work and write legibly, otherwise no partial credit will be given.
- **This should strictly be your own work; any form of collaboration will be penalized.**

Name : Elaine Shyu

Student ID : _____

Problem	Points	Score
1	10	10
2	15	15
3	15	15
4	15	15
5	20	17
6	10	10
7	15	9
Total	100	91

94

$\lceil \log_{10}(13) \rceil = 2$
 $2(4) = 8$
 0001 0111

Problem 1 (10 points)

1. (4 points) How many bits are required to encode a color spectrum capable of supporting 16 million colors using:

a. Decimal digits in BCD

4 bits for each digit in BCD

$10^x = 16000000$

$x = 8$

$8(4) = 32 \text{ bits}$

$\lceil \log_{10}(16 \text{ million}) \rceil \rightarrow 8 \text{ BCD digits}$

b. Hexadecimal representation

4 bits for each digit in hex

$16^x = 16000000$

$x = 6$

$6(4) = 24 \text{ bits}$

$\lceil \log_{16}(16 \text{ million}) \rceil \rightarrow 6 \text{ hex digits}$

Which representation is more efficient? Why?

hexadecimal is more efficient because you can represent the range 0-15 numbers in a 4-bit value, but for BCD, you can have 0-9.

only represent

2. (6 points) Fill in the missing entries in the table.

$5(16^2) + 16 + 7$
 $8^2(5) + 8 + 7$

Radix	Digit vector \underline{x}	Value x in decimal
16	$(5, 1, 7)$	1303
8	$(5, 1, 7)$	335
7	$(4, 5, 3, 2)$	1640

$1640/7$
 $234/7$
 $33/7$
 $4/7$

remainder
 2
 3
 5
 4

check

$4(7^3) + 5(7^2) + 3(7) + 2 = 1640 \checkmark$

Problem 2 (15 points)

15

$a + b = b + a$	$ab = ba$	Commutativity
$a + (bc) = (a + b)(a + c)$	$a(b + c) = (ab) + (ac)$	Distributivity
$a + (b + c) = (a + b) + c = a + b + c$	$a(bc) = (ab)c = abc$	Associativity
$a + a = a$	$aa = a$	Idempotency
$a + a' = 1$	$aa' = 0$	Complement
$1 + a = 1$	$0a = 0$	
$0 + a = a$	$1a = a$	Identity
$(a')' = a$		Involution
$a + ab = a$	$a(a + b) = a$	Absorption
$a + a'b = a + b$	$a(a' + b) = ab$	Simplification
$(a + b)' = a'b'$	$(ab)' = a' + b'$	DeMorgan's law

Given $E(a, b, c, d) = (ab + c)'(ac + (b' + c' + a'cd)') + a((b + c)(b + d) + c)'$, which of the following represents the same function as $E(a, b, c, d)$? Show all your work.

- $a + b + c + d'$
- $a' + b + c$
- $b + c' + d$

- $a'b'c'd$
- $ab'c'$
- $b'cd'$

DeMorgan's
Distributivity

DeMorgan's
absorption

absorption

DeMorgan's

DeMorgan's


distributivity

distributivity

commutativity

Complement


$$\begin{aligned}
 & ((ab + c)'(ac + (b' + c' + a'cd)') + a((b + c)(b + d) + c)')' \\
 & ((ab)'c') (ac + (b' + (c' + a'cd)')) + a((b + cd) + c)' \\
 & ((a' + b')c') (ac + (b' + (c' + a'd))) + a(b + (cd + c))' \quad \text{absorption} \\
 & ((a' + b')c') (ac + (b' + c' + a'd)) + a((b + c)')' \\
 & c'(a' + b') (ac + (bc(a'd)')) + a(b'c') \\
 & c'(a' + b') (ac + (bc(a'd))) + a(b'c') \\
 & c'(a' + b') (ac + bca + bcd') + a(b'c') \\
 & c'(a' + b') (c(a + ab + cd')) + a(b'c') \\
 & c'(a' + b') (a + ab + cd') + a(b'c')
 \end{aligned}$$

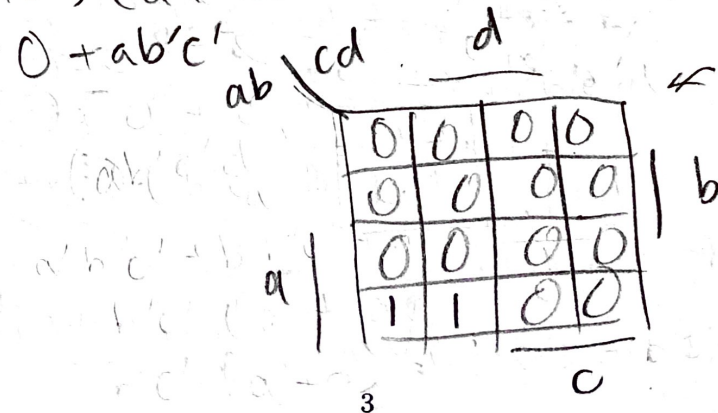

no way to represent this other ways
∴ only one answer

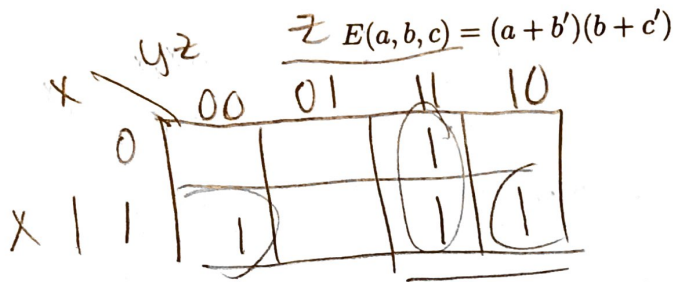Problem 3 (15 points)

Show if the gate G , described by $G(x, y, z) = \text{one-set}\{3, 4, 6, 7\}$, can implement NOT and AND gates. Assume that 0 and 1 are available. If it can, then use G gates to implement the following expression and show the corresponding network of G gates




$$G(x, y, z) = zy + z'x$$



$$G(0, y, z) = zy + z'(0) = zy \rightarrow \text{AND gate} \quad \checkmark$$

$$G(1, 0, z) = z(0) + z'(1) = z' \rightarrow \text{NOT gate} \quad \checkmark$$

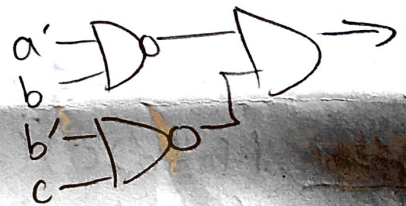
$$\begin{aligned} E(a, b, c) &= (a + b')(b + c') \\ &= ((a + b')(b + c'))'' \\ &= ((a + b')' + (b + c')')' \\ &= (a'b + b'c)' \end{aligned}$$



Ideas
- bubble
 \Rightarrow

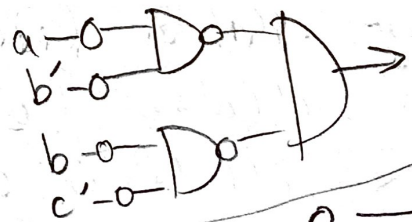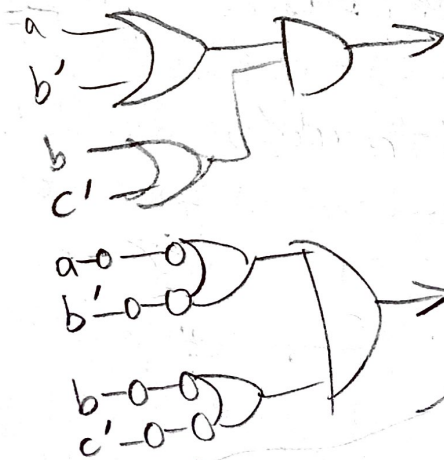

Using G gates:

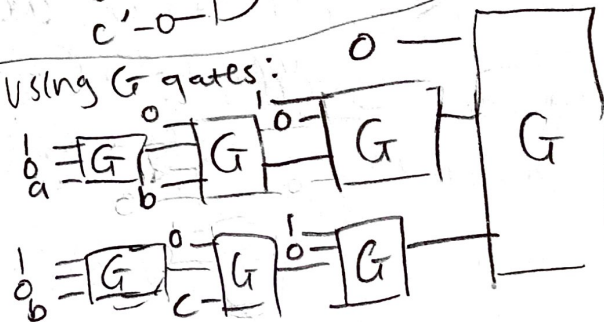

$$\text{NAND} = G(1, 0, G(0, y, z))$$


$$G(0, G(1, 0, G(0, G(1, 0, a), b)), G(1, 0, G(0, G(1, 0, b), c)))$$

\downarrow AND \downarrow NOT \downarrow AND \downarrow not \downarrow NOT \downarrow AND \downarrow not


$$\text{AND}(\text{NOT}(\text{AND}(\text{NOT}(a), b)), \text{NOT}(\text{AND}(\text{NOT}(b), c)))$$

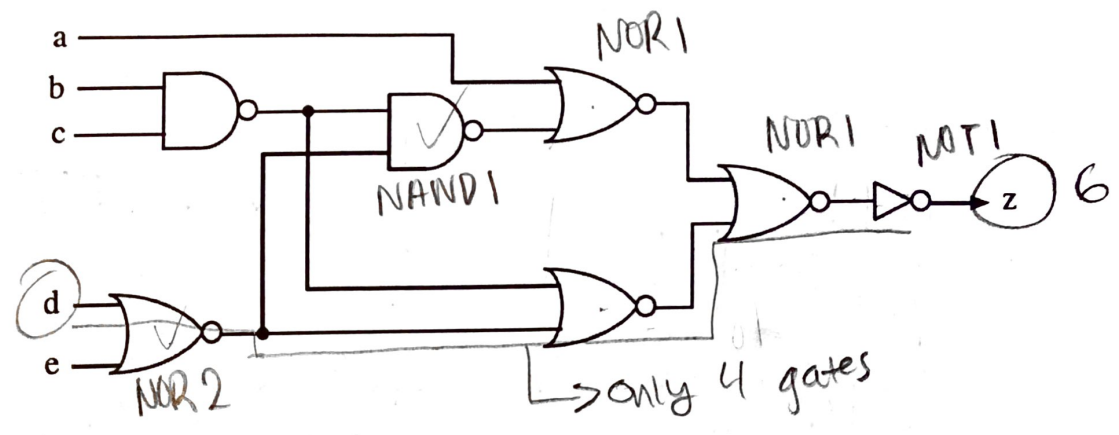Problem 4 (15 points)

With the help of the table below, determine the low to high propagation delay $t_{pLH}(d, z)$ of the output z of the network shown below. Assume the network output has a load of 6.




Gate Type	Fan-in	Propagation Delays (ns)		Load Factor
		t_{pLH}	t_{pHL}	
NOT	1	$0.02 + 0.038L$	$0.05 + 0.017L$	1.0
NAND	2	$0.05 + 0.038L$	$0.08 + 0.027L$	1.0
NOR	2	$0.06 + 0.075L$	$0.07 + 0.016L$	1.0

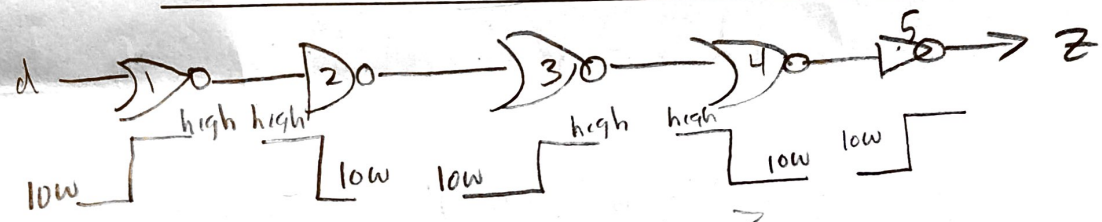

$$(0.06 + 0.075(2)) + (0.08 + 0.027(1)) + (0.06 + 0.075(1)) + (0.07 + 0.016(1)) + (0.02 + 0.038(6))$$

$$0.786 \text{ ns}$$

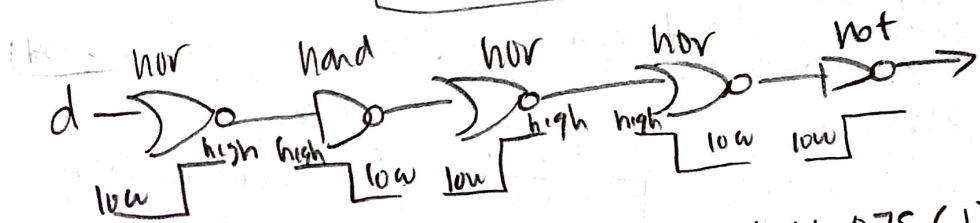

$$0.06 + 0.075(2) + (0.08 + 0.027(1)) + 0.06 + 0.075(1) + 0.07 + 0.016(1) + (0.02 + 0.038(6)) = 0.786 \checkmark$$

Problem 5 (20 points)

Obtain a two-level gate network of the following system.

Inputs: $x, y \in \{0, 1, 2, 3\}$
 Outputs: $z \in \{0, 1, 2, 3\}$
 Function: $z = \{3xy + 1\} \text{ mod } 4$

1. (2 points) Complete the switching table using binary encoding for all values.

x	y		x_1	x_0	y_1	y_0	z_1	z_0
0	0	1	0	0	0	0	0	0
0	1	1	0	0	0	1	0	1
0	2	1	0	0	1	0	0	1
0	3	1	0	0	1	1	0	1
1	0	3	0	1	0	0	0	1
1	1	3	0	1	0	1	0	0
1	2	2	0	1	1	0	1	0
1	3	2	0	1	1	1	1	0
2	0	3	1	0	0	0	0	1
2	1	3	1	0	0	1	0	1
2	2	3	1	0	1	0	0	1
2	3	3	1	0	1	1	0	1
3	0	2	1	1	0	0	0	1
3	1	2	1	1	0	1	0	1
3	2	0	1	1	1	0	1	1
3	3	0	1	1	1	1	1	1

x, x_0	y, y_0	z_1	z_0
00	00	0	0
01	01	0	1
11	01	0	1
10	01	0	1
00	10	0	1
01	10	0	0
11	10	1	0
10	10	1	0

2. (5 points) Show the switching expressions of z_1 and z_0 in sum of minterms form.

$$z_1 = \sum m(6, 7, 9, 11, 13, 14)$$

$$z_0 = \sum m(0, 1, 2, 3, 4, 8, 9, 10, 11, 12, 14)$$

NAND-NAND:

$$z_1: \text{NAND}(\text{NAND}(x, y_0, y_1'), \text{NAND}(y_0, x_0', x_1), \text{NAND}(x_0, y_0', y_1), \text{NAND}(y_1, x_0, x_1'))$$

$$z_0: \text{NAND}(y_0, x_0)$$

3. (8 points) Show the minimal sum of products expressions of z_1 and z_0 . In each case, show a K-map, indicate all prime implicants, and all essential prime implicants. Show NAND-NAND networks.

z_1

x, x_0	y, y_0	z_1
00	00	0
01	01	0
11	01	0
10	01	0
00	10	0
01	10	1
11	10	1
10	10	1

PI: $x_1 y_0 y_1'$
 $y_0 x_0' x_1$
 $x_0 y_0' y_1$
 $y_1 x_0 x_1'$

EPI: same as PI, all essential

z_0

x, x_0	y, y_0	z_0
00	00	1
01	01	1
11	01	1
10	01	1
00	10	1
01	10	1
11	10	1
10	10	1

prime implicants:
 y_0', x_0'
 essential prime implicants:
 y_0', x_0'


SOP: $y_0' + x_0'$

$(y_0' + x_0')$

SOP: $x_1 y_0 y_1' + y_0 x_0' x_1 + x_0 y_0' y_1 + y_1 x_0 x_1'$

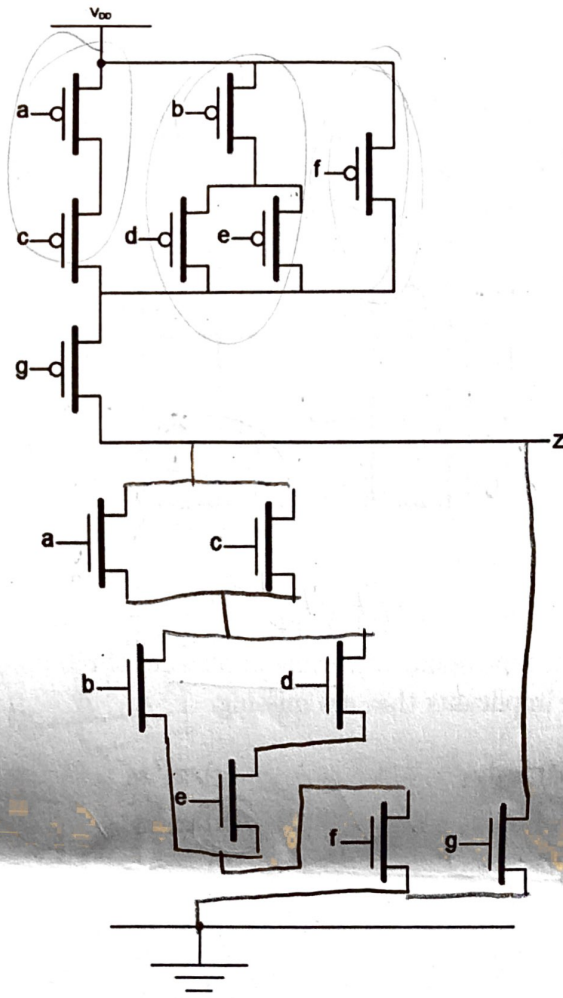Problem 6 (10 points)

We are given the following partial CMOS network.



1. (5 points)

Write the expression for the pull-up network. From this, derive the expression for the pull-down network using switching algebra.

2. (5 points) Connect NMOS transistors to complete the circuit according to the pull-down expression. Please only add missing wires.

$$1) \quad z = (a'c' + b'(d'+e') + f')g' \leftarrow \text{pull up}$$


$$\begin{aligned} z' &= (a'c' + b'(d'+e') + f')g' \\ &= ((a'c')' (b'(d'+e'))' f) + g \\ &= (a+c) (b+(d'+e'))' f + g \end{aligned}$$

$$z' = ((a+c) (b+ed) f + g) \leftarrow \text{pull down}$$

Problem 7 (15 points)


For $f(x_3, x_2, x_1, x_0) = (x_3 + x_2' + x_1 + x_0)(x_3 + x_2' + x_1' + x_0)(x_3' + x_2 + x_1 + x_0')(x_3' + x_2' + x_1 + x_0)(x_3' + x_2' + x_1 + x_0')(x_3' + x_2' + x_1' + x_0)$

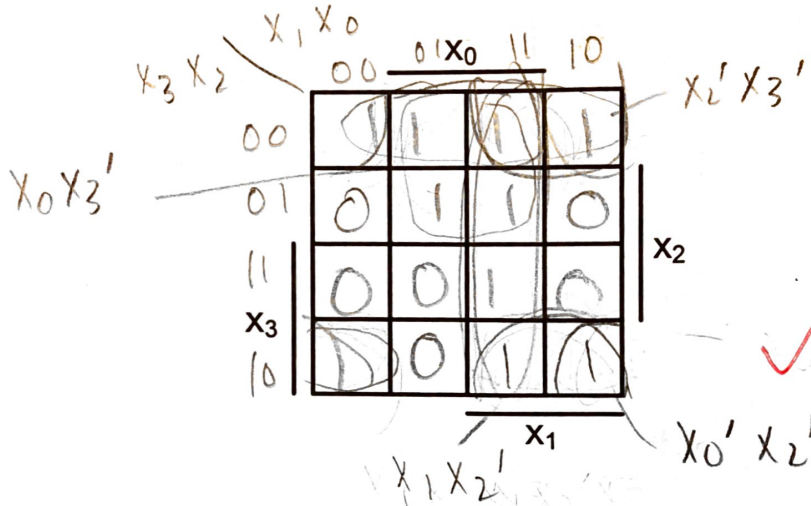1. (2 points) Fill out the following K-map.



2. (4 points) Which of the given expressions are prime implicants of the function given above? Circle all that apply. Write down any prime implicants that are missing.

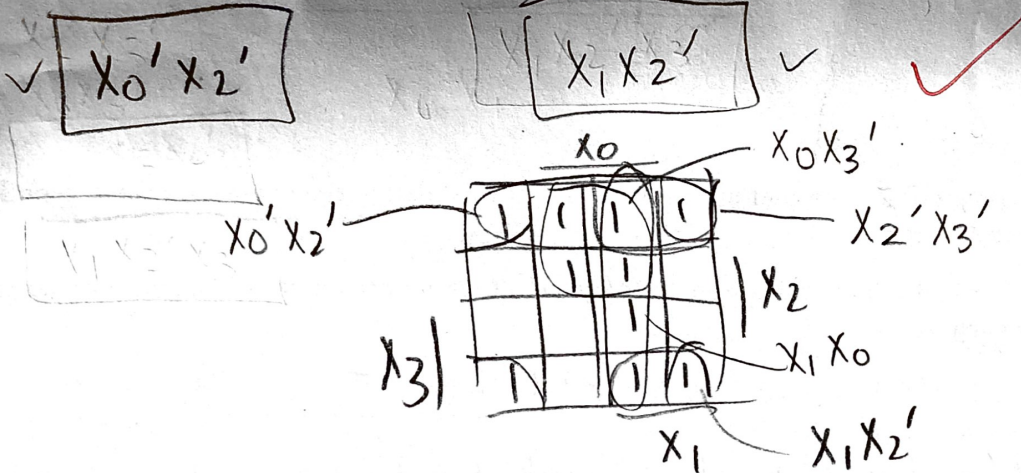- (a) x_1
- (d) $x_3'x_1$
- (g) $x_2'x_0$
- (j) $x_3'x_2'x_1$
- (b) x_3x_1
- (e) $x_3'x_0$
- (h) x_1x_0
- (k) $x_2x_1x_0$
- (c) $x_3'x_2'$
- (f) x_2x_1
- (i) x_1x_0'
- (l) $x_3x_2x_1x_0$



3. (2 points) Write down the complete set of essential prime implicants.

$x_0x_3', x_0'x_2', x_1x_0$

4. (1 point) Write the minimal sum of products expression for f . Is it unique?

$x_0'x_2' + x_1x_0 + x_0x_3'$

Yes, it is unique.