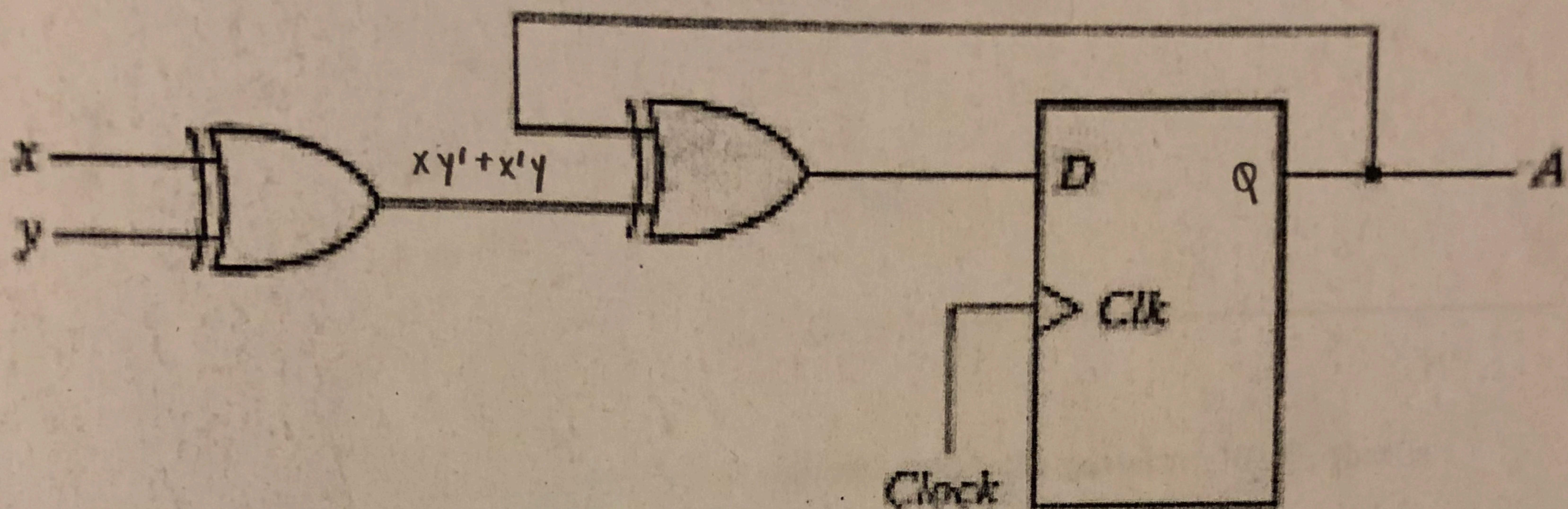


Problem 3 (15 points) We have a D flip flop circuit below. Provide the state transition table and state transition diagram.



Circuit diagram

PS	NS
0	1
1	0

$$D(t) = (x \oplus y) \oplus Q(t)$$

XOR	
0	1
0	0 1
1	1 0

PS = Q(t)	Input (XY)				Input (XY)				$Q_0 Q_1$
	00	01	10	11	00	01	10	11	
0	0	1	1	0	0	1	1	0	
1	1	0	0	1	1	0	0	1	

NS, Z

$D(t)$

$$D(t) = Q(t+1)$$

Q	Input (XY)			
	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$$D(t) = Qx'y' + Q'y'x + Qxy + Q'xy'$$

State diagram missing

