

# [CS M51A FALL 19] SOLUTION TO QUIZ 2

Duration: 30 minutes. Closed books and notes. Total: 30 points

TAs

10/25/2019

## Problem 1 (20 Points)

Consider the gate network in Figure 1.

 


Figure 1: Gate network

- a. Determine the switching expressions for the outputs  $F_i$  and  $C_{i+1}$ . Using AND, OR, NOT, XOR expressions as appropriate fill in the following table.

$M$	$S_1 S_0$	Expression for $F_i$	Expression for $C_{I+1}$
0	00		
0	01		
0	10		
1	10		
1	11		

**Solution**

a.  $F_i = (S_1 B_i) \oplus [(A_i \oplus S_0) \oplus (M \cdot C_i)]$

$$C_{i+1} = (S_0 \oplus A_i)(M \cdot C_i) + (S_1 B_i)[(A_i \oplus S_0) \oplus (M \cdot C_i)]$$

$M$	$S_1 S_0$	Expression for $F_i$	Expression for $C_{I+1}$
0	00	$A_i$	0
0	01	$A'_i$	0
0	10	$A_i \oplus B_i$	$A_i B_i$
1	10	$C_i \oplus A_i \oplus B_i$	$C_i A_i + (C_i \oplus A_i) B_i$
1	11	$C_i \oplus A'_i \oplus B_i$	$C_i A'_i + (C_i \oplus A'_i) B_i$

b. Using the gate characteristics given below, determine equation for the propagation delay  $t_{pLH}$  of the path going from the input  $A_i$  to the output  $C_{i+1}$ . You don't need to calculate the final value. Assume that  $C_i = 0$ ,  $B_i = 1$ ,  $S_1 = 1$ , and  $S_0 = 1$ . The output  $C_{i+1}$  has a load  $L = 3$  on the output. What is the size of the network in equivalent gates?

*AND*:  $t_{pLH} = 0.15 + 0.037L$ ,  $t_{pHL} = 0.16 + 0.017L$ , input load factor = 1, size = 2

*OR*:  $t_{pLH} = 0.12 + 0.037L$ ,  $t_{pHL} = 0.2 + 0.019L$ , input load factor = 1, size = 2

*XOR*: size = 3

wrt left input:  $t_{pLH} = 0.3 + 0.036L$ ,  $t_{pHL} = 0.3 + 0.021L$ , input load factor = 1.1

wrt right input:  $t_{pLH} = 0.16 + 0.036L$ ,  $t_{pHL} = 0.15 + 0.020L$ , input load factor = 2.1

**Solution**

b. The path is  $X_1 \rightarrow X_2 \rightarrow A_4 \rightarrow O_1$ :

$$\begin{aligned} t_{pLH} &= t_{pLH} + t_{pLH} + t_{pLH} + t_{pLH} \\ &= [0.16 + 0.036 \times (1.1 + 1)] + [0.3 + 0.036 \times (1 + 2.1)] \\ &\quad + [0.15 + 0.037 \times 1] + [0.12 + 0.037 \times 3] \end{aligned}$$

The size of the network is  $4 \times 2 + 1 \times 2 + 3 \times 3 = 19$  equivalent gates.

**Problem 2 (10 points)**

Give switching expressions describing the function of the circuit in Figure 2 and show that the circuit is valid.

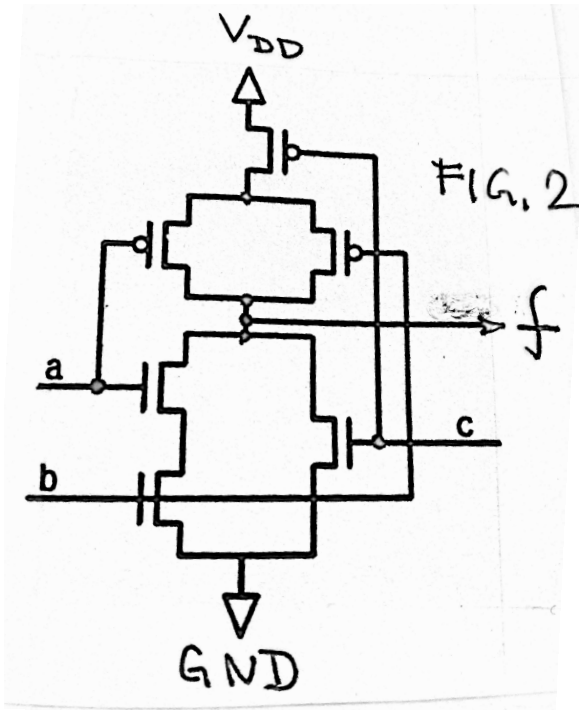


Figure 2: CMOS Circuitk

***Solution***

From the Pull Down Network:  $f' = ab + c$  and  $f = (ab + c)' = (a' + b')c'$

From the Pull Up Network:  $f = (a' + b')c'$  confirming the validity of the network.