

# [CS M51A FALL 18] MIDTERM EXAM

Date: 10/30/18

- The midterm is closed book, and up to 4 sheets (= 8 pages) of summary notes are allowed. You can use a calculator but not smart phones.
- For multiple choice questions, wrong answers may have a negative score value so choose carefully. It is possible that questions can have multiple answers.
- Please show all your work and write legibly, otherwise no partial credit will be given.
- This should strictly be your own work; any form of collaboration will be penalized.

Name : \_\_\_\_\_

Student ID : \_\_\_\_\_

Problem	Points	Score
1	10	10
2	15	15
3	15	11
4	15	15
5	20	20
6	10	10
7	15	8
Total	100	89

16,000,000

Problem 1 (10 points)

1. (4 points) How many bits are required to encode a color spectrum capable of supporting 16 million colors using:

a. Decimal digits in BCD

4 x 8 = 32

(although 3 can be eliminated since the tens millions place has a max. value of 1)

b. Hexadecimal representation

F -----  
16<sup>5</sup> 16<sup>4</sup> 16<sup>3</sup> 16<sup>2</sup> 16<sup>1</sup> 16<sup>0</sup>

6 ⇒ 6 x 4 = 24

Which representation is more efficient? Why?

Hexadecimal is more efficient because it takes up considerably fewer bits than BCD does.

2. (6 points) Fill in the missing entries in the table.

Radix	Digit vector $\underline{x}$	Value $x$ in decimal
16	(5, 1, 7)	1303
8	(5, 1, 7)	335
7	(4, 5, 3, 2)	1640

5 1 7  
16<sup>2</sup> 16<sup>1</sup> 16<sup>0</sup>

4 5 3 2  
7<sup>3</sup> 7<sup>2</sup> 7<sup>1</sup> 7<sup>0</sup>

5 1 7  
8<sup>2</sup> 8<sup>1</sup> 8<sup>0</sup>

Problem 2 (15 points)

$a + b = b + a$	$ab = ba$	Commutativity
$a + (bc) = (a + b)(a + c)$	$a(b + c) = (ab) + (ac)$	Distributivity
$a + (b + c) = (a + b) + c = a + b + c$	$a(bc) = (ab)c = abc$	Associativity
$a + a = a$	$aa = a$	Idempotency
$a + a' = 1$	$aa' = 0$	Complement
$1 + a = 1$	$0a = 0$	
$0 + a = a$	$1a = a$	Identity
$(a')' = a$		Involution
$a + ab = a$	$a(a + b) = a$	Absorption
$a + a'b = a + b$	$a(a' + b) = ab$	Simplification
$(a + b)' = a'b'$	$(ab)' = a' + b'$	DeMorgan's law

Given  $E(a, b, c, d) = (ab + c)'(ac + (b' + c' + a'd)') + a((b + c)(b + d) + c)'$ , which of the following represents the same function as  $E(a, b, c, d)$ ? Show all your work.

- $a + b + c + d'$
- $a' + b + c$
- $b + c' + d$

- $a'b'c'd$
- $ab'c'$
- $b'cd'$

$E(a, b, c, d) = (ab + c)'(ac + (b' + c' + a'd)') + a((b + c)(b + d) + c)'$   
 $\xrightarrow{\text{DeMorgan's}} E(a, b, c, d) = \underline{(a' + b')c'}(ac + bc(a + d')) + a(b'c')$   
 $= c'((a' + b')(ac + bc(a + d')) + ab')$   
 $= c'((a' + b')(ac + abc + bcd')) + ab'$   
 $= c'(a'ac + a'abc + a'bcd' + b'ac + b'abc + b'bcd' + ab')$   
 $= c'(a'bcd' + b'ac + ab')$   
 $= \underline{ab'c'}$

### Problem 3 (15 points)

Show if the gate G, described by  $G(x, y, z) = \text{one-set}\{3, 4, 6, 7\}$ , can implement NOT and AND gates. Assume that 0 and 1 are available. If it can, then use G gates to implement the following expression and show the corresponding network of G gates

$$E(a, b, c) = (a + b')(b + c')$$

x	y	z	G
0	0	0	0
1	0	0	0
2	0	1	0
3	0	1	1
4	1	0	1
5	1	0	0
6	1	1	1
7	1	1	1

$$G = x'yz + xy'z' + xyz' + xyz$$

0	0	1	0
1	0	1	1
2	1	0	1
3	1	0	0

$$G = yz + xz'$$

$$G(1, 0, z) = z'$$

NOT ✓

$$G(0, y, z) = yz$$

AND ✓

$$E(a, b, c) = ab + b'b' + ac' + b'c' \quad \checkmark \text{ distributivity}$$

$$= ab + ac' + b'c'$$

$$= ((ab)' \cdot (ac')' \cdot (b'c')')'$$

$$= \text{NOT}(\text{AND}(a, b)) \cdot \text{NOT}(\text{AND}(a, \text{NOT}(c)))$$

$$= \text{NOT}(\text{AND}(\text{AND}(a, b), \text{AND}(a, \text{NOT}(c))))$$

$$= G(1, 0, G(0, G(1, 0, G(0, a, b)), G(0, G(1, 0,$$

$$G(0, a, G(1, 0, c))) G(1, 0, G(0, G(1, 0, b), G(1, 0, c))))))$$


~~NW~~ missing

11

12 G gates

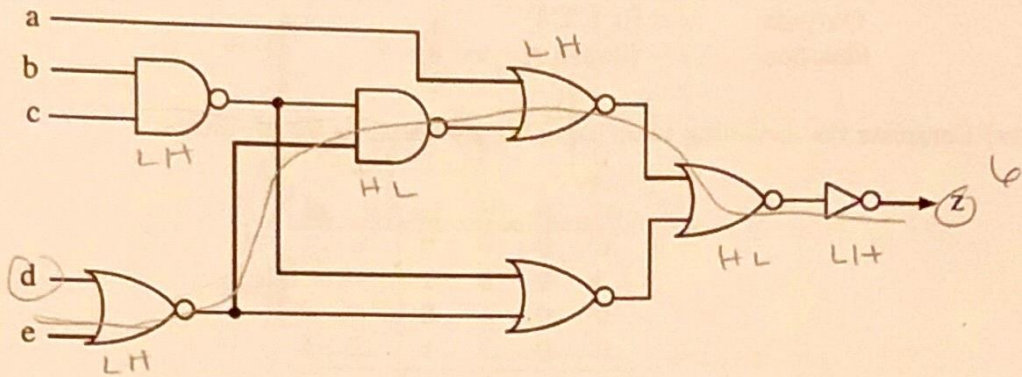
### Problem 4 (15 points)

With the help of the table below, determine the low to high propagation delay  $t_{pLH}(d, z)$  of the output  $z$  of the network shown below. Assume the network output has a load of 6.



NOR worse than NAND for LH

Gate Type	Fan-in	Propagation Delays (ns)		Load Factor
		$t_{pLH}$	$t_{pHL}$	
NOT	1	$0.02 + 0.038L$	$0.05 + 0.017L$	1.0
NAND	2	$0.05 + 0.038L$	$0.08 + 0.027L$	1.0
NOR	2	$0.06 + 0.075L$	$0.07 + 0.016L$	1.0

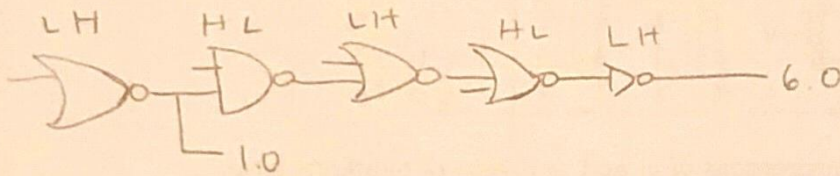

$$0.06 + 0.075(2) = 0.21$$

$$0.08 + 0.027(1) = 0.107$$

$$0.06 + 0.075(1) = 0.135$$

$$0.07 + 0.016(1) = 0.086$$

$$0.02 + 0.038(6) = 0.248$$

$$t_{pLH}(d, z) = 0.786$$

**Problem 5 (20 points)**

Obtain a two-level gate network of the following system.

Inputs:  $x, y \in \{0, 1, 2, 3\}$   
 Outputs:  $z \in \{0, 1, 2, 3\}$   
 Function:  $z = \{3xy + 1\} \pmod 4$

1. (2 points) Complete the switching table using binary encoding for all values.

$3xy+1$	$x$	$y$	$x_1$	$x_0$	$y_1$	$y_0$	$z_1$	$z_0$	$z$
1	0	0	0	0	0	0	0	1	1
1	0	1	0	0	0	1	0	1	1
1	0	2	0	0	1	0	0	1	1
1	0	3	0	0	1	1	0	1	1
4	1	0	0	1	0	0	0	1	1
7	1	1	0	1	0	1	0	0	3
10	1	2	0	1	1	0	1	1	2
13	1	3	0	1	1	1	1	0	2
7	2	0	1	0	0	0	0	1	3
13	2	1	1	0	0	1	0	1	1
19	2	2	1	0	1	0	1	1	3
1	2	3	1	0	1	1	1	1	3
10	3	0	1	1	0	0	0	1	1
19	3	1	1	1	0	1	1	0	2
14	3	2	1	1	1	0	1	1	3
16	3	3	1	1	1	1	0	0	0

2. (5 points) Show the switching expressions of  $z_1$  and  $z_0$  in sum of minterms form.

$$z_1 = \sum m(6, 7, 9, 11, 13, 14)$$

$$z_0 = \sum m(0, 1, 2, 3, 4, 6, 8, 9, 10, 11, 12, 14)$$

3. (8 points) Show the minimal sum of products expressions of  $z_1$  and  $z_0$ . In each case, show a K-map, indicate all prime implicants, and all essential prime implicants. Show NAND-NAND networks.

$z_1$ :

	$y_0$			
	0	0	0	0
	0	0	1	1
$x_0$	0	1	0	1
	0	1	1	0
	$y_1$			

PI:  $y_0 y_1' x_1, y_0 x_0' x_1, y_1 x_0 x_1', y_0' y_1 x_0$

All are essential.

$$z_1 = y_0 y_1' x_1 + y_0 x_0' x_1 + y_1 x_0 x_1' + y_0' y_1 x_0$$


↓ NAND-NAND

$$z_1 = \left( (y_0 y_1' x_1)' \cdot (y_0 x_0' x_1)' \cdot (y_1 x_0 x_1')' \cdot (y_0' y_1 x_0)' \right)'$$

$z_0$  is at back of exam

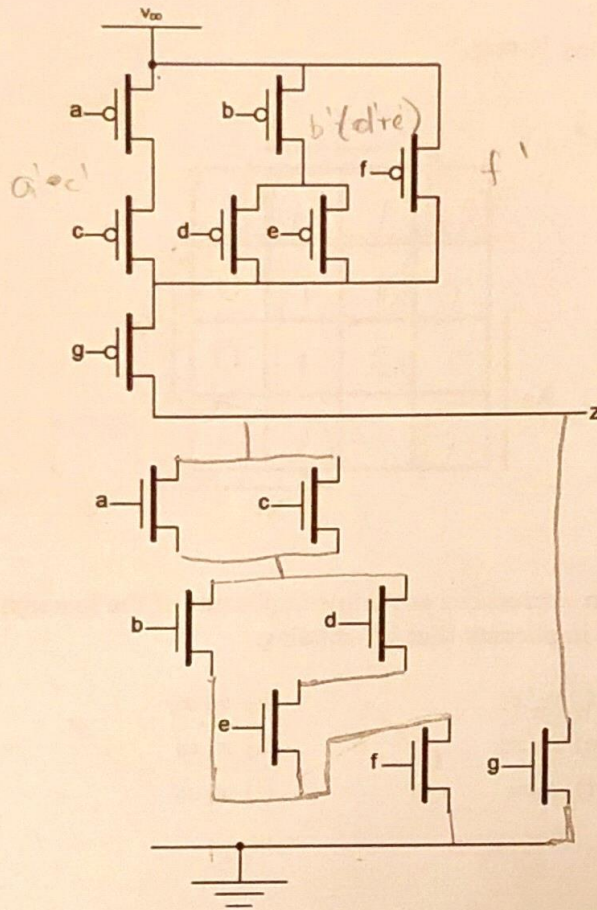Problem 6 (10 points)

We are given the following partial CMOS network.



1. (5 points)

Write the expression for the pull-up network. From this, derive the expression for the pull-down network using switching algebra.

2. (5 points) Connect NMOS transistors to complete the circuit according to the pull-down expression. Please only add missing wires.

$$z = g' (a'c' + b'(d'+e') + f')$$


$$z' = (g' (a'c' + b'(d'+e') + f'))' \leftarrow \text{de Morgan's}$$

$$= g + (a+c)(b+de)(f)$$

Problem 7 (15 points)

For  $f(x_3, x_2, x_1, x_0) = (x_3 + x_2' + x_1 + x_0)(x_3 + x_2' + x_1' + x_0)(x_3' + x_2 + x_1 + x_0')(x_3' + x_2' + x_1 + x_0)(x_3' + x_2' + x_1 + x_0')(x_3' + x_2' + x_1' + x_0)$

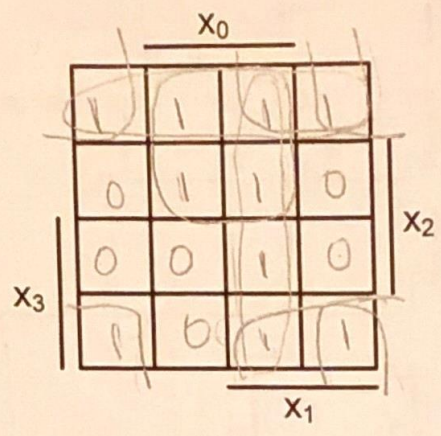1. (2 points) Fill out the following K-map.



2. (4 points) Which of the given expressions are prime implicants of the function given above? Circle all that apply. Write down any prime implicants that are missing.

- (a)  $x_1$
- (d)  $x_3'x_1$
- (g)  $x_2'x_0$
- (j)  $x_3'x_2'x_1$
- (b)  $x_3x_1$
- (e)  $x_3'x_0$  ✓
- (h)  $x_1x_0$  ✓
- (k)  $x_2x_1x_0$
- (c)  $x_3'x_2'$  ✓
- (f)  $x_2x_1$
- (i)  $x_1x_0'$
- (l)  $x_3x_2x_1x_0$

Handwritten notes for question 2:  $x_0'x_2'$  (circled),  $x_3'x_0$ ,  $x_0x_1$ ,  $x_2'x_1$  (circled),  $x_3'x_2'$ . An arrow points from the circled  $x_2'x_1$  to the word "missing" with an arrow pointing to the circled  $x_0'x_2'$ .

3. (2 points) Write down the complete set of essential prime implicants.

Handwritten answer:  $x_0x_1, x_3'x_0, x_2'x_0'$

4. (1 point) Write the minimal sum of products expression for  $f$ . Is it unique?

Handwritten answer:  $f = x_0x_1 + x_3'x_0 + x_0'x_2'$  Yes. it is unique



5.3)

$$\Sigma m(0, 1, 2, 3, 4, 6, 8, 9, 10, 11, 12, 14)$$

$z_0$

	$y_0$			
$y_0$	1	1	1	1
	1	0	0	1
	1	0	0	1
	1	1	1	1

$x_1$

$y_1$

PI:  $x_0'$ ,  $y_0'$ ,  $x_0 y_0'$ ,  $x_0 y_0$

both are essential:

$$z_0 = x_0' + y_0'$$

NAND-NAND

$$z_0 = (x_0 y_0)'$$