

[CS M51A F19] SOLUTION TO QUIZ 3

Date: 11/15/19

TAs

Quiz Problems (30 points total)

Problem 1 (15 points)

Design a pattern recognizer which takes a stream of binary bits as input, one bit at each clock. The output is 1 when it detects a string of 001, 011 or 100. The input signal is $x(t)$, and the output signal is $z(t)$.

- (7 points) Fill in the empty slots in the state transition and output table.

Solution

PS	$x = 0$	$x = 1$
S_{init}	$S_0, 0$	$S_1, 0$
S_0	$S_{00}, 0$	$S_{01}, 0$
S_1	$S_{10}, 0$	$S_{11}, 0$
S_{00}	$S_{00}, 0$	$S_{01}, 1$
S_{01}	$S_{10}, 0$	$S_{11}, 1$
S_{10}	$S_{00}, 1$	$S_{01}, 0$
S_{11}	$S_{10}, 0$	$S_{11}, 0$
	NS, z	

- (8 points) Minimize the number of states in the transition table, and show the final minimized table. Use G_1, G_2, \dots for the states in the minimal state table.

Solution Looking at the output of the previous table, we first get P_1 as shown:

$$P_1 = (S_{init}, S_0, S_1, S_{11}) \text{ (output 0/0)}, (S_{00}, S_{01}) \text{ (output 0/1)}, \text{ and } (S_{10}) \text{ (output is 1/0)}.$$

	group 1				group 2		g3
	S_{init}	S_0	S_1	S_{11}	S_{00}	S_{01}	S_{10}
0	1	2	3	3	2	3	
1	1	2	1	1	2	1	

$$P_2 = (S_{init}), (S_0), (S_1, S_{11}), (S_{00}), (S_{01}), (S_{10})$$


	g1	g2	g3		g4	g5	g6
	S_{init}	S_0	S_1	S_{11}	S_{00}	S_{01}	S_{10}
0			6	6			
1			3	3			

Since $P_3 = P_2$, we stop. By naming each group, we can write the following table.

PS	$x = 0$	$x = 1$
$G1$	$G2, 0$	$G3, 0$
$G2$	$G4, 0$	$G5, 0$
$G3$	$G6, 0$	$G3, 0$
$G4$	$G4, 0$	$G5, 1$
$G5$	$G6, 0$	$G3, 1$
$G6$	$G4, 1$	$G5, 0$
	NS, z	

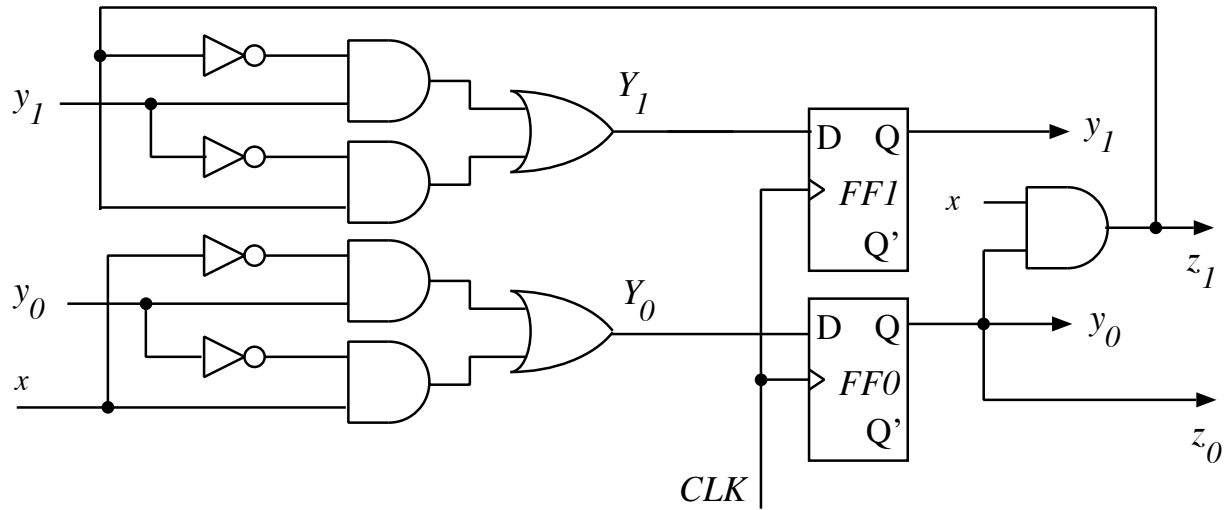Problem 2 (15 points)

For the canonical sequential network shown bellow, determine:



a. (3 points) The switching expressions for the next-state variables and the outputs:

$$Y_1 =$$

$$Y_0 =$$

$$z_1 =$$

$$z_0 =$$

Solution

$$Y_1 = xy_0 \oplus y_1$$

$$Y_0 = x \oplus y_0$$

$$z_1 = xy_0$$

$$z_0 = y_0$$

b. (4 points) The next-state and the output table (binary-level):

<i>PS</i>	y_1y_0	$x = 0$	$x = 1$
<i>A</i>	00	00,00	01,00
<i>B</i>	01		
<i>C</i>	10		
<i>D</i>	11		
		Y_1Y_0, z_1z_0	

Solution

PS	y_1y_0	$x = 0$	$x = 1$
A	00	00,00	01,00
B	01	01,01	10,11
C	10	10,00	11,00
D	11	11,01	00,11
		Y_1Y_0, z_1z_0	

c. (4 points) The next-state and the output table (high-level). Let $z = 2z_1 + z_0$:

PS	$x = 0$	$x = 1$
A	$A, 0$	$B, 0$
B		
C		
D		
		NS, z

Solution

PS	$x = 0$	$x = 1$
A	$A, 0$	$B, 0$
B	$B, 1$	$C, 3$
C	$C, 0$	$D, 0$
D	$D, 1$	$A, 3$
		NS, z

d. (2 points) Is this a minimal FSM? If not, find the minimal FSM.

Solution

Not minimal.

$P_1 = (\{A, C\}, \{B, D\}) = P_2$. The minimal FSM is

PS	$x = 0$	$x = 1$
A	$A, 0$	$B, 0$
B	$B, 1$	$A, 3$
		NS, z

If the initial state is A and the input is $x(0, 5) = 011010$, show $z(0, 5)$

Solution

t	0	1	2	3	4	5
$x(t)$	0	1	1	0	1	0
$s(t)$	A	A	B	C	C	D
$z(t)$	0	0	3	0	0	1