

Problem 1 (20 points)

a) $(25)_{11} = (x)_y$

Find base y , such that the number of non-leading zeros in x is maximum.

Example:

The number of non-leading zeros in 10021 is 2.

The number of non-leading zeros in 204003 is 3.

b) $(A1965321)_{16} = (a)_8$

Find the value for a .

a) $(25)_{11} = (5)_{10} + (22)_{11} = (27)_{10}$

$(27)_{10} = (11011)_2 \Rightarrow 1 \text{ 0's}$ $(1000)_3$

$(27)_{10} = (300)_3 \times \Rightarrow 2 \text{ 0's} \Rightarrow \text{Most zero's}$

$(27)_{10} = (123)_4 = 0 \text{ 0's}$

Base $y = 3$

7

b) $(A1965321)_{16} = (a)_8$

$= (1010 \ 0001 \ 1001 \ 0110 \ 0101 \ 0011 \ 0010 \ 0001)_2$

$= (24145451441)_8$

$= (a)_8$

10


18

Problem 2 (20 points)

Create a state transition table that has 8 states, which satisfies the following conditions:


- 1) After minimization, it should have only 3 states.
- 2) Some states which are 2-equivalent are not 3-equivalent.

P.S.	0	1
S_{init}	$S_0/0$	$S_1/0$
S_0	$S_{00}/0$	$S_{01}/0$
S_1	$S_{10}/0$	$S_{11}/0$
S_{00}	$S_{00}/0$	$S_{01}/0$
S_{01}	$S_{10}/0$	$S_{11}/0$
S_{10}	$S_{00}/0$	$S_{101}/1$
S_{11}	$S_{10}/0$	$S_{11}/0$
S_{101}	$S_{10}/0$	$S_{11}/0$

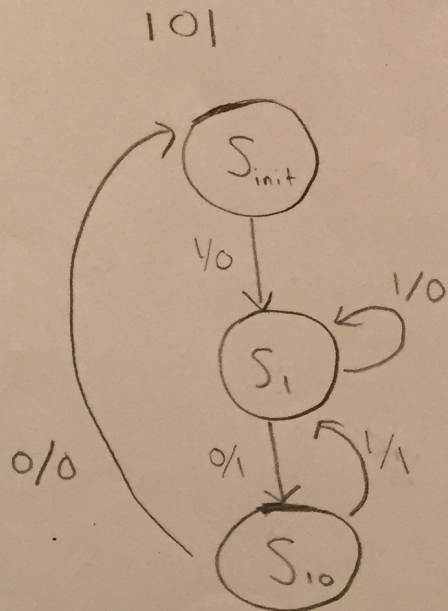

in	0	1	00	01	11	10	S_{10}
1	1	2	1	2	2	2	
1	1	1	1	1	1	1	

didn't show the minimized group →

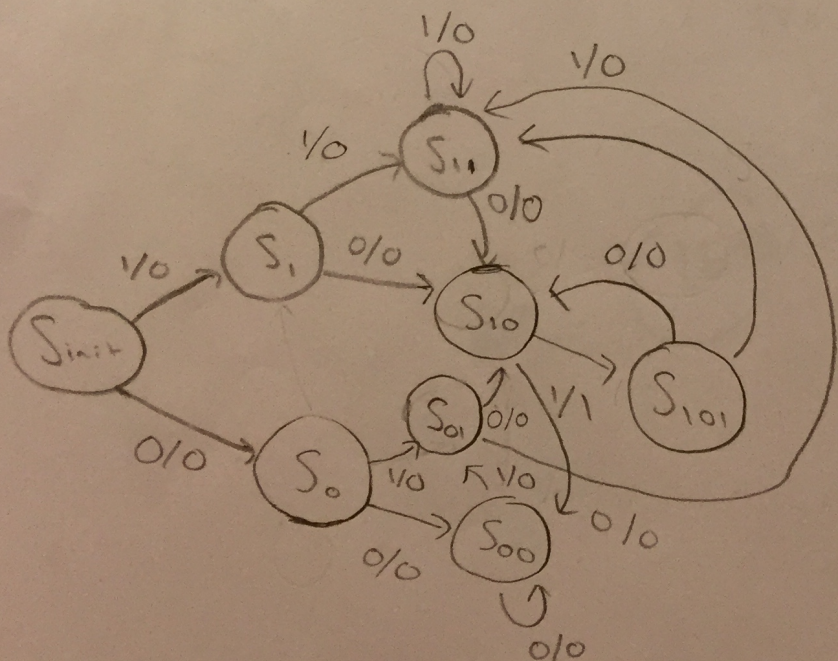

Problem 3 (20 points)

For a K-map, M denotes the number of prime implicants of the K-map, and N denotes the number of essential prime implicants of the K-map. Draw a 4×4 K-map that has the largest value of $P = M - N$ among all the 4×4 K-maps. For example, in the following 4×4 K-map, $M = 3$, $N = 2$, $P = M - N = 1$

	x_0				
	0	0	0	0	
	1	1	0	0	x_2
x_3	1	1	1	0	
	0	0	1	0	
	x_1				

	$x_1 x_0$	00	01	11	10
$x_3 x_2$	00	1	1		1
	01		1	1	1
	11			1	
	10		1	1	1

$M = 12$
 $N = 0$

$P = 12 - 0$

$P = 12$

No grouping of PIs.

~~15-2~~ = 17

Problem 4 (20 points)

$$F(a,b,c,d,e,f) = ((a+b'c)'(a'+de'+f))' + (a'b')$$

a	b	E(a,b)
0	0	1
0	1	0
1	0	1
1	1	1

$$= (a+b'c) + (a'+de'+f)' + \frac{(a'b')}{(a+b)}$$

$$= a + b'c + (af'(d'+e)) + a'b'$$

$$= (a+b'c+a'b')f + (a+b'c+ad'+ae'+a'b')f'$$

a) Use only the "E" gate defined above to implement Boolean function F. You can use constants 0 and 1.

b) Implement the Boolean function F using only multiplexers.


a) $E(a,b) = a'b' + ab' + ab \Rightarrow E(a,b) = a + a'b' \Rightarrow E(a,b) = a + b'$

NOT) $E(0,b) = b'$

$$E(0, E(a,b)) = a'b$$


$$E(a, E(0,b)) = a + b$$

Let $\triangle E = E(a,b)$ as a gate

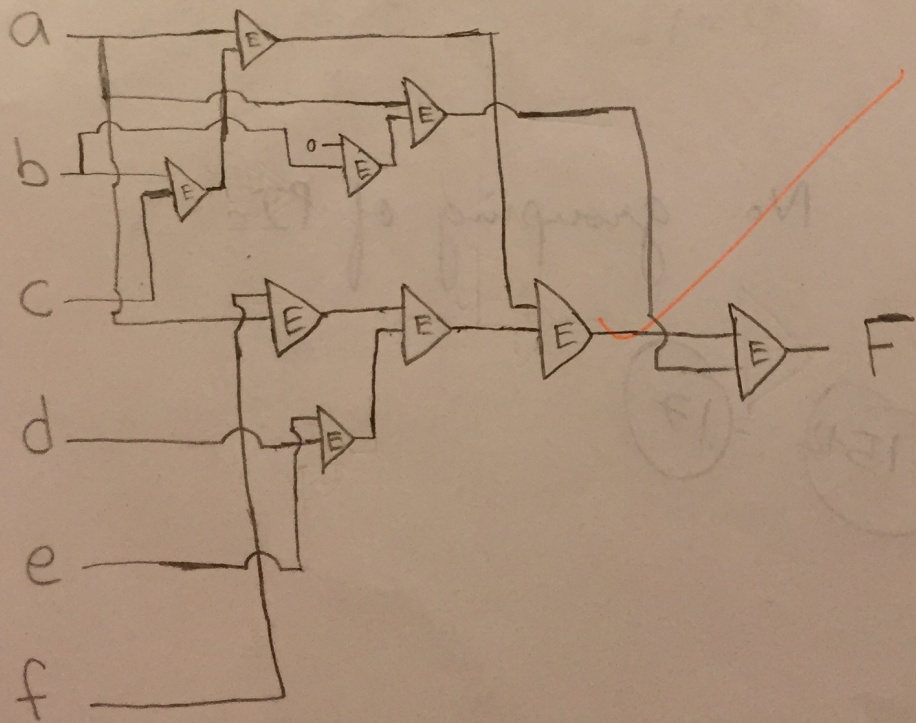


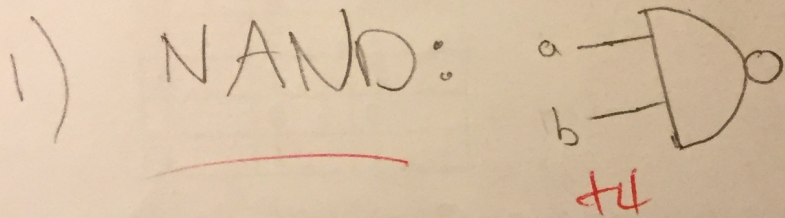Problem 5 (20 points)


Find all the 2 input gates which form universal sets by itself (Universal set with only one gate).
You can use constants 0 and 1.





$$E(a,b) = (ab)'$$
$$= a' + b'$$

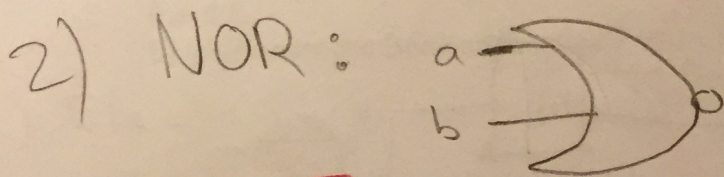


$$E(a,b) = (a+b)'$$
$$= a'b'$$

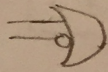3) $E(a,b) = a + b'$ \Rightarrow 

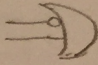4) $E(a,b) = a' + b$ \Rightarrow 

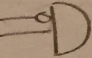5) $E(a,b) = \overline{a'b}$ \Rightarrow 

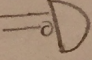6) $E(a,b) = \overline{ab'}$ \Rightarrow 

$+10$

but
missing proof.

$+3$