

Problem 1 (20 points)

Use only the "E" gate defined below to implement Boolean function:

$$F = w'xy' + wxz + w'x'z + wx'y'z'$$







You may also use constants 0 and 1 as inputs.

a	b	c	E(a,b,c)
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$$(a+b+c)(a'+b'+c')$$


$$ab'+ac'+a'b+bc'+a'c+b'c$$

$$E(a,1,1) = a' \text{ NOT}$$

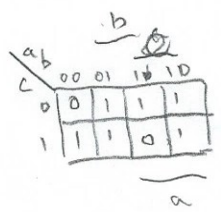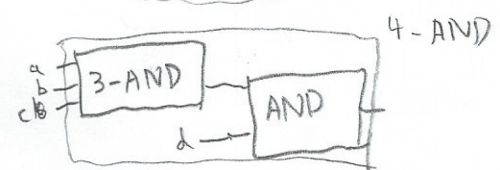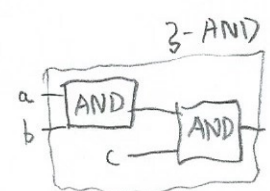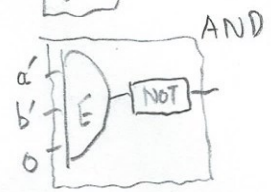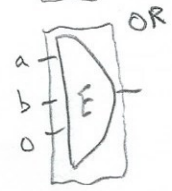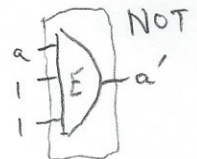

$$ab' + bc' + a'c$$

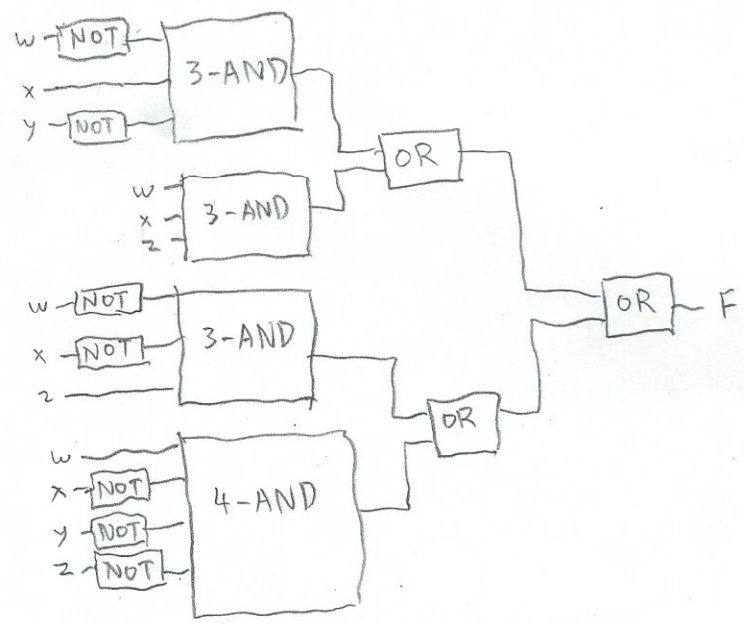
$$E(a,b,0) = ab' + b = a + b \text{ OR}$$



Problem 2 (20 points)

Given the network below, calculate the critical path delay. Consider L → H delay when calculating the critical path.

Gate	Fan-in	t_{pLH}	t_{pHL}
AND	2	$0.15 + 0.037L$	$0.16 + 0.017L$
AND	3	$0.20 + 0.038L$	$0.18 + 0.018L$
OR	2	$0.12 + 0.037L$	$0.20 + 0.019L$
OR	3	$0.12 + 0.038L$	$0.34 + 0.022L$

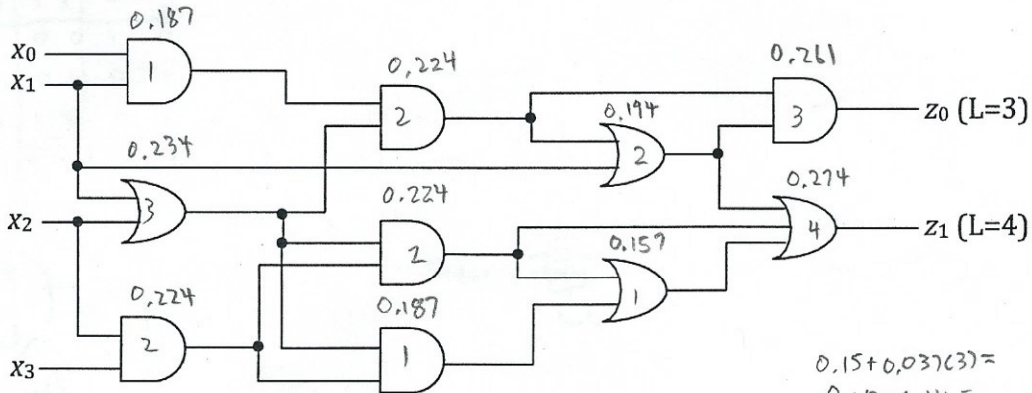

$$0.15 + 0.037(1) = 0.187$$

$$0.12 + 0.037(3) = 0.12 + 0.111 = 0.231$$

$$0.15 + 0.037(2) = 0.15 + 0.074 = 0.224$$

$$0.12 + 0.037(2) = 0.12 + 0.074 = 0.194$$

$$0.12 + 0.037(1) = 0.157$$

$$0.15 + 0.037(3) = 0.15 + 0.111 = 0.261$$

$$0.12 + 0.038(4) = 0.12 + 0.152 = 0.274$$

$$\begin{array}{r} 0.187 \\ 0.224 \\ 0.194 \\ + 0.274 \\ \hline \end{array}$$

$$\begin{array}{r} 21 \\ 0.231 \\ 0.224 \\ 0.194 \\ + 0.274 \\ \hline 0.926 \end{array}$$

$$\begin{array}{r} 0.224 \\ 0.224 \\ 0.157 \\ + 0.274 \\ \hline \end{array}$$

$$\begin{array}{r} 21 \\ 0.231 \\ 0.224 \\ 0.194 \\ 0.274 \\ \hline 0.923 \end{array}$$

0.926

0.923

+7

Problem 3 (20 points)

Four 4-bit numbers A, B, C, and D are given as inputs. $E=A+B$, $F=C+D$. Design a system that outputs the larger number between E and F. If $E=F$, output either E or F. You can use any type of gates to implement your design.

Full Adder:

c_{in}	x	y	z	c_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1





z:

x	y	c_{in}	z
0	0	0	0
0	1	0	1
1	0	0	1
1	1	0	0

$z = xy'c_{in} + x'y'c_{in} + x'y'c_{in} + x'y'c_{in}$
 $c_{out} = xy + xc_{in} + yc_{in}$

c_{out} :

x	y	c_{in}	c_{out}
0	0	0	0
0	0	1	0
0	1	1	1
1	1	1	1

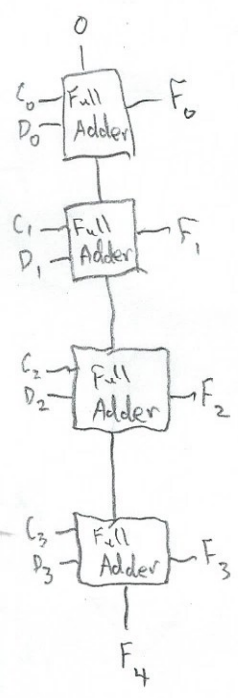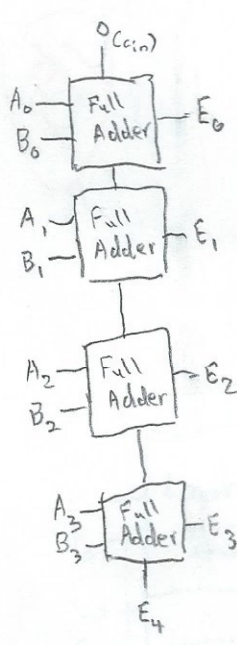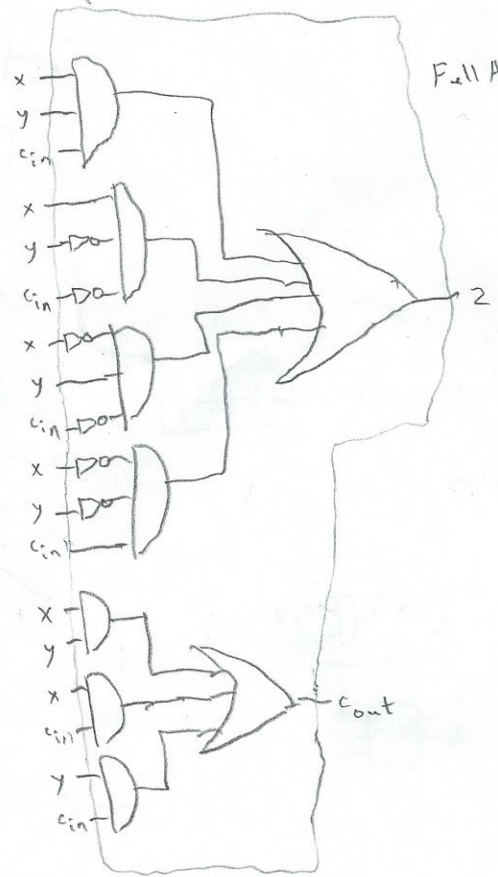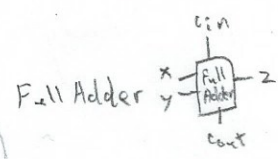

+7

Comparator:

c_{in}	x	y	z	c_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	1	1

c_{in} : 0 if $x < y$ so far
 1 if $x > y$ so far
 z : 1 if $c_{out} = 1$
 y : 0 if $c_{out} = 0$

z:

x	y	c_{in}	z
0	0	0	0
0	1	0	1
1	0	0	1
1	1	0	0

c_{out} :

x	y	c_{in}	c_{out}
0	0	0	0
0	0	1	0
0	1	1	1
1	1	1	1



$z = x + y$
 $c_{out} = xy' + xc_{in} + yc_{in}$

Next Page

Problem 3) Extra Page


$$z = x + y$$

$$c_{out} = xy' + xc_{in} + y'c_{in}$$

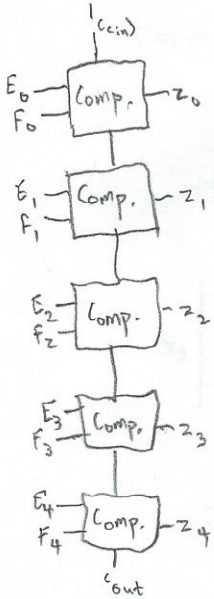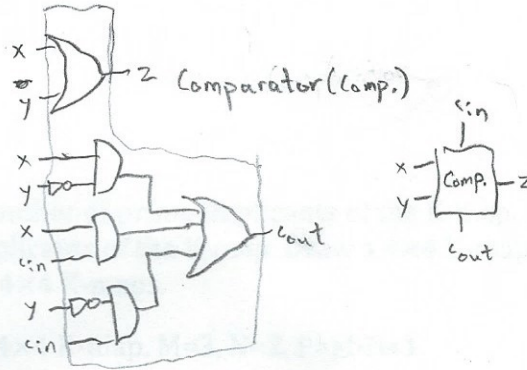

+ 7




a	b	c	d
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

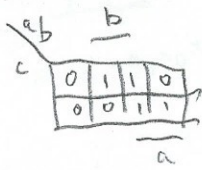

$$d = ac + bc'$$



+ b

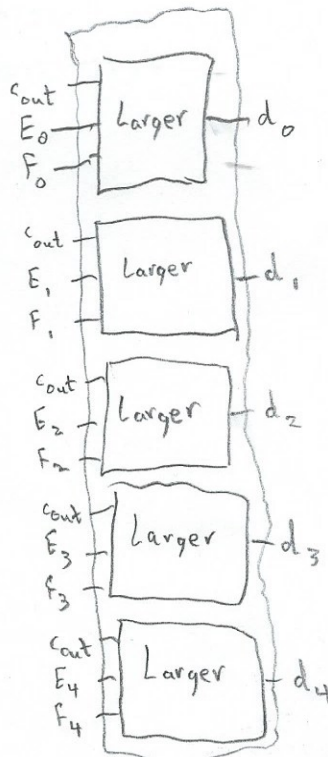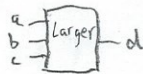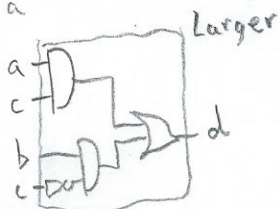

✓

20

Problem 4 (20 points)


For a K-map, M denotes the number of prime implicants of the K-map, and N denotes the number of essential prime implicants of the K-map. Draw a 4x4 K-map that has the largest value of $P=M-N$ among all the 4x4 K-maps.

For example, in the following 4x4 K-map, $M=3$, $N=2$, $P=M-N=1$.

	x_0				
	0	0	0	0	
	1	1	0	0	} x_2
} x_3	1	1	1	0	
	0	0	1	0	
	x_1				

0	0	0	0
1	1	1	0
1	0	1	0
1	1	1	0

$M=8$
 $N=0$
 $P=8-0=8$

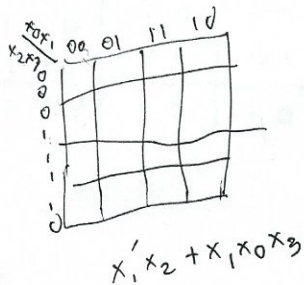

0	1	0	0
1	1	1	0
1	0	1	1
1	1	1	0

$M=12$
 $N=0$
 $P=12-0=12$



Problem 5 (20 points)

20

Use only multiplexers to design a system with input $x \in \{0,1,2, \dots, 8\}$, outputs y and z that implements the following equation

$$(x)_{10} = (yz)_3$$

In the system, x is encoded as $x_3x_2x_1x_0$ in binary. y is encoded as y_1y_0 in binary, and z is encoded as z_1z_0 in binary.


Note that the outputs y and z represent the two digits of a base-3 number.

For example, if $x=7$ ($x_3x_2x_1x_0=0111$), then the system will solve: $(7)_{10} = (21)_3$. Thus $y = 2$ ($y_1y_0=10$) and $z = 1$ ($z_1z_0=01$).


x_3	x_2	x_1	x_0	y_1	y_0	z_1	z_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	1	0	0	0
0	1	1	1	1	0	0	1
1	0	0	0	1	0	1	0

~~$$y_1 = x_3x_2x_1x_0' + x_3x_2x_1'x_0 + x_3x_2x_1x_0'$$

$$= x_3x_2x_1 + x_3x_2x_1'x_0'$$~~

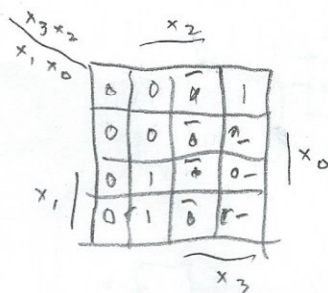


$$y_1 = x_3 + x_2x_1$$

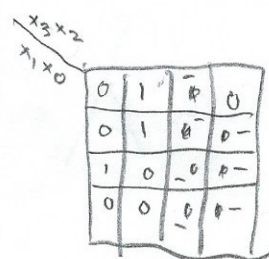


~~$$y_0 = x_1x_2 + x_2'x_0x_1$$
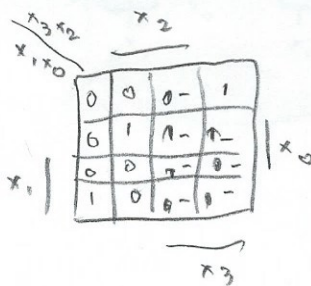
$$z_2 = x_3x_2 + x_1x_3 + x_0x_3 + x_2x_0x_1$$~~




~~$$z_1 = x_3 + x_2'x_0'x_1 + x_2x_0x_1'$$~~

$$z_1 = x_3 + x_2'x_0'x_1 + x_2x_0x_1'$$

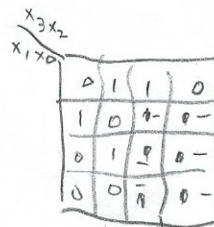

$$z_0 = x_2x_0'x_1' + x_0x_1x_2 + x_2'x_0x_1'$$
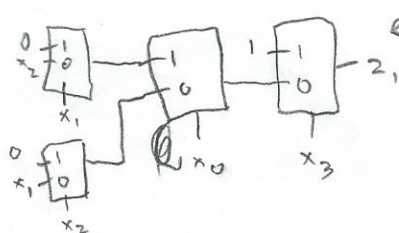
$$\begin{aligned} \sum_{x_3} 1 &= x_3 \\ \sum_{x_3'} 1 &= x_2'x_0'x_1 + x_2x_0x_1' \end{aligned} \begin{cases} \sum_{x_3'x_0} 1 = x_2x_1' \\ \sum_{x_3'x_0'} 1 = x_2x_1 \\ \sum_{x_3'x_0} x_2 = 0 \\ \sum_{x_3'x_0'} x_2 = x_1 \end{cases}$$



Replace z , portion of answer with this.

Next Page

$$\begin{aligned}
 y_1 &= x_3 + x_2 x_1 \\
 y_0 &= x_1 x_2 + x_2' x_0 x_1 \\
 z_1 &= x_3 + x_2' x_3 x_1 + x_2 x_0 x_1' \\
 z_0 &= x_2 x_0' x_1' + x_0 x_1 x_2 + x_2' x_0 x_1'
 \end{aligned}$$

Problem 5) Extra Page

$$\begin{aligned}
 y_1 \\
 f_{x_3} &= 1 \\
 f_{x_3'} &= x_2 x_1 \begin{cases} f_{x_3' x_2} = x_1 \\ f_{x_3' x_2'} = 0 \end{cases}
 \end{aligned}$$

$$\begin{aligned}
 y_0 \\
 f_{x_1} &= x_0 x_2' \begin{cases} f_{x_1 x_0} = 0 \\ f_{x_1 x_2'} = x_0 \end{cases} \\
 f_{x_1'} &= x_2
 \end{aligned}$$

$$\begin{aligned}
 z_1 \\
 f_{x_3} &= 1 \\
 f_{x_3'} &= x_2 x_0 x_1' \begin{cases} f_{x_3' x_0} = x_2 x_1' \\ f_{x_3' x_0'} = 0 \end{cases} \begin{cases} f_{x_3' x_0 x_1} = 0 \\ f_{x_3' x_0 x_1'} = x_2 \end{cases}
 \end{aligned}$$

$$\begin{aligned}
 z_0 \\
 f_{x_2} &= x_0' x_1' + x_0 x_1 \begin{cases} f_{x_2 x_0} = x_1 \\ f_{x_2 x_0'} = x_1' \end{cases} \begin{cases} f_{x_2 x_0' x_1} = 0 \\ f_{x_2 x_0' x_1'} = 1 \end{cases} \\
 f_{x_2'} &= x_0 x_1' \begin{cases} f_{x_2' x_1} = 0 \\ f_{x_2' x_1'} = x_0 \end{cases}
 \end{aligned}$$

