 


Problem 1 (20 points)

Obtain a high-level description (state transition table) of the network shown in the figure below. The system has two inputs (x_1 and x_0) and a single output z .



$$J_1 = y_0 x_0' + y_0' x_1 x_0$$

$$K_1 = y_0' x_0'$$

For a JK flip-flop, $Q(t+1) = Q(t)K'(t) + Q'(t)J(t) \rightarrow Q_1(t+1) = Q_1(t)K_1'(t) + Q_1'(t)J_1(t)$

$$\begin{aligned} Q_1(t+1) &= Q_1(t)(y_0' x_0')' + Q_1'(t)(y_0 x_0' + y_0' x_1 x_0) \\ &= Q_1(t)(y_0 + x_0) + Q_1'(t)(y_0 x_0' + y_0' x_1 x_0) \\ &= q_1 q_0 + q_1 x_0 + q_1' q_0 y_0' + q_1' q_0' x_1 x_0 \end{aligned}$$

Let $q_1 = Q_1(t)$, $q_0 = Q_0(t)$

K-map for $Q_1(t+1)$

	x_1			
	0	0	1	0
q_0	1	1	0	0
	1	1	1	1
	0	0	1	1
	x_0			

	x_1, x_0			
q_1, q_0	00	01	11	10
00	0	0	1	0
01	1	1	0	0
11	1	1	1	1
10	0	0	1	1
	$Q_1(t+1)$			

Table 1

$$J_0 = y_1' x_0'$$

$$K_0 = y_1 x_1$$

$$y_1' y_0 + y_0 x_1' + y_0 y_1' x_0'$$

$$\begin{aligned} Q_0(t+1) &= Q_0(t)(y_1 x_1)' + Q_0'(t)(y_1' x_0') \\ &= q_0 q_1' + q_0 x_1' + q_0' q_1' x_0' \end{aligned}$$

Problem 2 (20 points)



Using 1 T flip-flop, 1 SR flip-flop, and at most 8 JK flip-flops, design a system as described below. Use any gates to implement your combinational logic.

Input: $x(t) \in \{0,1\}$
 Output: $z(t) \in \{0,1\}$
 Function: $z(t) = \begin{cases} 1 & , \text{if } x(t-11, t-8)=1110, x(t-7, t-4)=10-0 \text{ or } 0-01, x(t-3, t)=1-00 \\ 0 & , \text{otherwise} \end{cases}$


For example, for the given input sequence $x(t-11, t) = 111010001100$, the output $z(t) = 1$. For the input sequence $x(t-11, t) = 111000101000$, the output $z(t) = 0$.

Note that we can create a D flip-flop from a JK flip flop by letting $J = x(t), K = x'(t)$.

 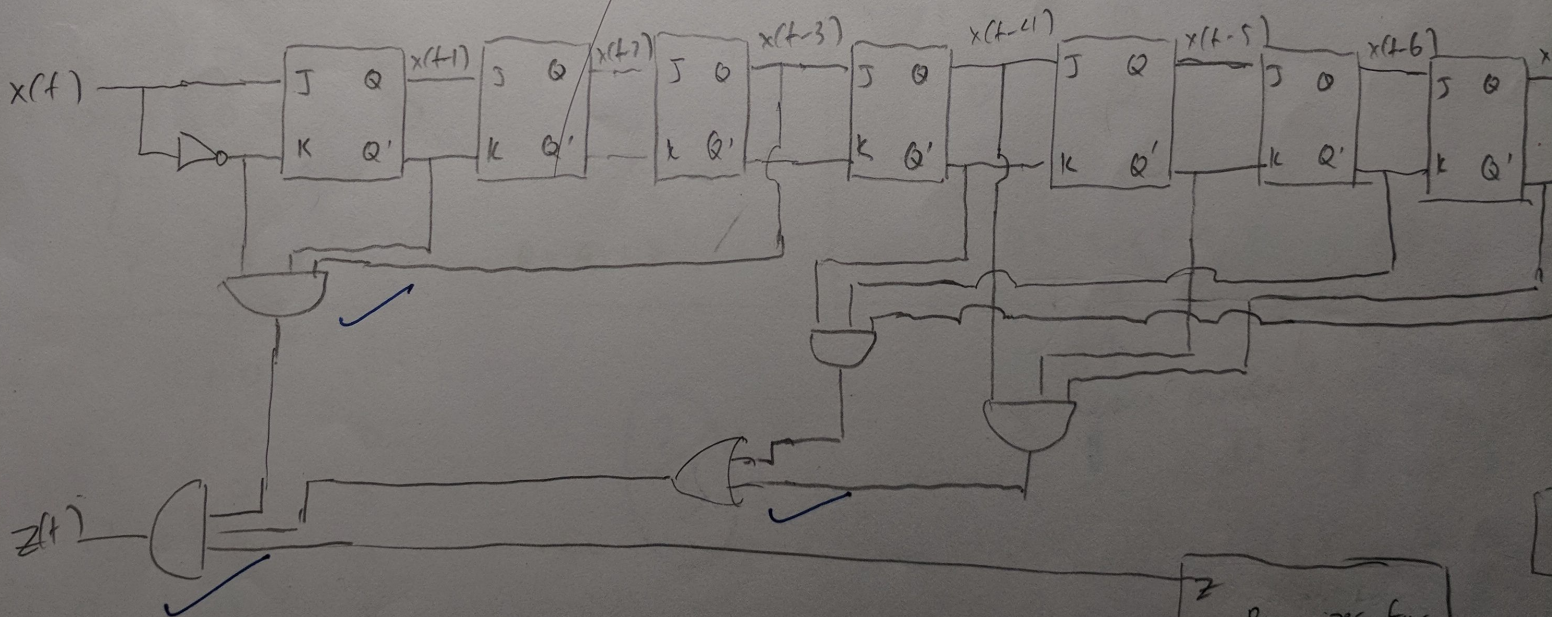The patterns at $x(t-7, t-4)$ and $x(t-3, t)$ can be recognized using combinational logic and D flip flops.



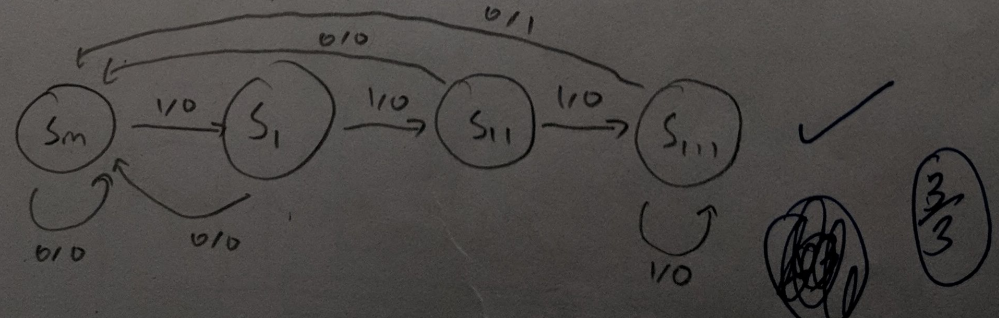We use the T flip-flop and the SR flip-flop to recognize 1110



Let S_0 be represented by 00
 S_1 by 01
 S_{11} by 11

12

Problem 3 (20 points)

Design a system that generates a pattern of either "UCLA" or "USC" based on an input signal.

As soon as the input bit turns 1, the pattern generator starts to output "UCLA."
 If the input bit turns 0 (0 is less than 1), the pattern generator starts to output "USC."

Some examples:


1. If the input sequence of $x(t-13, t) = 11110000001111$, the output sequence of $z(t-13, t) = \text{UCLAUSCUSCUCLA}$.
2. If the input sequence of $x(t-9, t) = 1111001111$, the output sequence of $z(t-9, t) = \text{UCLAUSUCLA}$.

Use the least number of bits for character encoding, and the minimal number of flip-flops and 4:1 multiplexers. (2 select inputs)

Let z_2, z_1, z_0 be the output bits, with

$U = 000$
 $C = 001$
 $L = 010$
 $A = 011$
 $S = 100$

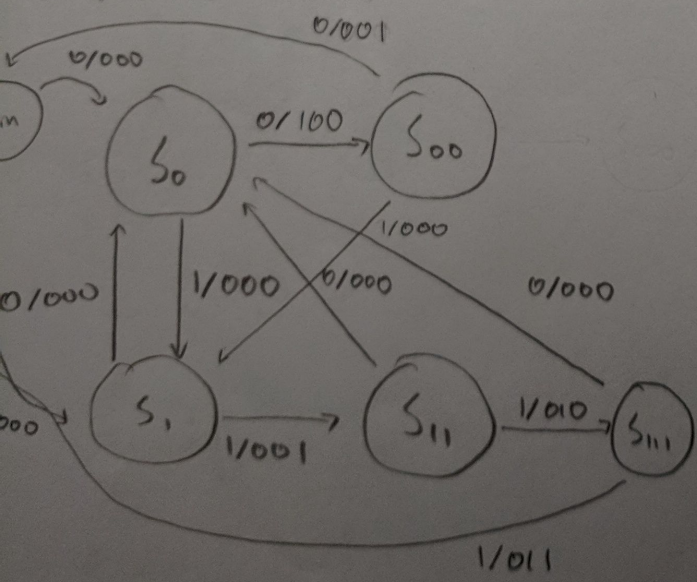We have the following state transition diagram:



Let $S_m = 000$
 $S_0 = 001$
 $S_{00} = 010$
 $S_1 = 011$
 $S_{11} = 100$

	PS			NS, z_2, z_1, z_0	
	q_2	q_1	q_0	$x=0$	$x=1$
	0	0	0	001, 000	011, 000
	0	0	1	010, 100	011, 000
	0	1	0	000, 001	011, 000
	0	1	1	001, 000	100, 001
	1	0	0	001, 000	101, 010
	1	0	1	001, 000	

Problem 4 (20 points)


Design a pattern recognizer for 00-01 using only flip-flops as defined below and NOR gates.

- Input: $x(t) \in \{0,1\}$
- Output: $z(t) \in \{0,1\}$
- Function: $z(t) = \begin{cases} 1 & , \text{if } x(t-4, t) = 00-01 \\ 0 & , \text{otherwise} \end{cases}$

3 inputs to flipflop

A	B	C	Q_{next}
0	0	0	0
0	0	1	1
0	1	0	Q
0	1	1	Q'
1	0	0	0
1	0	1	1
1	1	0	Q'
1	1	1	Q

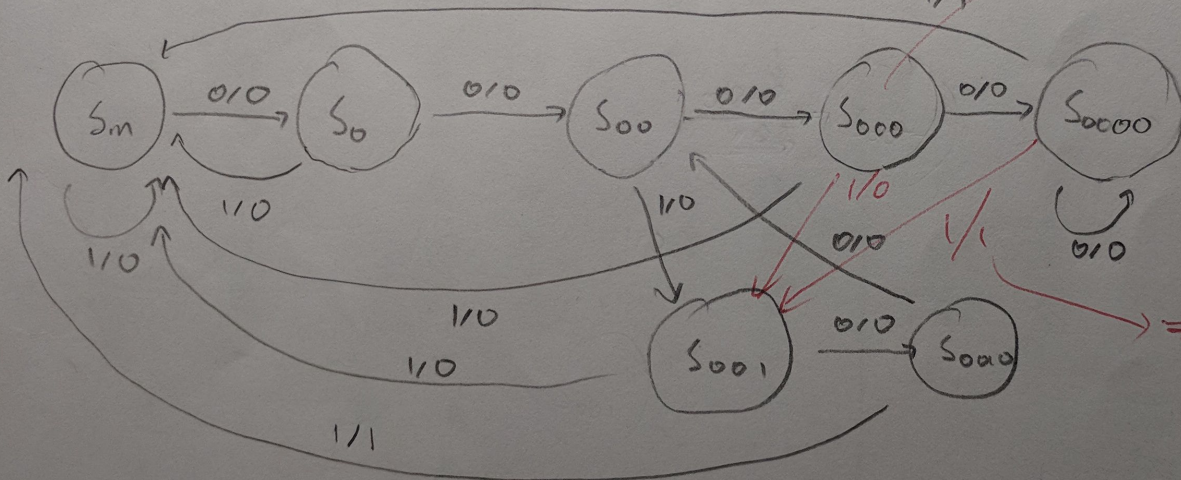have the following state transition diagram



000101

-2pts

to handle overlap pattern

0000101

State transition table

- $S_m = 000$
- $S_0 = 001$
- $S_{00} = 010$
- $S_{000} = 011$
- $S_{0001} = 100$
- $S_{00010} = 101$
- $S_{0000} = 110$

PS	Input	
	$x=0$	$x=1$
000	001, 0	000, 0
001	010, 0	000, 0
010	011, 0	100, 0
011	110, 0	000, 0
100	101, 0	000, 0
101	010, 0	000, 1
110	110, 0	000, 1


Problem 5 (20 points)

Design a system that detects the pattern of consecutive 0s followed by consecutive 1s in the most recent five bits from the input stream. In other words, the input pattern must have 0 in the start, 1 in the end, and change from 0 to 1 only once.

For example, if the input sequence $x(t-10, t) = 01001000100$, the output $z(t)$ should be 0 because $x(t-4, t) = 00100$ does not have 1 in the end. The past output $z(t-1)$ is also 0 because $x(t-5, t-1) = 00010$ does not have 1 in the end.

However, if the input sequence $x(t-10, t) = 01111100001$, the output $z(t)$ should be 1 because $x(t-4, t) = 00001$ consists of four consecutive 0s and consecutive 1s – the last bit 1. You may assume that flip-flops are initialized to 0, so the output $z(t-10, t) = \underline{01111000001}$.

 - Use only flip-flops and 8:1 multiplexers. No other gates are allowed.



check if $x(t-4) = 0$ and $x(t) = 1$
 Then check if middle is 000, 001, 011, or 111

$$S = x(t-3)'x(t-2)'x(t-1)' + x(t-3)'x(t-2)'x(t-1) + x(t-3)'x(t-2)x(t-1)' + x(t-3)x(t-2)'x(t-1) + x(t-3)x(t-2)x(t-1)'$$

output 1 if both of these conditions are true

