 


Problem 1 (20 points)

Obtain a high level description (state transition table) of the network shown in the figure below. The system has two input bits x_1 and x_0 with output bit z .



(y_1, y_0)	(input x_1, x_0)				
<u>PS</u>	<u>00</u>	<u>01</u>	<u>10</u>	<u>11</u>	
00	01/1	00/1	01/1	10/1	
01	11/0	01/0	11/0	01/0	
10	00/0	10/0	00/0	10/0	
11	11/0	11/0	10/0	10/0	

(NS $y_1(t+1)y_0(t+1), z$)

* The output depends on y_1 and y_0 , not $y_1(t+1)$ and $y_0(t+1)$, as described by TA before exam

Problem 1 Extra Page

$$\bar{y}_1 = x_0' y_0 + x_1 x_0' y_0'$$

$$K_1 = x_0' y_0'$$

$$y_0 = x_0' y_1'$$

$$K_0 = x_1 y_1'$$

x_1	x_0	y_1	y_0	y_1	K_1	y_0	K_0	$y_1(t+1)$	$y_0(t+1)$	z
0	0	0	0	0	-	1	0	0	1	1
0	0	0	-	-	0	1	0	1	-	0
0	0	-	0	0	-	0	0	0	0	0
0	0	-	-	-	0	0	0	1	-	0
0	-	0	0	0	0	0	0	0	0	1
0	-	0	-	0	0	0	0	-	1	0
0	-	-	0	0	0	0	0	1	-	0
0	-	-	-	0	0	0	0	-	0	0
1	0	0	0	0	-	1	0	0	-	1
1	0	0	-	-	0	1	0	1	-	0
1	0	-	0	0	-	0	1	0	0	0
1	0	-	-	-	0	0	-	1	0	0
1	-	0	0	1	0	0	0	1	0	-
1	-	0	-	0	0	0	0	0	1	0
1	-	-	0	-	0	0	1	-	0	0
1	-	-	-	0	0	0	-	0	0	0

Problem 2 (20 points)

20

Design a state transition table such that it initially has 8 states, and after minimization, reduces down to 3 states.


<u>PS</u>	<u>0</u>	<u>1</u>
A	A, 0	A, 0
B	A, 0	A, 0
C	A, 0	A, 0
D	A, 0	A, 1
E	A, 0	A, 1
F	A, 1	A, 0
G	A, 1	A, 0
H	A, 1	A, 0

nice


reduces
to

<u>PS</u>	<u>0</u>	<u>1</u>
A	A, 0	A, 0
D	A, 0	A, 1
F	A, 1	A, 0




A:

 

B:

 


what are these from?

   


*Assumes difference not greater than 8.

 Some arbitrary limit must be imposed and I chose 8.



Works for A > B

Works for B > A

 

outputs 1 if difference is three (for B > A)

Problem 4 (20 points)

9 — for op. missing
 +7 not optimized
 16 ~~looks~~
 maps us + correct

Using **OK flip-flops** as designed below and **multiplexers** for logic, design a **minimum system**

which has the following behaviors:

Input set: {a, b, c} {a, b, c, d}

Output: 1 if $x(t-n, t) = a[b|c]+d*a$

0 otherwise

Notes:

Overlaps can occur. For example adada would output 00101

| means OR

* means 0 or more of the previous character



+ means 1 or more of the previous character

$$y_2(t+1) = x_1'x_0y_1y_0 + x_1x_0'y_1y_0 + x_0y_1y_0' + x_1y_1y_0' + x_1x_0y_1$$



$$y_1(t+1) = x_1'x_0' + x_1x_0y_1$$

$$D(x) = OK(x', x)$$

Prev State Q(t)	OK			
	00	01	10	11
0	1	1	0	-
1	-	1	0	0
	Nxt State Q(t+1)			

  

(y1, y0)	(x1, x0)		a, d	
PS	00	01	10	11
00	01/0	00/0	00/0	00/0
01	01/0	10/0	10/0	00/0
10	01/0	10/0	10/0	11/0
11	01/1	00/0	00/0	11/0

  

(NS, Z)

Problem 3 (20 points)

~~14~~ 20

any logical unit BUT address

Given two 1-bit input streams A and B, output 1 if the difference between the number of times the pattern "001" appears in stream A and "101" appears in stream B is 3. If the difference between the number of their appearances is not 3, then the output is 0. You may use any type of flip flops or logical units of your choosing.

For example:


A: 001000000

B: 101010101

Would output: 000000001. Notice that the B pattern overlaps.


y_1, y_0

x

 

↓
outputs 1 when we see B

(subtract 1 from count) 0/0

 

↓
outputs 1 when we see B

(add 1 to count)

PS	0	1
00	01/0	00/0
01	10/0	00/0
10	10/0	00/1
11	-	-

$z_n = x y_n$

$y_0^{(n+1)} = x' y_1 y_0$

$y_1^{(n+1)} = x' (y_1 \otimes y_0)$

PS	0	1
00	00/0	01/0
01	10/0	01/0
10	00/0	01/1
11	-	-

$z_n = x y_n$

$y_1^{(n+1)} = x' y_1 y_0$

$y_2^{(n+1)} = x$

WORK ON

BACK OF PAGE



Problem 4 Extra Page

$$Z = x_1' x_0 y_1 y_0$$




$$y_1^{(t+1)} = x_1' x_0 y_1 y_0 + x_1 x_0' y_1 y_0 + x_0 y_1 y_0' + x_1 y_1 y_0' + x_1 x_0 y_1$$

$$y_0^{(t+1)} = x_1' x_0' + x_1 x_0 y_1$$

$$D(x) = OK(x, x)$$

  

Not optimized

   

Problem 5 (20 points)

Given 6 2-bit numbers as input, {A, B, C, D, E, F}, design a system such that the system finds the maximum sum between any of the 2 inputs. You may only use multiplexers to implement this system.

For example, if all the inputs are 01, then the maximum sum output should be 010.

Sum of two numbers:

$$Z = z_2 z_1 z_0$$


~~7, 1, 2, 3~~
~~+~~
~~7, 2, 3~~

<u>a₁</u>	<u>a₀</u>	<u>b₁</u>	<u>b₀</u>
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

$$z_0 = a_0 \oplus b_0$$

$$z_1 = (a_1 \oplus b_1) \oplus a_0 b_0$$

$$z_2 = a_1 b_1$$

 

+ Implement the above for all possible combos:

- AB, AC, AD, AE, AF
- BC, BD, BE, BF
- CD, CE, CF
- DE, DF
- EF

Run each z_2, z_1, z_0 into a priority decoder (with higher # = higher priority), take the OR of all resulting A's, b's, ..., z's, i's, o's, run those into their respective places in a priority decoder, and the output of that is the maximum sum output.