

CS m51A: Logic Design of Digital Systems
UCLA Computer Science Department
Winter 2010
Midterm 1

Time: 100 minutes

Note: Closed book, closed notes, no electronic computing or communications devices.

Name: Angelina Huang

Student ID: 803657204

Question	Points	Grades
1	15	15
2	15	15
3	15	14
4	20	20
5	20	18
6	15	15
Total	100	97

"The best way to predict the future is to invent it."
-Alan Kay

Question 1: Number System Conversion

Find the value of x in the following equations. Show your work for credit.

$$\begin{array}{r} 45056 \\ - 3072 \\ \hline 224 \end{array}$$

$$\begin{array}{r} 48352 \\ - 256 \\ \hline 224 \end{array}$$

$$\begin{array}{r} 256 \\ \times 12 \\ \hline 256 \\ + 512 \\ \hline 3072 \end{array}$$

$$\begin{array}{r} 256 \\ \times 16 \\ \hline 256 \\ 160 \\ \hline 4096 \\ - 4096 \\ \hline 0 \end{array}$$

a) $BCE0_{16} = x_4$

$$10111100\ 1110\ 0000 \rightarrow BCE0_{16}$$

$$x_4 = 23303200_4$$



$$11 \times 16^3 + 12 \times 16^2 + 14 \times 16 + 0 \times 16^0$$

$$45056 + 3072 + 224 + 0$$

$$= 48352$$

$$\begin{array}{r} 12088 \\ 4 \overline{)48352} \\ \quad 4 \\ \quad 8 \\ \quad 8 \\ \hline \quad 0 \\ 4 \overline{)11} \\ \quad 11 \\ \quad 0 \\ \hline \quad 0 \\ 4 \overline{)22} \\ \quad 22 \\ \quad 0 \\ \hline \quad 0 \\ 4 \overline{)12088} \\ \quad 12088 \\ \quad 0 \\ \hline \quad 0 \\ 4 \overline{)28} \\ \quad 28 \\ \quad 0 \\ \hline \quad 0 \\ 4 \overline{)22} \\ \quad 22 \\ \quad 0 \\ \hline \quad 0 \\ 4 \overline{)28} \\ \quad 28 \\ \quad 0 \\ \hline \quad 0 \\ 4 \overline{)18} \\ \quad 16 \\ \quad 2 \\ \hline \quad 2 \\ 4 \overline{)78} \\ \quad 76 \\ \quad 2 \\ \hline \quad 2 \\ 4 \overline{)78} \\ \quad 76 \\ \quad 2 \\ \hline \quad 2 \\ 4 \overline{)0} \\ \quad 0 \\ \hline \quad 0 \end{array}$$

b) $251_8 = x_6$

$$251_8$$

$$2 \times 8^2 + 5 \times 8^1 + 1 \cdot 8^0$$

$$128 + 40 + 1$$

$$128$$

$$169$$

$$\begin{array}{r} 28 \\ 6 \overline{)169} \\ \quad 12 \\ \quad 49 \\ \quad 48 \\ \hline \quad 1 \\ 6 \overline{)28} \\ \quad 24 \\ \quad 4 \\ \hline \quad 0 \\ 6 \overline{)14} \\ \quad 12 \\ \quad 2 \\ \hline \quad 0 \end{array}$$

$$x_6 = 441_6$$



Question 2: Universal Set

Prove that the operation represented by the switching expression $xy + x'y'z$ is universal.
You can use the constants 1 and 0.

$$(x \rightarrow z) \rightarrow (y \rightarrow z)$$

$xy + x'y'z$ is universal

$$\begin{array}{c} x \\ 0 \\ 1 \end{array} \quad \boxed{xy + x'y'z} \quad \begin{array}{c} x' \\ \text{NOT} \end{array} \quad \checkmark$$
$$x \cdot 0 + x' \cdot 1 = 1$$
$$0 + x' = x'$$

$$\begin{array}{c} x \\ y \\ 0 \end{array} \quad \boxed{xy + x'y'z} \quad \begin{array}{c} xy \\ \text{AND} \end{array} \quad \checkmark$$
$$xy + x' \cdot y' \cdot 0 = xy$$

since {AND, NOT}, which is a universal set,
can be formed from $xy + x'y'z$, then the
switching expression $xy + x'y'z$ must be
universal as well.

Question 3: Boolean Algebra

a) Simplify the following switching expression, using Boolean algebra. Show your work for credit.

$$f = ((a' + b)'(c + ab' + ad')' + d')'$$


$$\begin{aligned}
 f &= ((a' + b)'(c + ab' + ad')' + d')' \\
 &= ((ab')((c + ab' + ad')' + d'))' \\
 &= ((ab')[(c + a(b' + d'))' + d'])' \\
 &\quad [(ab')[c' \cdot [a(b' + d')]]' + d'] \\
 &= [(ab)[c' \cdot [a' + (b' + d')]]] + d' \\
 &= [(ab)[c' \cdot (a' + bd)]] + d' \\
 &= [(ab)[a'c' + bc'd] + d'] \\
 &= [a'b'c' + ab'bc'd + d'] \\
 &= 0 \cdot b'c' + a \cdot 0 \cdot c'd + d' \\
 &= 0 + 0 + d' \\
 &= d' \quad \text{Complement Missed}
 \end{aligned}$$

(-1)

Question 4:

Give an example of a function of four variables with four prime implicants and seven minterms. For credit, provide the K-map, showing the prime implicants.

$$\Sigma m: (3, 6, 10, 11, 13, 14, 15)$$

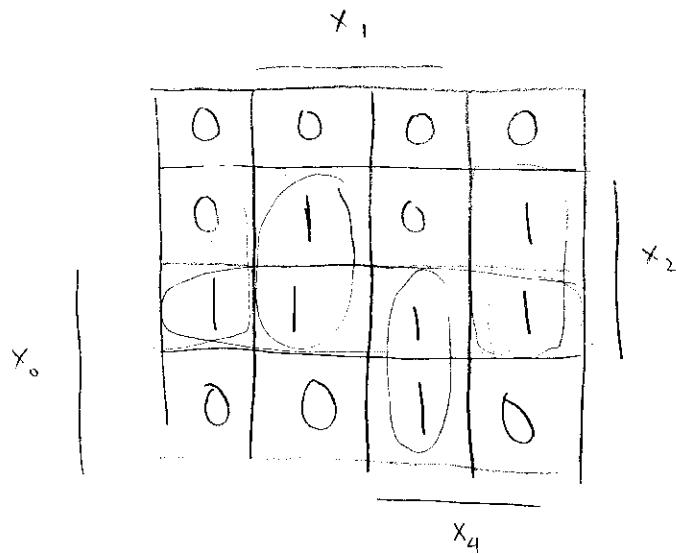

$$Z = \cancel{x_0x_2} + \cancel{x_1x_2x_4} + \cancel{x_0x_1x_4} + \cancel{x_1'x_2x_4}$$

minterms:

0110	6
0011	3
1010	10
1110	14
1111	15
1011	11
1101	13

Question 5: NOR-NOR network

Give a minimal NOR-NOR network that implements the subtraction of x from y,


$$\underline{y}(y_1, y_0) - \underline{x}(x_1, x_0) = \underline{r}(r_1, r_0).$$

For example if $x=10$ and $y=11$, then $r=01$. Assume that an input where x is greater than y is never given.

a) Provide the truth table.

y_1, y_0	x_1, x_0	r_1, r_0	
00	00	00	$0-0=0$
01	00	01	$1-0=1$
01	01	00	$1-1=0$
10	00	10	$2-0=2$
10	01	01	$2-1=1$
10	10	00	$2-2=0$
11	00	11	$3-0=3$
11	01	10	$3-1=2$
11	10	01	$3-2=1$
11	11	00	$3-3=0$

b) Provide the K-maps.

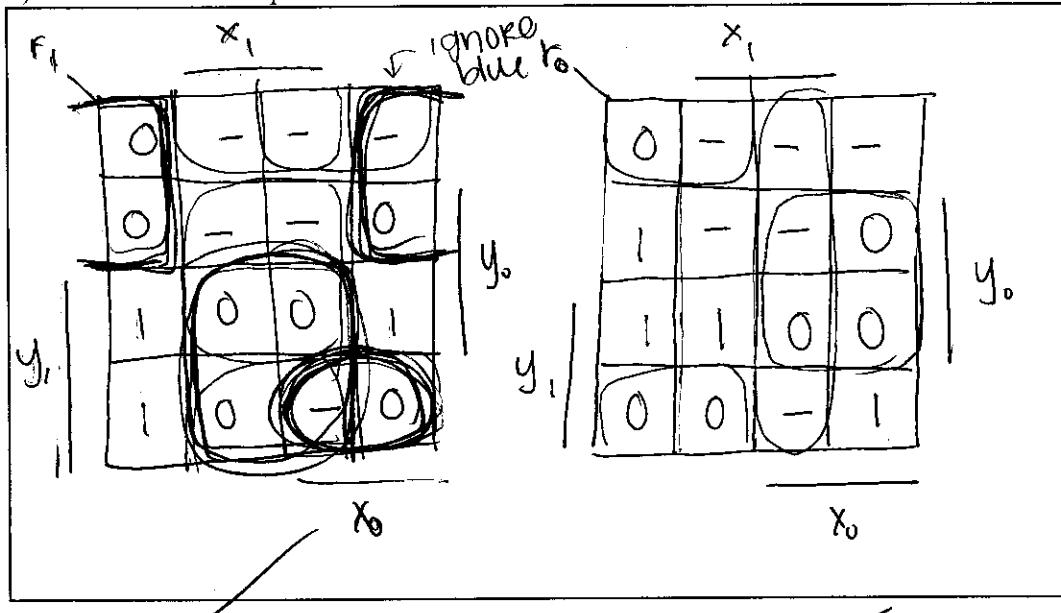

c) Provide the switching expressions.

$$r_1 = (y_1 + x_1)(x_1' + y_1')(y_1' + x_0' + y_0)$$

$$r_1 = (x_1 + y_1)(x_1' + y_1')(x_0' + y_0 + y_1')$$


$\times \quad (-2)$

$$r_0 = (y_0 + x_0)(x_0' + y_0')$$

$$r_0 = (x_0 + y_0)(x_0' + y_0')$$



d) Provide a minimal NOR-NOR network. Assume you have the negation of the input bits available.

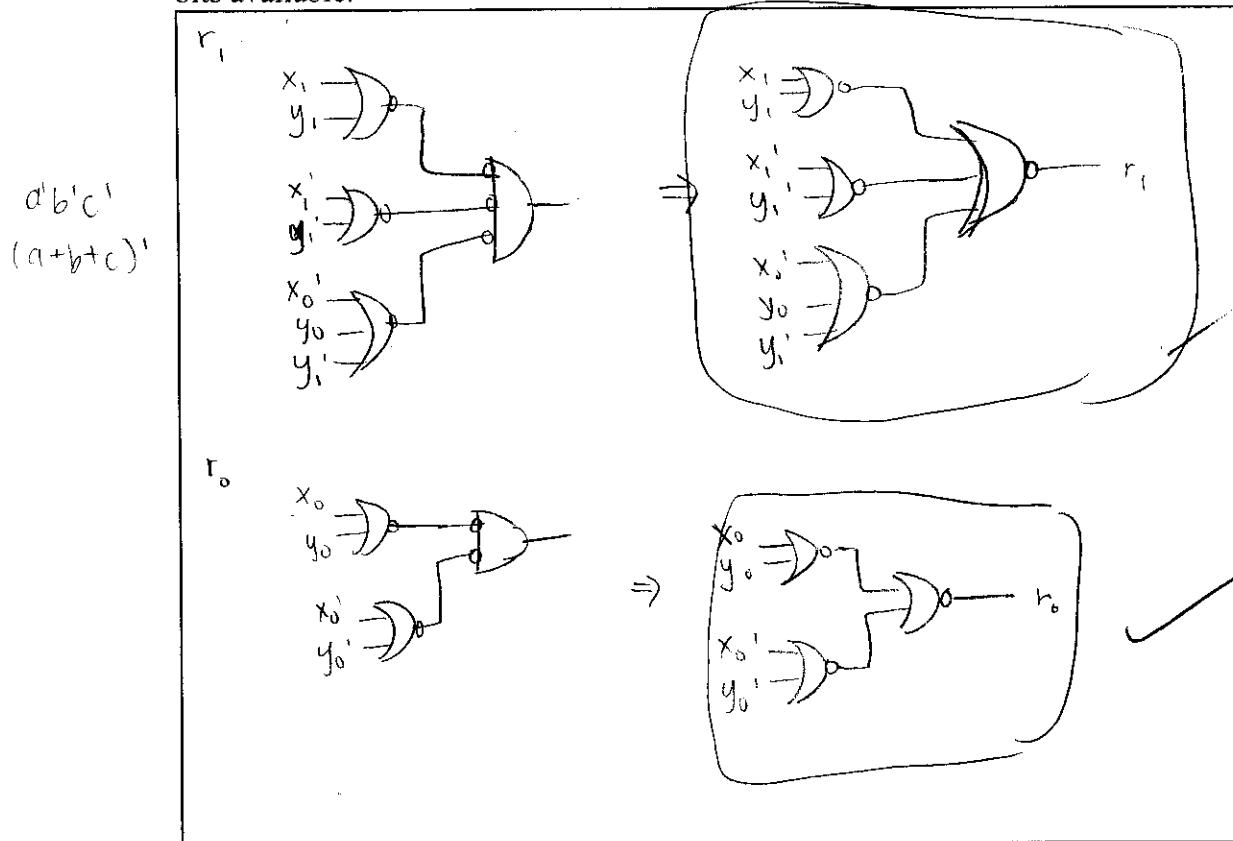

Question 6:

Give a minimal NAND-NAND implementation for the following function

$$f = a'b'c + b'c'd' + a'b'c'd + a'bc$$

For credit, show your work. Assume you have the negation of the input bits available.

